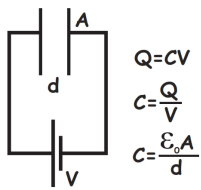


CAPACITANCE

CAPACITANCE




Capacitance Depends on

1. Distance between plates
2. Area of plates
3. Medium b/w plates

Capacitance is Independent of

1. Charge
2. Potential difference

Unit Of Capacitance = Farad

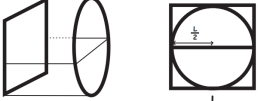

$$A_{\text{eff}} = \pi \left(\frac{L}{2}\right)^2 = \pi \frac{L^2}{4}$$

$$C = \frac{\epsilon_0 A_{\text{eff}}}{d} = \frac{\pi \epsilon_0 L^2}{4d}$$

ENERGY STORED

Work done by battery = QV (100%)




- 50% Energy stored in capacitor = $\frac{1}{2}QV = \frac{CV^2}{2}$
- 50% Energy dissipated = $\frac{1}{2}QV = \frac{CV^2}{2}$

Variation with plate separation

1. $Q=CV = \frac{\epsilon_0 AV}{d}$
2. $C = \frac{\epsilon_0 A}{d} \quad C \propto \frac{1}{d}$
3. $V = \frac{Q}{C} = \frac{Qd}{\epsilon_0 A}$
4. $E = \frac{Q}{A\epsilon_0} = \frac{V}{d}$
5. $F = \frac{Q^2}{2A\epsilon_0} = \frac{CV^2}{2d}$
6. $U = \frac{CV^2}{2}$ OR $U = \frac{Q^2}{2C} = \frac{Q^2 d}{2\epsilon_0 A}$

$$= \frac{\epsilon_0 AV^2}{2d}$$


DIELECTRIC IN CAPACITOR

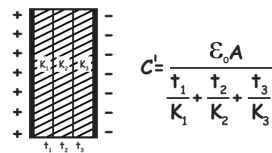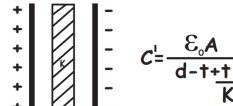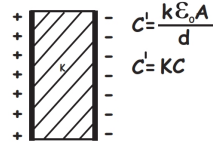


Dielectric inserted in capacitor

- | Dielectric removed | Battery remains connected |
|-----------------------|---------------------------|
| 1. $C = KC$ | 1. $C' = KC$ |
| 2. $Q = Q$ | 2. $Q' = KQ$ |
| 3. $V' = \frac{V}{K}$ | 3. $V' = V$ |
| 4. $E' = \frac{E}{K}$ | 4. $E' = E$ |
| 5. $U' = \frac{U}{K}$ | 5. $U' = KU$ |


SPHERICAL CAPACITOR

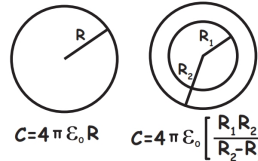

REDISTRIBUTION OF CHARGE

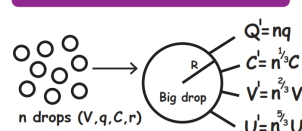

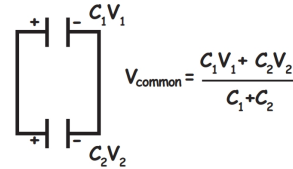Connecting two charged capacitors - Case 1




Initial Energy → Heat loss → Final Energy

$$U_i = \frac{C_1 V_1^2}{2} + \frac{C_2 V_2^2}{2}$$

$$U_f = \frac{1}{2} (C_1 + C_2) \left(\frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \right)^2$$

$$\text{Energy loss} = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 - V_2)^2$$

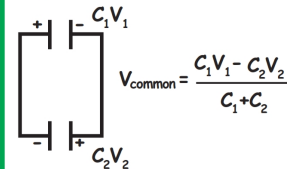
Connecting two charged capacitors - Case 2



$$\text{Energy loss} = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 + V_2)^2$$

Grouping of capacitors

1. Series combination

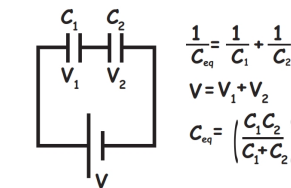


Voltage divider rule


$$V \propto \frac{1}{C}$$

$$V_1 = \left(\frac{C_2}{C_1 + C_2} \right) V \quad V_2 = \left(\frac{C_1}{C_1 + C_2} \right) V$$


2. Parallel combination

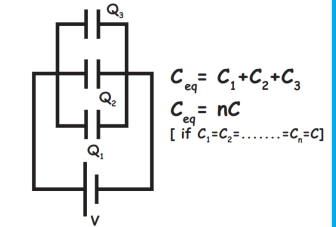


Charge divider rule $Q \propto C$

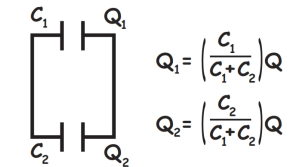

WHEATSTONE'S BRIDGE

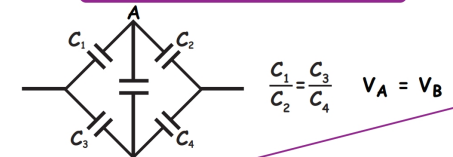


$$C = \frac{3\epsilon_0 A}{d}$$

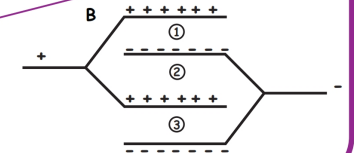


MULTIPLE DIELECTRICS


1. Series combination

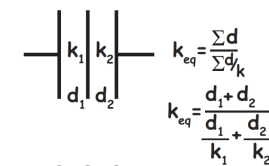


2. Parallel combination

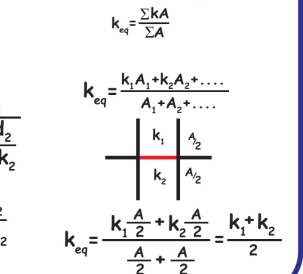

ELECTRIC FIELD

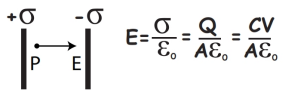


when plate separation doubled

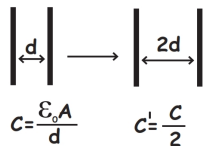

POTENTIAL

$$V = Ed = \frac{Qd}{A\epsilon_0}$$

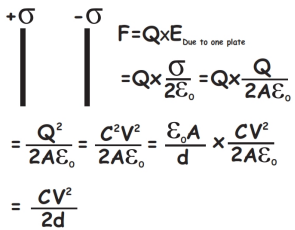Force b/w plates of a parallel plate capacitor



Battery connected
d → 2d

1. $V = \text{Constant}$
2. $C' = \frac{C}{2}$
3. $Q = CV, Q' = \frac{Q}{2}$
4. $E = \frac{V}{d}, E' = \frac{E}{2}$
5. $F = \frac{CV^2}{2d}, F' = \frac{F}{4}$
6. $U = \frac{CV^2}{2}, U' = \frac{U}{2}$

Battery Disconnected
d → 2d

1. $Q = \text{Constant}$
2. $C' = \frac{C}{2}$
3. $V = \frac{Q}{C}, V' = 2V$
4. $E = \frac{Q}{A\epsilon_0} = \text{Constant}$
5. $F = \frac{Q^2}{2A\epsilon_0} = \text{Constant}$
6. $U = \frac{Q^2}{2C}, U' = 2U$