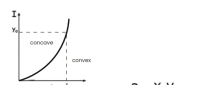
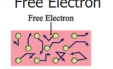


# CURRENT ELECTRICITY

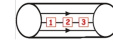

## 01 ELECTRIC CURRENT

Current  $I = \frac{q}{t}$   
 Average current  $I_{av} = \frac{\Delta q}{\Delta t}$   
 Instantaneous current  $I_{inst} = \frac{dq}{dt}$   
 Average current  $I_{av}$   
 =  $\frac{\text{area under } I-t \text{ graph}}{\text{total time taken}}$   
  
 Concave area =  $\frac{2}{3} \times \text{base} \times \text{height}$   
 Convex area =  $\frac{1}{3} \times \text{base} \times \text{height}$

## 02 DRIFT VELOCITY

Free Electron  
  
 $\langle KE \rangle = \frac{3}{2} kT$   
 $\langle \frac{1}{2} mv^2 \rangle \approx 10^{-21} J$   
 Avg. Speed = 105 m/s  
 Electrons are in random motion  
 Avg. velocity =  $\frac{\vec{v}_1 + \vec{v}_2 + \vec{v}_3 + \dots + \vec{v}_n}{n} = 0$   
 $I_{net} = 0$   
 E accelerates the electrons  
 $\vec{v} = u + at$   
 $v_d = at$   
 $v_d = \frac{eE}{m} \tau$   
 $E = \frac{V}{l}$   
 $v_d = \frac{eV}{m l} \tau$

## 03 FACTORS AFFECTING DRIFT VELOCITY

- Dependence on shape  
 1) Uniform shape  
  
 $v_d = \frac{eE}{m} \tau$   
 Here E is uniform so,  
 $V_{d1} = V_{d2} = V_{d3}$   $E_1 = E_2 = E_3$   
 2) Non Uniform shape  
  
 $E_1 > E_2 > E_3$   
 $V_{d1} \propto E$   $V_{d1} > V_{d2} > V_{d3}$   
 3) Relation B/w Current & Drift velocity  
 $I = nAV_d e$   
 $n = \text{no. of } e\text{'s per unit volume}$

## 04 OHM'S LAW

$V = I \times R$   
 Voltage (volts (V)) = Current (Amperes (A))  $\times$  Resistance (ohms( $\Omega$ ))  
 $R = \frac{\rho l}{A}$   
 $\rho = \frac{RA}{l} = \frac{m}{ne^2 \tau}$   
 Slope =  $\tan \theta = R$   
 Depends on  
 1. Material (n &  $\tau$  changes)  
 2. Temperature (n &  $\tau$  changes)  
 3. Dimension (Length & Area)  
 Non-Ohmic Conductor  
 V-I graph is not linear  
 Slope of tangent  $\frac{dv}{dI} = R$   
 Resistance is not constant  
 1) Slope = +ve Resistance = +ve  
 $V \uparrow$  then  $I \uparrow$   
 2) Slope = 0 Resistance = 0  
 3) Slope = -ve Resistance = -ve  
 $V \uparrow$  then  $I \downarrow$

## 05 CURRENT DENSITY

$J = \frac{I}{A} = n v_d$   
 $I = \frac{V}{R} = \frac{V}{\rho l/A} = \frac{EA}{\rho}$   $J = \frac{E}{\rho}$   $J \propto E$   
 Uniform cross section  
 $E_1 = E_2 = E_3$   
 $\therefore J_1 = J_2 = J_3$   
 Non-Uniform cross-section  
 $E_1 > E_2 > E_3$   $J \propto \frac{I}{A}$   
 $\therefore J_1 > J_2 > J_3$   
 But current is same  
 $I_1 = I_2 = I_3$

## 06 DEPENDANCE OF R ON DIMENSION

$R = \frac{\rho l}{A} = \frac{\rho l}{bh}$   
 $R = \frac{\rho h}{lb}$   
 $R = \frac{\rho b}{lh}$   
 $\frac{R_{max}}{R_{min}} = \frac{(\text{max length})^2}{(\text{min length})^2}$

## 07 CUTTING & STRETCHING OF WIRE

Cutting of wire  
 $R_1 \propto l_1$   
 $R_2 \propto l_2$   
 $R_3 \propto l_3$   
 Stretching of wire  
 Before stretching  $A_1$   $l_1$   
 After stretching  $A_2$   $l_2$   
 $\frac{R_1}{R_2} = \left(\frac{l_1}{l_2}\right)^2 = \left(\frac{A_2}{A_1}\right)^2 = \left(\frac{r_2}{r_1}\right)^4 = \left(\frac{d_2}{d_1}\right)^4$   
 If l become n then R become  $n^2 R$   
 If r become  $r/n$  then R become  $n^4 R$   
 If change in length  $> 10\%$   $\frac{R_2 - R_1}{R_1} \times 100 = \frac{l_2^2 - l_1^2}{l_1^2} \times 100$   
 If change in length  $< 10\%$   
 1) % change in  $R = 2 \times$  % change in length  
 2) % change in  $R = 2 \times$  % change in area  
 3) % change in  $R = 4 \times$  % change in radius

## 08 TEMPERATURE DEPENDANCE OF RESISTANCE

Metals,  $\alpha = +ve$   
 If  $T \uparrow R \uparrow$   
 Alloy  
 For semiconductor  $\alpha = -ve$   
 If  $T \uparrow R \downarrow$   
 $\alpha = \frac{\Delta R}{R \Delta T}$   
 Variation of resistance with temperature  
 Equivalent temp. Coefficient  
 SERIES:  
 $\alpha_s = \frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$   
 if  $R_1 = R_2$   $\alpha = \frac{\alpha_1 + \alpha_2}{2}$   
 PARALLEL:  
 $\alpha_p = \frac{\frac{\alpha_1}{R_1} + \frac{\alpha_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}$   
 if  $R_1 = R_2$   $\alpha = \frac{\alpha_1 + \alpha_2}{2}$

## 09 GROUPING OF RESISTANCE

Series Combination  
 Current is constant voltage is divided  
 $R_s = R_1 + R_2 + R_3 + \dots + R_n$   
 If resistors are identical:  $R_s = nR$   
 Parallel Combination  
 voltage is constant current is divided  
 $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$   
 If resistors are identical:  $R_p = \frac{R}{n}$   
 Shortcut for two resistors in parallel  
 $R_1, R_2$   
 $R_p = \frac{R_1 R_2}{R_1 + R_2}$   
 $R_p$  Bigger than largest value of resistance  
 $R_p$  Lower than smallest value of resistance

## 10 CURRENT & VOLTAGE DIVIDER RULE

Current Divider Rule  
 $V = \text{Constant } I \propto \frac{1}{R}$   
 $I_1 = \frac{I \times R_2}{R_1 + R_2}$   $I_2 = \frac{I \times R_1}{R_1 + R_2}$   
 Voltage Divider Rule  
 $V_1 = IR_1$   $V_2 = IR_2$   $V_3 = IR_3$   
 $V_1 = \frac{V \times R_1}{R_1 + R_2 + R_3}$   
 $V_2 = \frac{V \times R_2}{R_1 + R_2 + R_3}$   
 $V_3 = \frac{V \times R_3}{R_1 + R_2 + R_3}$

## 11 COLOUR CODING

1st Digit  
 2nd Digit  
 Multiplier  
 Tolerance  
 Resistor color code  


Color	Digit	Multiplier	Tolerance (%)
Black	0	$10^0$	
Brown	1	$10^1$	1
Red	2	$10^2$	2
Orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	0.5
Blue	6	$10^6$	0.25
Violet	7	$10^7$	0.1
Grey	8	$10^8$	
White	9	$10^9$	
Gold		$10^{-1}$	5
silver		$10^{-2}$	10
none			20

## 12 GEOMETRICAL DIAGRAM

Circle formed by wire having uniform resistance per unit length (r)  
 $R_{eff} = r a \left( \frac{\theta_1 \theta_2}{\theta_1 + \theta_2} \right)$   
 When resistance of wire forming circle is given  
 $R_{eff} = \frac{R}{2\pi} \left( \frac{\theta_1 \theta_2}{\theta_1 + \theta_2} \right)$

### 13 KIRCHHOFF'S LAW


#### 1. Junction Rule

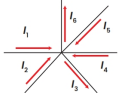


$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 + I_4 + I_5 = I_3 + I_6$$


#### 2. Open Circuit

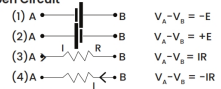

#### Closed Circuit

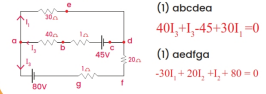

### 14 CELL & INTERNAL RESISTANCE

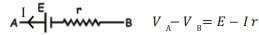

#### Terminal potential difference (TPD)

1) When current is drawn from cell

$$V = V_C - V_D = E - Ir$$

$$TPD < EMF$$

$$V = E - Ir = IR \Rightarrow I = \frac{E}{R+r}$$

So,  $V = \frac{E}{R+r} R$


2) When current is given to cell

$$V = V_C - V_D = E + Ir$$


$$TPD > EMF$$

### 15 CELL & INTERNAL RESISTANCE

#### 3) When cell is in open circuit

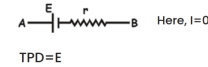

#### 3) When cell is in short circuit

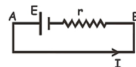


$$I = I_{max} = \frac{E}{r}$$

$$TPD = 0$$

### 16 CELL & INTERNAL RESISTANCE

Slope of graph = -r  
y intercept = E

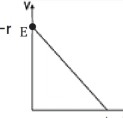

$$\text{Internal Resistance } r = \left( \frac{E - V}{V} \right) R$$

Power delivered by cell during withdrawal of current


$$P = I^2 R = \left( \frac{E}{R+r} \right)^2 R$$

$$P_{max} = \frac{E^2}{4r} \text{, when } R=r$$



### 17 COMBINATION OF CELLS

#### 1) Series Combination

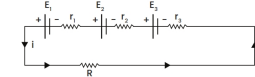

(a)  $E_{equivalent} = E_1 + E_2 + E_3 + \dots + E_n$

(b)  $r_{equivalent} = r_1 + r_2 + r_3 + \dots + r_n$

(c) Current,  $i = \frac{\sum E_i}{\sum r_i + R}$

(d) If all cells have equal emf E and equal internal resistance r then  $I = \frac{nE}{nr + R}$

1) if  $nr > R \Rightarrow i = \frac{E}{r}$

2) if  $nr < R \Rightarrow i = \frac{nE}{R}$


(e) Power dissipated in circuit  $P = I^2 R = \left( \frac{nE}{nr + R} \right)^2 R$

Conditions for maximum power:  $R = nr$

$$P_{max} = nE^2/4r$$

### 19 COMBINATION OF CELLS

#### Infinite resistors

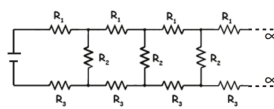

$$R_{eq} = \frac{R_1 + R_2}{2} \left[ 1 + \sqrt{1 + \frac{4R_2}{R_1 + R_3}} \right]$$

If all resistors are equal  $R_{eq} = R(1 + \sqrt{3})$

### 18 COMBINATION OF CELLS

#### 2) Parallel Combination

a)  $E_{equivalent} = \frac{E_1 + E_2 + E_3 + \dots + E_n}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots + \frac{1}{r_n}}$

b)  $r_{equivalent} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots + \frac{1}{r_n}}$


(c) If all cells have equal emf E & internal resistance r then  $E_{equivalent} = E$

$$r_{equivalent} = \frac{r}{n} \Rightarrow \text{current } I = \frac{E}{\frac{r}{n} + R}$$

(d) Power dissipated in the circuit:  $P = I^2 R = \left( \frac{nE}{\frac{r}{n} + R} \right)^2 R$

Conditions for maximum power  $R = \frac{r}{n}$

#### 3) Mixed Combination

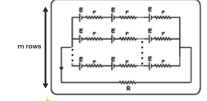

$$r_{sum} = \frac{nr}{m}$$

Total emf =  $E_{sum} = nE$

$$I = \frac{E_{sum}}{R + r_{sum}} = \frac{nE}{R + \frac{nr}{m}}$$

$$P_{max} = \frac{E_{sum}^2}{4R} = \frac{mnE^2}{4R} \quad [\because R = \frac{nr}{m}]$$

n cells connected in series and there are m such branches in the circuit.  
Internal resistance of cells connected in a row = nr

### 20 3D CIRCUIT

Edge  $R_{eq} = \frac{7R}{12}$

Face  $R_{eq} = \frac{3R}{4}$

Body  $R_{eq} = \frac{5R}{6}$


### 21 WHEATSTONE BRIDGE

#### 1) Balanced WSB

Balanced Condition:  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$V_P = V_Q$$

Current through G = 0

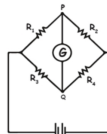

#### 2) Unbalanced WSB


$$V_P \neq V_Q$$

if  $\frac{R_1}{R_2} > \frac{R_3}{R_4}$

then  $V_Q > V_P$




### 22 METER BRIDGE

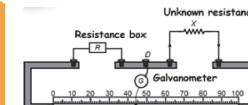

$$\frac{P}{Q} = \frac{R}{X} = \frac{l}{100 - l}$$

#### POTENTIOMETER

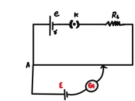

### 23 POTENTIOMETER

#### POTENTIAL

$$V_{AB} = \left( \frac{e}{r + R_p + R} \right) R$$

where, R = Resistance of potentiometer wire

#### POTENTIAL GRADIENT

$$x = \frac{V_{AB}}{L} = \frac{eR}{r + R_p + R} = \left( \frac{e}{r + R_p + R} \right) \frac{R}{L}$$



#### 1. COMPARISON OF CELL

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$
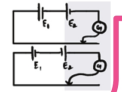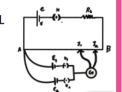
#### 2. BOTH BATTERIES ARE CONNECTED TOGETHER


(Once with some polarity then with opposite polarity)

$$\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2}$$



## 24 POTENTIOMETER
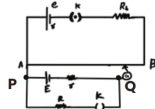
### 3. CALCULATION OF INTERNAL RESISTANCE



$$r = R \left( \frac{E}{V} - 1 \right) = R \left( \frac{l_1}{l_2} - 1 \right)$$

$E = V_{PQ}$  when key is open

$V = V_{PQ}$  when key is close

## 25 HEATING EFFECT OF ELECTRIC CURRENT

### POWER

$$P = \frac{dH}{dt} = VI = \frac{V^2}{R} = I^2R$$

### ELECTRIC KETTLE

Time taken for first coil -  $t_1$ , time taken for second coil -  $t_2$

If they are connected in series

$$t_s = t_1 + t_2$$

If they are connected in parallel

$$t_p = \frac{t_1 t_2}{t_1 + t_2}$$

### BULB

$$P_{\text{rated}} = \frac{V_{\text{rated}}^2}{R} \Rightarrow R = \frac{V_{\text{rated}}^2}{P_{\text{rated}}}$$

### CONNECTED IN SERIES



$$P_{\text{dissipated}} = I^2R$$

$$P_{\text{dissipated}} \propto R$$

$$\text{Brightness} \propto R$$

## 26 HEATING EFFECT OF ELECTRIC CURRENT

$$V_1 P_1 \quad V_2 P_2$$

$$P_{\text{dissipated}} \propto \frac{(V_{\text{rated}})^2}{P_{\text{rated}}}$$

$$P_d (\text{brightness}) \propto \frac{1}{P_{\text{rated}}}$$



If  $(P_1) > (P_2) > (P_3)$ , then  $P_{d1} < P_{d2} < P_{d3}$   
Brightness :  $B_3 > B_2 > B_1$

### CONNECTED IN PARALLEL

$$V_1 P_1 \quad V_2 P_2$$

$$P_{\text{rated}} = \frac{(V_{\text{rated}})^2}{R}$$

$$P_d = \frac{V^2}{R} \Rightarrow P_d \propto \frac{1}{R}$$


$$\Rightarrow P_d (\text{brightness}) \propto \frac{1}{\left( \frac{(V_{\text{rated}})^2}{P_{\text{rated}}} \right)^2} \Rightarrow P_{\text{brightness}} \propto \frac{P_{\text{rated}}}{(V_{\text{rated}})^2}$$

$$P_d (\text{brightness}) \propto P_{\text{rated}}$$

if  $(P_1)_R > (P_2)_R$

$\Rightarrow \text{Brightness } (P_d)_1 > (P_d)_2$

## 27 HEATING EFFECT OF ELECTRIC CURRENT

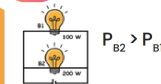

$$P_{B2} > P_{B1}$$

### COMBINATION OF BULBS

#### SERIES

$$P_1 \quad P_2$$

$$\text{TOTAL POWER}$$

$$P = \frac{P_1 P_2}{P_1 + P_2}$$

#### PARALLEL

$$P = P_1 + P_2$$

## 28 HEATING EFFECT OF ELECTRIC CURRENT

### FUSED BULB



If bulb 2 is fused then,

for bulb 3	for bulb 1
R ↓	V ↓
V ↑	P ↓
P ↑	B ↓
B ↓	

If bulb is added in parallel:-  
for example if bulb 3 is added in parallel to 2 then

for bulb 3	for bulb 1
R ↓	V ↑
V ↓	P ↑
P ↓	B ↑
B ↓	

## 29 CONVERSION OF GALVANOMETER

### Current sensitivity

$$S_i = \frac{\theta}{I}$$

where,  $\theta$  = angle of deflection in galvanometer  
 $I$  = Corresponding current in galvanometer

Unit:  $\frac{\text{divisions}}{\text{ampere}}$  or  $\frac{\text{rad}}{\text{A}}$


### Voltage sensitivity

$$S_v = \frac{\theta}{V}$$

where,  $\theta$  = angle of deflection in galvanometer  
 $V$  = corresponding voltage across galvanometer

Unit:  $\frac{\text{divisions}}{\text{voltage}}$  or  $\frac{\text{rad}}{\text{V}}$

### GALVANOMETER TO AMMETER

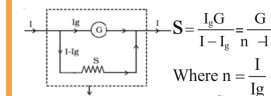


$$\text{Where } n = \frac{I}{I_g}$$

$$\text{RESISTANCE OF AMMETER } R = \frac{GS}{G + S}$$

RESISTANCE OF IDEAL AMMETER = 0

### GALVANOMETER TO VOLTMETER

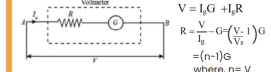

$$\text{RESISTANCE OF VOLTMETER} = G + R$$

RESISTANCE OF IDEAL VOLTMETER =  $\infty$