

# CAPACITOR



## 1 Capacitor



Capacitor is a passive device of the circuit which stores electrical energy or charge. It is also known as **condenser**.

$$C = \frac{Q}{V} \quad \text{or} \quad C = \frac{\epsilon_0 A}{d}$$

Capacitance is measured in **Farad (F)**

**Q** = Charge


**A** = Area

**V** = Voltage

**d** = Diameter

## 2 Combination

### i Series

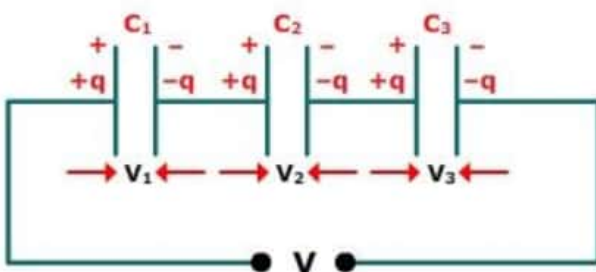

- Charge stored on each capacitor is same and equal to the magnitude of the charge, which comes from the battery..

$$Q = q_1 = q_2 = q_3$$


- The sum of voltage across the individual capacitor is equal to the voltage of the battery.

$$V = V_1 + V_2 + V_3$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

- Equivalent capacitance of the capacitor is always less than the smallest value of the capacitance of the capacitor in the circuit.

### ii Parallel

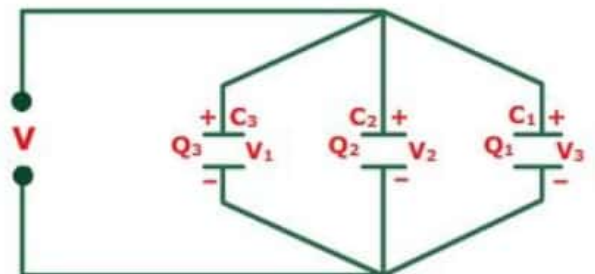

- The Voltage across each capacitor is the same, and it is equal to the voltage of the battery.

$$V = V_1 = V_2 = V_3$$

- The sum of the charge stored on an individual capacitor is equal to the magnitude of the charge, which comes from the battery.

$$Q = q_1 + q_2 + q_3$$

$$C_{eq} = C_1 + C_2 + C_3$$

- Equivalent capacitance of the capacitor is always greater than the largest value of the capacitance of the capacitor in the circuit.

