
GROUPING OF CELLS ?

CELLS IN SERIES

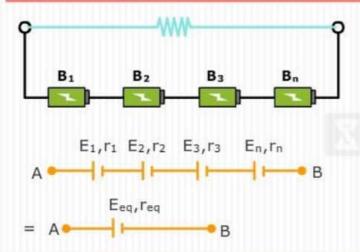

Equivalent EMF

$$E_{eq} = E_1 + E_2 + \dots + E_n$$

Equivalent internal resistance


$$r_{eq} = r_1 + r_2 + r_3 + r_4 + \dots r_n$$

In n cells each of emf E are arranged in series and if r is internal resistance of each cell, then the total emf is equal to

and, current in the circuit, $I = \frac{nE}{R + nr}$

$$I = \frac{nE}{R + nr}$$

CELLS IN PARALLEL

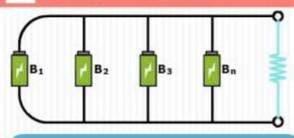


$$E_{eq} = \frac{E_1/r_1 + E_2/E_2 + \dots ... E_n/r_n}{1/r_1 + 1/r_2 + \dots + 1/r_n}$$
1 1 1 1 1

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

If m cells, each of emf E and internal resistance r be connected in parallel and if this combination is connected to an external resistance (R) then the emf of the circuit = E.

internal resistance of the circuit = $\frac{\Gamma}{m}$

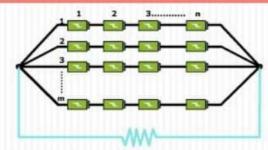and
$$I = \frac{E}{R + \frac{r}{m}} = \frac{mE}{mR + r}$$



n = number of rows

m = number of cells in each row

Current
$$I = \frac{mE}{R + \frac{mr}{p}}$$

for maximum current nR = mr

ELECTRICAL POWER

Power,
$$P = \frac{V.dq}{dt} = VI = I^2 R = \frac{V^2}{R}$$

Work, W = VIt =
$$I^2 Rt = \frac{V^2}{R} t$$

Heat,
$$H = I^2 Rt Joule = \frac{I^2 Rt}{4.2}$$
 calorie

