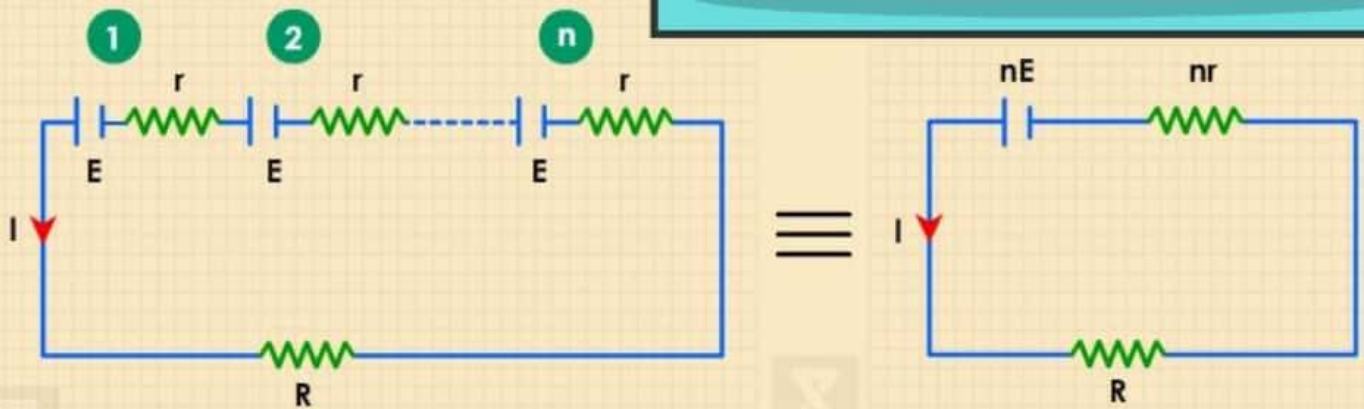




CELLS AND ELECTRIC POWER

COMBINATIONS OF CELLS

1 CELL IN SERIES




- ➔ Net EMF of the cells = nE ,
- ➔ Total internal resistance = nr ,
- ➔ Hence total resistance of the circuit = $nr + R$,

$$I = \frac{\text{net EMF}}{\text{Total Resistance}} = \frac{nE}{nr + R}$$

Case I If $nr \ll R$, then $I \cong nE/R$ i.e. current obtained from the cells is approximately equal to **n times** the current obtained from a single cell.

Case II If $nr \gg R$, then $I \cong nE/nr = E/r$ i.e. current obtained from the combination of n cells is nearly **the same** as obtained from a single cell.

2 CELL IN PARALLEL

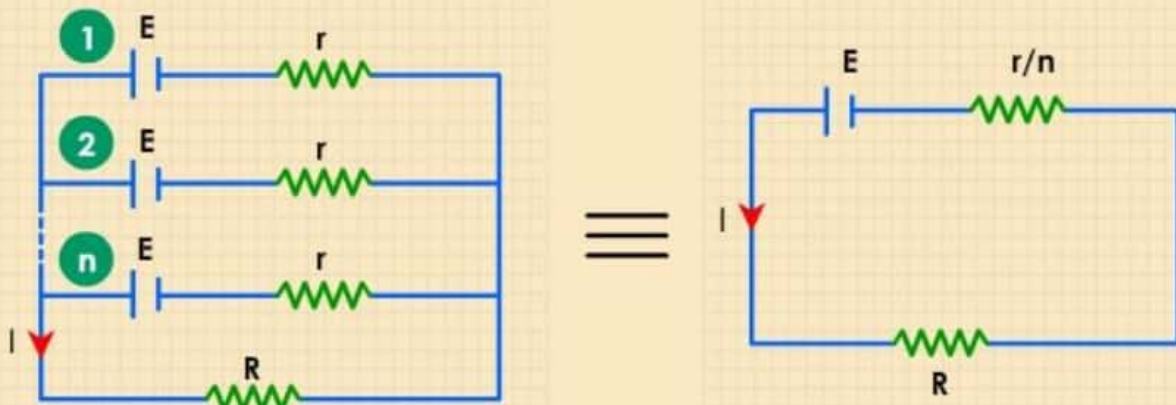

When E.M.F's and internal resistance of all the cells are equal


- E.M.F of battery = E.
- Total internal resistance of the combination of n cells = r/n
- Total resistance of the circuit = (r/n) + R

$$I = \frac{\text{net E.M.F}}{\text{Total Resistance}} = \frac{E}{(r/n)+R} = \frac{nE}{r+nR}$$

Case I If $r \ll R$, the $I \cong nE/nR = E/R$; then total current obtained from combination is approximately equal to current given by one cells only.


Case II If $r \gg R$, then $I \cong nE/r$; then total current is approximately equal to n times the current given by one cell.

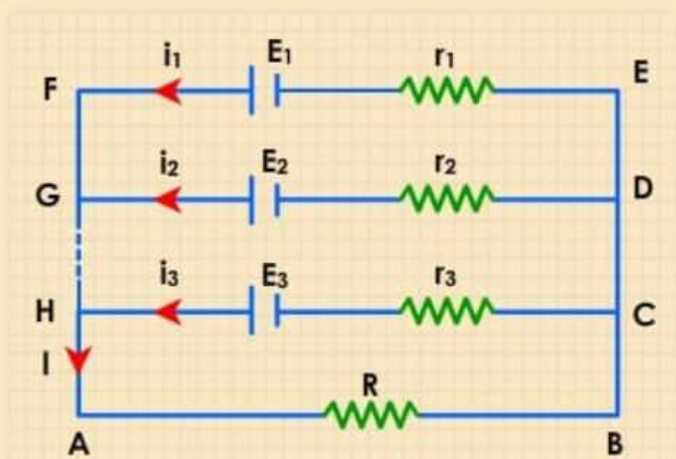When E.M.F's and internal resistance of all the cells connected in parallel are different



$$I = \frac{\sum_{i=0}^n \frac{E_i}{r_i}}{1+R \sum_i \frac{1}{r_i}} \text{ and } E_{eq.} = \frac{\sum \frac{E_i}{r_i}}{\sum \frac{1}{r_i}}, r_{eq.} = \frac{1}{\sum \frac{1}{r_i}}$$

3 CELL IN MIXED GROUPING

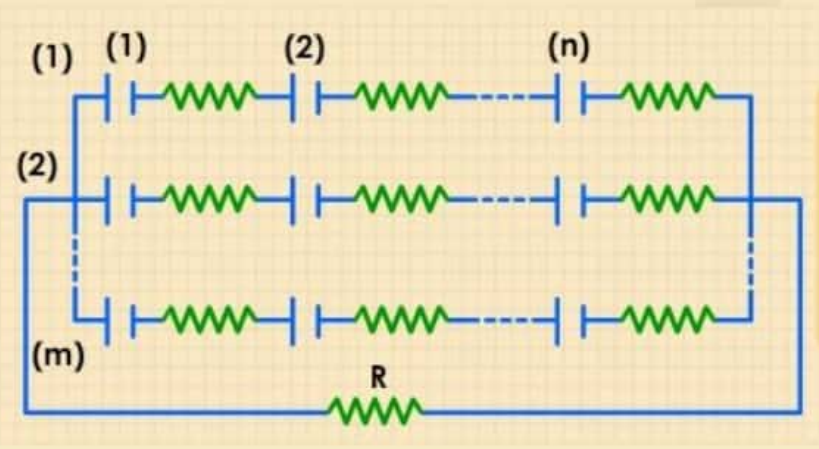

Total resistance of the circuit = $\left[\left(\frac{nr}{m} \right) + R \right]$

$$I = \frac{\text{net E.M.F}}{\text{Total Resistance}} = \frac{nE}{(nr/m)+R} = \frac{nmE}{nr+mR}$$

ELECTRICAL POWER

The energy liberated per second in a device is called its power. The electrical power P delivered by an electrical device is given by

$P = \frac{dq}{dt} V$
 $P = VI$
 $P = I^2R$
 $P = \frac{V^2}{R}$
 watt