
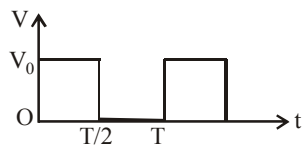


### Diagram Based Questions :

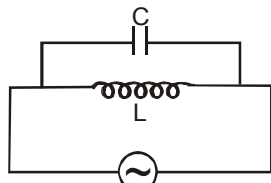1. The r.m.s. value of potential difference  $V$  shown in the figure is




- (a)  $V_0$  (b)  $V_0/\sqrt{2}$   
 (c)  $V_0/2$  (d)  $V_0/\sqrt{3}$
2. For the circuit shown in the fig., the current through the inductor is  $0.9\text{ A}$  while the current through the condenser is  $0.4\text{ A}$ . Then




$$V = V_0 \sin \omega t$$

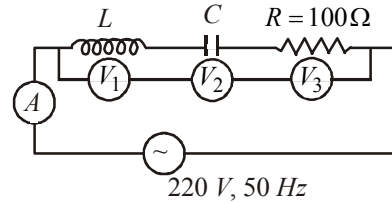
- (a) current drawn from source  $I = 1.13\text{ A}$   
 (b)  $\omega = 1/(1.5 LC)$   
 (c)  $I = 0.5\text{ A}$   
 (d)  $I = 0.6\text{ A}$
3. In the given circuit the reading of voltmeter  $V_1$  and  $V_2$  are  $300\text{ V}$  each. The reading of the voltmeter  $V_3$  and ammeter  $A$  are respectively



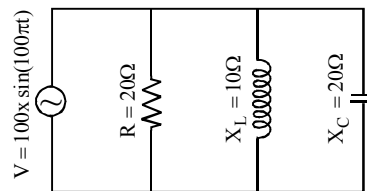- (a)  $150\text{ V}$  and  $2.2\text{ A}$  (b)  $220\text{ V}$  and  $2.0\text{ A}$   
 (c)  $220\text{ V}$  and  $2.0\text{ A}$  (d)  $100\text{ V}$  and  $2.0\text{ A}$
4. In the given circuit, the current drawn from the source is



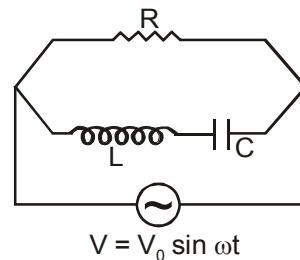- (a)  $20\text{ A}$  (b)  $10\text{ A}$   
 (c)  $5\text{ A}$  (d)  $5\sqrt{2}\text{ A}$
5. The current in resistance  $R$  at resonance is



- (a) zero  
 (b) minimum but finite  
 (c) maximum but finite  
 (d) infinite

# Solution

1. (b)  $V_{\text{rms}} = \sqrt{\frac{(T/2)V_0^2 + 0}{T}} = \frac{V_0}{\sqrt{2}}$ .
2. (c) The current drawn by inductor and capacitor will be in opposite phase. Hence net current drawn from generator  
 $= I_L - I_C = 0.9 - 0.4 = 0.5$  amp.
3. (b) As  $V_L = V_C = 300$  V, resonance will take place  
 $\therefore V_R = 220$  V  
Current,  $I = \frac{220}{100} = 2.2$  A  
 $\therefore$  reading of  $V_3 = 220$  V  
and reading of  $A = 2.2$  A
4. (d) Current,  $I = \frac{V}{Z}$
5. (c) At resonance  $X_L = X_C \Rightarrow Z = R$  & current is maximum but finite, which is  $I_{\text{max}} = \frac{E}{R}$ , where E is applied voltage.