

# Alternating Current (AC)

- Assertion (A):** In a series LCR circuit at resonance, the voltage across the capacitor or inductor may be more than the applied voltage.

**Reason (R):** At resonance in a series LCR circuit, the voltages across inductor and capacitor are out of phase.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** Average power consumed in an ac circuit is equal to average power consumed by resistors in the circuit.

**Reason (R):** Average power consumed by capacitor and inductor is zero

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** Peak voltage across the resistance can be greater than the peak voltage of the source in an series LCR circuit.

**Reason (R):** Peak voltage across the inductor can be greater than the peak voltage of the source in an series LCR circuit.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** The power rating of an element in AC circuit refers to average power rating.

**Reason (R):** A given value for AC voltage or current is usually its average value.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** Average power consumed in a circuit is never negative.

**Reason (R):** Instantaneous power is always positive.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** At an airport, a person is made to walk through the doorway of a metal detector.

**Reason (R):** Metal detector works on the principle of resonance in AC circuits.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false
- Assertion (A):** Smaller the band width, sharper the resonance and easier it is to tune an LCR circuit.

**Reason (R):** Resonant frequency is arithmetic mean of half power frequencies.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
(3) (A) is true but (R) is false  
(4) Both (A) and (R) are false



8. **Assertion (A):** At resonance in AC circuits current and emf are in phase.

**Reason (R):** At resonance in AC circuits, current is maximum.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false

9. **Assertion (A):** At frequency greater than resonant frequency, circuit is inductive in nature.

**Reason (R):** Reciprocal of reactance is called susceptance.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false

10. **Assertion (A):** If the resistance of a series resonant LCR circuit is decreased, then the peak current versus frequency graph will be taller and narrower.

**Reason (R):** If the resistance of a series resonant LCR circuit decreased, then its resonance will be unaffected.


- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false

11. **Assertion (A):** The impedance of series L-C-R circuit can be greater, equal or less than the resistance.

**Reason (R):** The minimum impedance of series LCR circuit depends over angular frequency of applied emf.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false

12.

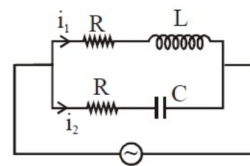

**Assertion (A):** Current  $i_1$  &  $i_2$  can not be in same phase.

**Reason (R):** If  $X_L = X_C$ ,  $i_1$  &  $i_2$  may be in same phase.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false


13. **Assertion (A):** A capacitor of suitable capacitance can be used in an A.C. circuit in place of the choke coil.

**Reason (R):** A capacitor blocks D.C. and allows A.C. only.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)
- (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)
- (3) (A) is true but (R) is false
- (4) Both (A) and (R) are false

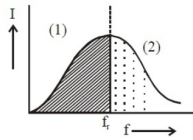
14. **Assertion (A):** For series RLC network, power factor of circuit in region (1) is positive and in region (2) is negative.

**Reason (R):** Overall nature of circuit in region (1) is inductive while in region (2) is capacitive.



- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

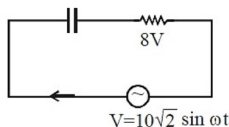15. **Assertion (A):** KVL rule is also being applied in AC circuit shown below.



**Reason (R):**  $V_C$  in the circuit = 2V.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

16. **Assertion (A):** When frequency is greater than resonance frequency in a series LCR circuit, it will be an inductive circuit.

**Reason (R):** Resultant voltage will lead the current.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

17. **Assertion (A):** The moving coil ammeters or voltmeters can't be employed to measure alternating current or voltage respectively.

**Reason (R):** If an alternating current is passed through a moving coil ammeter or voltmeter, then the average value of torque experienced by the coil is zero.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

18. **Assertion (A):** In ac supply we cannot feel any fluctuations of current in bulbs.

**Reason (R):** House hold ac supply has very low frequency.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

19. **Assertion (A):** 220V, 50 Hz appliance implies that potential difference in bulb is always 220V.

**Reason (R):** Every appliance is specified with its peak tolerable voltage.

- (1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)  
 (2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)  
 (3) (A) is true but (R) is false  
 (4) Both (A) and (R) are false

**20. Assertion (A):** Transformer does not work on dc

**Reason (R):** dc neither changes in magnitude nor in direction.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

**21. Assertion (A):** Choke coil is preferred over a resistor to adjust current in an ac circuit.

**Reason (R):** Power factor for inductance is zero.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

**22. Assertion (A):** The divisions are equally marked on the scale of ac ammeter.

**Reason (R):** Heat produced is directly proportional to the current.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

**23. Assertion (A):** An electric lamp is connected in series with a long solenoid of copper with air core and then connected to ac source. If an iron rod is inserted in solenoid, the lamp will become dim.

**Reason (R):** If an iron rod is inserted in solenoid, the inductance of solenoid increases.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

**24. Assertion (A):** For an electric lamp connected in series with a variable capacitor and ac source, its brightness increases with increase of capacitance.

**Reason (R):** Capacitive reactance decreases with increase in capacitance of capacitor.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

**25. Assertion (A):** In series RL ac circuit voltage leads the current.

**Reason (R):** In series LCR circuit current may lead the voltage.

(1) Both (A) & (R) are true and the (R) is the correct explanation of the (A)

(2) Both (A) & (R) are true but the (R) is not the correct explanation of the (A)

(3) (A) is true but (R) is false

(4) Both (A) and (R) are false

### ANSWER KEY

|             |           |           |           |           |           |          |          |          |          |           |           |           |           |           |           |           |           |           |           |           |
|-------------|-----------|-----------|-----------|-----------|-----------|----------|----------|----------|----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| <b>Que.</b> | <b>1</b>  | <b>2</b>  | <b>3</b>  | <b>4</b>  | <b>5</b>  | <b>6</b> | <b>7</b> | <b>8</b> | <b>9</b> | <b>10</b> | <b>11</b> | <b>12</b> | <b>13</b> | <b>14</b> | <b>15</b> | <b>16</b> | <b>17</b> | <b>18</b> | <b>19</b> | <b>20</b> |
| <b>Ans.</b> | 2         | 1         | 4         | 3         | 3         | 2        | 3        | 3        | 2        | 2         | 4         | 3         | 2         | 4         | 3         | 1         | 1         | 3         | 4         | 3         |
| <b>Que.</b> | <b>21</b> | <b>22</b> | <b>23</b> | <b>24</b> | <b>25</b> |          |          |          |          |           |           |           |           |           |           |           |           |           |           |           |
| <b>Ans.</b> | 1         | 4         | 1         | 1         | 2         |          |          |          |          |           |           |           |           |           |           |           |           |           |           |           |