



Alternating Current

ALTERNATING CURRENT

DC current



unidirectional current

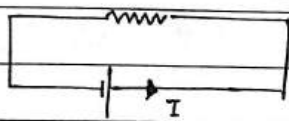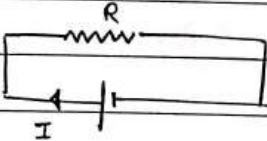


Variable DC source

it does not mean constant current, it means same direction.

A/c Current




Bi-directional current is called A/c

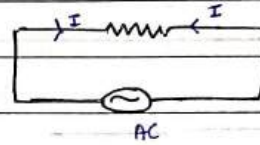


Q A current is varying from +5A to +15 Amp sinusoidally then this current is.

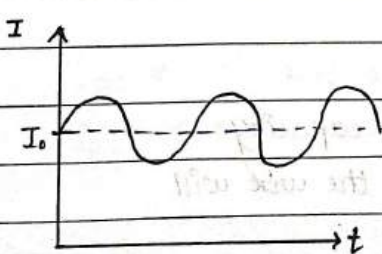a) AC

~~b) DC~~ because the current is always positive







D/C

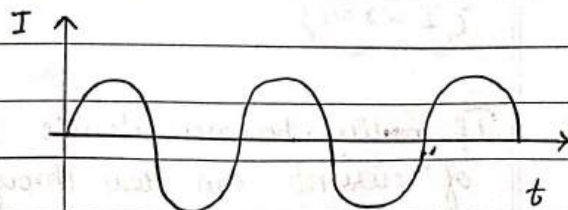

A/c

Sine wave A/c



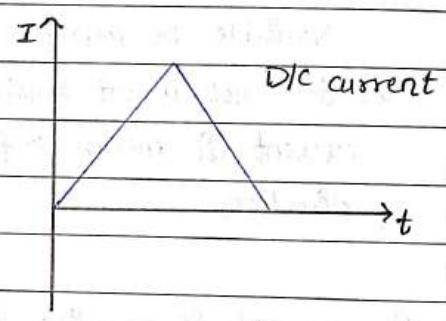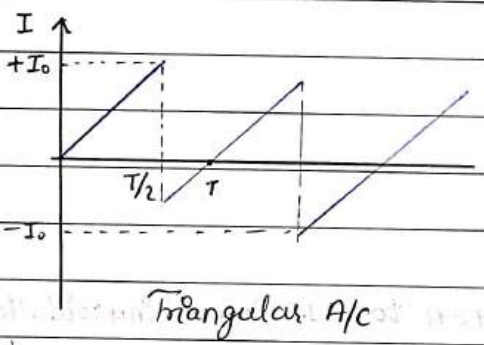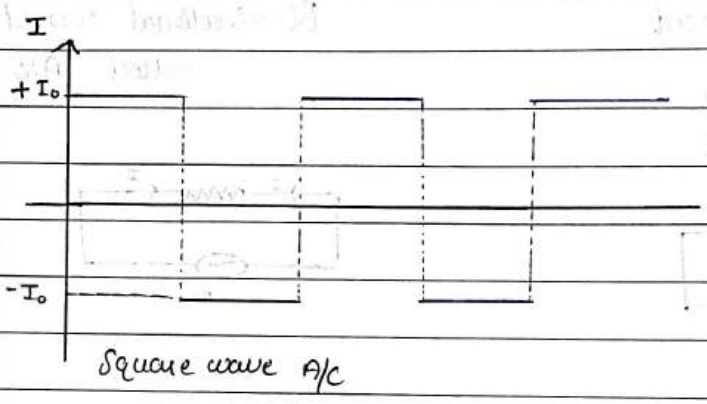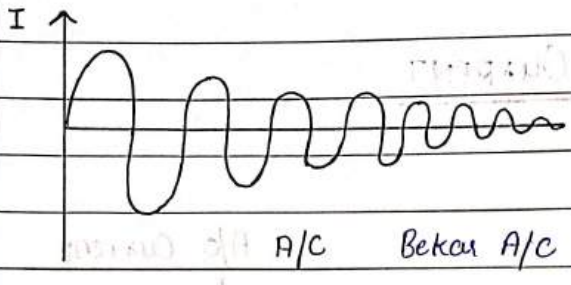

D/C flows through cross section area of wire
 ↳ use single wire



$I \propto r^{3/2}$

Q If radius becomes double then capacity of current can flow through the wire will

ANS $\frac{I_1}{I_2} = \frac{r_1^{3/2}}{r_2^{3/2}}$


$$\frac{I_1}{I_2} = \left(\frac{r}{2r}\right)^{3/2}$$

$$\frac{I_1}{I_2} = \frac{1}{(2)^{3/2}}$$

$$I_2 = I_1 (2)^{3/2}$$

$$I_2 = 2\sqrt{2} I_1$$

But A/C flows through surface area.

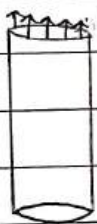

due to variable current

↳ magnetic flux would change

↳ ∴ high resistance will develop across the cross section area

↓
hence current prefer to go from surface area

↓
hence we prefer multivise connection for A/C

DISADVANTAGE OF D/C

D/C can't be supply over large distance

Power loss is maximum in transmission

D/C supply at constant voltage (can't be step-up and step-down)

$$I_{D/C} \propto r^{3/2} \text{ (cross section area)}$$

$$I_{A/C} \propto \text{surface area}$$

Disadvantage of A/C → skin effect and Corona discharge.




- 5) A/C can't be stored
- 6) DC can be stored

DC current is measured by moving coil galvanometer.
 A/C ($f=100\text{ Hz}$) can't be measured by moving coil galvanometer due to inertia.

Moving coil galvanometer	Hot wire ammeter
Torque on current carrying coil	Heat loss
Only DC can be measure	Both A/C & D/C can be measured.
$\theta \propto I$	$\theta \propto I^2$
Linear scale	Non linear scale

Find average value of $\sin(\omega t)$ in full cycle ?

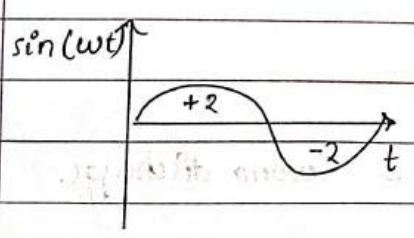Ans $\langle \sin \omega t \rangle = \frac{\int_0^T \sin \omega t \, dt}{\int_0^T dt} = \frac{-[\cos \omega t]_0^T}{\omega T} = \frac{-1}{\omega T} [\cos(\frac{2\pi}{T} \times T) - \cos 0]$
 $= \frac{-1}{\omega T} (1 - 1) = 0$



$$\langle \cos \omega t \rangle_{\text{full cycle}} = 0$$

$$\langle \sin \omega t \cdot \cos \omega t \rangle = 0$$

$$\langle \sin 2\omega t \rangle = 0$$

$$\sin(2\theta) = 2\sin\theta \cdot \cos\theta$$


$$\langle \sin(\omega t + \pi) \rangle = 0$$



full cycle

Find average of $\sin \omega t$ in half cycle.

$$\begin{aligned} \langle \sin \omega t \rangle_{\text{Half cycle}} &= \frac{\int_0^{T/2} \sin \omega t \, dt}{\int_0^{T/2} dt} = \frac{-[\cos \omega t]_0^{T/2}}{\omega (T/2)} = - \left[\frac{\cos(\frac{\omega T}{2}) - \cos 0}{\omega \times T/2} \right] \\ &= - \frac{[\cos \pi - 1]}{\frac{\omega T}{2}} \end{aligned}$$
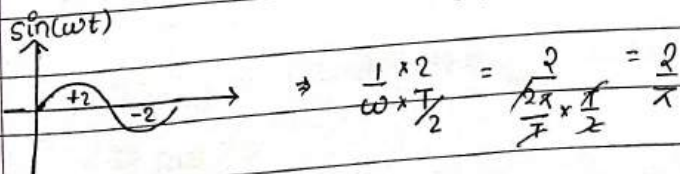
$$\text{MR}^* \quad \langle \sin \omega t \rangle_{\text{Half cycle}} = \frac{\int_0^{T/2} \sin \omega t \, d\omega t}{\int_0^{T/2} dt} = - \frac{[-1 - 1]}{\frac{\omega T}{2}} = \frac{2}{\pi}$$



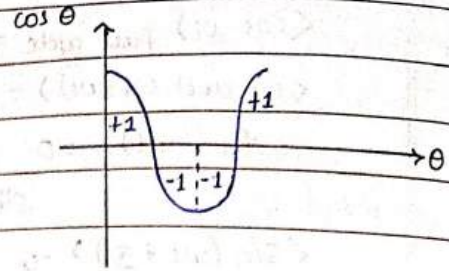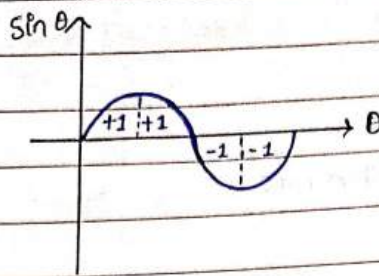

$$* \langle \cos(\omega t) \rangle_{\text{Half cycle}} = \frac{2}{\pi}$$

$$* \langle \sin^2(\omega t) \rangle_{\text{full cycle}} = \frac{1}{2}$$

$$* \langle \cos(\omega t) \rangle_{\text{full cycle}} = 0$$

$$* \langle \sin^2(\omega t) \rangle_{\text{Half cycle}} = \frac{1}{2}$$

$$* \langle \sin(\omega t) \rangle_{\text{Half cycle}} = \frac{2}{\pi}$$

$$\langle \cos^2(\omega t) \rangle_{\text{full/Half}} = \frac{1}{2}$$

$$* \langle \sin(\omega t) \rangle_{\text{full cycle}} = 0$$

$$\langle \sin^2(\omega t) \rangle = \frac{\int_0^T \sin^2(\omega t) dt}{\int_0^T dt}$$

$$\sin^2(\omega t) = \frac{1 - \cos(2\omega t)}{2}$$


$$\int_0^T \left(\frac{1}{2} - \frac{\cos(2\omega t)}{2} \right) dt = \int_0^T \frac{1}{2} dt - \int_0^T \frac{\cos(2\omega t)}{2} dt$$

$$\int_0^T dt$$

$$\Rightarrow \frac{\frac{1}{2} T}{T} = \frac{1}{2}$$

Q Avg value of $\sin(\omega t)$ in half cycle may be??

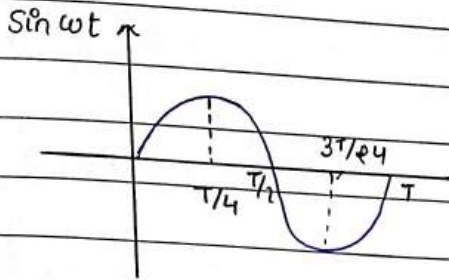- a) zero b) $2/\pi$ c) $1/\pi$ d) both (a) and b



$$\langle \sin(\omega t) \rangle_{\text{Half cycle}} = 0$$

when I consider from $\pi/4$ to $3\pi/4$

$$\langle \sin^2(\omega t) \rangle_{\text{full/half}} = \frac{1}{2}$$

$$\langle \sin(\omega t) \rangle_{\text{full}} = \langle \cos(\omega t) \rangle_{\text{half}} = 0$$

$$\langle \sin(\omega t) \cos(\omega t) \rangle_{\text{full}} = 0$$

$$\langle \sin(\omega t) \rangle_{\text{Half cycle}} = 2/\pi$$

ALTERNATING CURRENT [sinusoidal]

$$I = I_0 \sin(\omega t + \phi)$$

I_0 = maximum current (Peak current)

I = Instantaneous current

ω = Angular frequency

ϕ = Phase difference (initial)

R.M.S. current = root mean square current

$$I_{\text{RMS}} = \sqrt{\langle I^2 \rangle}$$

$$I_{\text{RMS}} = \sqrt{\langle I_0^2 \sin^2(\omega t + \phi) \rangle}$$

$$I_{\text{RMS}} = \frac{I_0}{\sqrt{2}}$$

$$\langle I \rangle_{\text{Half}} = \langle I_0 \sin(\omega t + \phi) \rangle_{\text{Half}} = I_0 \langle \sin(\omega t + \phi) \rangle_{\text{Half}} = \frac{2 I_0}{\pi}$$

$$\langle I \rangle_{\text{full}} = 0$$

Q Electricity bill me kiska paisa dete hai ?

a) current b) voltage

c) Power, ~~set~~ Heat

$$H = I_{DC}^2 R t \quad \text{--- ①}$$

$$\langle H \rangle = \langle I_{AC}^2 \rangle R t \quad \text{--- ②}$$

$$\text{①} = \text{②}$$

$$I_{DC}^2 R t = \langle I_{AC}^2 \rangle R t$$

$$I_{DC} = \sqrt{\langle I_{AC}^2 \rangle} = I_{RMS}$$

effective current of AC

virtual current

Hot wire ammeter

reads this current.

$$I_{DC} = I_{RMS}$$

Q The voltage of domestic AC is 220V. What does this represent.

1) Mean voltage 2) Peak voltage

3) Root mean voltage ~~4)~~ Root mean square voltage.

Q The equation of an alternating voltage is $v = 100\sqrt{2} \sin 100\pi t$ volt. The RMS value of voltage and frequency will be.

a) 100V, 50Hz b) 50V, 100Hz

c) 150V, 50Hz d) 200V, 50Hz

Ans $RMS = \frac{V_0}{\sqrt{2}} = \frac{100\sqrt{2}}{\sqrt{2}} = 100$

$$100\pi = 2\pi f$$

$$f = 50 \text{ Hz}$$

Q Equation of alternating current is given by $I = 10\sqrt{2} \sin(100\pi t + \frac{\pi}{6})$.
The time taken by current to reach the root mean square value from $t=0$ is t then the value of t is.

~~a)~~ $\frac{1}{200}$ s (b) $\frac{1}{250}$ s

c) $\frac{1}{200}$ s (d) $\frac{1}{800}$ s

Ans $I = \frac{I_0}{\sqrt{2}} = \frac{10\sqrt{2}}{\sqrt{2}} = 10$

$$10 = 10\sqrt{2} \sin(100\pi t + \frac{\pi}{6})$$

$$100\pi t + \frac{\pi}{6} = \frac{\pi}{4}$$

$$100\pi t = \frac{2\pi}{24 \times 12}$$

$$t = \frac{1}{1200}$$

Q In the AC current, the current is expressed as $I = 100 \sin 200\pi t$.
In this circuit the current rises from zero to peak value in time

~~a)~~ $\frac{1}{400}$ s (b) $\frac{1}{300}$ s

c) $\frac{1}{100}$ s (d) $\frac{1}{200}$ s

Ans $100 = 100 \sin 200\pi t$

$$200\pi t = \frac{\pi}{2}$$

$$t = \frac{1}{400}$$

Q The phase difference between current and voltage in term an AC circuits is $\frac{\pi}{4}$ radian. If the frequency of AC is 50 Hz, then the phase difference is equivalent to the time difference of,

- a) 0.75s b) 10.5ms
- ~~c) 2.5ms~~ d) 0.25ms

ANS $\frac{\Delta\phi}{2\pi} T = \Delta t$

~~MIT~~
 $\frac{\Delta\phi}{2\pi} = \frac{\Delta x}{\lambda} = \frac{\Delta t}{T}$

$$\Delta t = \frac{\pi}{4 \times 2\pi f} = \frac{1}{8} \times \frac{1}{50}$$

$$\Delta t = \frac{2.5 \times 1000 \times 10^{-3}}{400} = 2.5 \text{ms}$$

Q The peak value of an alternating emf $E = E_0 \sin \omega t$ is 10 volt and its frequency is 50 Hz.

At a time $t = \frac{1}{600}$ the instantaneous value of the emf is.

- 1) 1 volt 2) $5\sqrt{3}$ v
- ~~3) 5 volt~~ 4) 10V

ANS $E = 10 \sin 2\pi \times 50 \times \frac{1}{600}$

$$E = 10 \times \frac{1}{2} = 5V$$

Q The time required for a 50 Hz sinusoidal alternating current to change its value from zero to the rms value.

- a) $1.5 \times 10^{-2} \text{s}$ ~~b) $2.5 \times 10^{-3} \text{s}$~~
- c) 10^{-1}s d) 10^{-6}s

Ans


$$I = I_0 \sin(\omega t)$$

$$\frac{I_0}{\sqrt{2}} = I_0 \sin(2\pi f t)$$


$$2\pi f t = \frac{\pi}{4}$$

$$2\pi \times 50 t = \frac{\pi}{4}$$
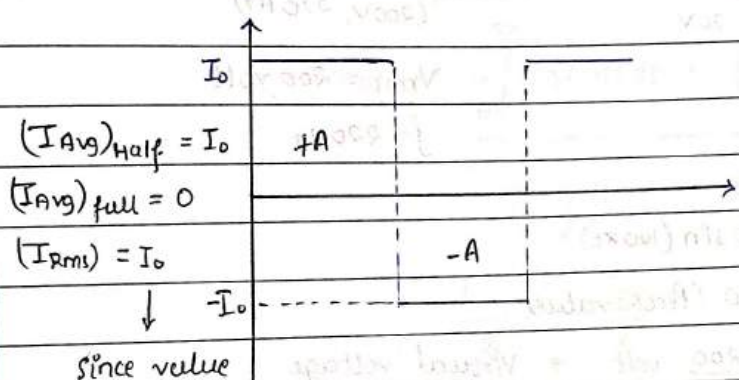
$$t = \frac{1000 \times 10^{-3}}{400} = 2.5 \times 10^{-3} \text{ s}$$



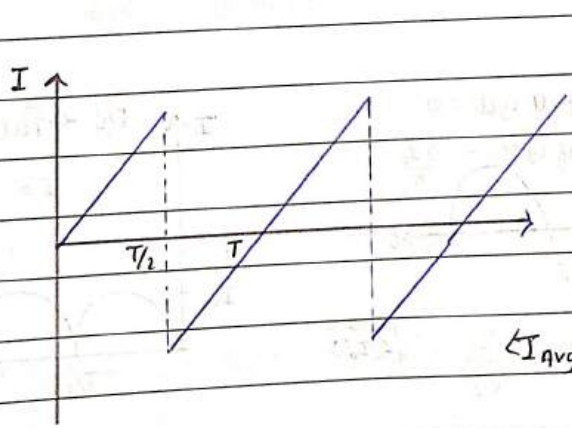since value of I_0 is same, only direction is changing. Square wave A/C



$$(I_{avg})_{half} = \frac{\int_0^{T/2} I \cdot dt}{\int_0^{T/2} dt}$$

$$= \frac{\frac{1}{2} \times \frac{T}{2} \times I_0}{\frac{T}{2}}$$

$$= \frac{I_0}{2}$$

$$I_{rms} = \frac{I_0}{\sqrt{3}}$$



If $I = 10 \sin(\omega t + \frac{\pi}{6})$ then find Avg Current

$\rightarrow \langle I \rangle_{full} = 0$

$\langle I \rangle_{half} = \frac{2I_0}{\pi} = \frac{20}{\pi}$

$\langle I \rangle_{rms} = \frac{10}{\sqrt{2}}$ Amp

Half/full

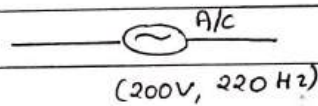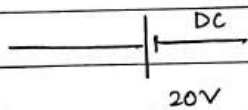

$V_{rms} = 200$ volt

$f = 220$ Hz





$V = 200 \sin(100\pi t)$

$V_0 = 200$ (Peak value)

$V_{rms} = \frac{200}{\sqrt{2}}$ volt \rightarrow Virtual voltage
 effective voltage

reading of voltmeter

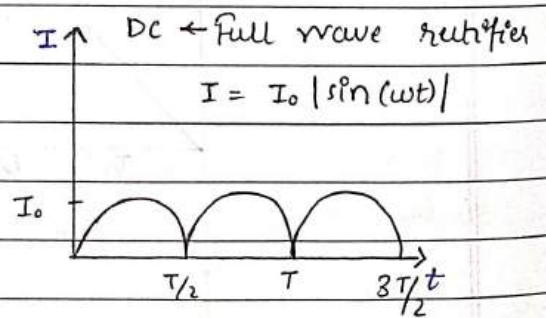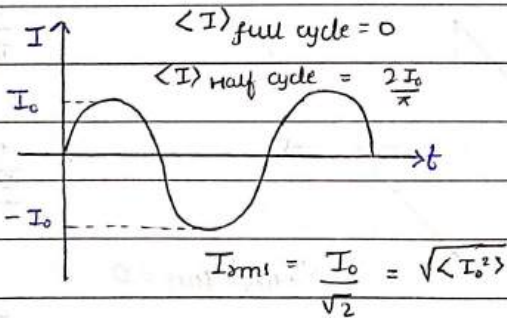$(V_{avg})_{half} = \frac{2 \times 200}{\pi}$




$\langle I \rangle_{half} = \frac{2I_0}{\pi}$

$\langle I \rangle_{full} = \frac{2I_0}{\pi}$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

DC (Half wave rectifier)

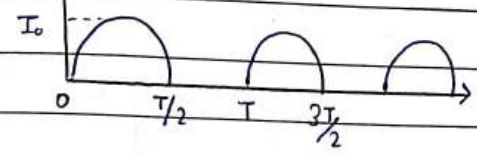

$$I = I_0 \sin(\omega t)$$

$$\langle I \rangle_{half} = \frac{2I_0}{\pi}$$

$$\langle I \rangle_{full} = \frac{I_0 \int_0^{T/2} \sin(\omega t) dt + \int_{T/2}^T 0 dt}{\int_0^T dt}$$

$$= \frac{2I_0}{\pi} = \frac{I_0}{\pi}$$

$$I_{rms} = \sqrt{\langle I^2 \rangle} = \frac{I_0}{\sqrt{2} \times \sqrt{2}} = \frac{I_0}{2}$$

A/C and D/C Mixture

$I = \overbrace{4}^{DC} + \overbrace{5 \sin(\omega t)}^{AC}$

$$\langle I \rangle_{full\ cycle} = \langle 4 + 5 \sin(\omega t) \rangle_{full\ cycle} = \langle 4 \rangle + 5 \langle \sin(\omega t) \rangle$$

$$= 4 + 5 \times 0 = 4 \text{ Ans}$$

$$\langle I \rangle_{half\ cycle} = \langle 4 + 5 \sin(\omega t) \rangle_{half\ cycle} = \langle 4 \rangle + 5 \langle \sin(\omega t) \rangle_{half\ cycle}$$

$$= 4 + 5 \times \frac{2}{\pi}$$

$$= 4 + \frac{10}{\pi}$$

$$I_{\text{RMS}} = ?$$

$$I^2 = (4 + 5 \sin(\omega t))^2$$

$$= 16 + 25 \sin^2(\omega t) + 40 \sin(\omega t)$$

$$\langle I^2 \rangle = \langle 16 + 25 \sin^2(\omega t) + 40 \sin(\omega t) \rangle$$

$$= \langle 16 \rangle + 25 \langle \sin^2(\omega t) \rangle + 40 \langle \sin(\omega t) \rangle$$

$$= 16 + 25 \times \frac{1}{2} + 0$$

$$\sqrt{\langle I^2 \rangle} = \sqrt{28.5}$$

$$I_{\text{RMS}} = \sqrt{\frac{(4)^2 + (5)^2}{2}}$$

Eg: $I = a + b \cos(\omega t)$

$$I_{\text{RMS}} = \sqrt{\frac{a^2 + b^2}{2}}$$

$$I = a \sin(\omega t) + b \cos(\omega t)$$

$$I_{\text{RMS}} = \sqrt{\frac{a^2 + b^2}{2}}$$

Q An alternating current is given by $I = I_1 \cos \omega t + I_2 \sin \omega t$
The RMS value of current is given by

a) $\frac{I_1 + I_2}{\sqrt{2}}$ b) $\frac{(I_1 + I_2)^2}{2}$


~~c)~~ $\frac{\sqrt{I_1^2 + I_2^2}}{2}$ d) $\frac{\sqrt{I_1^2 + I_2^2}}{2}$

Q If instantaneous current in a circuit is given by $I = (2 + 3 \sin \omega t)^n$, then the effective value of resulting current is

a) $\sqrt{\frac{17}{2}}$ A b) $\sqrt{\frac{2}{17}}$ A $I_{rms} = \sqrt{\frac{2^2+3^2}{2}}$


c) $\sqrt{\frac{3}{\sqrt{2}}}$ A d) $\sqrt{2\sqrt{2}}$ $3\sqrt{2}$ A $= \sqrt{\frac{4+9}{2}} = \sqrt{\frac{17}{2}}$ Amp

Q Find Avg current between 0 to 4 sec.

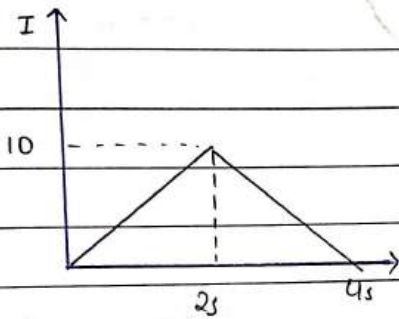

$$\langle I \rangle = \frac{\int_0^4 I dt}{\int_0^4 dt} = \frac{\frac{1}{2} \times 4 \times 10}{4} = 5 \text{ Amp}$$

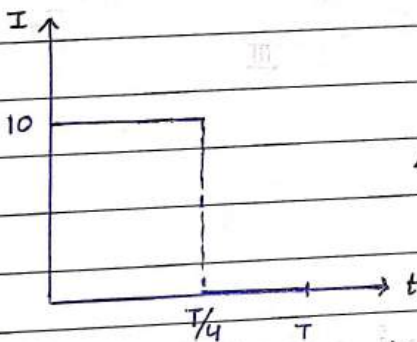Q Find Avg and rms current between (0 to T)



$$\langle I \rangle = \frac{\int_0^T I dt}{\int_0^T dt} = \frac{10 \times T/4}{T} = 2.5 \text{ Amp}$$

* $I_{rms} = \sqrt{\langle I^2 \rangle}$

$$\langle I^2 \rangle = \frac{\int_0^{T/4} I^2 dt + \int_{T/4}^T 0 dt}{\int_0^T dt}$$



$$\langle I^2 \rangle = \frac{100 \frac{T}{4} + 0}{T} = 25 \text{ Amp}$$

$$\sqrt{\langle I^2 \rangle} = \sqrt{25} = 5 \text{ Amp}$$


Imp

Graph of A/C Current

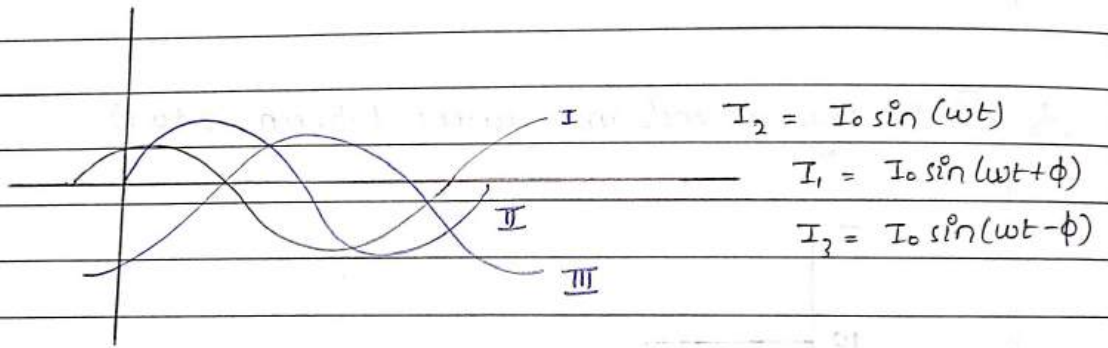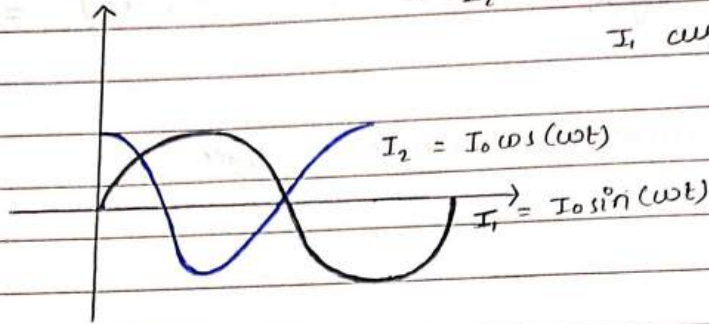I_2 current leads
 I_1 current by $\frac{\pi}{2}$



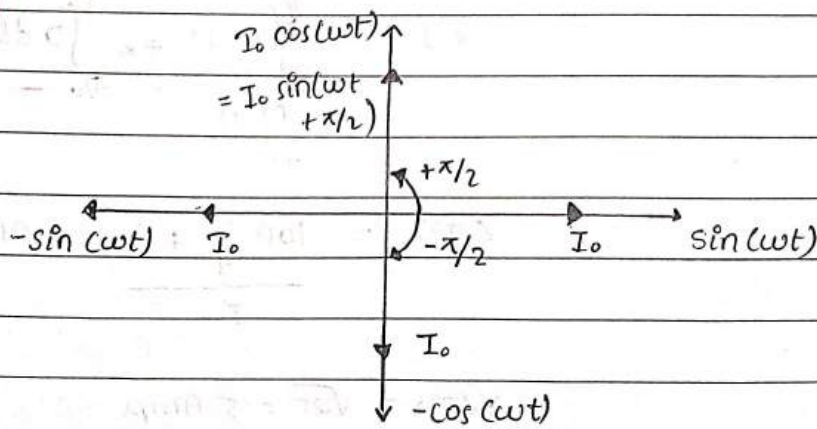Representation of AC current and voltage by Phasor diagram



$$I_1 = 4 \sin(\omega t + \frac{\pi}{6})$$


$$I_2 = 5 \cos(\omega t - \frac{\pi}{3})$$

$$I_3 = 4 \cos(\omega t - \frac{\pi}{2})$$

$$I_4 = 3 \cos(\omega t)$$

$$I_5 = -4 \sin(\omega t)$$
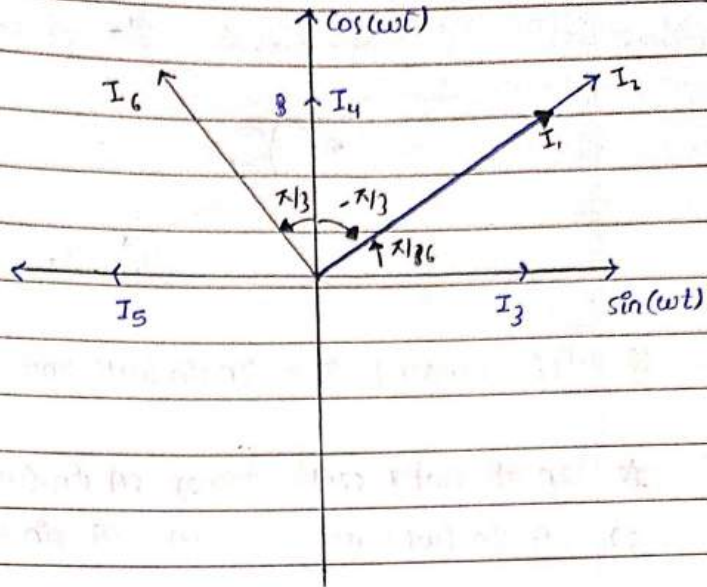
$$I_6 = 4 \cos(\omega t + \frac{\pi}{3})$$




Q Two AC are superimposed

$$I_1 = 3 \sin(\omega t)$$

$$I_2 = 3 \cos(\omega t + \frac{\pi}{6})$$

then find $I_1 + I_2$

ANS

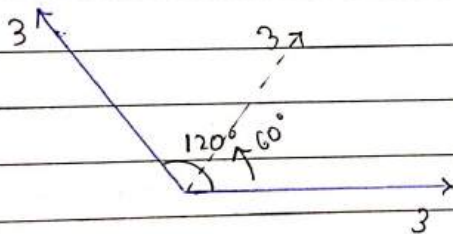


$$I_{net} = 3 \sin(\omega t + \frac{\pi}{3})$$

Q Two A/C are superimposed then find $I = I_1 + I_2$

$$I_1 = 4 \sin(\omega t - \frac{\pi}{6})$$
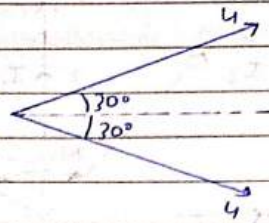
$$I_2 = 4 \sin \cos(\omega t - \frac{\pi}{3})$$



$$I_{net} = 4\sqrt{3} \sin(\omega t)$$


Q If current $I_1 = 3A \sin(\omega t)$ and $I_2 = 4A \cos(\omega t)$

1) $5A \sin(\omega t + 53^\circ)$


2) $5A \sin(\omega t + 37^\circ)$

3) $5A \sin(\omega t + 45^\circ)$

4) $5A \sin(\omega t + 30^\circ)$

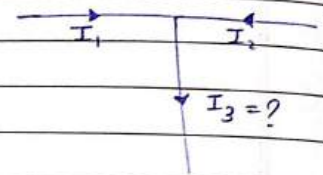

Ans

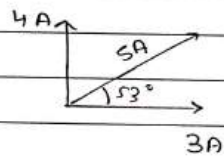


$$\Rightarrow 5A \sin(\omega t + 53^\circ)$$

Q $I_1 = 3 \sin(\omega t)$

$I_2 = 5 \cos(\omega t)$

find $I_1 + I_2$

Ans

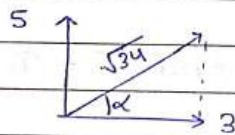

$$\tan \alpha = \frac{5}{3}$$

$$\alpha = \tan^{-1}\left(\frac{5}{3}\right)$$

$$I = \sqrt{34} \sin\left(\omega t + \tan^{-1}\left(\frac{5}{3}\right)\right)$$


A/C →	Important		
	Sinusoidal A/C	Square A/C	Triangular A/C
(I) Avg full	0	0	0
(I) Avg half	$\frac{2I_0}{\pi}$	I_0	$\frac{I_0}{2}$
(I) rms	$\frac{I_0}{\sqrt{2}}$	I_0	$\frac{I_0}{\sqrt{3}}$

Q Assertion (A): Average value of current in half cycle of an AC circuit cannot be zero.

Reason (R): For positive half cycle average value of current is i_0/π where i_0 is the peak value of current.

- a) Both A and R are true & R is the correct explanation of A
- b) Both A and R are true but R is not the correct explanation of A
- c) A is true but R is false
- ~~d) A is false and R is also false~~

A/C source across pure resistance

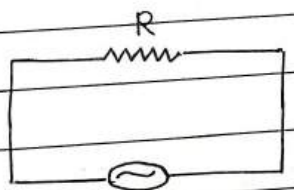

$E_B = E_0 \sin(\omega t)$
↑

Peak emf of battery.

Potential drop across Resistance = E_B (emf of battery)

$V_R = E_B$

$IR = E_0 \sin(\omega t)$

$I = \frac{E_0 \sin(\omega t)}{R}$

$$I = I_0 \sin(\omega t)$$

↓
peak current


$$x = A \sin(\omega t + \phi)$$

Phase
 $\phi \rightarrow$ initial phase


$$V_R = E_0 \sin(\omega t) \quad \text{--- ①}$$

$$I_R = I_0 \sin(\omega t) \quad \text{--- ②}$$

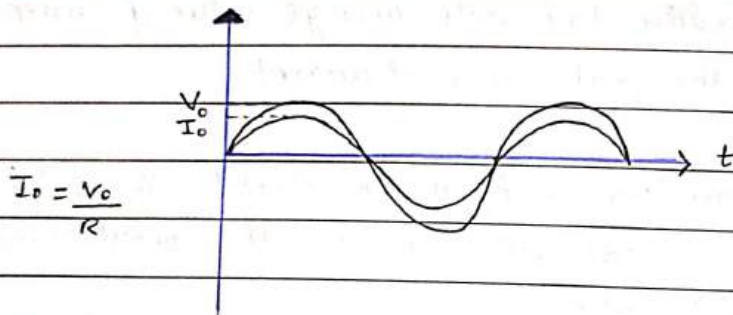Current and voltage are in same phase
in pure resistive circuit.



Phase diagram

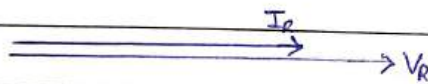

Power loss across resistance

$$P = V_t I_t$$

$$P = E_0 \sin(\omega t) I_0 \sin(\omega t)$$

$$P = E_0 I_0 \sin^2(\omega t)$$

$$\langle P \rangle = E_0 I_0 \langle \sin^2(\omega t) \rangle$$

$$\langle P \rangle = \frac{I_0 E_0}{2}$$

$$\langle P \rangle_{\text{loss}} = \frac{I_0^2 R}{2}$$


$$\langle P \rangle_{\text{loss}} = \left(\frac{I_0}{\sqrt{2}} \right)^2 R$$

$$\langle P \rangle_{\text{loss}} = I_{\text{RMS}}^2 R$$

$$\langle P \rangle_{\text{loss}} = \frac{E_{\text{RMS}}^2}{R} = E_{\text{RMS}} I_{\text{RMS}}$$

$$E_0 = I_0 R$$

$$E_{\text{RMS}} = I_{\text{RMS}} R$$

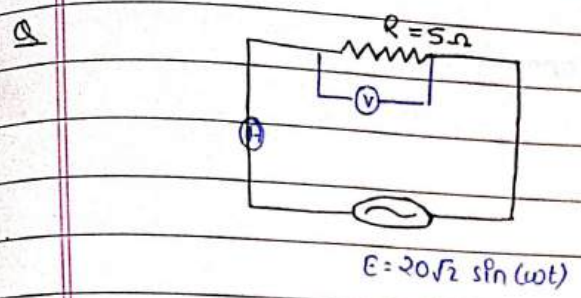

Ans $I_{RMS} = \frac{E_{RMS}}{R} = \frac{20\sqrt{2}}{\sqrt{2} \cdot 5} = 4A$

Reading of
Ammeter

Reading of Voltmeter = RMS voltage = $\frac{E_0}{\sqrt{2}} = 20V$ Ans


Power loss = $I_{RMS}^2 R$
= $16 \times 5 = 80W$ Ans

Q What is the approximate peak value of an alternating current producing four times the heat produced per second by a steady current of 2A in a resistor?

- a) 2.8A (b) 4.0A
- ~~c) 5.6A~~ (d) 8.0A

Ans $(P)_{AC} = 4 \times I^2 R$
 $I_{RMS}^2 R = 4 \times 4 R$
 $I_{RMS} = 4$
 $\frac{I_0}{\sqrt{2}} = 4$
 $I_0 = 4\sqrt{2}$
 $= 5.6A$ Ans

A/c Source across Pure Capacitor.

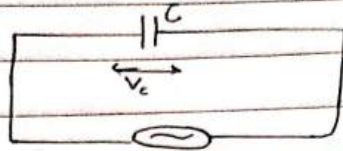

$$E_B = E_0 \sin(\omega t)$$

$$V_c = E_B$$

$$\frac{q}{C} = E_0 \sin(\omega t)$$

$$q = CE_0 \sin(\omega t)$$

$$I = \frac{dq}{dt}$$

$$I = \frac{dCE_0 \sin(\omega t)}{dt}$$

$$I = CE_0 \frac{d \sin(\omega t)}{dt}$$

$$I = CE_0 \cos(\omega t) \omega$$

$$I = CE_0 \omega \cos(\omega t)$$

$$I = \frac{E_0 \cos(\omega t)}{X_c}$$

$X_c =$ Capacitive Resistance Reactance

By comparing $X_c = \frac{1}{\omega C}$


$$I = \frac{E_0 \cos(\omega t)}{\frac{1}{\omega C}}$$

$$I_c = I_0 \cos(\omega t)$$

$$V_c = E_0 \sin(\omega t)$$


Current leads voltage by $\frac{\pi}{2}$

Phasor diagram

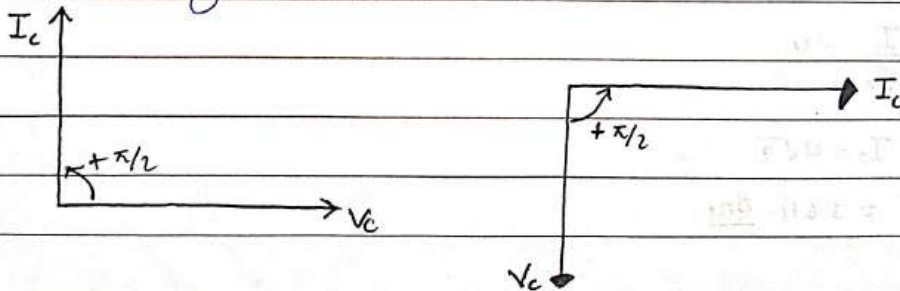

$$I_c = I_0 (\sin \omega t + \frac{\pi}{2})$$

$$V_c = V_0 (\sin \omega t)$$

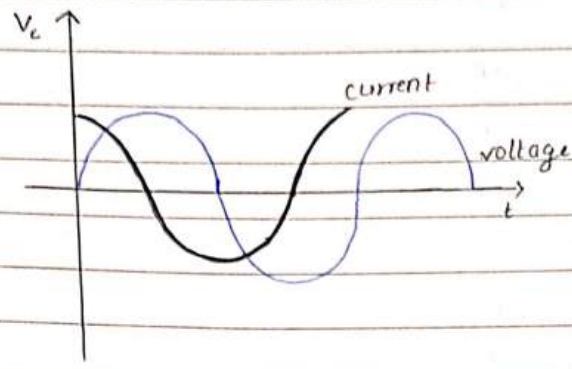


$$I_0 = \frac{E_0}{X_c}$$

$$I_{rms} = \frac{E_{rms}}{X_c}$$

$$X_c = \frac{1}{\omega C} \Omega$$

$$X_c \propto \frac{1}{C}$$

$$X_c \propto \frac{1}{\omega}$$

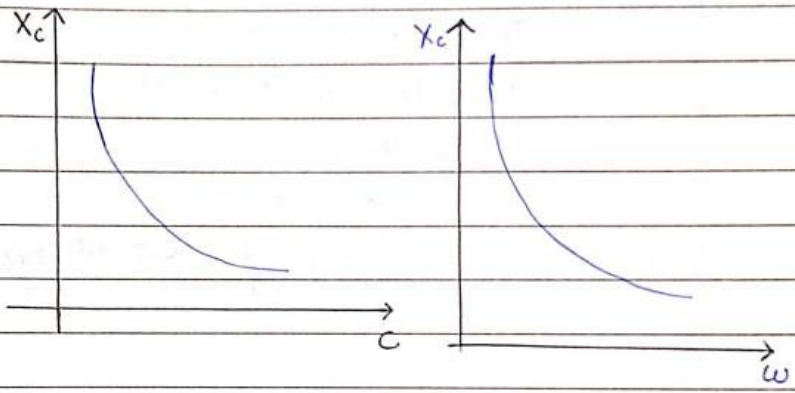

For DC source

$$f=0$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \infty$$

Capacitor will behave as broken wire for DC source



∴ Capacitor is DC filter,

For High frequency $f \propto 1/C$

$$X_c = \frac{1}{2\pi f C} \approx 0$$

Capacitor will behave as simple wire.

Q A $40 \mu\text{F}$ capacitor is connected to a 200V , 50Hz AC supply. The RMS value of the current in the circuit is nearly.

a) 1.7A b) 2.05A

c) 2.5A d) 25.1A

Ans $E_{\text{RMS}} = 200\text{V}$

$$E_{\text{RMS}} = I_{\text{RMS}} X_c$$

$$200 = I_{\text{RMS}} \frac{1}{\omega C}$$

$$I_{\text{RMS}} = 200 \times 2\pi f \times 40 \times 10^{-6}$$

$$I_{\text{RMS}} = 200 \times 2\pi \times 50 \times 40 \times 10^{-6}$$

$$= 4\pi \times 5 \times 4 \times 10^{-2}$$

$$= 0.16 \times 5\pi$$

$$= 0.8 \times \frac{22}{7} = \frac{17.6}{7} = 2.5\text{A}$$

* Q A small signal voltage $v(t) = V_0 \sin(\omega t)$ is applied across an ideal capacitor C .

a) Current $I(t)$ is in phase with voltage $v(t)$.

b) Current $I(t)$ leads voltage $v(t)$ by 180° .

c) Current $I(t)$ lags voltage $v(t)$ by 90° .

d) Over a full cycle the capacitor C does not consume any energy from the voltage source.

Ans Power loss in capacitor

$$P = V_e I_e$$


$$P = E_0 \sin(\omega t) \cdot I_0 \cos(\omega t)$$

$$\langle P \rangle = E_0 I_0 \langle \sin(\omega t) \cdot \cos(\omega t) \rangle$$

$$\langle P \rangle \text{ Avg Power loss in pure capacitor} = 0$$

Pure capacitive circuit is wattless circuit.

A/C source across pure inductor

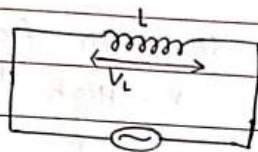

$L =$ self inductance

$$E_B = E_0 \sin(\omega t)$$

$$V_L = E_B$$

$$L \frac{dI}{dt} = E_0 \sin(\omega t)$$

$$\int dI = \int \frac{E_0 \sin(\omega t) dt}{L}$$

$$I = \frac{E_0}{L} \int \sin(\omega t) dt$$

$$I = \frac{-\cos(\omega t) E_0}{\omega L}$$

$$I = \frac{-E_0 \cos(\omega t)}{\omega L}$$

$$I = \frac{E_0 \sin(\omega t - \frac{\pi}{2})}{\omega L}$$

$$I = \frac{E_0 \sin(\omega t - \frac{\pi}{2})}{X_L}$$

$$X_L = \omega L$$


inductive reactance

$$V_L = E_0 \sin(\omega t)$$

$$I_L = I_0 \sin(\omega t - \frac{\pi}{2})$$

Voltage leads current by $\frac{\pi}{2}$

Phasor diagram

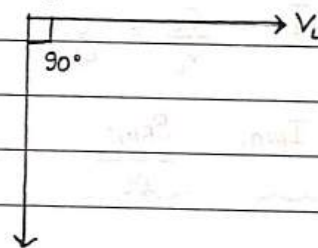


Inductive Reactance (X_L)

$$X_L = \omega L = 2\pi f L$$

$$X_L \propto \omega$$

$$X_L \propto L$$

$$X_L \propto f$$

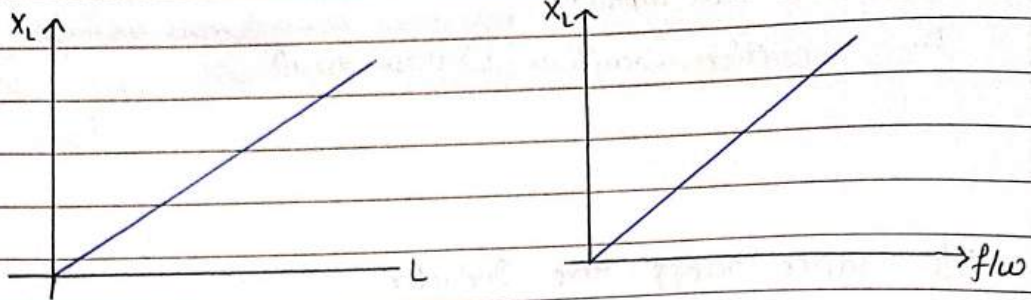

For D/C

$$f=0$$

$X_L = 0$ behave
as simple wire
for D/C

For high frequency A/C

$$X_L = \text{High} [f = \infty, X_L = \infty]$$



A/C filter

Power loss in inductor

$$P = V_e I_e$$

$$= I_0 E_0 \sin(\omega t) (-\cos(\omega t))$$

$$\langle P \rangle = -I_0 E_0 \langle \sin(\omega t) \cos(\omega t) \rangle = 0$$



Pure inductor is

also a wattless circuit

$$I_0 = \frac{E_0}{X_L} = \frac{E_0}{\omega L}$$

$$I_{RMS} = \frac{E_{RMS}}{\omega L}$$

Q Assertion (A): Inductive reactance of an inductor in DC circuit is zero.

Reason (R): Angular frequency of DC circuit is zero.


- a) Both A & R are true and R is the correct explanation of A
 b) Both A & R are true and R is not the correct explanation of A
 c) A is true but R is false
 d) A is false and R is also false.

Q Assertion (A): The alternating current lags behind the emf by a phase angle of $\pi/2$, when AC flows through an inductor.

Reason (R): The inductive reactance increases as the frequency of AC source decreases.

- a) Both A & R are true and R is the correct explanation of A
 b) Both A & R are true and R is not the correct explanation of A.
 c) A is true but R is false
 d) A is false and R is also false.

Series L-R Circuit

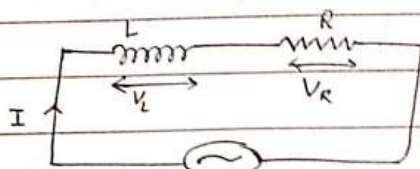



$$E = E_0 \sin(\omega t)$$

$$E_t = (V_L)_t + (V_R)_t$$

$$E_0 = (V_0)_R + (V_0)_L \quad \times$$

$$(I_R)_t = (I_L)_t$$

Phasor diagram.

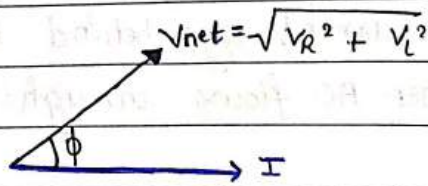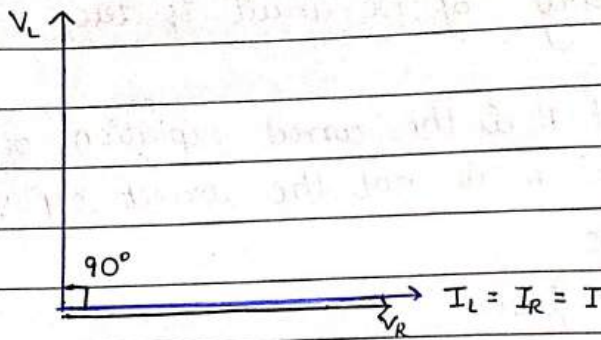

$$V_{net} = "IZ" = \sqrt{V_R^2 + V_L^2}$$

Complete
resistance

Impedance

$$IZ = \sqrt{I^2 R^2 + I^2 X_L^2}$$


$$Z = \sqrt{R^2 + X_L^2}$$

$$V_{net} = E_0 \sin(\omega t)$$

$$I = \frac{E_0}{Z} \sin(\omega t - \phi)$$

$$I_{rms} = \frac{E_{rms}}{Z}$$

$$I_0 = \frac{E_0}{Z}$$

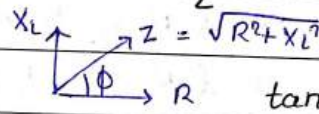

$$\tan \phi = \frac{V_L}{V_R} = \frac{X_L}{R}$$

$$\cos \phi = \frac{V_R}{V_{net}} = \frac{R}{Z}$$

Q An AC voltage is applied to a resistance R and an inductor L in series. If R and the inductor inductive reactance are both equal to 3Ω , the phase difference between the applied voltage and the current in the circuit is.

a) $\pi/6$ ~~b) $\pi/4$~~


c) $\pi/2$ (d) zero

Ans $\tan \phi = \frac{X_L}{R} = \frac{3}{3} = 1$

$$\phi = \pi/4$$

Q Impedence of the circuit shown in the figure is.

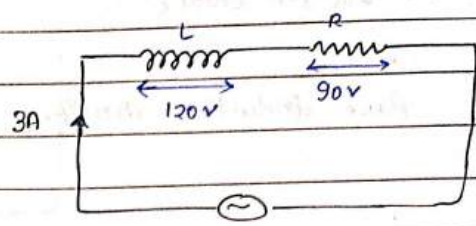- a) $100\ \Omega$ ~~b) $50\ \Omega$~~
 c) $30\ \Omega$ d) $40\ \Omega$.



Ans $V_L = 120V$
 $V_L = I X_L$
 $X_L = \frac{120}{3} = 40\ \Omega$

$$V = IR \qquad Z = \sqrt{R^2 + X_L^2}$$

$$90 = 3 \times R \qquad = 50\ \Omega$$

$$R = 30\ \Omega$$

Q A coil has resistance $30\ \Omega$ and inductive reactance $20\ \Omega$ at $50\ \text{Hz}$ frequency. If an AC source of $200\ \text{V}$, $100\ \text{Hz}$ is connected across the coil the current in the coil will be.

- a) $2\ \text{A}$ ~~b) $4\ \text{A}$~~
 c) $8.0\ \text{A}$ d) $20/\sqrt{13}\ \text{A}$

Ans X_L at $100\ \text{Hz} = 20 \times 2 = 40\ \Omega$ ($\because X_L \propto f$)
 $Z = \sqrt{R^2 + X_L^2} = 50\ \Omega$
 $I = \frac{V}{Z} = \frac{200}{50} = 4\ \text{A}$

Q In an AC source the current flowing is $I = 5 \sin(100t - \pi/2)$ Ampere and the potential difference is $V = 200 \sin(100t)$ volts. The power consumption is equal to.

- a) $20\ \text{W}$ ~~b) $0\ \text{W}$~~
 c) $1000\ \text{W}$ d) $40\ \text{W}$.


$$\Rightarrow I = 5 \sin(100t - \pi/2)$$

$$V = 200 \sin(100t)$$

↓

Pure Inductive circuit.

SERIES R-C circuit

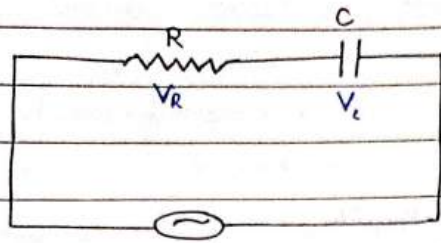


$$E = E_0 \sin(\omega t)$$

$$(V_R)_t + (V_C)_t = E_t$$

$$(V_R)_R + (V_C)_C = E_0 X$$


$$I = I_R = I_C$$

Phasor diagram

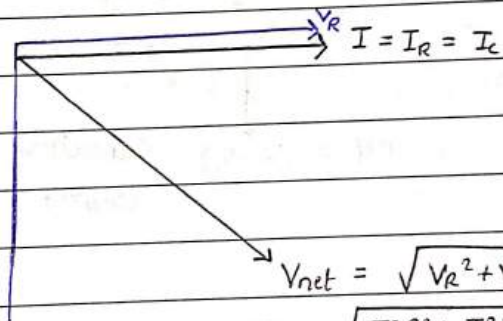


$$I Z = \sqrt{I^2 R^2 + I^2 X_C^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$

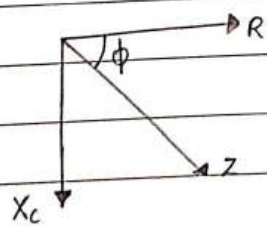
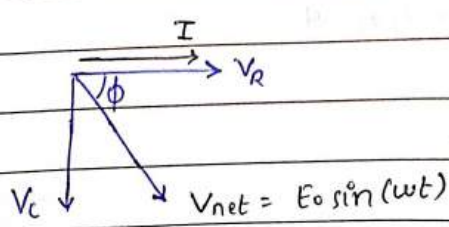
$$\tan \phi = \frac{V_C}{V_R} = \frac{X_C}{R}$$




$$V_{net} = E_0 \sin(\omega t)$$

$$I = I_0 \sin(\omega t + \phi)$$


$$I_0 = \frac{E_0}{Z}$$

Pure L-C circuit.

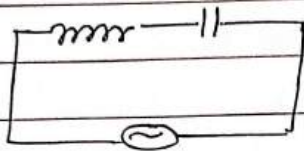


$$E = E_0 \sin(\omega t)$$


$$\langle P \rangle_{Avg} = 0$$

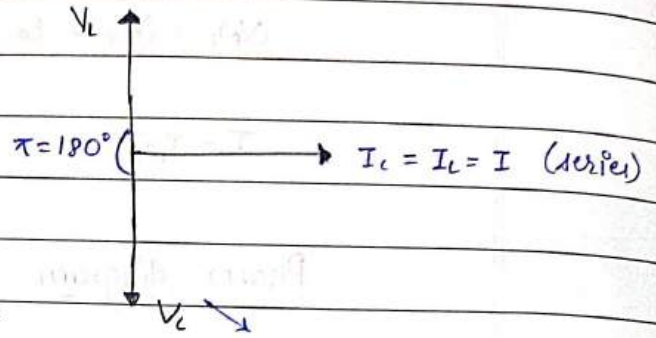

If $V_C > V_L$

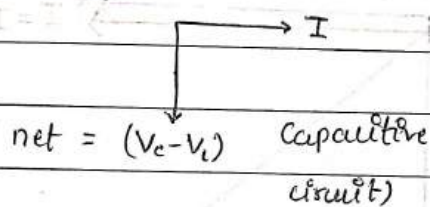


If $V_L > V_C$ (Inductive)

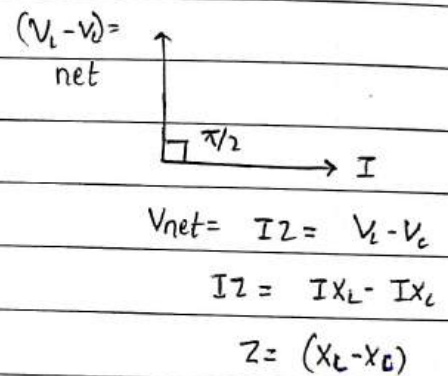

$$X_L = 10 \Omega \quad X_C = 6 \Omega$$

Q

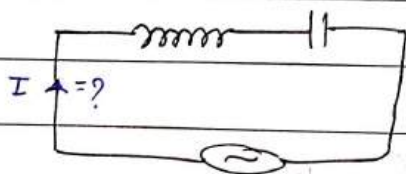

$$E = 20 \sin(\omega t)$$

Ans
$$I_{rms} = \frac{E_{rms}}{Z} = \frac{20}{\sqrt{2} \times 4} = \frac{5}{\sqrt{2}} \text{ A.}$$

Q A coil of self inductance L is connected in series with a bulb B and an AC source. Brightness of the Bulb decreases when.

- a) a capacitance of reactance $X_c = X_L$ is included in the same circuit
- b) an iron rod is inserted in the coil
- c) frequency of the AC source is decreased
- d) No of turns in the coil is reduced.

ANS If $X_L \uparrow$ $I \downarrow$ ($\because I = \frac{V}{X_L}$)

In 1st case $I = \frac{V}{Z}$ and $Z = X_c - X_L$

If $X_c = X_L$

$$Z = 0$$

$$I = \infty$$

In 2nd case

$$\mu_m > \mu_0$$

$$L = \mu_m I A n^2$$

$$L \uparrow$$

$$\uparrow X_L = \omega L \uparrow$$

$$P \quad I \downarrow$$

In 3rd case

$$X_L = \omega L$$

$$\downarrow \omega \uparrow \quad X_L \uparrow \downarrow$$

$$I \downarrow \uparrow$$

In fourth case


$$X_L = \omega L$$

$$\downarrow L = \mu_0 I A n^2 \downarrow$$

$$X_L \downarrow$$

$$I \uparrow$$

Series LCR circuit

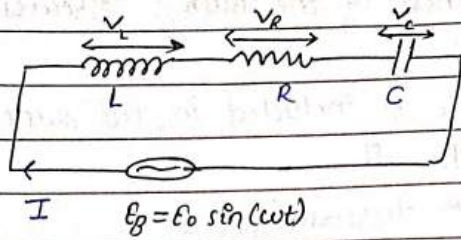

$$E_B = E_0 \sin(\omega t)$$

$$I_R \neq I_L \neq I_C \text{ (Wrong)}$$

$$I = I_R = I_L = I_C$$


$$E_B = (V_R)_t + (V_L)_t + (V_C)_t \text{ (at any time)}$$

energy conservation

supply
by battery

$$(E_0)_B = (V_0)_R + (V_0)_L + (V_0)_C \rightarrow \text{Wrong}$$

Peak of all at
different time.

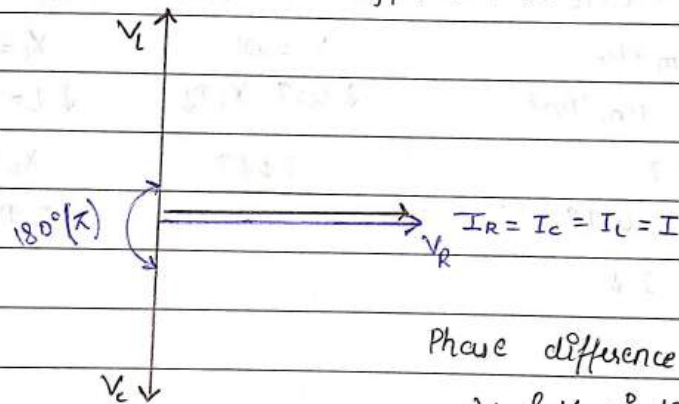


Phase difference between
 V_L & V_C is $180^\circ (\pi)$

Now three cases are possible

Case - 1

$V_L > V_C$ (Inductive LCR circuit)

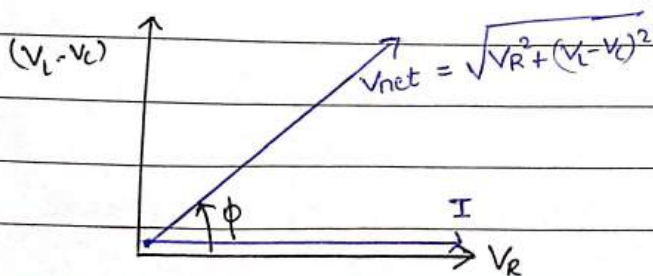

Let Z = total Resistance


Z = Impedance

$$IZ = \sqrt{IR^2 + (IX_L - IX_C)^2}$$

~~$$IZ = \sqrt{I^2 R^2 + (IX_L - IX_C)^2}$$~~

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Q

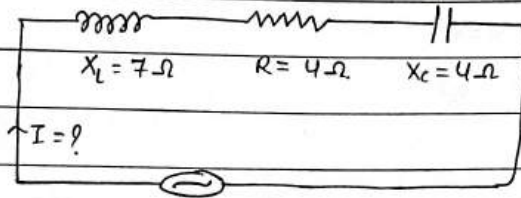

$$E = 20\sqrt{2} \sin(\omega t)$$

Ans
$$I_{RMS} = \frac{E_{RMS}}{Z} = \frac{20\sqrt{2}}{\sqrt{2} Z} = \frac{20}{Z}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{16 + 9} = 5\Omega$$

$$I_{RMS} = 4A \text{ Ans}$$

Case-2

$V_L < V_C$ (capacitive circuit)


$X_L < X_C$

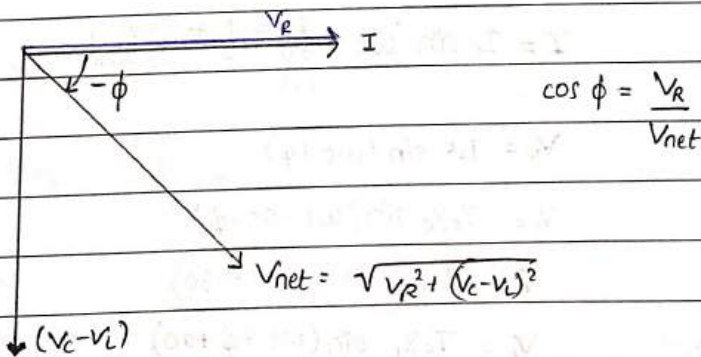

$$IZ = \sqrt{(IR)^2 + (IX_C - IX_L)^2}$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

Impedance triangle

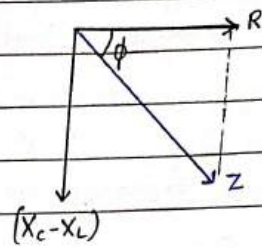


$$\tan \phi = \frac{|X_c - X_L|}{R}$$

$$\cos \phi = \frac{R}{Z}$$

$$I_0 = \frac{E_0}{Z}$$

$$I_{RMS} = \frac{E_{RMS}}{Z}$$

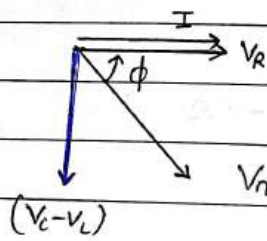

$$V_{net} = E_0 \sin(\omega t)$$

$$\cos \phi = \frac{R}{Z}$$

$$\tan \phi = \frac{|X_L - X_C|}{R}$$

Equation of current

$$I = I_0 \sin(\omega t + \phi) \quad \left[I_0 = \frac{E_0}{Z} \right]$$

$$V_R = I_0 R \sin(\omega t + \phi)$$

$$V_C = I_0 X_C \sin(\omega t - (90 - \phi))$$

$$V_C = I_0 X_C \sin(\omega t + \phi - 90)$$


$$V_L = I_0 X_L \sin(\omega t + \phi + 90)$$

Case-3

$$V_L = V_C \text{ (Pure resistive)}$$



Resonance condition

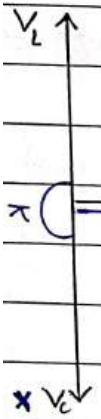

$$V_{net} = V_R = E_0 \sin(\omega t)$$

$$Z = R$$

$$Z = R$$

$$Z_{min} = R$$

$$\phi = 0^\circ \quad V_{net} = V_R$$

$$\cos \phi = 1$$

Resonance Condition

$$V_L = V_C$$

$$I X_L = I X_C$$

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$



$$\omega^2 = \frac{1}{LC}$$

$$\text{resonance angular frequency} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Pure Resistance


Pure inductive circuit

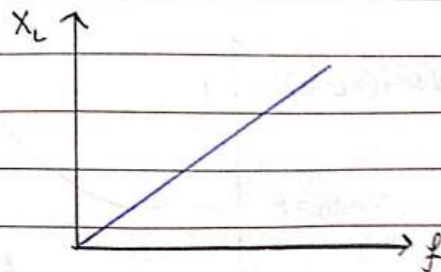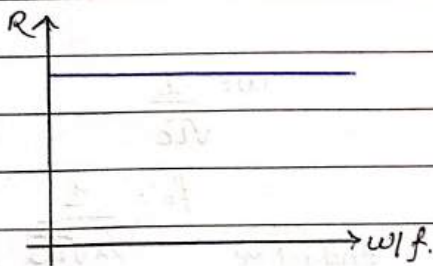


Pure capacitive circuit

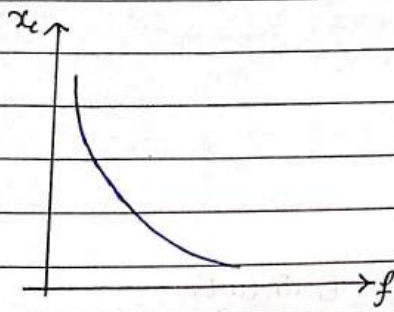


(R-L) circuit

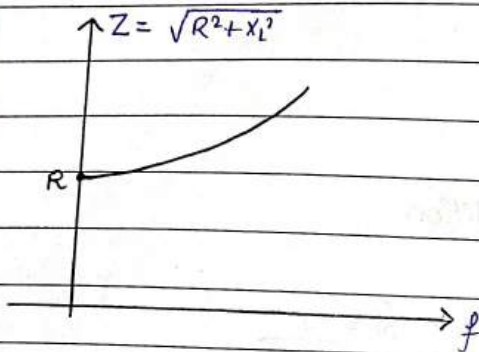


(R-C) circuit

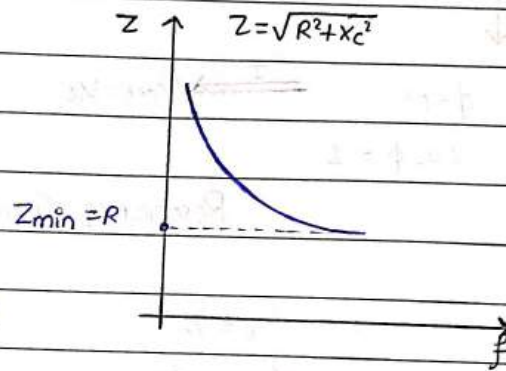

L-C circuit.

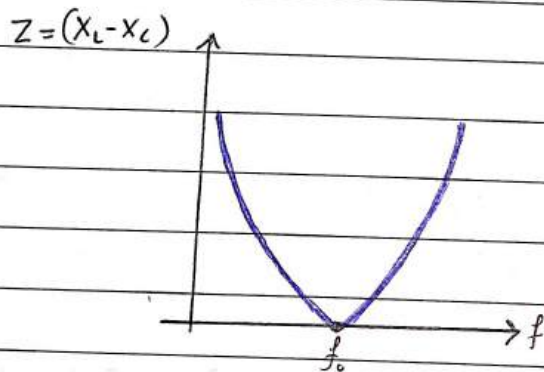

Series LCR.

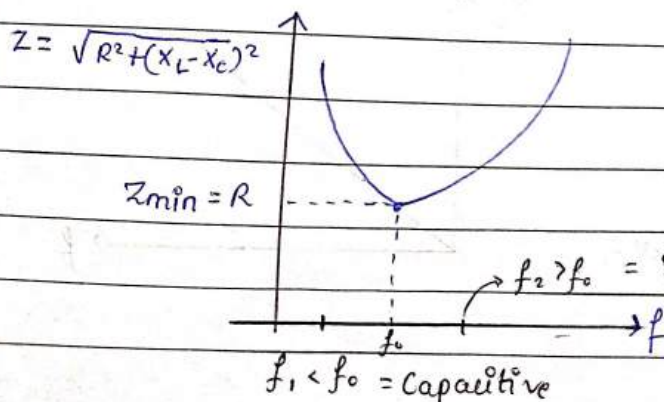

$$\omega = \frac{1}{\sqrt{LC}}$$


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$f_2 > f_0 = \text{Inductive}$

$f_1 < f_0 = \text{Capacitive}$

By increase in frequency Z first \downarrow and then \uparrow increases.

Power loss in A/C circuit

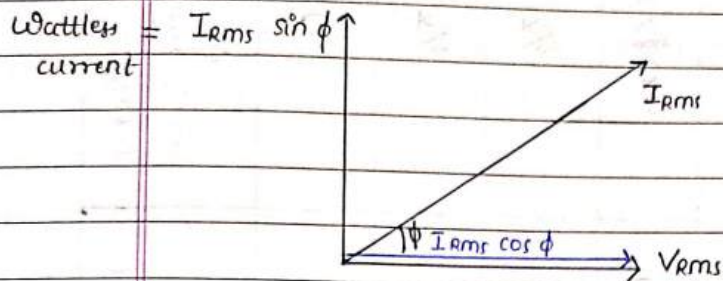

$$\text{Wattless current} = (I_{rms}) \sin \phi$$

$$\langle P \rangle = I_{rms} \cdot V_{rms} \cos \phi$$

$$\langle P \rangle = V_{rms} \cdot I_{rms} \cos \phi$$

Power factor

$$\langle P \rangle = \frac{V_{rms}^2}{Z} \cos \phi \quad [I_{rms} = \frac{V_{rms}}{Z}]$$

$$\langle P \rangle = V_{rms} I_{rms} \cos \phi$$

Pure resistive

$$\phi = 0^\circ$$

$$\cos 0^\circ = 1$$

$$\langle P \rangle = V_{rms} \cdot I_{rms}$$

Pure inductor.

$$\cos \phi = 0 \quad (\phi = 90^\circ)$$

$$\langle P \rangle = 0$$


Pure capacitor

$$\phi = 90^\circ$$

$$\cos \phi = 0$$

$$\langle P \rangle = 0$$

Series R-L

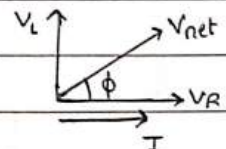

$$\cos \phi = \frac{V_R}{V_{net}} = \frac{R}{Z}$$

$$\langle P \rangle = V_{rms} \cdot I_{rms} \frac{R}{Z}$$

$$\frac{P_o}{Z} = P_{rms}$$

Circuit	Phase difference between I and V	Power factor $\cos \phi = \frac{R}{Z}$	Impedance (Z)	Who leads	Power loss
Pure Resistive	0	1 [cos 0°]	R	Same phase	$P = I_{rms} \cdot V_{rms}$
Pure Capacitive	$\pi/2$	Zero (cos $\pi/2$)	$X_C = \frac{1}{\omega C}$	Current	Zero
Pure Inductive	$\pi/2$	Zero	$X_L = \omega L$	Voltage	Zero
R-L	$0 < \phi < \pi/2$	between 0 to 1	$Z = \sqrt{R^2 + X_L^2}$	Voltage	$P = I_{rms} \cdot V_{rms} \cdot \frac{R}{Z}$
R-C	$0 < \phi < \pi/2$	between 0 to 1	$Z = \sqrt{R^2 + X_C^2}$	Current	$P = I_{rms} \cdot V_{rms} \cdot \frac{R}{Z}$
L-C	$\pi/2$	Zero	$Z = X_L - X_C$	Depends	Zero
Series LCR	$0 \leq \phi < \pi/2$	1 or between 0 to 1.	$Z = \sqrt{R^2 + (X_L - X_C)^2}$	Depends	$P = I_{rms}^2 R$

Q The instantaneous values of alternating current and voltages in a circuit are.

$$i = \frac{1}{\sqrt{2}} \sin(100\pi t) \text{ ampere}$$

$$e = \frac{1}{\sqrt{2}} \sin(100\pi t + \frac{\pi}{3}) \text{ volt}$$

The average power in watts consumed in the circuit is.

- a) $\frac{1}{4}$ b) $\frac{\sqrt{3}}{4}$
 c) $\frac{1}{2}$ ~~d) $\frac{1}{8}$~~

$$\Rightarrow \langle P \rangle = I_{\text{rms}} \cdot V_{\text{rms}} \cdot \cos \phi$$

$$\Rightarrow \frac{1}{2} \times \frac{1}{2} \times \frac{1}{2} = \frac{1}{8} \text{ Ans}$$


Q A circuit when connected to an AC source of 12V gives a current of 0.2A. The same circuit when connected to a DC source of 12V, gives a current of 0.4A. The circuit is.

- ~~a) series LR~~ b) series RC
 c) series LC ~~d) series LCR~~

Ans When the circuit is connected to a DC source the value of current increases or it does not fall to zero which means capacitor is definitely not present in the circuit.

Q In the following circuit the emf of source is $E_0 = 200 \text{ V}$ and $R = 20 \Omega$, $L = 0.1 \text{ Henry}$, $C = 10.6 \text{ farad}$ and frequency is variable then the current at frequency $f=0$ and $f=\infty$ is.

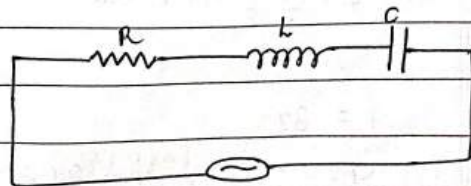- 1) zero, 10A
 2) 10A, zero
 3) 10A, 10A
~~4) zero, zero.~~




At $f=0$ At $f=\infty$
 $X_C = \infty$ $X_L = \infty$

Q In an LCR circuit $L = 8.0$ henry, $C = 0.5 \mu F$ and $R = 100$ ohm are in series. The resonance angular frequency is.

- ~~a)~~ 500 rad/s b) 600 rad/s
 c) 800 rad/s d) 1000 rad/s.

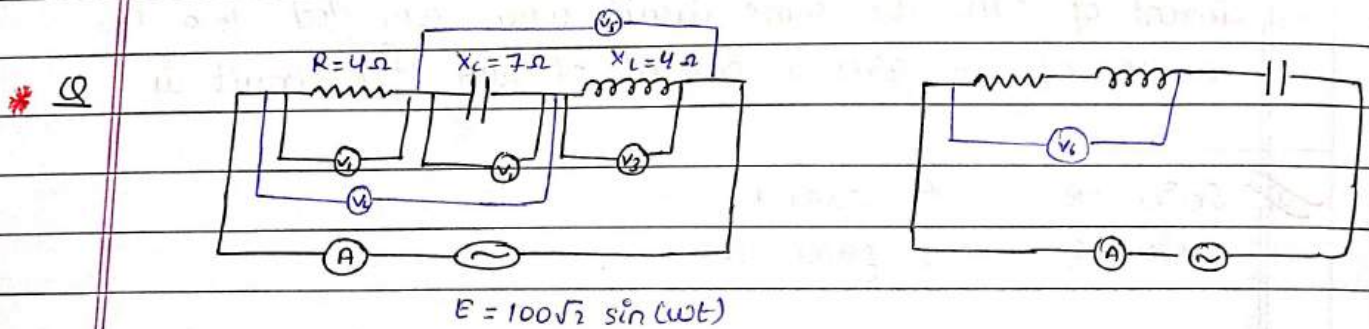Ans
$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 0.5 \times 10^{-6}}} = \frac{1}{2 \times 10^{-3}} = \frac{1000}{2} = 500$$



Find reading of V_1, V_2, V_3, V_4 , V_s, V_i and (A) & impedance, Power factor & Power loss.

Ans
$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$Z = \sqrt{16 + 9}$$

$$Z = 5 \Omega.$$

$$A = I_{rms} = \frac{E_{rms}}{Z} = \frac{100\sqrt{2}}{\sqrt{2} \times 5} = 20 A$$

$$\cos \phi = \frac{R}{Z} = \text{Power factor} = \frac{4}{5}$$

$$\phi = 37^\circ$$

$$\langle P \rangle = I_{rms} \cdot V_{rms} \cos \phi = I_{rms}^2 Z \cos \phi = (20)^2 \times 4 = 1600 W$$

$$V_1 = I_{rms} \times R$$

$$= 20 \times 4 = 80V$$

$$V_2 = I_{rms} \times X_C$$

$$= 20 \times 7 = 140V$$

$$V_3 = I_{rms} \times X_L$$

$$= 20 \times 4 = 80V$$

$$V_4 = I_{rms} \times \sqrt{R^2 + X_C^2}$$

$$= 20 \times \sqrt{65}$$

$$= 20\sqrt{65}$$

OR

$$V_4 = \sqrt{(V_R)_{rms}^2 + (V_C)_{rms}^2}$$

$$V_4 = \sqrt{(80)^2 + (140)^2}$$

$$V_5 = (X_C - X_L) I_{rms}$$

$$= 3 \times 20 = 60V$$

OR

$$V_5 = V_C - V_L = 140 - 80 = 60V$$


$$V_6 = (\sqrt{R^2 + X_L^2}) I_{rms}$$

$$= \sqrt{32} \times 20$$

$$= 20\sqrt{32}$$


OR
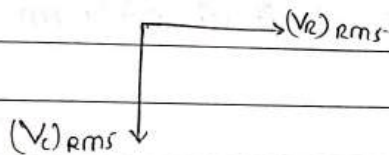
$$\sqrt{(V_L)_{rms}^2 + (V_R)_{rms}^2} = \sqrt{(80)^2 + (80)^2}$$



Find equation of current

$$\Rightarrow I = I_0$$

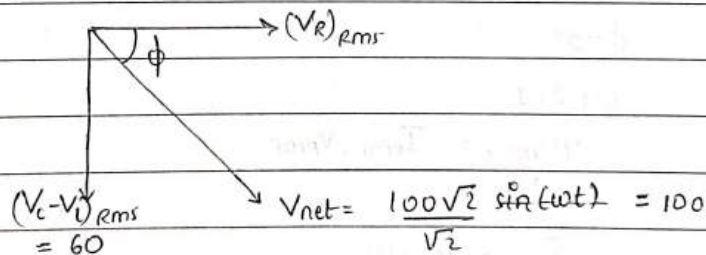Nature of this LC circuit = Capacitive ($X_C > X_L$)

$$\tan \phi = \frac{V_C - V_L}{V_R} = \frac{360}{480} = \frac{3}{4}$$

$$\phi = 37^\circ$$

$$I_0 = \frac{V_0}{Z} = \frac{100\sqrt{2}}{5} = 20\sqrt{2}$$

$$I = 20\sqrt{2} \sin(\omega t + 37^\circ)$$

$$V_R = 80\sqrt{2} \sin(\omega t + 37^\circ)$$

$$V_C = \frac{140}{80}\sqrt{2} \sin(\omega t + 37^\circ - 90^\circ)$$

$$V_C = 140\sqrt{2} \sin(\omega t - 53^\circ)$$

$$V_L = 80\sqrt{2} \sin(\omega t + 37^\circ + 90^\circ)$$

ELECTRICAL RESONANCE

Electrical resonance is said to take place in a series LCR circuit when the circuit allows maximum current for a given frequency of the source of alternating supply for which capacitive reactance becomes equal to the inductive reactance. Impedance of this LCR circuit is minimum & hence current is maximum.

$$X_L = X_C$$

$$V_L = V_C$$

$$Z_{\min} = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$V_{\text{net}} = V_R$$

$$\vec{V} = \vec{I}$$

$$\phi = 0^\circ$$

$$\cos \phi = 1$$

$$\langle P \rangle_{\max} = I_{\text{RMS}} \cdot V_{\text{RMS}}$$

↓

$$I_{\max} = \text{maximum}$$

Q In a series LCR circuit, the capacitance C is changed to $4C$. To keep the resonant frequency same, the inductance must be changed by

- a) $2L$ (b) $L/2$
c) $4L$ ~~$L/4$~~

Ans $\omega = \frac{1}{\sqrt{LC}}$
 $\sqrt{LC} = \text{constant}$
 $\therefore L' = \frac{L}{4}$

Q A bulb rated 60W at 220V is connected across a household supply of alternating voltage of 220V. Calculate the maximum instantaneous current through the filament.

Ans (a) $I_{\text{rms}} = \frac{E_{\text{rms}} (P)}{V^2}$

$$I_0 = \frac{220 \times 60 \sqrt{2}}{220 \times 220}$$

$$I_0 = \frac{6\sqrt{2}}{22}$$

Q A transistor-oscillator using a resonant circuit with an inductor L (of negligible resistance) and a capacitor C in series produces oscillations of frequency f . If L is doubled and C is changed to $4C$, the frequency will be


- a) $f/2$ (b) $f/4$
c) $8f$ ~~$f/2\sqrt{2}$~~

Ans $f = \frac{1}{2\pi\sqrt{LC}}$ $f' = \frac{1}{2\pi\sqrt{2L \times 4C}} = \frac{f}{2\sqrt{2}}$


Q A series LCR circuit is connected to an AC voltage source. When L is removed from the circuit, the phase difference between current and voltage is $\pi/3$. If instead C is removed from the circuit, the phase difference is again $\pi/3$ between current & voltage. The power factor of the circuit is.

- a) zero b) 0.5
 c) 1.0 d) -1.0

ANS

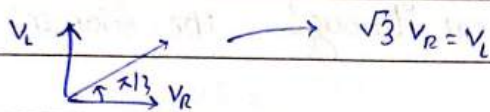

since angle is same

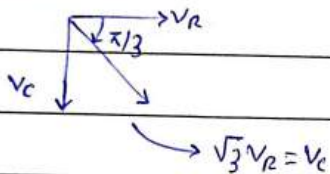

in both $\therefore V_L = V_C$

$\therefore Z = R$ [Resonance condition]

$$\cos \phi = \frac{Z}{R} = 1$$

OR $\phi = 0^\circ$ [for resonance]

OR

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{0}{V_R} = 0^\circ$$

$$\phi = 0^\circ$$

$$\cos \phi = \cos 0^\circ = 1$$

Q The equation of an alternating voltage is $V = 220 \sin(\omega t + \frac{\pi}{6})$ and the equation for current is $I = 10 \sin(\omega t + \frac{\pi}{6})$. The impedance (in ohm) of the circuit is.

- a) 11 (b) 44
c) 20 ~~(d) 22~~

Ans $I_0 = \frac{E_0}{Z}$

$Z = \frac{220}{10} = 22 \Omega$



Q A coil and a bulb are connected in series with a 12 volt direct current source. A soft iron core is now inserted in the coil. then

- ~~a)~~ The intensity of the bulb remains same
b) The intensity of the bulb decreases
c) The intensity of the bulb increases
d) Nothing can be said.

Ans Because $X_L = 0$ [$X_L = \omega L = 2\pi f H_0 l A n^2$]
 $f = 0$
 $\therefore X_L = 0$


Q In a series RLC circuit, potential difference across R, L and C are 30, 60 and 100V respectively as shown in the figure. The emf of source (in volts) is.

- a) 190
~~b) 50~~
c) 70
d) 40

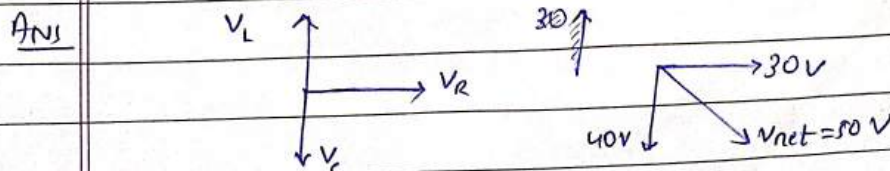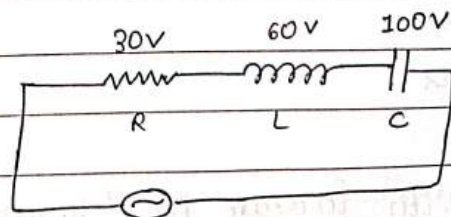


Q In a series RLC circuit, the rms voltage across the resistor and the inductor are respectively 400 V & 700 V. If the equation for the applied voltage is $E = 500\sqrt{2} \sin \omega t$, then the peak voltage across the capacitor is.

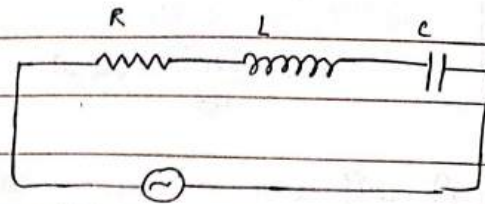- a) 1200 V (b) $1200\sqrt{2}$ V
 c) 400 V ~~(d)~~ $400\sqrt{2}$ V



$$E = 500\sqrt{2} \sin(\omega t)$$

Ans $E_{\text{rms}} = 500$

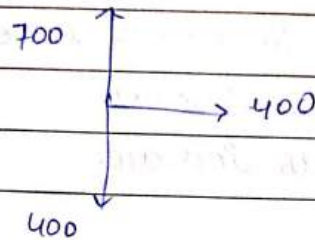

$$(V_C)_{\text{rms}} = 400$$

$$(V_C)_c = 400\sqrt{2}$$

Q In series LCR circuit, the phase difference between voltage across L and voltage across C is.

a) Zero

~~b) π~~

c) $\pi/2$


d) 2π

With increase in frequency of an A.C. supply, the impedance of an LCR series circuit.

- a) Remains constant
- b) Decreases
- c) Increases
- ~~d)~~ Decreases at first, becomes minimum and then increases.

Q Figure shows a series LCR circuit, connected to a variable frequency 200V source $C=80\mu\text{F}$ and $R=40\Omega$. The source frequency which drives the circuit at resonance is.

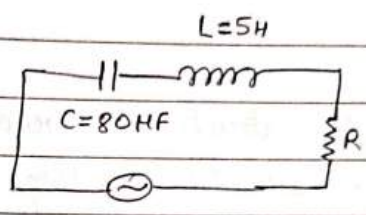
- a) 25 Hz ~~b)~~ $\frac{25}{\pi}$ Hz
- c) 50 Hz d) $\frac{50}{\pi}$ Hz



Ans $f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi \times 20 \times 10^{-3} \times 5} = \frac{1000}{40\pi} = \frac{25}{\pi}$ Hz

Q The reading of the ammeter is

- ~~a)~~ 2A
- b) 3A
- c) 2A
- d) 1A

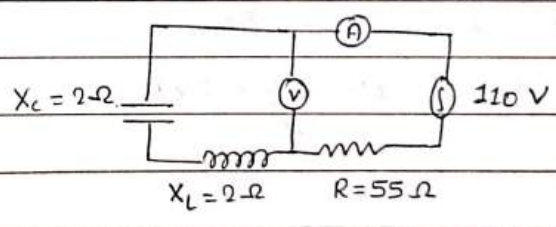


Ans $Z = \sqrt{R^2 + (X_L - X_C)^2}$
 $Z = R$
 $I_{rms} = \frac{E_{rms}}{Z} = \frac{110}{55} = 2A$ Ans

Q The potential differences across the resistance, capacitance and inductance are 80V, 40V and 100V respectively in a LCR circuit. The power factor of the circuit is:-

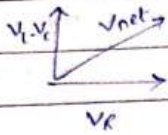1) 0.4 (b) 0.5


~~0.8~~ (c) 1.0

Ans $\cos \phi = \frac{V_R}{V_{net}} = \frac{80}{100} = 0.8$



Q In the given circuit the reading of voltmeters V_1 and V_2 are 300 volts each. The reading of the voltmeter V_3 and ammeter A is respectively.

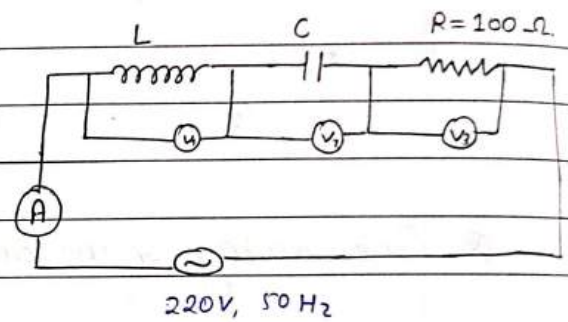- a) 150V, 2.2A ~~b) 220V, 2.2A~~
 c) 200V, 2.0A d) 100V, 2.0A




Ans Resonance condition

$$I = \frac{220}{100} = 2.2 \text{ A}$$

Q In a box Z unknown elements, L or R or any other combination, an AC voltage $E = E_0 \sin(\omega t + \phi + \frac{\pi}{4})$. Then unknown element in the box may be.

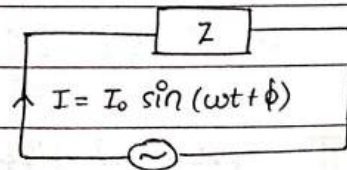- a) Only capacitor
~~b) Inductor and resistor both~~
 c) Either, capacitor, resistor and inductor
 or only capacitor and resistor
 d) Only resistor.



Q In a series LCR circuit which is connected to an AC voltage source, choose the incorrect statement.

- a) Algebraic sum of instantaneous voltage across L, C, R is a variable
- b) $(V_L)_{inst} + (V_C)_{inst} + (V_R)_{inst} = (V_{source})_{inst}$
- c) Voltage across inductor, capacitor, resistance behave as a vector
- d) Current is same in inductor, capacitor and resistance.

Q Assertion (A):- If an inductor coil is connected to DC source, the current supplied by it is I_1 . If the same coil is connected with an AC source of same voltage. Then current is I_2 . Then $I_2 < I_1$.

Reason (R):- In an AC circuit, inductor coil offers more resistance.

- a) Both A and R are true and R is the correct explanation of A.
- b) Both A and R are true but R is not the correct explanation of A
- c) A is true but R is false
- d) A is false and R is also false.

Q Assertion (A): Capacitor serves as a barrier for DC and offers an easy path to AC.

Reason (R): Capacitive reactance is directly proportional to frequency.

- a) Both A and R are true & R is the correct explanation of A
- b) Both A and R are true but R is not the correct explanation of A
- c) A is true but R is false
- d) Both A & R are false.

Q Assertion (A): In series LCR circuit, voltage across capacitor is always less than the applied voltage.

Reason (R): In series, LCR circuit $V = \sqrt{V_R^2 + (V_L + V_C)^2}$

- a) Both A and R are correct and R is the correct explanation of A.
 b) Both A and R are correct but R is not the correct explanation of A.
 c) A is true but R is false
~~d) Both A and R are false.~~

Q Assertion (A):- If $X_C > X_L$, ϕ is positive and the circuit is predominantly capacitive. The current in the circuit leads the source voltage.

Reason (R):- If $X_C > X_L$, ϕ is negative and the circuit is predominantly inductive. The current in the circuit lags the source voltage.

- a) Both A and R are true and R is the correct explanation of A.
 b) Both A and R are true but R is not the correct explanation of A.
~~c) A is true but R is false~~
 d) Both A and R are false.

Q Assertion (A):- Resonance phenomenon is exhibited by a circuit only, if both L and C are present in the circuit.

Reason:- Voltage across L and C does not cancel each other and the current amplitude is V_m/R , the total source voltage appearing across R causes resonance



- a) Both A and R are true R is the correct explanation of A
- b) Both A and R are false but R is not the correct explanation of A.
- c) Both A and R are false
- ~~d) A is true but R is false.~~

Q A capacitor acts as an infinite resistance for.


- ~~a) DC~~
- b) AC
- c) DC as well as AC
- d) neither AC nor DC.

Q Assertion (A):- At resonance, power of LCR series circuit is zero.
Reason (R) :- At resonance, $X_L > X_C$.

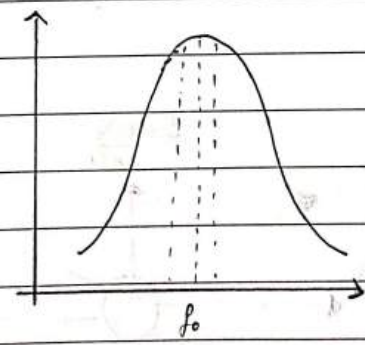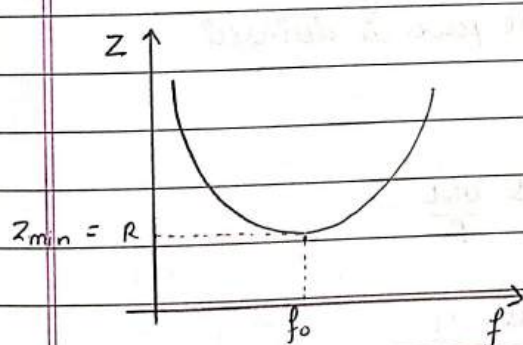- a) Both A and R are true and R is the correct explanation of A
- b) Both A and R are true but R is not the correct explanation of A
- ~~c) Both A and R are false~~
- d) A is true but R is false






Radio
↓
series LCR
circuit

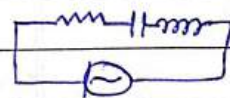

Ramlal ka

Radio $f = \frac{1}{2\pi\sqrt{LC}} = 98.3 \text{ Hz}$

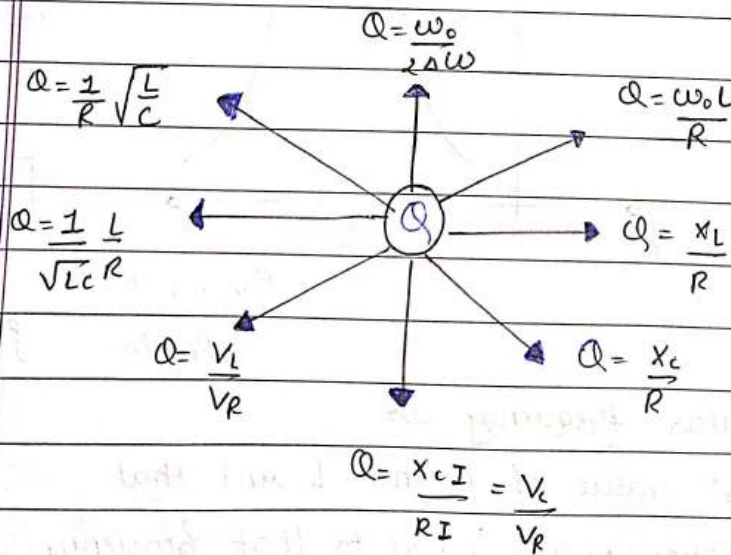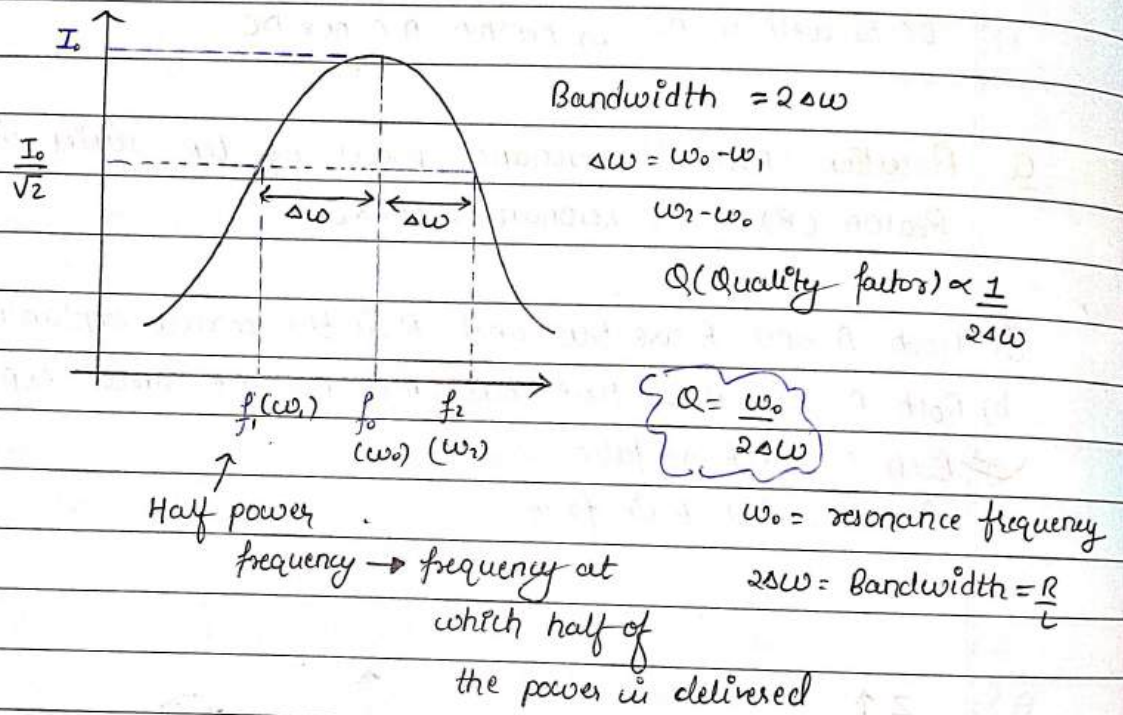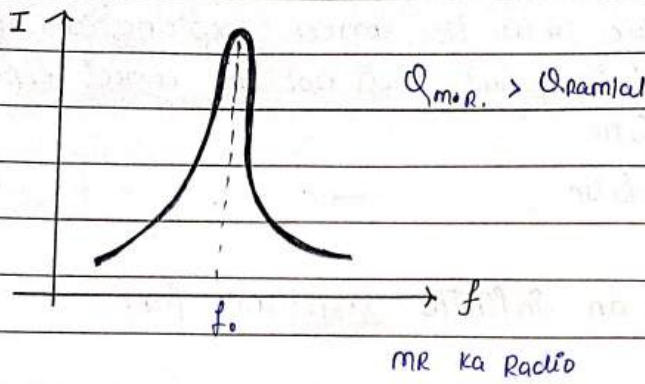To get a particular frequency we change value of C and L such that $\frac{1}{2\pi\sqrt{LC}}$ has value equal to that frequency.



Q Bandwidth of the resonant L-C-R circuit is.


- ~~a)~~ R/L b) R/2L
c) 2R/L d) 4R/L

Q Which of the following combinations should be selected for better tuning of an LCR circuit used for communication.

- a) $R = 20\Omega, L = 1.5H, C = 35\mu F$
b) $R = 25\Omega, L = 2.5H, C = 45\mu F$
~~c) $R = 15\Omega, L = 3.5H, C = 30\mu F$~~
d) $R = 25\Omega, L = 1.5H, C = 45\mu F$

Ans $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$


PARALLEL R-L Circuit

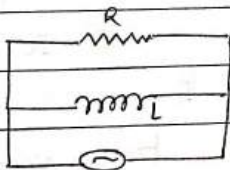

$E_0 = E_0 \sin(\omega t)$

$(E_R)_t = (E_L)_t = E_0$

$(I_R)_t \neq (I_L)_t$

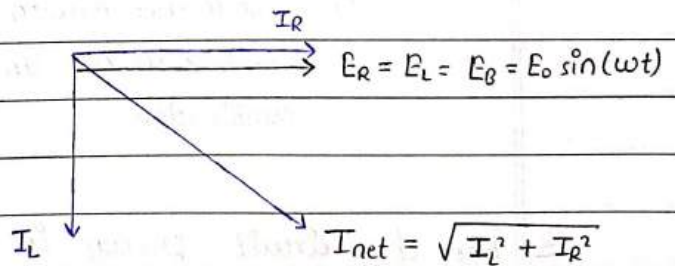

$I_{net} = \sqrt{I_L^2 + I_R^2}$

$I_{net} = \sqrt{\left(\frac{E_0}{X_L}\right)^2 + \left(\frac{E_0}{R}\right)^2} = \frac{E_0}{Z}$


* Reciprocal of impedance is admittance

$E_L = I_L X_L$

$E_R = I_R R$

$E = I_{net} Z$


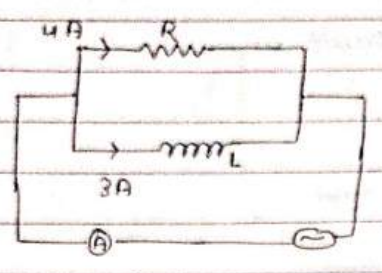
$\frac{1}{Z} = \sqrt{\frac{1}{X_L^2} + \frac{1}{R^2}}$



Find reading of ammeter.

$$I_{net} = \sqrt{I_L^2 + I_R^2} = \sqrt{16 + 9} = \sqrt{25} = 5A$$

PARALLEL L-C circuit

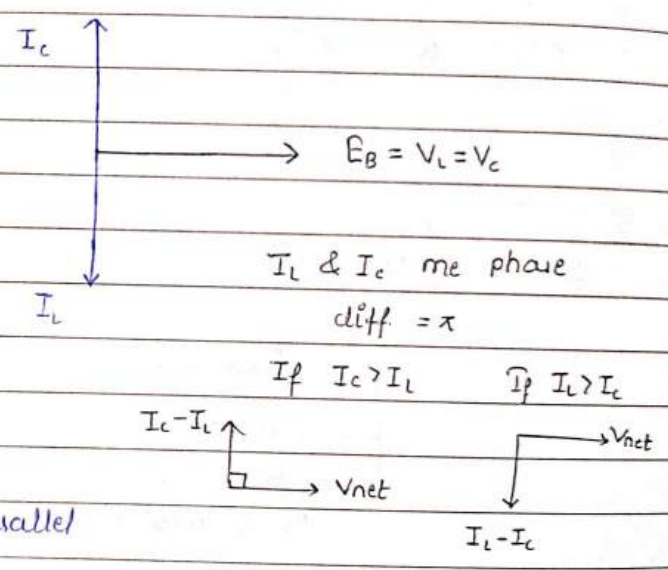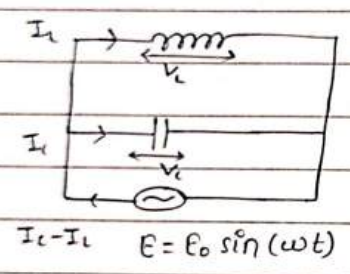


$$(V_C)_t = (V_L)_t = E_0$$

Phase difference between V_L and V_C is 2π in parallel combination.

Q For the circuit shown in the figure the current through the inductor is $1A$, while the current through the condenser is $0.4A$, then the current I drawn from the source is

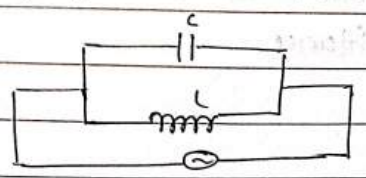
- (a) $2\sqrt{2}A$
- (b) $1.65A$
- (c) $1.2A$
- (d) $2.0A$



Ans $I_{net} = I_L - I_C = 1.6 - 0.4 = 1.2$

Q In the alternating current circuit shown in the figure, the currents through resistor and capacitor are 3A and 4A respectively. The current drawn from the generator is


- 1) 7A (2) 1A
 5A (d) 12A

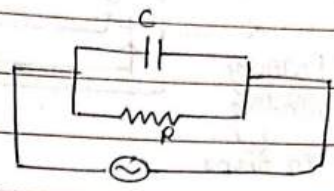


TRANSFORMER. [To ^{step} set up & step down the voltage]

- Based on mutual inductance
- use to step-up or step-down alternating current voltage
- only ^{for} of A/C source not for D/C
- Step up → Power house
- Step down → sub station.

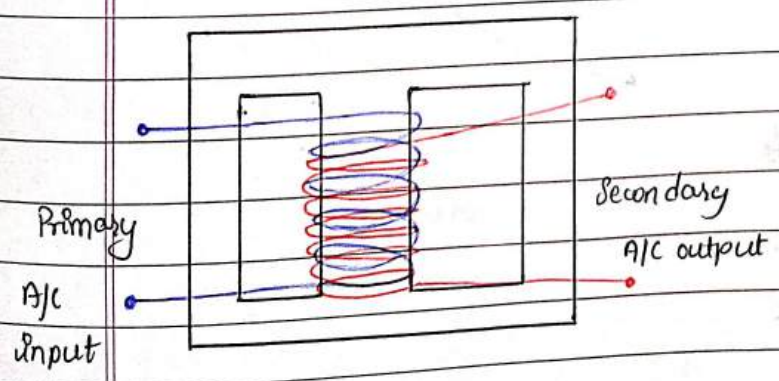- $\eta_{efficient} \leq 95\%$
- For ideal transformer ($P_{loss} = 0$)
 $\eta_{ideal} = 100\%$



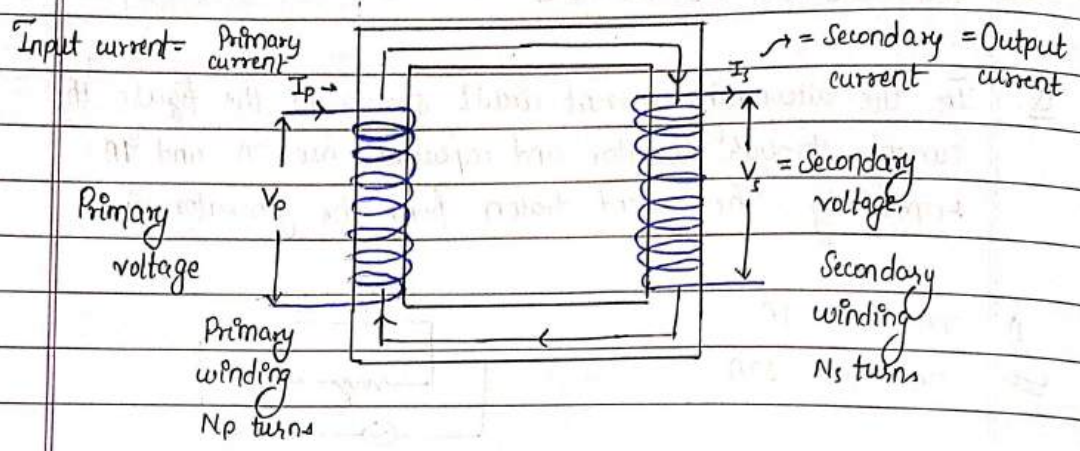

total flux passing through primary coil = $N_p \phi_o = \phi_p$
 total flux passing through secondary coil = $N_s \phi_o = \phi_s$

$$\phi_p = N_p \phi_o \quad \text{--- (1)}$$

$$\phi_s = N_s \phi_o \quad \text{--- (2) } \rightarrow \text{differentiate w.r.t. time}$$

flux passing through primary coil and secondary coil is not same but flux through one turn of primary coil and one turn of secondary coil is same.

$$\frac{d\phi_p}{dt} = N_p \frac{d\phi_o}{dt}$$

$$\frac{d\phi_s}{dt} = N_s \frac{d\phi_o}{dt}$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$V_s (V_{out}) = \frac{N_s}{N_p} V_p$$

$$\frac{V_{in}}{V_{out}} = \frac{N_p}{N_s}$$

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \text{Transformation ratio}$$

Voltage \propto No of turns

$$\frac{V_{out}}{V_{in}} = \frac{N_s}{N_p}$$

$$V_{out} = \frac{N_s}{N_p} V_{in}$$

$$\text{If } N_s = N_p$$

$$V_{in} = V_{out}$$

Ideal transformer

energy loss = zero

$$P_{in} = P_{out}$$

$$V_p I_p = V_s I_s$$

$$\frac{I_p}{I_s} = \frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$\frac{I_s}{I_p} = \frac{N_p}{N_s} \quad I \propto \frac{1}{\text{No of turns}}$$

Step up transformer

$$V_{out} > V_{in}$$

$$N_s > N_p$$

$$I_s < I_p$$

$$V_s > V_p$$

$$P_{in} = P_{out}$$

$$I \propto \frac{1}{\text{No of turns}}$$

No of turns

$V \propto$ No of turns

$$\eta = \frac{P_{out}}{P_{in}} = 100\%$$

Step down transformer

$$V_{out} < V_{in}$$

$$N_s < N_p$$

$$I_s > I_p$$

$$V_s < V_p$$

$$P_{in} = P_{out}$$

$$\eta = \frac{P_{out}}{P_{in}} = 100\%$$

Q The ratio of secondary to the primary turns in a transformer is 3:2. If the power output be P , the input power neglecting all losses must be equal to.

- a) $5P$ ~~b) P~~
c) $1.5P$ d) $2.5P$

⇒ Power is independent of no. of turns.

Q An ideal transformer has 100 turns in the primary and 250 turns in the secondary. The peak value of the AC is 28V. The RMS secondary voltage is nearest to

- ~~a) 50~~ b) 70
c) 100 d) 40

Ans $\frac{N_s}{N_p} = \frac{(V_s)_0}{(V_p)_0}$

$$(V_s)_0 = \frac{250 \times 28}{100} = 70 \text{ V}$$

$$(V_s)_{\text{RMS}} = \frac{70}{\sqrt{2}} = 50 \text{ V}$$

A step down transformer is used in a 1000V line to deliver 20A at 120V at the secondary coil. If the efficiency of the transformer is 80% the current drawn from the line is.

- 3A b) 30A
0.3A d) 2.4A

Ans

$$I_p = ?$$

$$I_s = 20 \text{ A}$$

$$V_s = 120 \text{ V}$$

$$V_p = 1000$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_s I_s}{V_p I_p} = \frac{80}{100}$$

$$\frac{3 \times 1000 \times 20}{1000 I_p} = \frac{4 \times 80}{100}$$

$$I_p = 3 \text{ A} \quad \text{Ans}$$

Q A current of 5 A is flowing at 220 V in the primary of a transformer. If the voltage produced in the secondary coil is 2200 V and 50% power is lost then the current in the secondary will be.

- ~~a) 0.25 A~~ (b) 0.5 A
c) 2.5 A (d) 5 A

Ans

$$P_{out} = \frac{1}{2} P_{in}$$

$$V_s = 2200$$

$$I_p = 5 \text{ A}$$

$$V_s I_s = \frac{1}{2} V_p I_p$$

$$V_p = 220$$

$$2200 I_s = \frac{1}{2} \times 220 \times 5$$

$$I_s = 0.25 \text{ A} \quad \text{Ans}$$

Q A 220 volt input is supplied to a transformer. The output circuit draws a current of 2.0 A at 440 volts. If the efficiency of the transformer is 80%, the current drawn by the primary windings of the transformer is.

a) 3.6 A (b) 2.8 A

c) 2.5 A ~~(d)~~ 5.0 A

Ans $P_{in} \times \frac{80}{100} = P_{out}$

$$V_p I_p \times \frac{80}{100} = V_s I_s$$

$$220 \times I_p \times \frac{80}{100} = 440 \times 2$$

$$I_p = 5 \text{ A} \quad \text{Ans}$$

Q The primary and secondary coils of a transformer have 50 and 1500 turns respectively. If the magnetic flux ϕ linked with the primary coil is given by $\phi = \phi_0 + t^2$ where ϕ is in webers, t is time in seconds and ϕ_0 is constant, the output voltage across the secondary coil is.

~~(a)~~ 120 volt (b) 220 volt

c) 30 volt (d) 90 volt

Ans $N_p = 50$ $N_s = 1500$

$$\frac{N_s}{N_p} = \frac{V_s}{V_p}$$

$$V_p = \frac{d\phi}{dt} = 4 \text{ V} \quad V_s = \frac{1500 \times 4}{50} = 120 \text{ V} \quad \text{Ans}$$

$$V_s = ?$$

* Q A transformer is used to light a 100W and 110V lamp from a 220 V mains. If the main current is 0.5 A, the efficiency of the transformer is approximately.

- a) 50% ~~b) 90%~~
c) 10% (d) 30%

Ans

$$I_p = 0.5A$$

$$I_s = ?$$

$$V_p = 220$$

$$V_s = 110$$

$$\frac{220}{110} = \frac{I_s}{I_p} \Rightarrow I_s = 1A$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_s I_s}{V_p I_p} = \frac{110 \times 1}{220 \times \frac{1}{2}} = \frac{110 \times 100}{220 \times \frac{1}{2}} = \frac{100}{110} \times 100 = 90.9\%$$

$\eta \approx 90\%$

Q The step-up transformer operates on a 230V line and supplies a load of 2 ampere. The ratio of the primary and secondary winding is 1:25. The current in the primary coil is

- a) 15A ~~b) 50A~~
c) 25A (d) 12.5A

Ans $\Rightarrow \frac{N_p}{N_s} = \frac{1}{25} = \frac{I_s}{I_p} = \frac{2}{I_p}$

$I_p = 50A$

Non ideal transformer me power loss.

- 1) Flux leakage:- There is always a some flux leakage. Not all the flux due to primary passes through the secondary
- 2) Resistance of the winding :- Some energy is lost in the form of heat dissipation. It can be minimized by using thick wire in case of high current, low voltage windings.
- 3) Eddy currents :- The alternating magnetic flux induces eddy currents in the iron core and causes heating. The loss can be minimized using laminated iron core.
- 4) Hysteresis:- The magnetisation of core is repeatedly reversed by alternating magnetic field. The resulting expenditure of energy in the core appears as heat and is kept to a


minimum by using a material which has a low magnetic hysteresis loss.

Q The core of the transformer is laminated because.

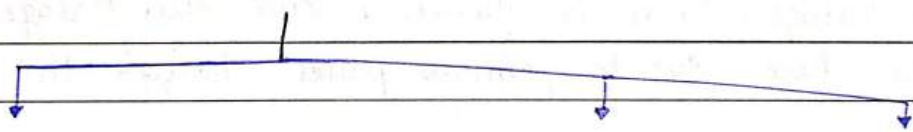- a) Ratio of voltage in primary and secondary may be increased
- b) Energy loss due to eddy currents may be minimised.
- c) the wt. of the transformer may be reduced
- d) rusting of the core may be prevented.



CHOKE COIL

Uses to control current in A/C circuit
 It uses to divide potential without power loss.
 → It is R-L circuit





Ideal choke coil	Practical choke coil	Bekas choke coil
↳ Pure inductor	↳ High X_L , low Resistance	↳ High R, low X_L
↳ $\langle P \rangle = 0$	↳ R-L circuit	↳ $\phi = \text{small}$
↳ $\phi = 90^\circ$	↳ $\phi = \text{High}$	↳ $\cos \phi = \text{high}$
↳ $\cos 90^\circ = 0$	↳ $\cos \phi = \text{low}$	↳ High Power loss.
	↳ Small Power loss	

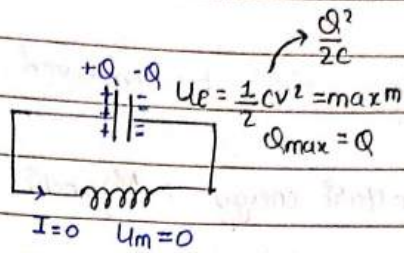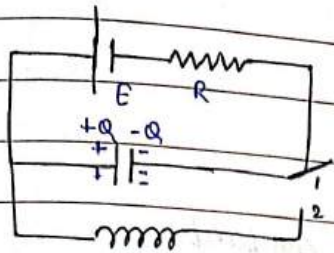L-C OSCILLATION → Always we energy conservation





at $t=0$

After some time

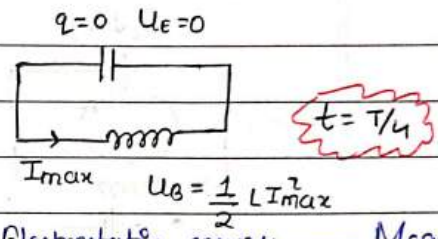
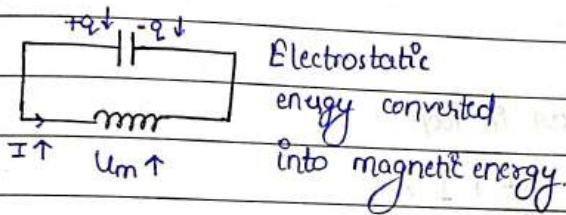


$t = T/4$



Electrostatic energy → Magnetic energy

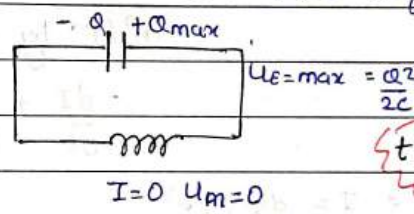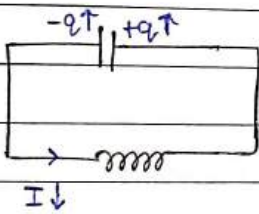

$t = T/2$

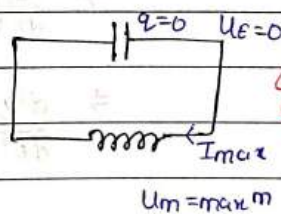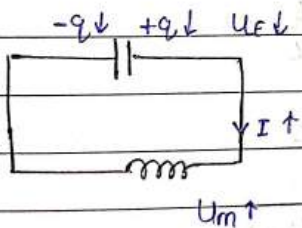


$t = 3T/4$

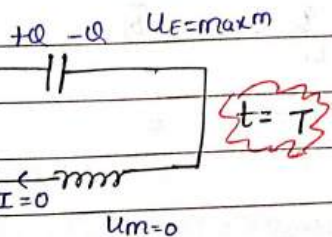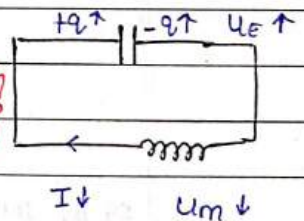


$t = T$

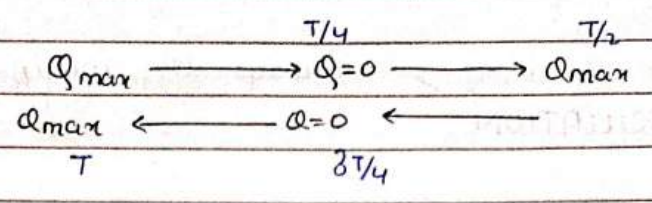Charge oscillate
 Current oscillate
 Electrostatic & magnetic energy oscillate



Energy will be conserved
 ↓
 Electrostatic energy + Magnetic energy = constant
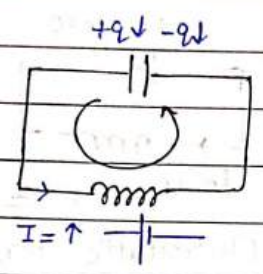
$$\frac{Q^2}{2C} + \frac{1}{2} LI^2 = \text{constant}$$



'KVL' in loop

$$-L \frac{dI}{dt} + \frac{q}{C} = 0$$

divide by L both side

$$-\frac{dI}{dt} + \frac{q}{LC} = 0$$

hint $\rightarrow I = -\frac{dq}{dt}$

$$\Rightarrow -\frac{d}{dt} \left(-\frac{dq}{dt} \right) + \frac{q}{LC} = 0$$

$$\Rightarrow \frac{d^2q}{dt^2} + \frac{q}{LC} = 0$$

eq of SHM

$$a \propto -x$$

$$a = -\omega^2 x$$

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

$$\frac{d^2x}{dt^2} + \omega^2 x = 0$$

$$x = A \sin(\omega t \pm \phi) \quad \text{--- (a)}$$

LC oscillation

$$\frac{d^2q}{dt^2} + \frac{q}{LC} = 0 \quad \text{--- (b)}$$

compare equation 'a' & 'b'.

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$q = q_0 \sin(\omega t \pm \phi)$$

$$q = Q \sin(\omega t \pm \phi)$$

If $q_{max} = Q_0$ at $t=0$ $\phi = ??$

$$Q_0 = Q_0 \sin(\phi)$$

$$\phi = \frac{\pi}{2}$$

$$q = Q_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$q = Q_0 \cos(\omega t)$$

differentiate q w.r.t time.


$$\frac{dq}{dt} = Q_0 \frac{d\cos(\omega t)}{dt}$$

$$I = -Q_0 \sin(\omega t) \omega$$

$$I = -Q_0 \omega \sin(\omega t)$$

$$I = -I_0 \sin(\omega t)$$

$$I_0 = Q_0 \omega$$

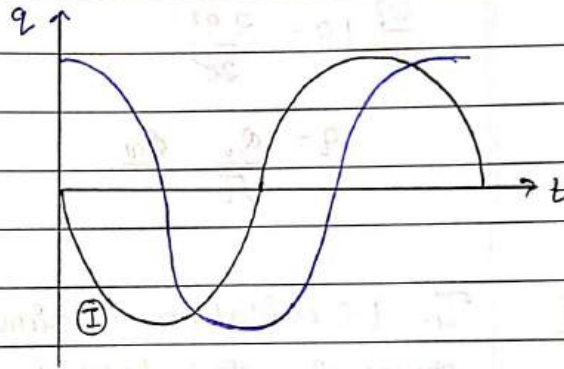

Prove that maxm energy stored in L & C is $\frac{Q_0^2}{2C}$

$$U_E + U_M = \text{const}^n$$

$$\frac{Q^2}{2C} + \frac{1}{2} L I^2 = \text{const}^n$$

$$\frac{Q_0^2 \cos^2 \omega t}{2C} + \frac{1}{2} L Q_0^2 \omega^2 \sin^2(\omega t) = \text{const}^n$$

$$\frac{Q_0^2 \cos^2 \omega t}{2C} + \frac{1}{2} \cancel{Q_0^2} \frac{1}{\cancel{LC}} \sin^2(\omega t) = \text{const}^n$$

$$\frac{Q_0^2}{2C} (\cos^2(\omega t) + \sin^2(\omega t)) = \text{const}^n$$

$$\frac{Q_0^2}{2C} = \text{constant.}$$

Q In L-C oscillation if max charge is Q_0 then find charge in capacitor when electrostatic energy equal to magnetic energy.

Ans $(U_E + U_B)_{\text{initial}} = (U_E + U_m)_{\text{final}}$

$$\frac{Q_0^2}{2C} + 0 = 2 \times U_E$$

↓
since $I=0$
when Q is max

$$\frac{Q_0^2}{2C} + 0 = \frac{2Q^2}{2C}$$

$$Q = \frac{Q_0}{\sqrt{2}} \quad \text{Ans}$$

Q In L-C oscillation maximum energy is U and maximum charge Q_0 , find charge & energy on inductor when charge on capacitor is $\frac{Q_0}{2}$.

Ans $(U_E + U_m)_i = (U_E + U_m)_f$

$$\frac{Q_0^2}{2C} + 0 = \frac{Q_0^2}{4} \times \frac{1}{2C} + U_m$$

$$U = \frac{U}{4} + U_m$$

$$U_m = \frac{3U}{4} \quad \text{Ans}$$

Q A condenser of capacity C is charged to a potential difference of V_1 . The plates of the condenser are then connected to an ideal inductor of inductance L . The current through the inductor when the potential difference across the condenser reduces to V_2 is.

- a) $\left(\frac{C(V_1 - V_2)^2}{L}\right)^{1/2}$ b) $\frac{C(V_1^2 - V_2^2)}{L}$
 c) $\frac{C(V_1^2 + V_2^2)}{L}$ ~~c)~~ $\left(\frac{C(V_1^2 - V_2^2)}{L}\right)^{1/2}$

Ans By energy conservation.

$$(U_E + U_M)_i = (U_E + U_M)_f$$

$$\frac{1}{2}CV_1^2 + 0 = \frac{1}{2}CV_2^2 + \frac{1}{2}LI^2$$

$$\left(\frac{C(V_1^2 - V_2^2)}{L}\right)^{1/2} = I$$

Q In an oscillating LC circuit, the maximum charge on the capacitor is Q . The charge on the capacitor, when energy is stored in capacitor is half of energy stored in inductor.

- a) $Q/2$ b) $Q/\sqrt{2}$
~~c)~~ $Q/\sqrt{3}$ d) $Q/3$

Ans $(U_E + U_B)_i = (U_E + U_B)_f$ $U_E = \frac{U_B}{2}$

$$\frac{Q^2}{2C} = U_E + 2U_E$$

$$\frac{Q^2}{2C} = \frac{3}{2} \frac{Q^2}{C}$$

$$Q = \frac{Q}{\sqrt{3}} \text{ Ans}$$

Q In oscillating L-C circuit, the total stored energy is u and maximum charge upon capacitor is Q . When the charge upon the capacitor is $\frac{Q}{4}$, the energy stored in the inductor is u .

ANS $(U_E + U_B)_P = (U_E + U_B)_I$

$$u = \frac{1}{2} \frac{Q^2}{(16)C} + u_B$$

$$u = \frac{Q^2}{32C} + u_B$$

$$u = \frac{u}{16} + u_B$$

$$u_B = \frac{15u}{16} \text{ Ans}$$


Q Switch is in position A for long time. At time $t=0$ it is switched to position B. Find the maximum charge that will accumulate on capacitor.

~~1) $\sqrt{LC} \frac{E}{R}$~~

2) $\frac{E}{\sqrt{LC} R}$

3) $\sqrt{\frac{L}{C}} \frac{E}{R}$

4) $\sqrt{\frac{C}{L}} \frac{E}{R}$

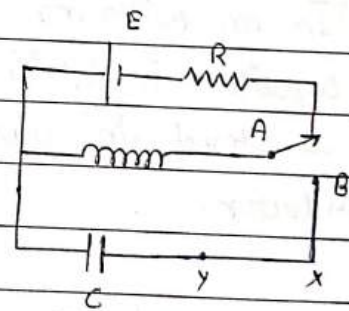

ANS $I_{max} = \frac{E}{R}$


$$(U_E + U_B)_i = (U_E + U_B)_f$$

$$\frac{1}{2} L \frac{E^2}{R^2} = \frac{1}{2} \frac{Q^2}{C}$$

$$Q = \sqrt{LC} \frac{E}{R}$$

Q A capacitor of capacitance C has initial charge Q_0 and connected to an inductor of inductance L as shown. At $t=0$ switch S is closed. The current through the inductor when energy in the capacitor is three times the energy of inductor is.

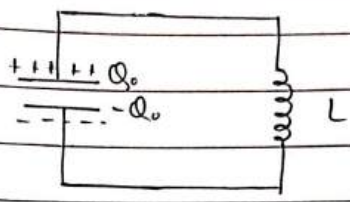- a) $\frac{Q_0}{2\sqrt{LC}}$ b) $\frac{Q_0}{\sqrt{LC}}$
 c) $\frac{2Q_0}{\sqrt{LC}}$ d) $\frac{4Q_0}{\sqrt{LC}}$



Ans $(U_E + U_B)_i = (U_E + U_B)_f$
 $\frac{Q^2}{2C} = 4U_B$
 $\frac{Q^2}{2C} = 4 \times \frac{1}{2} LI^2$
 $I = \frac{Q_0}{2\sqrt{LC}}$

Spring mass oscillation	L-C oscillation
mass (inertia)	$L \Rightarrow$ Inductance (inertia)
$KE = \frac{1}{2}mv^2$	$U_B = \frac{1}{2}LI^2$
speed	current (I)
$PE = \frac{1}{2}kx^2$	$U_E = \frac{Q^2}{2C}$
Position	charge
K	$\frac{1}{C}$