
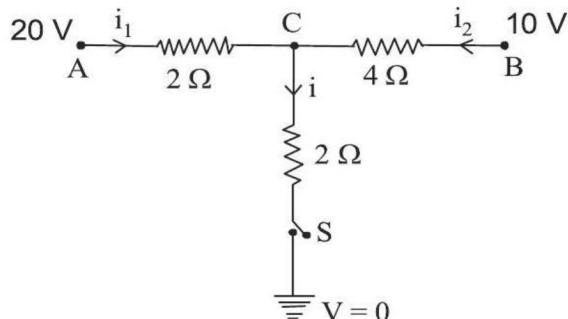


# Current Electricity

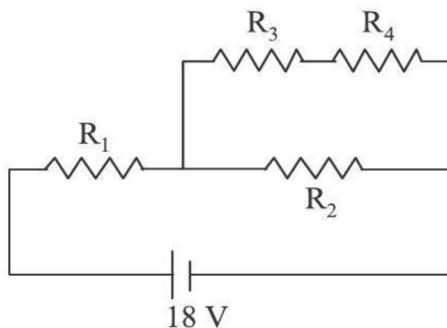
1. When the switch  $S$ , in the circuit shown, is closed then the value of current  $i$  (in ampere) will be:



2. A copper wire is stretched to make it 0.5% longer. The percentage change in its electrical resistance if its volume remains unchanged is:  
 3. In the given circuit the internal resistance of the 18 V cell is negligible. If  $R_1 = 400\Omega$ ,  $R_3 = 100\Omega$  and  $R_4 = 500\Omega$  and the reading of an ideal voltmeter across  $R_4$  is 5 V, then the value of  $R_2$  (in  $\Omega$ ) will be:




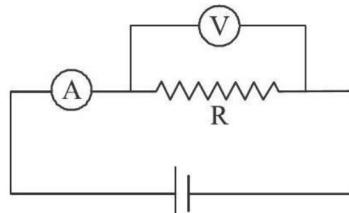4. A uniform metallic wire has a resistance of  $18\Omega$  and is bent into an equilateral triangle. Then, the resistance (in  $\Omega$ ) between any two vertices of the triangle is:  
 5. A 2 W carbon resistor is color coded with green, black, red and brown respectively. The maximum current (in mA) which can be passed through this resistor is:  
 6. The actual value of resistance  $R$ , shown in the figure is  $30\Omega$ . This is measured in an experiment as shown using the standard formula  $R = \frac{V}{I}$ , where  $V$  and  $I$  are the reading of the voltmeter and ammeter, respectively. If the measured value of  $R$  is 5% less, then the internal resistance (in  $\Omega$ ) of the voltmeter is:




7. A current of 2 mA was passed through an unknown resistor which dissipated a power of 4.4 W. Dissipated power (in watt) when an ideal power supply of 11 V is connected across it is:

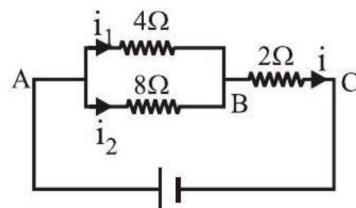8. The amount of charge  $Q$  passed in time  $t$  through a crosssection of a wire is  $Q = (5t^2 + 3t + 1)$  coulomb. The value of current (in ampere) at time  $t = 5$  s is
9. A current of 1 mA flows through a copper wire. How many electrons will pass through a given point in each second?
10. At what temperature (in  $^{\circ}\text{C}$ ) will the resistance of a copper wire becomes three times its value at  $0^{\circ}\text{C}$  ? (Temperature coefficient of resistance of copper is  $4 \times 10^{-3} / ^{\circ}\text{C}$ )
11. In the circuit shown in Fig, the current in  $4\Omega$  resistance is 1.2 A. What is the potential difference (in volt) between B and C ?




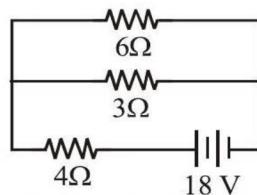12. A current of 30 A is registered when the terminals of a dry cell of emf 1.5 V are connected through an ammeter. (Neglect the ammeter resistance). The amount of heat produced (in joule) in the battery in 20 s is
13. A 100 watt bulb working on 200 volt has resistance  $R$  and a 200 watt bulb working on 100 volt has resistance  $S$ . If the  $R/S$  is  $\frac{8}{x}$ . Find the value of  $x$ .
14. The total power dissipated in watts in the circuit shown here is



15. In an ideal metre-bridge, the balancing length from the left end when standard resistance of  $1\Omega$  is in right gap is found to be 20 cm. The value of unknown resistance (in  $\Omega$ ) is

# SOLUTIONS

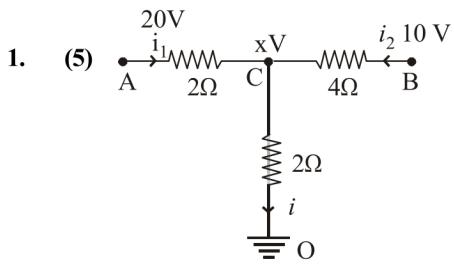

Let voltage at C = xV

From kirchhoff's current law,

$$\text{KCL} : i_1 + i_2 = i$$

$$\frac{20-x}{2} + \frac{10-x}{4} = \frac{x-0}{2} \Rightarrow x = 10$$

$$\therefore i = \frac{V}{R} = \frac{x}{R} = \frac{10}{2} = 5\text{A}$$


2. (1) Resistance,  $R = \frac{\rho \ell}{A}$

$$R = \rho \frac{\ell}{A} \times \frac{\ell}{\ell} = \frac{\rho \ell^2}{V} \quad [\because \text{Volume (V)} = A\ell.]$$

Since resistivity and volume remains constant therefore

% change in resistance
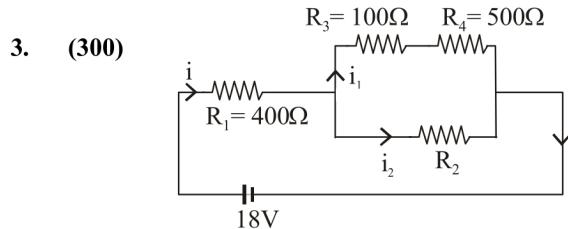
$$\frac{\Delta R}{R} = \frac{2\Delta\ell}{\ell} = 2 \times (0.5) = 1\%$$



Across  $R_4$  reading of voltmeter,  $V_4 = 5\text{V}$

$$\text{Current, } i_4 = \frac{V_4}{R_4} = 0.01\text{A}$$

$$V_3 = i_1 R_3 = 1\text{V}$$

$$V_3 + V_4 = 6\text{V} = V_2$$

$$V_1 + V_3 + V_4 = 18\text{V}$$


$$\Rightarrow V_1 = 12\text{V}$$

$$i = \frac{V_1}{R_1} = 0.03\text{A}$$

$$i = i_1 + i_2 \Rightarrow i_2 = i - i_1 = 0.03 - 0.01\text{A} = 0.02\text{A}$$

$$\therefore R_2 = \frac{V_2}{i_2} = \frac{6}{0.02} = 300\Omega$$

4. (4)

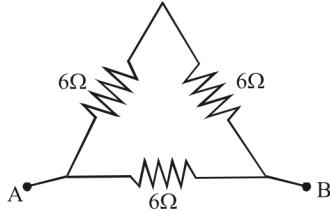

Resistance,  $R \propto l$  so resistance of each side of the equilateral triangle =  $6\Omega$

Resistance  $R_{eq}$  between any two vertices

$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{eq} = 4\Omega$$

5. (20) Colour code for carbon resistor

|     |     |    |    |   |    |       |    |     |   |
|-----|-----|----|----|---|----|-------|----|-----|---|
| Bl, | Br, | R, | O, | Y | G, | Blue, | V. | Gr, | W |
| 0   | 1   | 2  | 3  | 4 | 5  | 6     | 7  | 8   | 9 |

Resistance,  $R = AB \times C \pm D$

$\therefore$  Resistance,  $R = 50 \times 10^2 \Omega$

Now using formula, Power,  $P = i^2 R$

$$\therefore i = \sqrt{\frac{P}{R}} = \sqrt{\frac{2}{50 \times 10^2}} = 20 \text{ mA}$$

6. (570) using,  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$$0.95 R = \frac{RR_U}{R + R_U} \quad (\text{measured value } 5\% \text{ less than internal}$$

resistance of voltmeter)

$$\text{or, } 0.95 \times 30 = 0.05 R_U$$

$$\therefore R_U = 19 \times 30 = 570 \Omega$$

7. ( $11 \times 10^{-5}$ ) Power,  $P = I^2 R$

$$4.4 = 4 \times 10^{-6} \times R$$

$$\Rightarrow R = 1.1 \times 10^6 \Omega$$

When supply of 11 v is connected

$$\text{Power, } P' = \frac{V^2}{R} = \frac{11^2}{1.1} \times \frac{11^2}{1.1} \times 10^{-6} = 11 \times 10^{-5} \text{ W}$$

8. (53)  $I = \frac{dQ}{dt} = 10t + 3 = 10 \times 5 + 3 = 53 \text{ A}$

9. ( $6.25 \times 10^{15}$ ) Current,  $I = \frac{\text{Charge}}{\text{Time}}$ ;

as charge  $q = n \times 1.6 \times 10^{-19}$

$$10^{-3} \text{ amp} = \frac{n \times 1.6 \times 10^{-19}}{1 \text{ sec}} \Rightarrow n = 6.25 \times 10^{15}$$

10. (500)  $R_t = R_0(1 + \alpha t)$  at  $t^\circ C$   $R_t = 3R_0$

$$\alpha = 4 \times 10^{-3} / ^\circ C$$

$$3R_0 = R_0(1 + 4 \times 10^{-3} \times t)$$

$$\therefore 3 - 1 = 4 \times 10^{-3} t$$

$$\therefore t = \frac{2}{4 \times 10^{-3}} = 500^\circ C$$

11. (3.6) The potential difference across  $4\Omega$  resistance is given

$$\text{by } V = 4 \times i_1 = 4 \times 1.2 = 4.8 \text{ volt}$$

So, the potential across  $8\Omega$  resistance is also 4.8 volt.

$$\text{Current } i_2 = \frac{V}{8} = \frac{4.8}{8} = 0.6 \text{ amp}$$

$$\text{Current in } 2\Omega \text{ resistance } i = i_1 + i_2$$

$$\therefore i = 1.2 + 0.6 = 1.8 \text{ amp}$$

Potential difference across  $2\Omega$  resistance

$$V_{BC} = 1.8 \times 2 = 3.6 \text{ volts}$$

12. (900)  $i = \frac{E}{r} \Rightarrow 30 = \frac{1.5}{r}$

$$r = 0.05 \Omega \Rightarrow H = i^2 rt = (30)^2 \times 0.05 \times 20 = 900 \text{ J}$$

13. (1)  $P = V^2/R$

$$\Rightarrow R = V^2/P \times 10^4 / 100 = 400 \Omega$$


$$S = 10^4/200 = 0.5 \times 10^2 = 50 \Omega$$

$$R / S = 8$$

14. (54) Power dissipated  $= P = \frac{V^2}{R} = \frac{(18)^2}{6} = 54 \text{ W}$

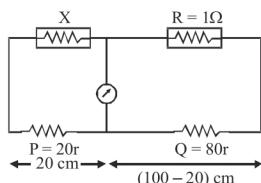15. (0.25) Let unknown resistance be  $X$ . Then condition of

Wheatstone's bridge gives  $\frac{X}{R} = \frac{20r}{80r}$ , where  $r$  is  
resistance of wire per cm.



$$\therefore X = \frac{20}{80} \times R = \frac{1}{4} \times 1 = 0.25 \Omega$$