

Logic Gate

Logic Gate

A digital circuit which either stops a signal or allows to pass through it is called a gate.


Logic gate has 1 or more input but only one output.

There are three basic logic gates:

- 1.) OR Gate
- 2.) AND Gate
- 3.) NOT Gate

OR GATE

0: low
1: high

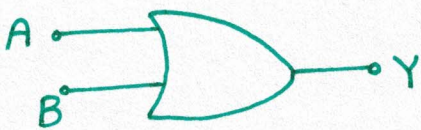


Boolean Algebra

$$\begin{aligned}0 + 0 &= 0 \\1 + 0 &= 1 \\0 + 1 &= 1 \\1 + 1 &= 1\end{aligned}$$

A	B	$Y = A + B$
0	0	0
1	0	1
0	1	1
1	1	1

(Higher one will sent forward)

AND GATE

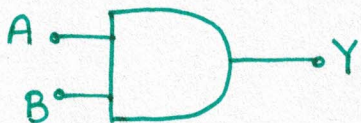


Both must be present
to get output

Boolean Algebra

$$\begin{aligned}0 \cdot 0 &= 0 \\1 \cdot 0 &= 0 \\0 \cdot 1 &= 0 \\1 \cdot 1 &= 1\end{aligned}$$

A	B	$Y = A \cdot B$
0	0	0
1	0	0
0	1	0
1	1	1

NOT GATE

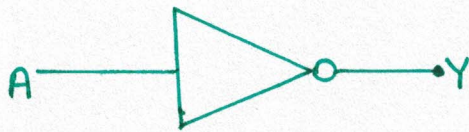

A	$Y = \bar{A}$
0	1
1	0

Boolean Algebra



$$\bar{0} = 1$$

$$\bar{1} = 0$$

COMBINATION OF GATES

NAND GATE

(NOT + AND)

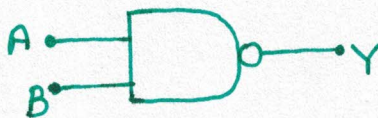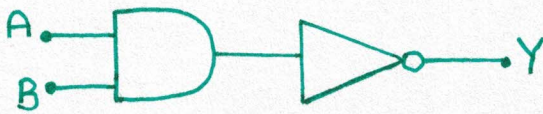

A	B	$Y = \overline{A \cdot B}$
0	0	1
1	0	1
0	1	1
1	1	0

$$\overline{0 \cdot 0} = 1$$



$$\overline{1 \cdot 0} = 1$$

$$\overline{0 \cdot 1} = 1$$

$$\overline{1 \cdot 1} = 0$$

NOR GATE

(NOT + OR)

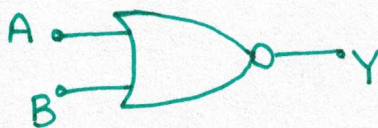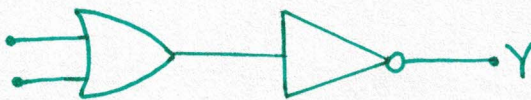

A	B	$Y = \overline{A + B}$
0	0	1
1	0	0
0	1	0
1	1	0


$$\overline{0 + 0} = 1$$

$$\overline{1 + 0} = 0$$


$$\overline{0 + 1} = 0$$

$$\overline{1 + 1} = 0$$


XOR GATE

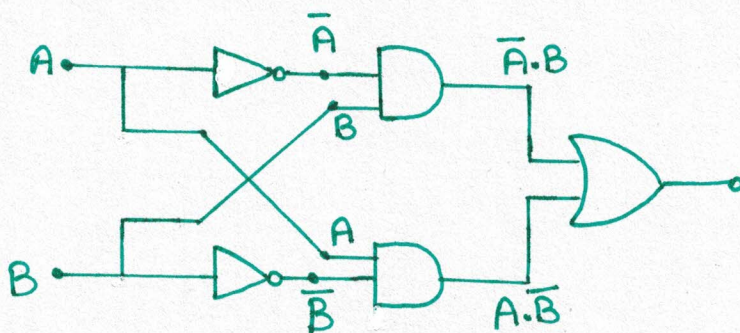


$$Y = \bar{A}B + A\bar{B}$$

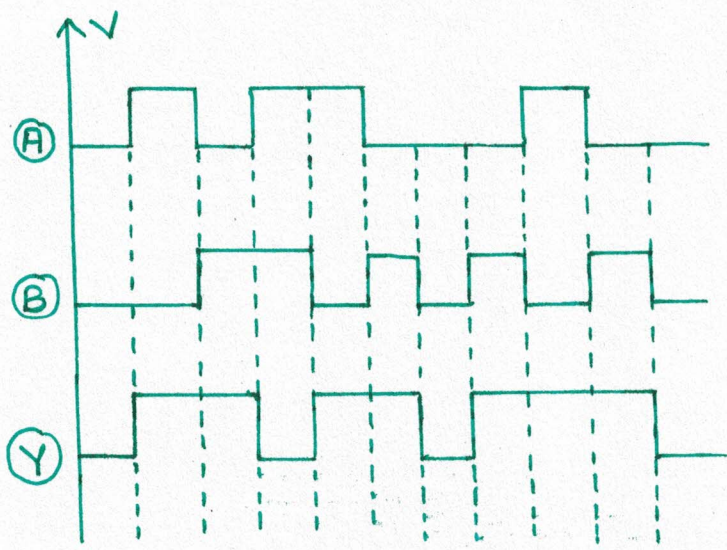

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	0

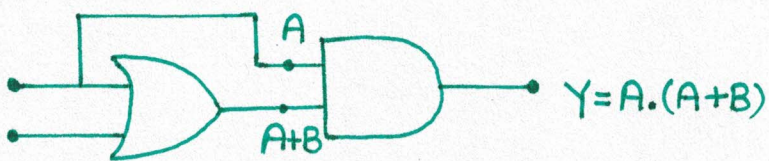

A	B	Y
0	0	0
1	0	1
0	1	0
1	1	1

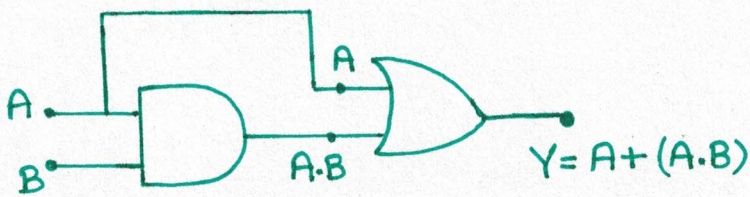

A	B	Y
0	0	0
1	0	1
0	1	0
1	1	1