

# Alternating Current

1. Alternating voltage (V) is represented by the equation

(a)  $V(t) = V_m e^{\omega t}$

(b)  $V(t) = V_m \sin \omega t$

(c)  $V(t) = V_m \cot \omega t$

(d)  $V(t) = V_m \tan \omega t$


▼ **Answer**

Answer: b

---



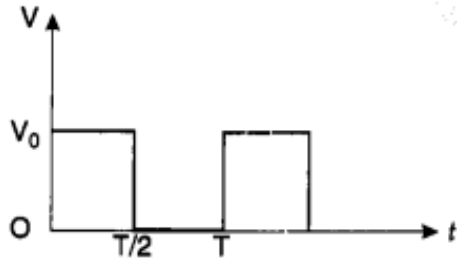2. The rms value of potential difference  $V$  shown in the figure is







- (a)  $\frac{V_0}{\sqrt{3}}$     (b)  $V_0$     (c)  $\frac{V_0}{\sqrt{2}}$     (d)  $\frac{V_0}{2}$

▼ **Answer**

Answer: c

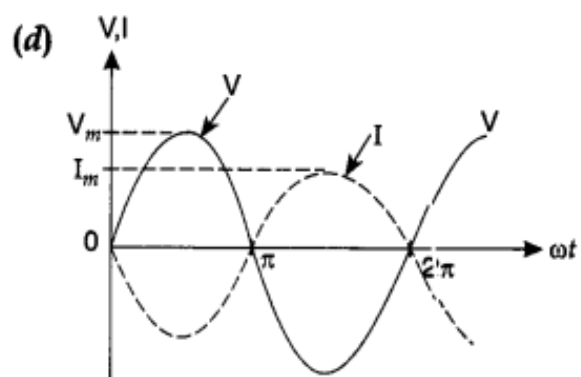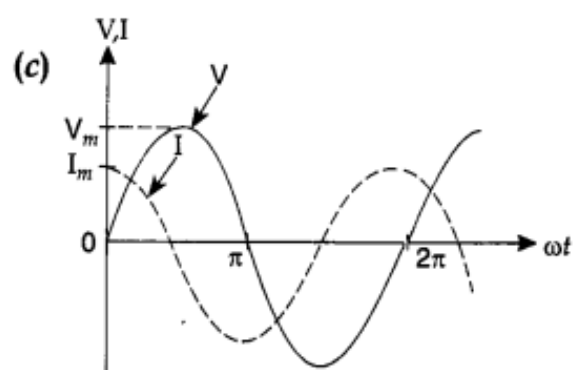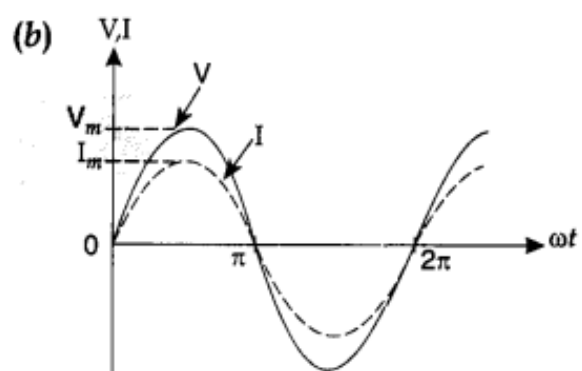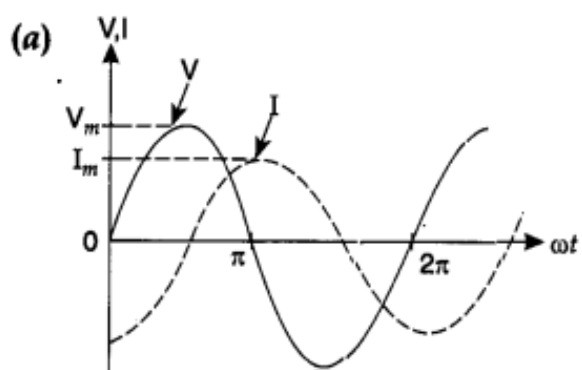3. The phase relationship between current and voltage in a pure resistive circuit is best represented by



▼ Answer

Answer: b

4. In the case of an inductor


- (a) voltage lags the current by  $\frac{\pi}{2}$
- (b) voltage leads the current by  $\frac{\pi}{2}$
- (c) voltage leads the current by  $\frac{\pi}{3}$
- (d) voltage leads the current by  $\frac{\pi}{4}$

▼ Answer

Answer: b

---

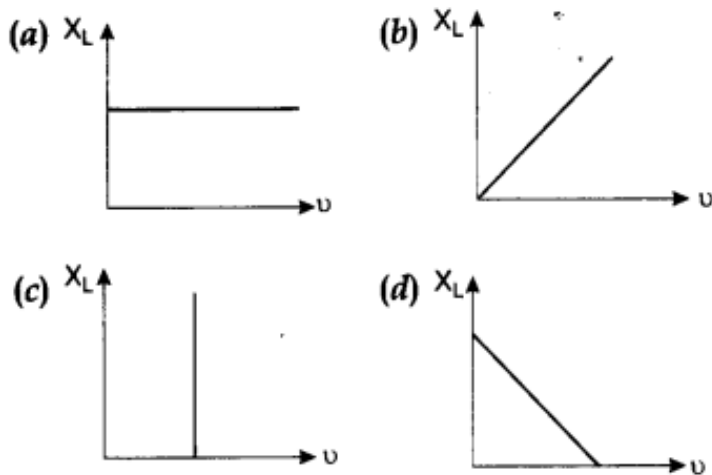5. Which of the following graphs represents the correct variation of inductive reactance  $X_L$  with frequency  $\omega$ ?



▼ Answer

Answer: b

---

6. In a pure capacitive circuit if the frequency of ac source is doubled, then its capacitive reactance will be


- (a) remains same
- (b) doubled
- (c) halved
- (d) zero

▼ Answer

Answer: c

---

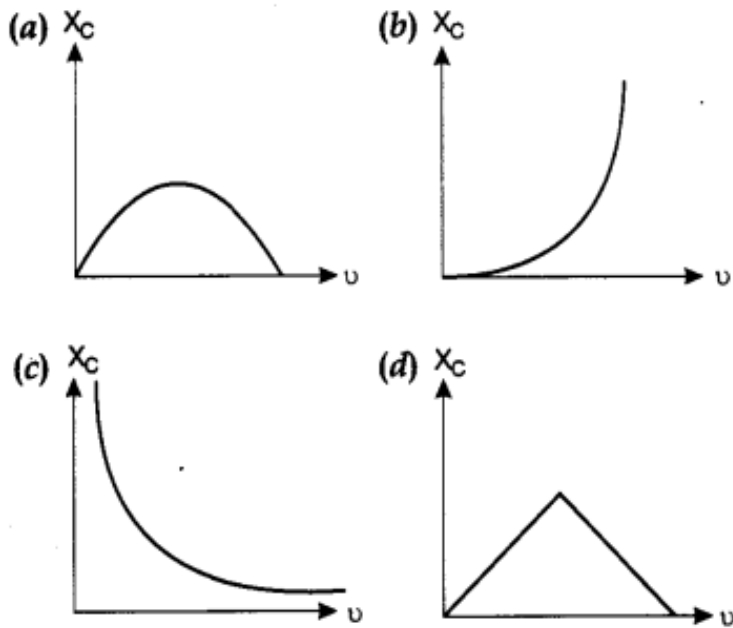7. Which of the following graphs represents the correct variation of capacitive reactance  $X_C$  with frequency  $\omega$ ?



▼ Answer

Answer: c

---

8. In an alternating current circuit consisting of elements in series, the current increases on increasing the frequency of supply. Which of the following elements are likely to constitute the circuit?

- (a) Only resistor
- (b) Resistor and inductor
- (c) Resistor and capacitor
- (d) Only inductor

▼ Answer

Answer: c

---

9. In which of the following circuits the maximum power dissipation is observed?

- (a) Pure capacitive circuit
- (b) Pure inductive circuit
- (c) Pure resistive circuit
- (d) None of these

▼ Answer

Answer: c

---

10. In series LCR circuit, the phase angle between supply voltage and current is

(a)  $\tan \phi = \frac{X_L - X_C}{R}$       (b)  $\tan \phi = \frac{R}{X_L - X_C}$   
(c)  $\tan \phi = \frac{R}{X_L + X_C}$       (d)  $\tan \phi = \frac{X_L + X_C}{R}$

▼ Answer

Answer: a

---

11. In a series LCR circuit the voltage across an inductor, capacitor and resistor are 20 V, 20 V and 40 V respectively. The phase difference between the applied voltage and the current in the circuit is

- (a)  $30^\circ$
- (b)  $45^\circ$
- (c)  $60^\circ$
- (d)  $0^\circ$

▼ Answer

Answer: d

---

12. At resonance frequency the impedance in series LCR circuit is

- (a) maximum
- (b) minimum
- (c) zero
- (d) infinity

▼ Answer

Answer: b

---

13. At resonant frequency the current amplitude in series LCR circuit is

- (a) maximum
- (b) minimum
- (c) zero
- (d) infinity

▼ Answer

Answer: a

---

14. Quality factor and power factor both have the dimensions of

- (a) time
- (b) frequency

- (c) work
- (d) angle

▼ **Answer**

Answer: d

---

15. The natural frequency ( $\omega_0$ ) of oscillations in LC circuit is given by

- (a)  $\frac{1}{2\pi} \frac{1}{\sqrt{LC}}$
- (b)  $\frac{1}{\pi} \frac{1}{\sqrt{2LC}}$
- (c)  $\frac{1}{\sqrt{LC}}$
- (d)  $\sqrt{LC}$

▼ **Answer**

Answer: c

---

16. A transformer works on the principle of

- (a) self induction
- (b) electrical inertia
- (c) mutual induction
- (d) magnetic effect of the electrical current

▼ **Answer**

Answer: c

---

17. For an ideal-step-down transformer, the quantity which is constant for both the coils is

- (a) current in the coils
- (b) voltage across the coils
- (c) resistance of coils
- (d) power in the coils

▼ **Answer**

Answer: d

---