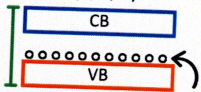
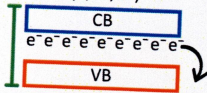


SEMICONDUCTORS

Classification of Semi-conductors

Extrinsic Semiconductors

P-type	N-type
Trivalent impurity is added (B, In, Al)	Pentavalent impurity is added (P, As, Sb)
	
$n_h \gg n_e$	$n_h \ll n_e$
$J \cong en_h V_h$	$J \cong en_e V_e$
$\sigma = \frac{1}{\rho} \cong en_h \mu_h$	$\sigma = \frac{1}{\rho} \cong en_e \mu_e$

Intrinsic Semi-conductors


Si $\rightarrow E_g = 1.1$ eV Ge $\rightarrow E_g = 0.68$ eV $n_e = n_h = n_i$	Conductivity of Semiconductors
$J = ne[V_e + V_h]$	$\sigma = e(n_e \mu_e + n_h \mu_h)$
	$\sigma = \frac{1}{\rho} = en[\mu_e + \mu_h]$

Mass Action Law


$n_i^2 = n_h n_e$	$n_i^2 \rightarrow$ intrinsic carrier density
-------------------	---



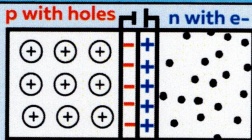
P-N Junction diode or Semi Conductor diode



P-N junction diode

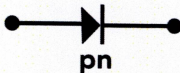

Forward Biasing

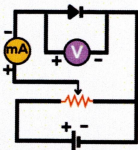

p end → connected with higher potential

n end → connected with lower potential


depletion layer decreases

$$V_p > V_n$$

$$V_p - V_n = \text{positive}$$

Forward current flows in circuit

Reverse Biasing

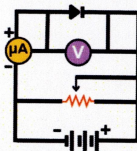

p end → connected with lower potential

n end → connected with higher potential


depletion layer increases

$$V_p < V_n$$

$$V_p - V_n = \text{negative}$$

Reverse current flows in circuit

Characteristic Graph

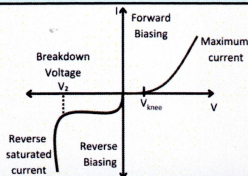


Behaviour in Circuit

Ideal Diode		Real Diode	
Forward Bias	Reverse Bias	$S_i \rightarrow V_{knee} = 0.7 \text{ Ge} \rightarrow V_{knee} = 0.3$	
$R \rightarrow 0$	$R \rightarrow \infty$	Forward Bias	Reverse Bias
Short circuit	Open circuit	Current flow from p to n	Current flow from n to p
$V_{knee} = 0$	$V_{knee} = 0$		
$I = \frac{V_{ext}}{R_{ext}}$	No current will flow	$I = \frac{V_{ext} - V_{knee}}{R_{ext} - R_f}$	No current passed

Application of p-n junction diode

Rectifier	Converts AC input to DC output
------------------	--------------------------------


Half-Wave Rectifier

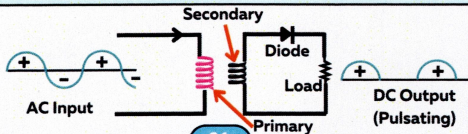

91



Full-Wave Rectifier

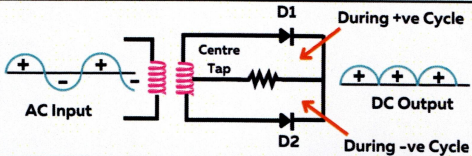


Light Emitting Diode

Less Power
Consumption/Power
losses/Heat losses

$$\lambda_{\text{emit}} = \frac{12400}{E_g} \text{ A}^\circ \cong 100\text{A}^\circ - 500\text{A}^\circ$$


Photo Diode

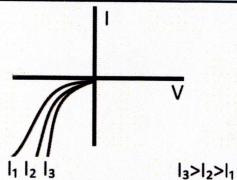- Normal diode in reverse biased
- Used for detection of light




Solar cell

No Biasing

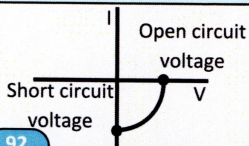



Zener Diode

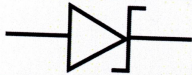It is used as voltage regular when used as reverse biased





Case (i) = $V_{\text{ext}} < V_z$
Behave as real diode

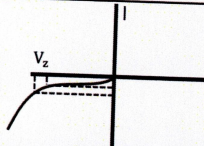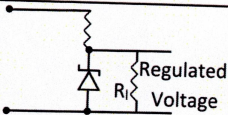Case (ii) = $V_{\text{ext}} \geq V_z$
 V_z will be fixed voltage
 $P_z = V_z I_z$



Transistors



Two junctions, Three terminal diodes

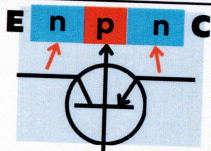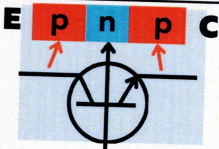

$$I_E = I_b + I_c$$


$$I_b \cong 5\% I_E$$

$$I_c \cong 95\% I_E$$

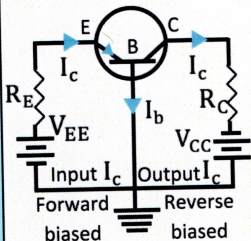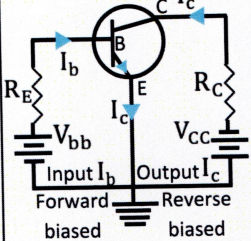Common Base		Common Emitter	
			
Current Gain	$\alpha = \frac{I_C}{I_E}$	Current Gain	$\beta = \frac{I_C}{I_B}$
Voltage Gain	$\alpha \frac{R_C}{R_E}$	Voltage Gain	$\beta \frac{R_C}{R_B}$
Power Gain	$\alpha^2 \frac{R_C}{R_E}$	Power Gain	$\beta^2 \frac{R_C}{R_B}$
Phase	Same phase	Phase	Opp. phase
Relation b/w α & β			
$\alpha = \frac{\beta}{\beta + 1}$		$\beta = \frac{\alpha}{1 - \alpha}$	

Transistor as a device

As an amplifier

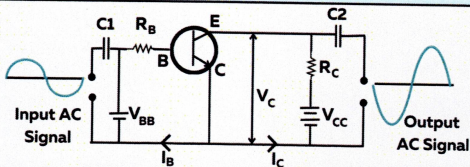

With increase in input voltage (beyond 0.6V) I_C increases and V_0 decreases (Active State)


As a Switch

With increase in input voltage
(0-0.6V)

$V_0 = V_{CC}$ max
(off state)

Non Conducting transistor

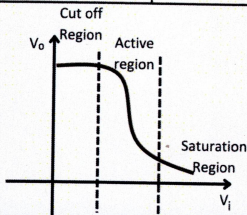I_C becomes max, output
voltage decreases slowly
(ON) Stage



Logic Gates

De Morgan Law

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$


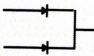

$$\overline{\overline{A} + \overline{B}} = AB$$

$$\overline{AB} = \overline{A} + \overline{B}$$





$$\overline{\overline{AB}} = A + B$$

Different Combinations


Input		OR	NOR	AND	NAND	X-OR	X-NOR
A	B						
0	0	0	1	0	1	0	1
0	1	1	0	0	1	1	0
1	0	1	0	0	1	1	0
1	1	1	0	1	0	0	1

Gate	Boolean Expression	Formed Using	Circuit Symbol	Electrical Circuit
NOT	$Y = \overline{A}$	CE Transistor		Key parallel with bulb
OR	$Y = A + B$			Two keys in parallel and in series with bulb

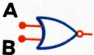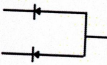

Gate	Boolean Expression	Formed Using	Circuit Symbol	Electrical Circuit
NOR	$Y = \overline{A + B}$	Diode + CE Transistor		Two keys in parallel and in parallel with bulb
AND	$Y = A \cdot B$			Two keys in series and in series with bulb
NAND	$Y = \overline{A \cdot B}$	CE + two diode		two keys in series and in parallel with bulb

Exclusive-OR/XOR

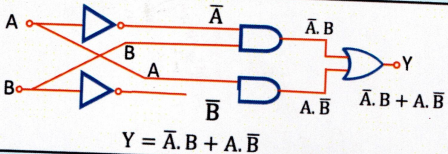

Symbol



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive- NOR



$$Y = \overline{\bar{A}.B + A.\bar{B}}$$



A	0	0	0	1
B	0	1	0	1
Y	1	0	0	1

