

# CAPACITOR



## 1

### Capacitor



Capacitor is a passive device of the circuit which stores electrical energy or charge. It is also known as **condenser**.

$$C = \frac{Q}{V} \quad \text{or} \quad C = \frac{\epsilon_0 A}{d}$$

Capacitance is measured in **Farad (F)**

**Q** = Charge

**A** = Area

**V** = Voltage


**d** = Diameter

## 2

### Combination

#### i

#### Series

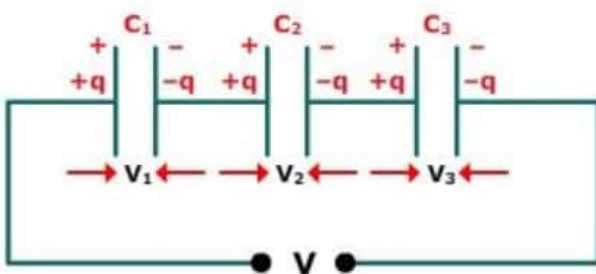

- Charge stored on each capacitor is same and equal to the magnitude of the charge, which comes from the battery..

$$Q = q_1 = q_2 = q_3$$

- The sum of voltage across the individual capacitor is equal to the voltage of the battery.


$$V = V_1 + V_2 + V_3$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

- Equivalent capacitance of the capacitor is always less than the smallest value of the capacitance of the capacitor in the circuit.

#### ii

#### Parallel

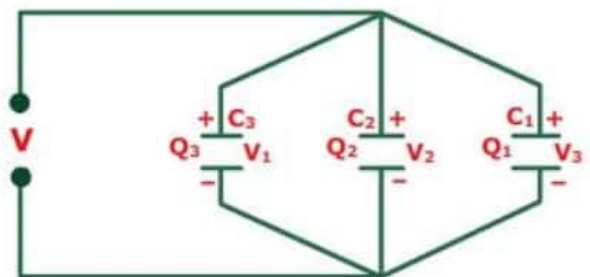

- The Voltage across each capacitor is the same, and it is equal to the voltage of the battery.

$$V = V_1 = V_2 = V_3$$

- The sum of the charge stored on an individual capacitor is equal to the magnitude of the charge, which comes from the battery.

$$Q = q_1 + q_2 + q_3$$

$$C_{eq} = C_1 + C_2 + C_3$$


- Equivalent capacitance of the capacitor is always greater than the largest value of the capacitance of the capacitor in the circuit.



# CIRCUIT SOLUTION


## CHARGING AND DISCHARGING OF A CAPACITOR

### CHARGING OF A CAPACITOR

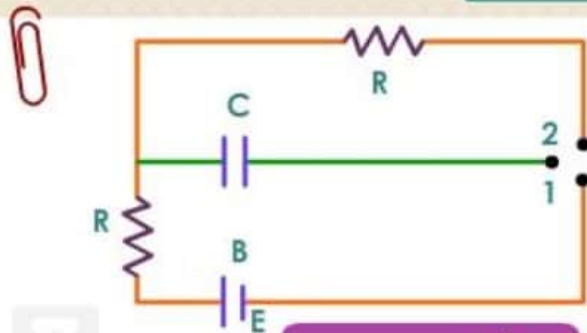


$$q = q_0 \left[ 1 - e^{-\frac{t}{RC}} \right]$$

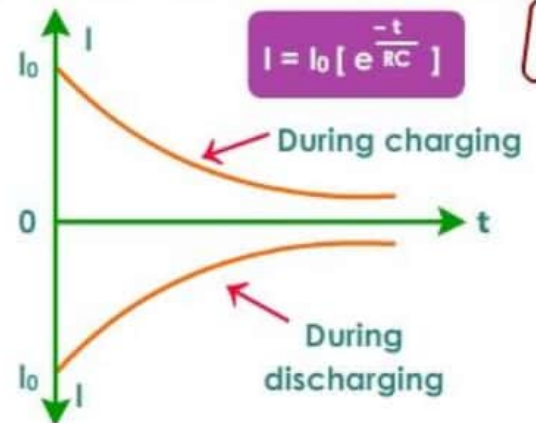Where  $q_0$  = maximum final value of charge at  $t = \infty$ .  
Time  $t = RC$  is known as **Time Constant**.




If  $t = RC = \tau$  = Time constant  
Then,  $I = 0.37 I_0$

### DISCHARGING OF A CAPACITOR

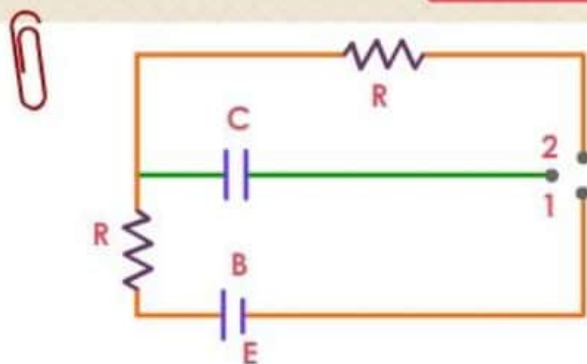
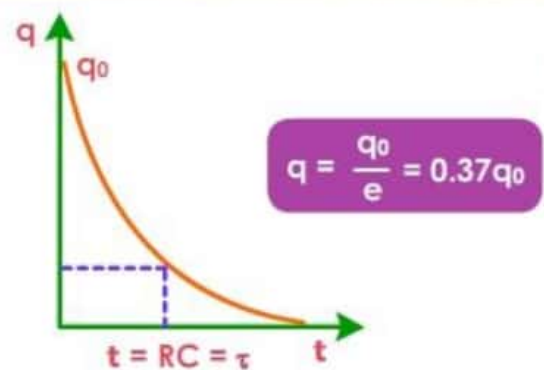
$$q = q_0 \left[ e^{-\frac{t}{RC}} \right]$$




If  $t = RC = \tau$  = time constant,  
Then,  $q = 0.37 q_0$
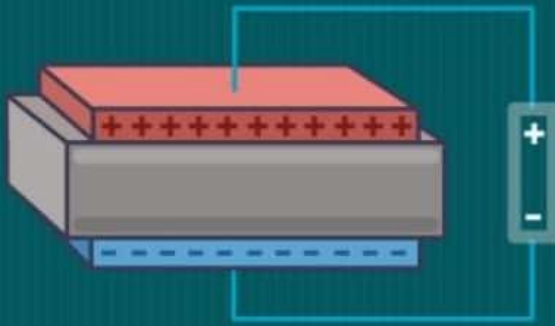
### FORCE BETWEEN THE PLATES OF A CAPACITOR

$$F = - \frac{d}{dx} \left[ \frac{q^2}{2\epsilon_0 A} x \right] = \frac{-1}{2} \frac{q^2}{\epsilon_0 A}$$


The negative sign implies that the force is attractive.





# CAPACITOR WITH DIELECTRIC

## 1. Without Dielectric

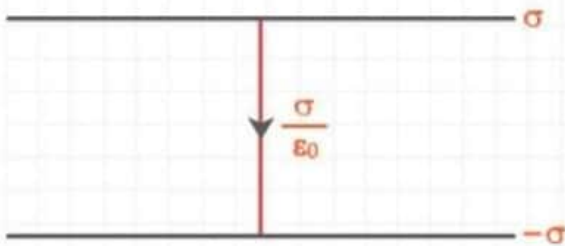

$$E = \frac{\sigma}{\epsilon_0}$$


## 2. With Dielectric



$$C = \frac{AK\epsilon_0}{d}$$


A = Area of Dielectric Slab

## 3. Dielectric Placed Vertically

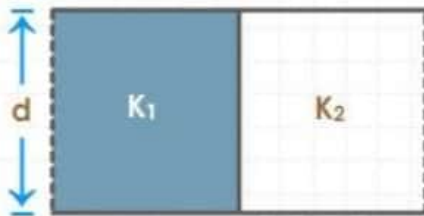

$$C = C_1 + C_2 \rightarrow C = \frac{\epsilon_0(K_1 + K_2)A}{2d}$$

## 4. Dielectric Placed Horizontally

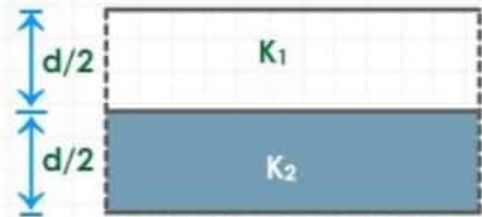

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \rightarrow C = \frac{2\epsilon_0 AK_1 K_2}{(K_1 + K_2)d}$$

## 5. Dielectric Placed Diagonally



$$C = \frac{\epsilon_0 AK_1 K_2}{(K_2 - K_1)} \log_e \frac{K_1}{K_2}$$

## 6. Capacitor With 3 Dielectrics



$$C = \frac{\epsilon_0 A}{d} \left[ \frac{K_1}{2} + \frac{K_2 K_3}{K_2 + K_3} \right]$$