


Chapter 7

Alternating Current

Series L-R, C-R & C-R Circuit

Series L-R Circuit

- Now consider an ac circuit consisting of a resistor of resistance R and an inductor of inductance L in series with an ac source generator.
- Suppose in phasor diagram, current is taken along positive x -direction. The V_R is also along positive x -direction and V_L along positive y -direction as we know that potential difference across a resistance in ac is in phase with current and it leads in phase by 90° with current across the inductor, and as we know $V_R = i_0 R$ & $V_0 = i_0 X_L$
 $i = i_0 \sin \omega t$

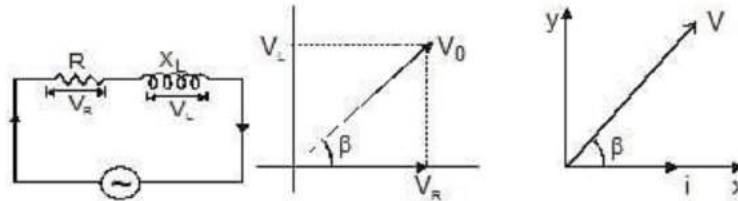

$$V_R(t) = i_0 R \sin \omega t$$

$$V_L(t) = i_0 X_L \sin (\omega t + \pi/2)$$

hence we can write

$$V(t) = i_0 R \sin \omega t + i_0 X_L \sin (\omega t + \pi/2)$$

$$V_0 = i_0 \sqrt{X_L^2 + R^2}$$

where $\sqrt{X_L^2 + R^2}$ is known as impedance (z) of the circuit.

now we can write

$$V_t = i_0 \sqrt{X_L^2 + R^2} \sin(\omega t + \beta)$$

$$\text{where } \tan \beta = \frac{X_L}{R}$$

$$\text{hence } \beta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Example 1. When 100 volt dc is applied across a coil, a current of 1 amp flows through it; when 100 V ac of 50 Hz is applied to the same coil, only 0.5 amp flows. Calculate the resistance of inductance of the coil.

Sol. In case of a coil, i.e., L - R circuit.

$$i = \frac{V}{Z} \text{ with } Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + (\omega L)^2}$$

So when dc is applied, $\omega = 0$, so $z = R$

$$\text{and hence } i = \frac{V}{R} \text{ i.e., } R = \frac{V}{i} = \frac{100}{0.5} = 200?$$

$$\text{but } z = \sqrt{R^2 + \omega^2 L^2} \text{ i.e., } \omega^2 L^2 = Z^2 - R^2$$

$$\text{i.e., } (2\pi fL)^2 = 200^2 - 100^2 = 3 \times 10^4 \text{ (as } \omega = 2\pi f)$$

$$\text{So, } L = \frac{\sqrt{3} \times 10^2}{2\pi \times 50} = \frac{\sqrt{3}}{\pi} \text{ H} = 0.55 \text{ H}$$

Example 2. A 12ohm resistance and an inductance of 0.05/p henry with negligible resistance are connected in series. Across the end of this circuit is connected a 130volt alternating voltage of frequency 50 cycles/second. Calculate the alternating current in the circuit and potential difference across the resistance and that across the inductance.

Sol. The impedance of the circuit is given by

$$Z = \sqrt{R^2 + \omega^2 L^2} = \sqrt{R^2 + (2\pi fL)^2}$$

$$= \sqrt{(12)^2 + [2 \times 3.14 \times 50 \times 0.05 / 3.14]^2} = \sqrt{(144 + 25)} = 13 \text{ ohm}$$

$$\text{Current in the circuit } i = E/Z = \frac{130}{13} = 10 \text{ amp}$$

Potential difference across resistance

$$V_R = iR = 10 \times 12 = 120 \text{ volt}$$

Inductive reactance of coil $X_L = \omega L = 2\pi fL$

$$\text{Therefore, } X_L = 2\pi \times 50 \times \left(\frac{0.05}{\pi}\right) = 5 \text{ ohm}$$

Potential difference across inductance

$$V_L = i \times X_L = 10 \times 5 = 50 \text{ volt}$$


Series C-R Circuit

Now consider an ac circuit consisting of a resistor of resistance R and an capacitor of capacitance C in series with an ac source generator.

Suppose in phasor diagram current is taken along positive x-direction. Then V_R is also along positive x-direction but V_C is along negative y-direction as potential



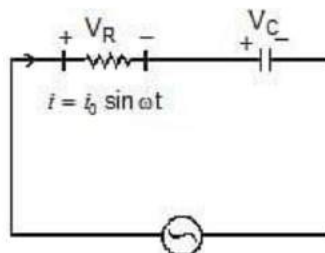difference across a capacitor in ac lags in phase by 90° with the current in the circuit. So we can write,




$$V_R = I_0 R \sin \omega t = V_{R_0} \sin \omega t$$

Potential difference across capacitor

$$V_C = I_0 X_C \sin(\omega t - \pi/2) = V_{C_0} \sin(\omega t - \pi/2)$$

Potential at any instant t
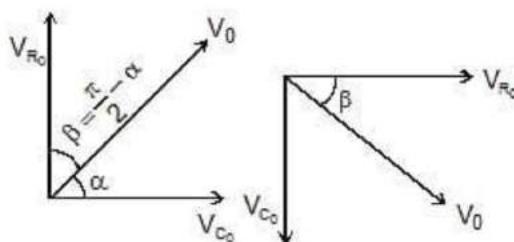
$$V(t) = V_{C_0} \sin(\omega t - \frac{\pi}{2}) + V_{R_0} \sin \omega t = V_0 \sin(\omega t - \pi/2 + \alpha)$$



$$V(t) = V_0 \sin (\omega t + b)$$

$$\tan \alpha = \frac{V_{R_0}}{V_{C_0}} = \frac{R}{X_C}$$

Example 3. An A.C. source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is i . If now the frequency of the source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of reactance to resistance at the original frequency.

Sol. At angular frequency ω , the current in R-C circuit is given by

$$i_{rms} = \frac{e_{rms}}{\sqrt{R^2 + (1/\omega^2 C^2)}} \dots (i)$$

When frequency is changed to $\omega/3$, the current is halved. Thus

$$\frac{i_{rms}}{2} = \frac{e_{rms}}{\sqrt{R^2 + (1/(\omega/3)^2 C^2)}} = \frac{e_{rms}}{\sqrt{R^2 + (9/\omega^2 C^2)}} \dots (ii)$$

From equations (i) and (ii), we have

$$\frac{1}{\sqrt{R^2 + (1/\omega^2 C^2)}} = \frac{2}{\sqrt{R^2 + (9/\omega^2 C^2)}}$$

$$\text{Solving this equation, we get } 3R^2 = \frac{5}{\omega^2 C^2}$$

$$\text{Hence, the ratio of reactance to resistance is } \frac{(1/\omega C)}{R} = \sqrt{\left(\frac{3}{5}\right)}$$

Example 4. A 50 W, 100 V lamp is to be connected to an ac mains of 200 V 50 Hz. What capacitance is essential to be put in series with the lamp?

Sol. As resistance of the lamp $R = \frac{V_s^2}{W} = \frac{100^2}{50} = 200\Omega$ and the maximum current $i = \frac{V}{R} = \frac{100}{200} = \frac{1}{2}A$; so when the lamp is put in series with a capacitance and run at 200 V ac, from $V = iZ$ we have,

$$Z = \frac{V}{i} = \frac{200}{(1/2)} = 400\Omega$$

$$\text{Now as in case of C-R circuit, } Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2},$$

$$\text{i.e., } R^2 + \left(\frac{1}{\omega C}\right)^2 = 160000$$

$$\text{or, } \left(\frac{1}{\omega C}\right)^2 = 16 \times 10^4 - (200)^2 = 12 \times 10^4$$

$$\text{So, } \frac{1}{\omega C} = \sqrt{12} \times 10^2$$

$$\text{or } C = \frac{1}{100\pi \times \sqrt{12} \times 10^2} F$$

$$\text{i.e., } C = \frac{100}{\pi\sqrt{12}} \mu\text{F} = 9.2 \mu\text{F}$$


L.C. Circuit

As shown in figure a capacitor and inductance are connected in series method and alternating voltage is applied across the circuit.

Let X_C is capacitance reactance,

X_L is Inductance reactance,

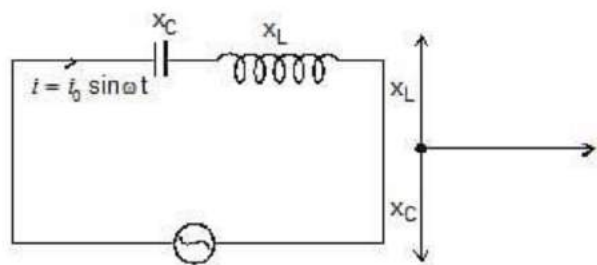$i = i_0 \sin \omega t$ current flowing through the circuit



$$V_C(t) = i_0 X_C \sin (\omega t - \pi/2)$$

$$V_L(t) = i_0 X_L \sin (\omega t + \pi/2)$$

$$\vec{V}_t = \vec{V}_C + \vec{V}_L$$

$$= i_0 X_C \sin \omega t \cos \pi/2 - i_0 X_C \cos \omega t \sin \pi/2 + i_0 X_L \sin \omega t \cos \pi/2 + i_0 X_L \cos \omega t \sin \pi/2$$

$$= i_0 \cos \omega t (X_L - X_C)$$

$$V(t) = V_0 \sin (\omega t + \pi/2)$$

$$V_0 = i_0 Z$$

(Z is impedance)

$X_L - X_C$

I

$$Z = (X_L - X_C)$$

$$\cos \phi = 0$$

$$V_{CO} = i_0 X_C ; X_{L_0} = i_0 X_L$$

Series L-C-R Circuit

Now consider an ac circuit consisting of a resistor of resistance R, a capacitor of capacitance C and an inductor of inductance L are in series with an ac source generator.

Suppose in a phasor diagram current is taken along positive x-direction. Then V_R is along positive x-direction, V_L along positive y-direction and V_C along negative y-direction, as potential difference across an inductor leads the current by 90° in phase while that across a capacitor, lags by 90° .

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

L - R - C circuit


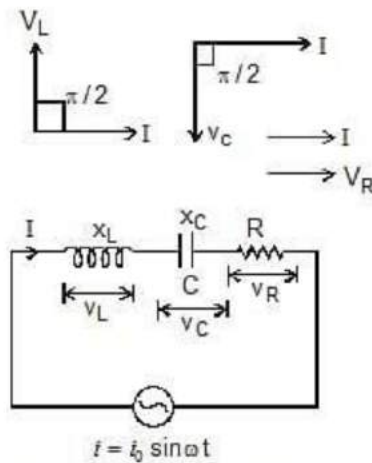


Fig : A series L-C-R circuit

Impedance phasor of above circuit

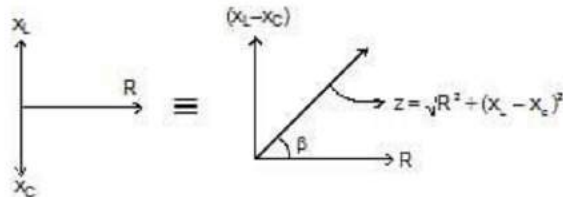


& Impedance triangle

$$z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

here β is phase angle By triangle $\tan \beta = \frac{X_L - X_C}{R}$

Power factor $\cos \phi = \frac{R}{Z}$

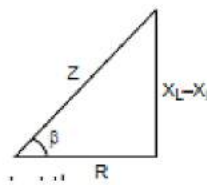

Let I be the current in the series circuit of any instant then

(1) Voltage $V(t) = V_0 \sin(\omega t + \beta) = i_0 Z \sin(\omega t + \beta)$

here $V_0 = i_0 Z$ & $V_{rms} = i_{rms} Z$

(2) $V_L(t) = V_{0L} \sin(\omega t + \pi/2)$ here voltage V_L across the inductance is ahead of current I in phase by $\pi/2$ rad

$V_{0L} = i_0 X_L$

(3) $V_C(t) = V_{0C} \sin(\omega t - \pi/2)$

here voltage V_C across the capacitance lags behind the current I in phase by $\pi/2$ rad

$V_{0C} = i_0 X_C$

(4) $V_R(t) = i_0 R \sin \omega t$

here voltage V_R across the resistor R has same phase as I

$V_{0R} = I_0 R$

Special Case:

(1) When $X_L > X_C$ or $V_L > V_C$ then emf is ahead of current by phase β which is given by

$\tan \beta = \frac{X_L - X_C}{R}$ or $\cos \phi = \frac{R}{Z}$

The series LCR circuit is said to be inductive

(2) When $X_L < X_C$ or $V_L < V_C$ then current is ahead of emf by phase angle β which is given by

$\tan \beta = \frac{X_C - X_L}{R}$ or $\cos \phi = \frac{R}{Z}$

The series LCR circuit is said to be capacitive

(3) When $X_L = X_C$ or $V_L = V_C$, $b = 0$, the emf and current will be in the same phase.

The series LCR circuit is said to be purely resistive. It may also be noted that

$i_0 = \frac{E_0}{Z}$ or $\frac{i_0}{\sqrt{2}} = \frac{E_0}{\sqrt{2} Z}$ or $I_{Rms} = \frac{E_{Rms}}{Z}$

Susceptance: The reciprocal of the reactance of an a.c. circuit is called its susceptance.


Admittance: The reciprocal of the impedance of an a.c. circuit is called its admittance.

Ex.10 Figure shows a series LCR circuit connected to a variable voltage source $V = 10 \sin(\omega t + \pi/4)$;

$$X_L = 10 \Omega, X_C = 6 \Omega, R = 3 \Omega$$

Calculate Z , i_0 , i_{rms} , v_{rms} , V_{L0} , V_{C0} , V_{R0} , b ,

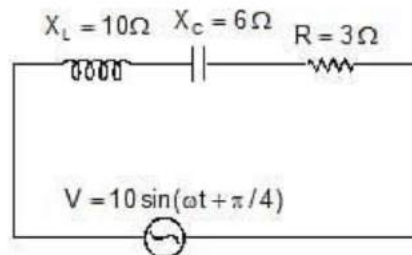V_{LRms} , V_{CRms} , V_{Rms} , $i(t)$, $V_L(t)$, $V_C(t)$, and $V_R(t)$



$$X_L > X_C$$

Sol. $V = 10 \sin(\omega t + \pi/4)$ so $V_0 = 10$ volt

$$V_{rms} = \frac{10}{\sqrt{2}} \text{ volt}$$

$$\text{Therefore, } Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{9 + 16} = 5$$

$$i_0 = \frac{V_0}{Z} = 2$$

$$i_{rms} = \frac{2}{\sqrt{2}} \text{ A}$$

$$V_{L0} = i_0 X_L = 20 \text{ volt}, V_{C0} = i_0 X_C = 12 \text{ volt}$$

$$V_{R0} = i_0 R = 6 \text{ volt}, V_{LRms} = \frac{20}{\sqrt{2}} \text{ volt}$$

$$V_{CRms} = \frac{12}{\sqrt{2}} \text{ volt}, V_{RRms} = \frac{6}{\sqrt{2}} \text{ volt}$$

$$\cos \beta = \frac{R}{Z} = \frac{3}{5} \Rightarrow \beta = 53^\circ$$

$$i(t) = 2 \sin(\omega t + \pi/4 - 53^\circ)$$

$$V_L(t) = 20 \sin(\omega t + \pi/4 - 53^\circ + \pi/2)$$

$$= 20 \sin(\omega t + \frac{3\pi}{4} - 53^\circ - \frac{\pi}{2}) = 12 \sin(\omega t - \frac{\pi}{4} - 53^\circ)$$

$$V_{R(t)} = V_{R0} \sin(\omega t + \frac{\pi}{4} - 53^\circ) = 6 \sin(\omega t + \frac{\pi}{4} - 53^\circ)$$

Ex.11 A resistor of resistance R , an inductor of inductance L and a capacitor of capacitance C all are connected in series with an a.c. supply. The resistance of R is 16 ohm and for a given frequency the inductive reactance of L is 24 ohm and capacitive reactance of C is 12 ohm. If the current in the circuit is 5 amp., find
(a) the potential difference across R , L and C (b) the impedance of the circuit
(c) the voltage of a.c. supply (d) phase angle

Sol. (a) Potential difference across resistance

$$V_R = iR = 5 \times 16 = 80 \text{ volt}$$

Potential difference across inductance

$$V_L = i \times (\omega L) = 5 \times 24 = 120 \text{ volt}$$

Alternating Current: Average & RMS Value

Alternating Current:

1. Alternating Current:

Until now, we have studied only circuits with direct current (dc) which flows only in one direction. The primary source of emf in such circuit is a battery. When a resistance is connected across the terminals of the battery, a current is established in the circuits, which flows in a unique direction from the positive terminal to the negative terminal via the external resistance.

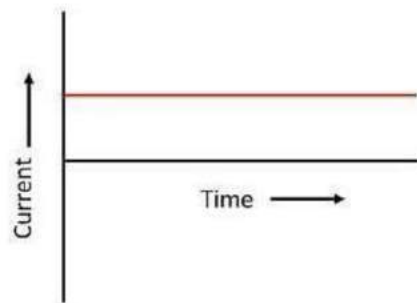


Fig: Direct current

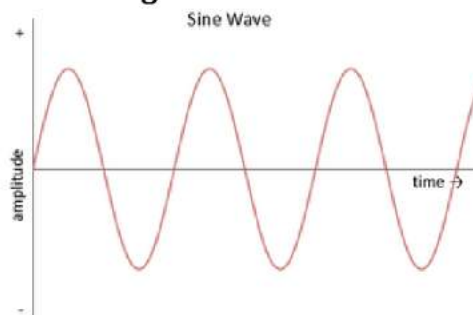


Fig: Alternating current

But most of the electric power generated and used in the world is in the form of **alternating current (ac)**, the magnitude of which changes continuously with time and direction is reversed periodically (as shown in figure III & IV) and it is given by $i = i_0 \sin(\omega t + \phi)$

Here i is instantaneous value of current i.e., the magnitude of current at any instant of time and i_0 is the maximum value of current which is called peak current or the current amplitude and the current repeats its value after each time interval T

$= \frac{2\pi}{\omega}$ as shown in figure. This time interval is called the time period and ω is angular frequency which is equal to 2π times of frequency f .
 $\omega = 2\pi f$

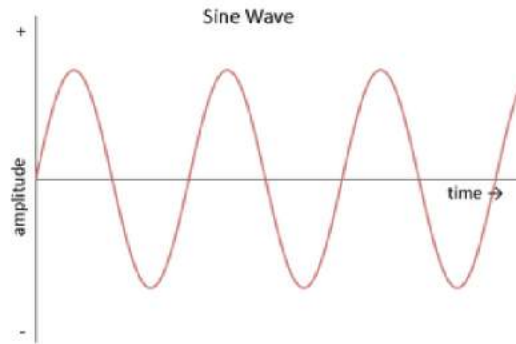


Fig: AC wave

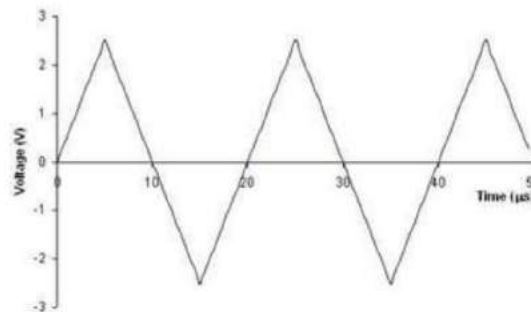



Fig: Triangular wave


The current is positive for half the time period and negative for remaining half period. It means that the direction of current is reversed after each half time period. The frequency of ac in India is 50 Hz.


An alternating voltage is given by:

$$V = V_0 \sin (\omega t + \phi)$$

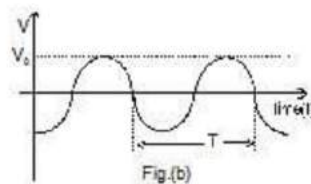It also varies alternatively as shown in the figure (b), where V is instantaneous voltage and V_0 is peak voltage. It is produced by ac generator also called as ac dynamo.



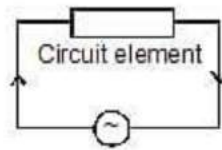AC Circuit: An ac circuit consists of circuit element i.e., resistor, capacitor, inductor or any combination of these and a generator that provides the alternating current as shown in figure. The ac source is represented by symbol  in the circuit.



2. AVERAGE AND RMS VALUE OF ALTERNATING CURRENT:

2.1 Average current (Mean current):

As we know an alternating current is given by

$$i = i_0 \sin(\omega t + \phi) \quad (1)$$

The mean or the average value of ac over any time T is given by

$$i_{avg} = \frac{\int_0^T i dt}{\int_0^T dt}$$

Using equation (1)

$$i_{avg} = \frac{\int_0^T i_0 \sin(\omega t + \phi) dt}{\int_0^T dt}$$

In one complete cycle, the average current


$$i_{avg} = -\frac{i_0}{T} \left[\frac{\cos(\omega t + \phi)}{\omega} \right]_0^T = -\frac{i_0}{T} \left[\frac{\cos(\omega T + \phi) - \cos \phi}{\omega} \right] = -\frac{i_0}{T} \left[\frac{\cos(2\pi + \phi) - \cos \phi}{\omega} \right] = 0 \quad (\text{as } \omega T = 2\pi)$$

Since ac is positive during the first half cycle and negative during the other half cycle so i_{avg} will be zero for long time also. Hence the dc instrument will indicate zero deflection when connected to a branch carrying ac current. So it is defined for either positive half cycle or negative half cycle.

$$i_{avg} = \frac{\int_0^{T/2} i_0 \sin(\omega t + \phi) dt}{\int_0^{T/2} dt} = \frac{2i_0}{\pi} \approx 0.637 i_0$$

$$\text{Similarly } V_{avg} = \frac{2V_0}{\pi} \approx 0.637 V_0$$

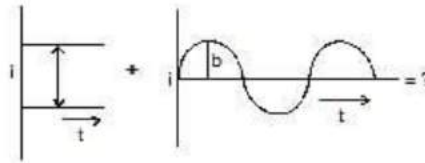Ex. 1 If a direct current of value a ampere is superimposed on an alternating current $i = b \sin \omega t$ flowing through a wire, what is the effective value of the resulting current in the circuit?



Ans: As current at any instant in the circuit will be,
 $i = i_{dc} + i_{ac} = a + b \sin \omega t$

$$\text{So, } i_{\text{eff}} = \left[\frac{\int_0^T i^2 dt}{\int_0^T dt} \right]^{1/2} = \left[\frac{1}{T} \int_0^T (a + b \sin \omega t)^2 dt \right]^{1/2}$$

$$\text{i.e., } = \left[\frac{1}{T} \int_0^T (a^2 + 2ab \sin \omega t + b^2 \sin^2 \omega t) dt \right]^{1/2}$$

but as

$$\frac{1}{T} \int_0^T \sin \omega t dt = 0 \text{ and } \frac{1}{T} \int_0^T \sin^2 \omega t dt = \frac{1}{2}$$

$$\text{So, } i_{\text{eff}} = \left[a^2 + \frac{1}{2} b^2 \right]^{1/2}$$

2.2 R.M.S Value of alternating current:

The notation rms refers to root mean square, which is given by square root of mean of square current.

$$\text{i.e., } i_{\text{rms}} = \sqrt{i_{\text{avg}}^2}$$

$$\begin{aligned} i_{\text{avg}}^2 &= \frac{\int_0^T i^2 dt}{\int_0^T dt} \\ &= \frac{1}{T} \int_0^T i_0^2 \sin^2(\omega t + \phi) dt = \frac{i_0^2}{2T} \int_0^T [1 - \cos 2(\omega t + \phi)] dt \end{aligned}$$

$$= \frac{i_0^2}{2T} \left[t - \frac{\sin 2(\omega t + \phi)}{2\omega} \right]_0^T = \frac{i_0^2}{2T} \left[T - \frac{\sin(4\pi + 2\phi) - \sin 2\phi}{2\omega} \right] = \frac{i_0^2}{2}$$

$$i_{rms} = \frac{i_0}{\sqrt{2}} \approx 0.707 i_0$$

Similarly the rms voltage is given by

$$V_{rms} = \frac{V_0}{\sqrt{2}} \approx 0.707 V_0$$

The significance of rms current and rms voltage may be shown by considering a resistance R carrying a current $i = i_0 \sin(\omega t + \phi)$

The voltage across the resistor will be

$$V_R = Ri = (i_0 R) \sin(\omega t + \phi)$$

The thermal energy developed in the resistor during the time t to $t + dt$ is

$$i^2 R dt = i_0^2 R \sin^2(\omega t + \phi) dt$$

The thermal energy developed in one time period is

$$U = \int_0^T i^2 R dt = R \int_0^T i_0^2 \sin^2(\omega t + \phi) dt = RT \left[\frac{1}{T} \int_0^T i_0^2 \sin^2(\omega t + \phi) dt \right] = i_{rms}^2 RT$$

It means the root mean square value of ac is that value of steady current, which would generate the same amount of heat in a given resistance in a given time.

So in ac circuits, current and ac voltage are measured in terms of their rms values.

Like when we say that the household supply is 220 V ac it means the rms value is 220 V and peak value is 311 V.

Ex. 2 If the voltage in an ac circuit is represented by the equation, $V = \sin(314t - \phi)$, calculate (a) peak and rms value of the voltage, (b) average voltage, (c) frequency of ac.

Ans: (a) For ac voltage,

$$V = V_0 \sin(\omega t - \phi)$$

The peak value of voltage

$$V_0 = 220\sqrt{2} = 311 \text{ V}$$

The rms value of voltage

$$V_{rms} = \frac{V_0}{\sqrt{2}}; V_{rms} = 220 \text{ V}$$

(b) Average voltage in full cycle is zero. Average voltage in half cycle is

$$V_{avg} = \frac{2}{\pi} V_0 = \frac{2}{\pi} \times 311 = 198.17 \text{ V}$$



(c) As $\omega = 2\pi f$, $2\omega f = 314$

$$\text{i.e., } f = \frac{314}{2 \times \pi} = 50 \text{ Hz}$$

Ex. 3 The electric current in a circuit is given by $i = i_0 (t/T)$ for some time. Calculate the rms current for the period $t = 0$ to $t = T$.

Ans: The mean square current is

$$(i^2)_{\text{avg}} = \frac{1}{T} \int_0^T i_0^2 (t/T)^2 dt = \frac{i_0^2}{T^3} \int_0^T t^2 dt = \frac{i_0^2}{3}$$

Thus, the rms current is

$$i_{\text{rms}} = \sqrt{i_{\text{avg}}^2} = \frac{i_0}{\sqrt{3}}$$

Resonance

8. Resonant Frequency

A series LCR circuit is said to be in the resonance condition when the current through it has its maximum value.

The current amplitude I_0 for a series LCR circuit is given by

$$I_0 = \frac{E_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

Clearly I_0 becomes zero both for $\omega \rightarrow 0$ and $\omega \rightarrow \infty$. The value of I_0 is maximum when


$$\omega L - \frac{1}{\omega C} = 0 \quad \text{or} \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

Then impedance will be minimum

$$Z_{\text{min}} = R$$

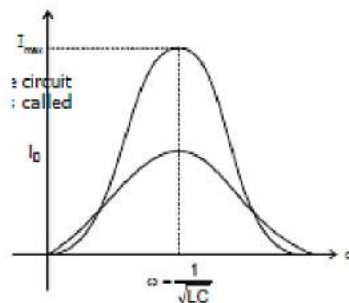The circuit is purely resistive. The current and voltage are in the same phase and the current in the circuit is maximum. This condition of the LCR circuit is called resonance condition.




The variance of I_0 v/s ω shown in following figure

$$I_{0\max} = \frac{V_0}{Z_{\min}} = \frac{V_0}{R}$$


$$\text{So } \cos \phi = \frac{R}{Z} = \frac{R}{R} = 1$$

$$V = V_0 \sin(\omega t)$$


Impedance phase of resonance circuit

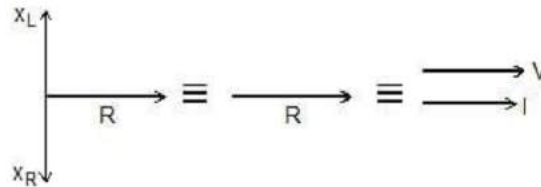

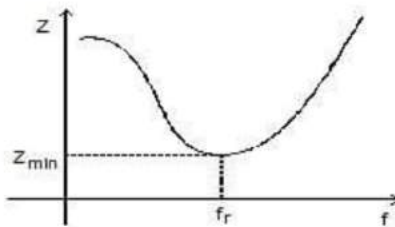Impedance of the circuit is minimum and heat generated in the circuit is maximum.



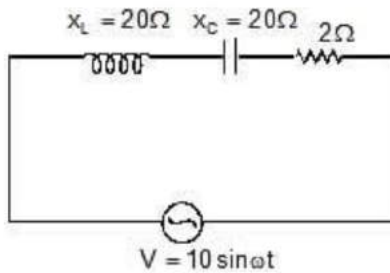Ex.15 In following LCR circuit find Z , $i(t)$, V_{OL} , V_{OL} at resonance frequency



Sol. $Z = Z_{\min} = R = 2\Omega$

$$i_0 = \frac{E_0}{Z} = \frac{10}{2} = 5A$$

$$i(t) = \frac{V(t)}{Z} = 5 \sin \omega t$$

$$V_{OL} = i_0 X_C = 100 \text{ volt}$$

$$V_{OL} = i_0 X_L = 100 \text{ volt}$$

☛ : Above circuit is used as voltage amplifier (magnification) as peak value of voltage by source is only 10 while we can have maximum voltage up to 100 (V_{OC} & V_{OL})

Ex.16 A series LCR with $R = 20\Omega$, $L = 1.5\text{ H}$ and $C = 35\text{ }\mu\text{F}$ is connected to a variable frequency 200 V a.c. supply. When the frequency of the supply equals the natural frequency of the circuit. What is the average power transferred to the circuit in one complete cycle?

Sol. When the frequency of the supply equals the natural frequency of the circuit, resonance occurs.

Therefore, $Z = R = 20\text{ ohm}$

$$i_{\text{rms}} = \frac{E_{\text{rms}}}{Z} = \frac{200}{20} = 10\text{ A}$$


Average power transferred/cycle

$$P = E_{\text{rms}} i_{\text{rms}} \cos 0^\circ = 200 \times 10 \times 1 = 2000\text{ watt}$$

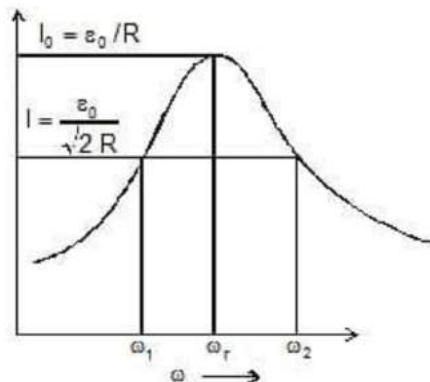8.1 Sharpness of Resonance (Q - factor):

The Q- factor of a series resonant circuit is defined as the ratio of the resonant frequency to the difference in two frequencies taken on the both sides of the

resonant frequency such that at each frequency, the current amplitude becomes $\frac{1}{\sqrt{2}}$ times the value of resonant frequency.



Mathematically Q-factor.

$$Q = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{\omega_r}{2\Delta\omega} = \frac{\text{Resonant frequency}}{\text{Band width}}$$

$$\text{or } Q = \frac{x_L}{R} = \frac{\omega_r L}{R}$$


9. Choke Coil:

A choke coil is simply an inductor with large inductance which is used to reduce current in a.c. circuit without much loss of energy.

Principle. A choke coil is based upon the principle that when a.c. flows through an inductor, the current lags behind the e.m.f. by a phase angle $\pi/2$.

Construction. A choke coil is basically an inductance. It consists of a large number of turns of insulated copper wire wound over a soft iron core. In order to minimize loss of electrical energy due to production of eddy currents, a laminated iron core is used.

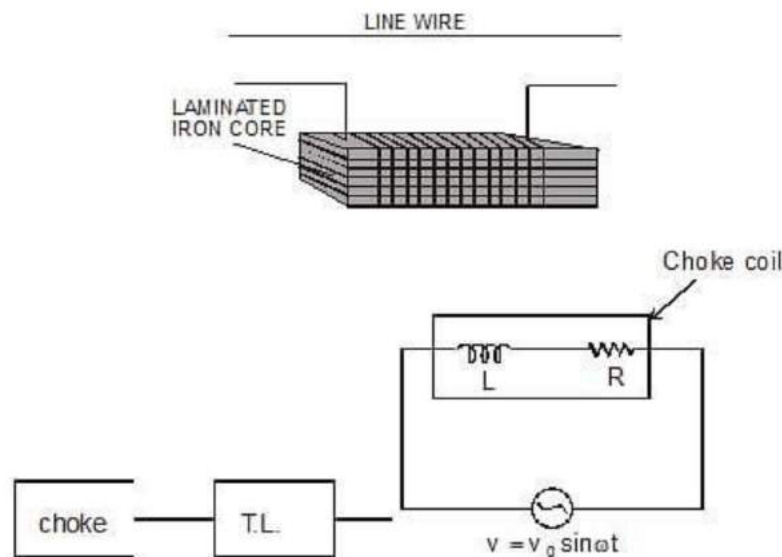In practice, a low frequency choke coil is made of insulated copper wire wound on a soft iron core, while a high frequency choke coil has air as core materials



Working: As shown in fig a choke is put in series across an electrical appliances of resistance R and is connected to an a.c. source.

Average power dissipated per cycle in the circuit is

$$P_{av} = V_{eff} I_{eff} \cos \phi = V_{eff} I_{eff} \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

Inductance L of the choke coil is very large so that $R \ll \omega L$. Then

Power factor $\cos \phi \cong \frac{R}{\omega L} \approx 0$


$$\tan \phi = \frac{X_L}{R}$$

Uses. In a.c. circuit, a choke coil is used to control the current in place of a resistance. If a resistance is used to control the current, the electrical energy will be wasted in

the form of heat. A choke coil decreases the current without wasting electrical energy in the form of heat.

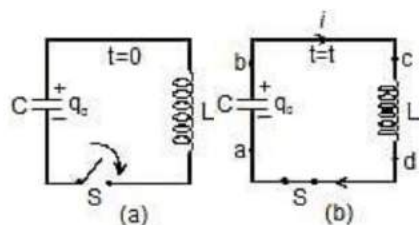10. OSCILLATIONS IN L-C CIRCUIT

If a charged capacitor C is short-circuited through an inductor L , the charge and current in the circuit start oscillating simple harmonically. If the resistance of the circuit is zero, no energy is dissipated as heat. Assume an ideal situation in which energy is not radiated away from the circuit. With these idealizations-zero resistance and no radiation, the oscillations in the circuit persist indefinitely and the energy is transferred from capacitor's electric field to the inductor's magnetic field back and forth. The total energy associated with the circuit is constant. This is analogous to the transfer of energy in an oscillating mechanical system from potential energy to kinetic energy and back, with constant total energy. Such an analogous mechanical system is an example of spring mass system.



Let us now derive an equation for the oscillations of charge and current in an L-C circuit. Refer figure (a): The capacitor is charged to a potential difference V such that charge on capacitor $q_0 = CV$

Here q_0 is the maximum charge on the capacitor. At time $t = 0$, it is connected to an inductor through a switch S . At time $t = 0$, the switch S is closed.

Refer figure (b): When the switch is closed, the capacitor starts discharging. Let at time t charge on the capacitor is q ($< q_0$) and since, it is further decreasing, there is a current i in the circuit in the direction shown in figure.

The potential difference across capacitor = potential difference across inductor, or $V_b - V_a = V_c - V_d$

$$\text{Therefore, } \frac{q}{C} = L \left(\frac{di}{dt} \right) \quad \dots(1)$$

Now, as the charge is decreasing, $i = \left(\frac{-dq}{dt} \right)$

$$\text{or } \frac{di}{dt} = - \frac{d^2q}{dt^2}$$

Substituting in equation (1), we get

$$\frac{q}{C} = -L \left(\frac{d^2q}{dt^2} \right)$$

$$\text{or } \frac{d^2 q}{dt^2} = - \left(\frac{1}{LC} \right) q \quad \dots(2)$$

This is the standard equation of simple harmonic motion $\left(\frac{d^2 x}{dt^2} = -\omega^2 x \right)$

$$\text{Here } \omega = \frac{1}{\sqrt{LC}} \quad \dots(3)$$

The general solution of equation (2), is

$$q = q_0 \cos(\omega t \pm \phi) \quad \dots(4)$$

In our case $\phi = 0$ as $q = q_0$ at $t = 0$.

Thus, we can say that the charge in the circuit oscillates with angular frequency ω given by equation (3). Thus,

In L - C oscillations, q , i and $\frac{di}{dt}$ all oscillate simple harmonically with same angular

frequency ω , but the phase difference between q and i or between i and $\frac{di}{dt}$ is $\frac{\pi}{2}$. Their amplitudes are q_0 , $q_0 \omega$ and $\omega^2 q_0$ respectively. So

$$q = q_0 \cos \omega t, \text{ then } \dots(5)$$

$$i = - \frac{dq}{dt} = q_0 \omega \sin \omega t \quad (6)$$

$$\text{and } \frac{di}{dt} = q_0 \omega^2 \cos \omega t \quad (7)$$


Potential energy in the capacitor

$$U_C = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \frac{q_0^2}{C} \cos^2 \omega t \quad \dots(8)$$

Potential energy in the inductor

$$U_L = \frac{1}{2} L i^2 = \frac{1}{2} \frac{q_0^2}{C} \sin^2 \omega t \quad \dots(9)$$

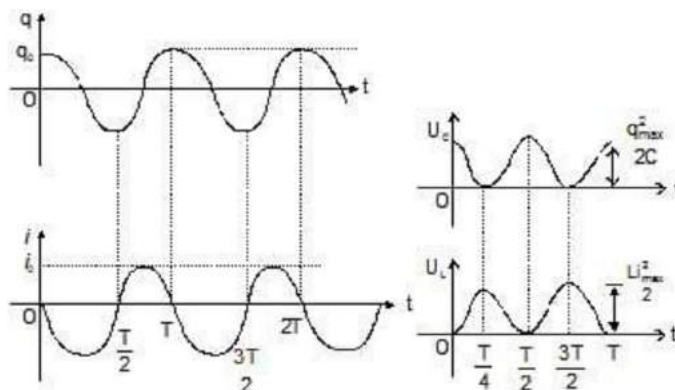Thus potential energy stored in the capacitor and that in the inductor also oscillates between maximum value and zero with double the frequency. All these quantities are shown in the figures that follows



Ex.17 A capacitor of capacitance $25\ \mu\text{F}$ is charged to $300\ \text{V}$. It is then connected across a $10\ \mu\text{H}$ inductor. The resistance of the circuit is negligible.

- Find the frequency of oscillation of the circuit.
- Find the potential difference across capacitor and magnitude of circuit current $1.2\ \text{ms}$ after the inductor and capacitor are connected.
- Find the magnetic energy and electric energy at $t = 0$ and $t = 1.2\ \text{ms}$.

Sol. (a) The frequency of oscillation of the circuit is

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Substituting the given values we have,
$$f = \frac{1}{2\pi\sqrt{(10 \times 10^{-3})(25 \times 10^{-6})}} = \frac{10^3}{\pi}\ \text{Hz}$$

(b) Charge across the capacitor at time t will be,

$$q = q_0 \cos \omega t$$

$$\text{and } i = -q_0 \omega \sin \omega t$$

$$\text{Here } q_0 = CV_0 = (25 \times 10^{-6})(300) = 7.5 \times 10^{-3}\ \text{C}$$

Now, charge is the capacitor after $t = 1.2 \times 10^{-3}\ \text{s}$ is,

$$q = (7.5 \times 10^{-3}) \cos (2\pi \times 318.3)(1.2 \times 10^{-3})\ \text{C} \\ = 5.53 \times 10^{-3}\ \text{C}$$

Therefore, P.D. across capacitor,

$$V = \frac{|q|}{C} = \frac{5.53 \times 10^{-3}}{25 \times 10^{-6}} = 221.2\ \text{volt}$$

The magnitude of current in the circuit at

$t = 1.2 \times 10^{-3}\ \text{s}$ is,

$$|i| = q_0 \omega \sin \omega t$$

$$= (7.5 \times 10^{-3})(2\pi)(318.3) \sin (2\pi \times 318.3)(1.2 \times 10^{-3})\ \text{A} = 10.13\ \text{A}$$

(c) At $t = 0$: Current in the circuit is zero. Hence $U_L = 0$

Charge on the capacitor is maximum

$$\text{Hence, } U_c = \frac{1}{2} \frac{q_0^2}{C}$$

$$\text{or } U_c = \frac{1}{2} \times \frac{(7.5 \times 10^{-3})^2}{(25 \times 10^{-6})} = 1.125\ \text{J}$$

Therefore, Total energy $E = U_L + U_c = 1.125\ \text{J}$

At $t = 1.2\ \text{ms}$

$$U_L = \frac{1}{2} Li^2 = \frac{1}{2} (10 \times 10^{-3}) (10.13)^2 = 0.513\ \text{J}$$



$$U_C = E - U_L = 1.125 - 0.513 = 0.612 \text{ J}$$

Other wise U_C can be calculated as,


$$U_C = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \times \frac{(5.53 \times 10^{-3})^2}{(25 \times 10^{-6})} = 0.612$$

Series AC Circuit

3. SERIES AC CIRCUIT

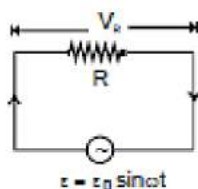3.1 When only Resistance is in an AC circuit

Consider a simple ac circuit consisting of a resistor of resistance R and an ac generator, as shown in the figure. According to Kirchhoff's loop law at any instant, the algebraic sum of the potential difference around a closed loop in a circuit must be zero.



$$\varepsilon - V_R = 0$$

$$\varepsilon - i_R R = 0$$

$$\varepsilon_0 \sin \omega t - i_R R = 0$$


$$i_R = \frac{\varepsilon_0}{R} \sin \omega t = i_0 \sin \omega t \text{ (i)}$$

where i_0 is the maximum current. $i_0 = \frac{\varepsilon_0}{R}$

From above equations, we see that the instantaneous voltage drop across the resistor

$$V_R = i_0 R \sin \omega t \dots \text{(ii)}$$

We see in equation (i) & (ii), i_R and V_R both vary as $\sin \omega t$ and reach their maximum values at the same time as shown in figure (a), they are said to be in phase. A phasor diagram is used to represent phase relationships. The lengths of the arrows correspond to V_0 and i_0 . The projections of the arrows onto the vertical axis give V_R and i_R . In case of the single-loop resistive circuit, the current and voltage phasors lie along the same line, as shown in figure (b), because i_R and V_R are in phase.

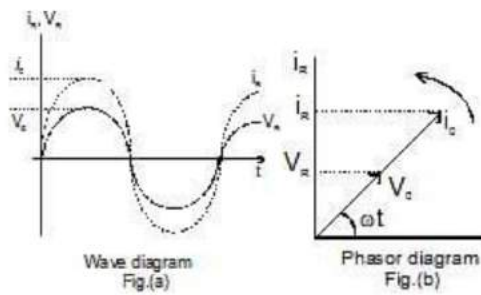


3.2 When only Inductor is in An AC circuit

Now consider an ac circuit consisting only of an Inductor of inductance L connected to the terminals of an ac generator, as shown in the figure. The induced emf across the inductor is given by $L di/dt$. On applying Kirchhoff's loop rule to the circuit

$$\varepsilon - V_L = 0 \Rightarrow \varepsilon - L \frac{di}{dt} = 0$$

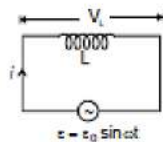When we rearrange this equation and substitute



$\varepsilon = \varepsilon_0 \sin \omega t$, we get

$$L \frac{di}{dt} = \varepsilon_0 \sin \omega t \dots (iii)$$

Integration of this expression gives the current as a function of time

$$i_L = \frac{\varepsilon_0}{L} \int \sin \omega t dt = -\frac{\varepsilon_0}{\omega L} \cos \omega t + C$$

For average value of current over one time period to be zero, $C = 0$

$$\text{Therefore, } i_L = -\frac{\varepsilon_0}{\omega L} \cos \omega t$$

When we use the trigonometric identity

$\cos \omega t = -\sin(\omega t - \pi/2)$, we can express equation as

$$i_L = \frac{\varepsilon_0}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right) \dots (iv)$$

From equation (iv), we see that the current reaches its maximum values when $\cos \omega t = 1$.

$$i_0 = \frac{\varepsilon_0}{\omega L} = \frac{\varepsilon_0}{X_L} \dots (v)$$

where the quantity X_L , called the inductive reactance, is

$$X_L = \omega L$$


The expression for the rms current is similar to equation (v), with ε_0 replaced by ε_{rms} .

Inductive reactance, like resistance, has unit of ohm.

$$V_L = L \frac{di}{dt} = \varepsilon_0 \sin \omega t = i_0 X_L \sin \omega t$$


We can think of equation (v) as Ohm's law for an inductive circuit.

On comparing result of equation (iv) with equation (iii), we can see that the current and voltage are out of phase with each other by $\pi/2$ rad, or 90° . A plot of voltage and current versus time is given in figure (a). The voltage reaches its maximum value one quarter of an oscillation period before the current reaches its maximum value. The corresponding phasor diagram for this circuit is shown in figure (b). Thus, we see that for a sinusoidal applied voltage, the current in an inductor always lags behind the voltage across the inductor by 90° .

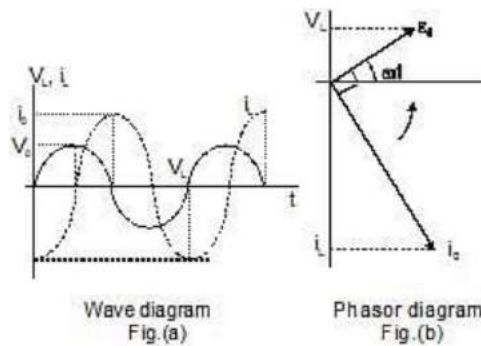

Ex.4 An inductor of inductance $L = 5 \text{ H}$ is connected to an

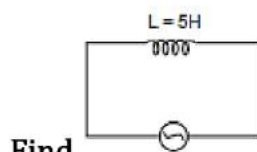AC source having voltage $v = 10 \sin (10t + \frac{\pi}{6})$



Find

- (i) Inductive Reactance (x_L)
- (ii) Peak & Rms voltage (V_0 & V_{rms})
- (iii) Peak & Rms current (I_0 & I_{rms})
- (iv) Instantaneous current ($I(t)$)

Sol. (i) $x_L = \omega L = 10 \times 5 = 50$

(ii) $v_0 = 10$

$$V_{\text{rms}} = \frac{10}{\sqrt{2}}$$


$$(iii) I_0 = \frac{V_0}{X_L} = \frac{1}{5}$$

$$I_{\text{rms}} = \frac{1}{5\sqrt{2}}$$

$$(iv) I(t) = \frac{1}{5} \sin(10t + \frac{\pi}{6} - \frac{\pi}{2})$$

3.3 When only Capacitor is in An AC circuit

Figure shows an ac circuit consisting of a capacitor of capacitance C connected across the terminals of an ac generator. On applying Kirchhoff's loop rule to this circuit, we get

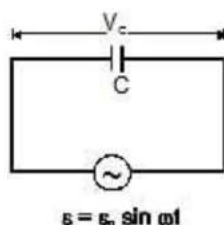

$$\varepsilon - V_C = 0$$

$$V_C = \varepsilon = \varepsilon_0 \sin \omega t \dots (vi)$$

where V_C is the instantaneous voltage drop across the capacitor. From the definition of capacitance, $V_C = Q/C$, and this value for V_C substituted into equation gives

$$Q = C \varepsilon_0 \sin \omega t$$

Since $i = dQ/dt$, on differentiating above equation gives the instantaneous current in the circuit.

$$i_C = \frac{dQ}{dt} = C \varepsilon_0 \omega \cos \omega t$$

Here again we see that the current is not in phase with the voltage drop across the capacitor, given by equation (vi). Using the trigonometric identity $\cos \omega t = \sin(\omega t + \pi/2)$, we can express this equation in the alternative form

$$i_C = \omega C \varepsilon_0 \sin\left(\omega t + \frac{\pi}{2}\right) \dots (vii)$$

From equation (vii), we see that the current in the circuit reaches its maximum value when $\cos \omega t = 1$.

$$i_0 = \omega C \varepsilon_0 = \frac{\varepsilon_0}{X_C}$$

Where X_C is called the capacitive reactance.


$$X_C = \frac{1}{\omega C}$$

The SI unit of X_C is also ohm. The rms current is given by an expression similar to equation with V_0 replaced by V_{rms} .

Combining equation (vi) & (vii), we can express the instantaneous voltage drop across the capacitor as

$$V_C = V_0 \sin \omega t = i_0 X_C \sin \omega t$$


Comparing the result of equation (v) with equation (vi), we see that the current is $\pi/2$ rad = 90° out of phase with the voltage across the capacitor. A plot of current and voltage versus time, shows that the current reaches its maximum value one quarter of a cycle sooner than the voltage reaches its maximum value. The corresponding phasor diagram is shown in the figure (b). Thus we see that for a sinusoidally applied emf, the current always leads the voltage across a capacitor by 90° .

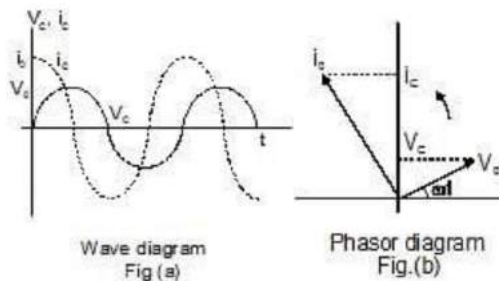

Brain Teaser

What is the reactance of a capacitor connected to a constant DC source?

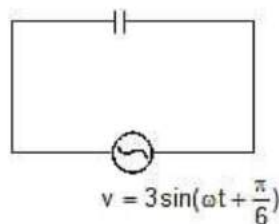Ex.5 A capacitor of capacitive reactance 5Ω is connected with A.C. source having voltage $V = 3 \sin(\omega t + \pi/6)$. Find rms and Peak voltage rms and peak current and instantaneous current



Sol. On comparing with

$$v = v_0 \sin(\omega t + \phi) \Rightarrow v_0 = 3$$

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{3}{\sqrt{2}} \Rightarrow I_{rms} = \frac{V_{rms}}{X_c} = \frac{3}{5\sqrt{2}}$$

$$I_0 = \frac{V_0}{X_c} = \frac{3}{5} \Rightarrow I(t) = I_0 \sin\left(\omega t + \frac{\pi}{6} + \frac{\pi}{2}\right)$$

Power in an AC Circuit

7. Power in an AC circuit

In case of a steady current the rate of doing work is given by,

$$P = Vi$$

In an alternating circuit, current and voltage both vary with time, so the work done by the source in time interval dt is given by

$$dW = Vi dt$$

Suppose in an ac, the current is leading the voltage by an angle ϕ . Then we can write,

$$V = V_0 \sin \omega t$$

$$\text{and } i = i_0 \sin (\omega t + \phi)$$

$$dW = V_0 i_0 \sin \omega t \sin (\omega t + \phi) dt$$

$$= V_0 i_0 (\sin^2 \omega t \cos \phi + \sin \omega t \cos \omega t \sin \phi) dt$$

The total work done in a complete cycle is

$$W = V_0 i_0 \cos \phi \int_0^T \sin^2 \omega t dt + V_0 i_0 \sin \phi \int_0^T \sin \omega t \cos \omega t dt$$

$$= \frac{1}{2} V_0 i_0 \cos \phi \int_0^T (1 - \cos 2\omega t) dt + \frac{1}{2} V_0 i_0 \sin \phi \int_0^T \sin 2\omega t dt = \frac{1}{2} V_0 i_0 T \cos \phi$$

The average power delivered by the source is, therefore,

$$P = \frac{W}{T} = \frac{1}{2} V_0 i_0 \cos \phi = \left(\frac{V_0}{\sqrt{2}}\right) \left(\frac{i_0}{\sqrt{2}}\right) (\cos \phi)$$

$$= V_{rms} i_{rms} \cos \phi$$

$$\text{or } \langle P \rangle_{\text{one cycle}} = V_{rms} i_{rms} \cos \phi$$

Here, the term $\cos \phi$ is known as **power factor**.

It is said to be leading if current leads voltage, lagging if current lags voltage. Thus, a power factor of 0.5 lagging means current lags the voltage by 60° (as $\cos^{-1} 0.5 = 60^\circ$).

The product of V_{rms} and i_{rms} gives the apparent power. While the true power is obtained by multiplying the apparent power by the power factor $\cos \phi$. Thus,

$$\text{and apparent power} = V_{rms} \times i_{rms}$$

$$\text{True power} = \text{apparent power} \times \text{power factor}$$


For $\phi = 0^\circ$, the current and voltage are in phase. The power is thus, maximum ($V_{rms} \times i_{rms}$). For

$\phi = 90^\circ$, the power is zero. The current is then stated as wattless. Such a case will arise when resistance in the circuit is zero. The circuit is purely inductive or capacitive.

Transformers

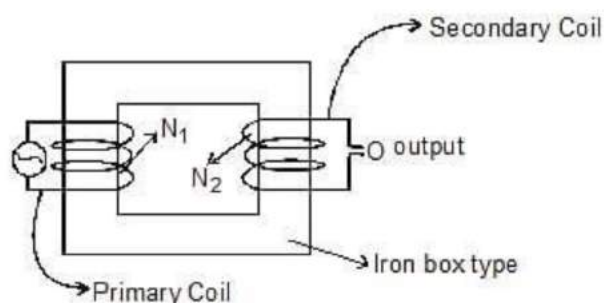11. Transformer:

A transformer is an electrical device for converting an alternating current at low voltage into that at high voltage or vice versa. If it increase the input voltage, it is called step up transformer and if it decreases the input voltage, it is called step down transformer.



Principle: It works on the principle of mutual induction, i.e., when a changing current is passed through one of the two inductively coupled coils, an induced emf is setup in the other coil.

Construction: A transformer essentially consists of two coils of insulated copper wire having different number of turns and wound on the same soft iron core. The coil to which electric energy is supplied is called the primary and the coil from which energy is drawn or output is obtained is called the secondary.

To prevent energy losses due to eddy currents, a laminated sheet is used. Because of high permeability of soft iron, the entire magnetic flux due to the current in the primary coil practically remains in the iron core and hence passes fully through the secondary.

Two types of arrangements are generally used for winding of primary and secondary coils in a transformer.

1. Core type: In this type, the primary and secondary coils are wound on separate limbs of the core.

2. Shell type: In this type the primary and secondary coils are wound one over another on the same limb of the iron core.



Theory: Consider the situation when no load is connected to the secondary, i.e., its terminals are open. Let N_1 and N_2 be the number of terminal in the primary and secondary respectively. Then Induced emf in the primary coil

$$V_p = -N_1 \frac{d\phi}{dt}$$

Induced emf in the secondary coil

$$V_s = -N_2 \frac{d\phi}{dt}$$

where ϕ is the magnetic flux linked with each turn of the primary or secondary at any instant. Thus

$$\frac{V_s}{V_p} = \frac{N_2}{N_1}$$

The ratio $\frac{N_2}{N_1}$ of the number of turns in the secondary to that in the primary called the turns ratio of the transformer. It is also called transformation ratio

for step up transformer: $N_2 > N_1$

for step down transformer: $N_1 > N_2$

Currents in primary and secondary: Assuming the transformer to be ideal one so that there are no energy loss, then

Input power = output power

$$\text{or } V_p I_p = V_s I_s$$

where I_p and I_s are the currents in the primary and secondary respectively.

$$\frac{I_p}{I_s} = \frac{V_s}{V_p} = \frac{N_2}{N_1}$$

Hence

Efficiency: The efficiency of a transformer is defined as

$$\eta = \frac{\text{Power output}}{\text{Power input}} \times 100\%$$

The efficiency of real transformer is fairly high (90 - 98%) though not 100%

Extra Portion For IIT-Mains

Explain with the help of a labelled diagram, the principle and working of an a.c. generator? Write the expression for the emf generated in the coil in terms of speed of rotation. Can the current produced by an a.c. generator be measured with a moving coil galvanometer.

Sol. AC generator: A dynamo or generator is a device which converts mechanical energy into electrical energy. It is based on the principle of electromagnetic induction.

Construction: It consists of the four main parts:



(i) **Field Magnet:** It produces the magnetic field. In the case of a low power dynamo, the magnetic field is generated by a permanent magnet, while in the case of large power dynamo, the magnetic field is produced by an electromagnet.


(ii) **Armature:** It consists of a large number of turns of insulated wire in the soft iron drum or ring. It can revolve around an axle between the two poles of the field magnet. The drum or ring serves the two purposes:

- (i) It serves as a support to coils and
- (ii) It increases the magnetic field due to air core being replaced by an iron core:

(iii) **Slip Rings:** The slip rings R_1 and R_2 are the two metal rings to which the ends of armature coil are connected. These rings are fixed to the shaft which rotates the armature coil so that the rings also rotate along with the armature.

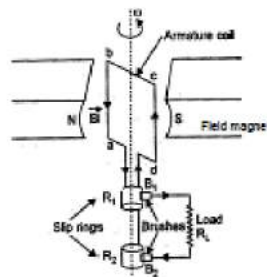(iv) **Brushes:** These are two flexible metal plates or carbon rods (B_1 and B_2) which are fixed and constantly touch the revolving rings. The output current in external load R_L is taken through these brushes.

Working: When the armature coil is rotated in the strong magnetic field, the magnetic flux linked with the coil changes and the current is induced in the coil, its direction being given by Fleming's right hand rule. Considering the armature to be in vertical position and as it rotates in anticlockwise direction, the wire ab moves upward and cd downward, so that the direction of induced current is shown in fig. In the external circuit, the current flows along $B_1 \rightarrow B_L \rightarrow B_2$. The direction of current remains unchanged during the first half turn of armature. During the second half revolution, the wire ab moves downward and cd upward, so the direction of current is reversed and in external circuit it flows along $B_2 \rightarrow R_L \rightarrow B_1$. Thus the direction of induced emf and current changes in the external circuit after each half revolution.



If N is the number of turns in coil, f the frequency of rotation. A area of coil and B the magnetic induction, then induced emf

$$e = -\frac{d\phi}{dt} = \frac{d}{dt}(NBA \cos 2\pi ft)$$

Obviously, the emf produced is alternating and hence the current is also alternating. Current produced by an ac generator cannot be measured by moving coil ammeter, because the average value of ac over fully cycle is zero.

