

# Alternating Current

## Question1

A coil of inductive reactance  $\frac{1}{\sqrt{3}}\Omega$  and a resistance  $1\Omega$  are connected in series to a 200 V, 50 Hz AC source. The time lag between voltage and current is

AP EAPCET 2025 - 26th May Morning Shift

Options:

A.

$$\frac{1}{1200} \text{ s}$$

B.

$$\frac{1}{600} \text{ s}$$

C.

$$\frac{1}{400} \text{ s}$$

D.

$$\frac{1}{800} \text{ s}$$

**Answer: B**

**Solution:**

First, find the angle by which the current lags the voltage. This angle is called  $\phi$ .

Find  $\tan \phi$ :

The formula is  $\tan \phi = \frac{X_L}{R}$ , where  $X_L$  is the inductive reactance and  $R$  is resistance.

Here,  $X_L = \frac{1}{\sqrt{3}} \Omega$  and  $R = 1 \Omega$ .



$$\text{So, } \tan \phi = \frac{\frac{1}{\sqrt{3}}}{1} = \frac{1}{\sqrt{3}}.$$

We know that  $\tan \frac{\pi}{6} = \frac{1}{\sqrt{3}}$ . So,  $\phi = \frac{\pi}{6}$ .

**Find the time period  $T$  of the AC supply:**

The frequency  $f = 50$  Hz, so  $T = \frac{1}{f} = \frac{1}{50}$  seconds.

**Find the time lag  $\Delta t$ :**

The time lag is given by  $\Delta t = \frac{\phi}{2\pi} \times T$ .

Put the values in:  $\Delta t = \frac{\frac{\pi}{6}}{2\pi} \times \frac{1}{50}$ .

Simplify it:  $\Delta t = \frac{1}{12} \times \frac{1}{50} = \frac{1}{600}$  seconds.

---

## Question2

**In a series LCR circuit, the voltages across the capacitor, resistor and inductor are in the ratio 2 : 3 : 6, if the voltage of the AC source in the circuit is 240 V , then the voltage across the inductor is**

**AP EAPCET 2025 - 26th May Evening Shift**

**Options:**

A.

240 V

B.

144 V

C.

96 V

D.

288 V

**Answer: D**

## Solution:

The voltages across the capacitor ( $V_C$ ), resistor ( $V_R$ ), and inductor ( $V_L$ ) have the ratio 2:3:6.

This means  $V_C = 2k$ ,  $V_R = 3k$ , and  $V_L = 6k$  for some number  $k$ .

The total voltage across the circuit is given by:  $V = \sqrt{V_R^2 + (V_L - V_C)^2}$  This formula is used because in an LCR circuit, resistor voltage is in phase with supply, while inductor and capacitor voltages are  $180^\circ$  out of phase with each other.

We are told the source voltage is 240 V:  $240 = \sqrt{(3k)^2 + (6k - 2k)^2}$

Simplifying inside the square root:  $(3k)^2 = 9k^2$ ,  $(6k - 2k)^2 = (4k)^2 = 16k^2$  So,  
 $240 = \sqrt{9k^2 + 16k^2} = \sqrt{25k^2} = 5k$

Now solve for  $k$ :  $5k = 240 \implies k = \frac{240}{5} = 48$

Now, calculate the voltage across the inductor:  $V_L = 6k = 6 \times 48 = 288 \text{ V}$

---

## Question 3

**If the voltage and current in an AC circuit are respectively  $50 \sin(50t) \text{ V}$  and  $50 \sin(50t + \frac{\pi}{4}) \text{ mA}$ , then the power dissipated in the circuit is nearly**

### AP EAPCET 2025 - 24th May Morning Shift

Options:

A.

1.296 W

B.

0.648 W

C.

0.884 W

D.

1.768 W



**Answer: C**

## Solution:

The formula to find the average (real) power in an AC circuit is:

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi \text{ where } \phi \text{ is the phase difference between voltage and current.}$$

The voltage is  $50 \sin(50t)$ , so its maximum (peak) value is 50 V.

The current is  $50 \sin(50t + \frac{\pi}{4})$ , so its peak value is  $50 \text{ mA} = 50 \times 10^{-3} \text{ A}$ .

The phase difference  $\phi$  between voltage and current is  $\frac{\pi}{4}$ .

To get the RMS (root mean square) values from the peak values, divide by  $\sqrt{2}$ :

$$V_{\text{rms}} = \frac{50}{\sqrt{2}}$$

$$I_{\text{rms}} = \frac{50 \times 10^{-3}}{\sqrt{2}}$$

Now, put these values into the power formula:

$$P = \frac{50}{\sqrt{2}} \times \frac{50 \times 10^{-3}}{\sqrt{2}} \times \cos\left(\frac{\pi}{4}\right)$$

$$\cos\left(\frac{\pi}{4}\right) \text{ is } \frac{1}{\sqrt{2}}.$$

So,

$$P = \frac{50}{\sqrt{2}} \times \frac{50}{\sqrt{2}} \times 10^{-3} \times \frac{1}{\sqrt{2}}$$

Multiply the numbers:

$$= \frac{50 \times 50 \times 10^{-3}}{\sqrt{2} \times \sqrt{2} \times \sqrt{2}}$$

$$\sqrt{2} \times \sqrt{2} \times \sqrt{2} = 2\sqrt{2}$$

$$= \frac{2500 \times 10^{-3}}{2\sqrt{2}}$$

$$= \frac{2.5}{2\sqrt{2}}$$

This is approximately equal to 0.884 W.

---

## Question4

**In a series resonant LCR circuit, for the power dissipated to become half of the maximum power dissipated, the current amplitude is**



## AP EAPCET 2025 - 23rd May Evening Shift

### Options:

A.

$\frac{1}{\sqrt{2}}$  times its maximum value.

B.

1/2 times its maximum value.

C.

twice its maximum value.

D.

$\sqrt{2}$  times its maximum value.

**Answer: A**

### Solution:

#### Given:

In a **series LCR circuit at resonance**, the **power dissipated** is maximum.

We need to find:

For the **power dissipated** to become **half of its maximum value**, what is the **current amplitude**?

#### Step 1: Relation between Power and Current

The average power dissipated in an AC circuit is given by:

$$P = I_{\text{rms}}^2 R$$

At resonance, the impedance is purely resistive ( $Z = R$ ), and the current is maximum ( $I = I_{\text{max}}$ ).

So maximum power is:

$$P_{\text{max}} = I_{\text{rms,max}}^2 R = \left( \frac{I_{\text{max}}}{\sqrt{2}} \right)^2 R = \frac{I_{\text{max}}^2 R}{2}$$

But we only need **relative power**, so we can use  $P \propto I^2$ .

#### Step 2: Condition for half power

We are told  $P = \frac{1}{2}P_{\max}$

So:

$$I^2 R = \frac{1}{2} I_{\max}^2 R$$

Simplify:

$$I = \frac{I_{\max}}{\sqrt{2}}$$

 **Final Answer:**

**Option A:**  $\frac{1}{\sqrt{2}}$  times its maximum value.

So the current amplitude becomes  $1/\sqrt{2}$  times its maximum value when the power is half of the maximum.

---

## Question5

**If a resistor of resistance  $4\Omega$ , a capacitor of capacitive reactance  $6\Omega$  and an inductor of inductive reactance  $9\Omega$  are connected in series with an AC source, then the impedance of the circuit is**

**AP EAPCET 2025 - 23rd May Morning Shift**

**Options:**

A.

$19\Omega$

B.

$11\Omega$

C.

$7\Omega$

D.

$5\Omega$

**Answer: D**

**Solution:**



Impedance,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
$$= \sqrt{4^2 + (9 - 6)^2} = \sqrt{16 + 9} = 5\Omega$$

---

## Question6

A resistor of  $450\Omega$  and an inductor are connected in series to an AC source of frequency  $\frac{75}{\pi}$  Hz. If the power factor of the circuit is 0.6 , then the inductance connected in the circuit is

**AP EAPCET 2025 - 22nd May Evening Shift**

**Options:**

A.

6 mH

B.

4 H

C.

4 mH

D.

6 H

**Answer: B**

**Solution:**

Power factor

$$\cos \phi = \frac{R}{Z}$$

$$0.6 = \frac{R}{\sqrt{R^2 + X_L^2}}$$

$$\Rightarrow 0.36 = \frac{R^2}{R^2 + (2\pi fL)^2}$$

$$\Rightarrow 0.36 = \frac{(450)^2}{(450)^2 + (2\pi \times \frac{75}{\pi} L)^2}$$

$$\Rightarrow 0.36 = \frac{(450)^2}{450^2 + (150L)^2}$$

Solving, we get

$$L = 4H$$

---

## Question7

For better tuning of a series  $LCR$  circuit in a communication system, the preferred combination is

### AP EAPCET 2025 - 22nd May Morning Shift

Options:

A.

$$R = 20\Omega : L = 15H : C = 35\mu F$$

B.

$$R = 15\Omega : L = 40H : C = 20\mu F$$

C.

$$R = 25\Omega : L = 15H : C = 45\mu F$$

D.

$$R = 15\Omega : L = 20H : C = 45\mu F$$

**Answer: B**

**Solution:**

For better tuning of a series  $LCR$  circuit in a communication system. Quality factor '  $Q$  ' should be high.

i.e.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

So, for high value of  $Q$ , value of  $R$  and  $C$  should be minimum and value  $L$  should be maximum.



---

## Question8

In an LCR series circuit, if the potential differences across inductor, capacitor and resistor are 60 V, 30 V and 40 V respectively, then the AC voltage applied to the circuit is

AP EAPCET 2025 - 21st May Evening Shift

Options:

A.

50 V

B.

70 V

C.

130 V

D.

60 V

**Answer: A**

**Solution:**

AC voltage applied to the circuit,

$$\begin{aligned} V &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{40^2 + (60 - 30)^2} \\ &= \sqrt{1600 + 900} = \sqrt{2500} \\ &= 50 \text{ V} \end{aligned}$$

---

## Question9

The resonant frequency of an LC circuit is  $f_0$ . If a dielectric slab of constant 16 is inserted completely between the plates of the capacitor, then the resonant frequency is

AP EAPCET 2025 - 21st May Morning Shift

Options:

A.

$$\frac{f}{2}$$

B.

26

C.

$$\frac{6}{4}$$

D.

4f

**Answer: C**

**Solution:**

Resonance frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

When dielectric material is introduced, then new capacitance,

$$C' = C_0K = 16C_0 = 16C$$

∴ New resonance frequency

$$\begin{aligned} f'_0 &= \frac{1}{2\pi\sqrt{LC'}} = \frac{1}{2\pi\sqrt{L \times 16C}} \\ &= \frac{1}{4} \times \frac{1}{2\pi\sqrt{LC}} = \frac{f_0}{4} \end{aligned}$$

---



## Question10

An alternating current is given by  $i = (3 \sin \omega t + 4 \cos \omega t)A$ . The rms current will be

AP EAPCET 2024 - 23th May Morning Shift

Options:

A.  $\frac{7}{\sqrt{2}}$  A

B.  $\frac{1}{\sqrt{2}}$  A

C.  $\frac{5}{\sqrt{2}}$  A

D.  $\frac{3}{\sqrt{2}}$  A

**Answer: C**

**Solution:**

The rms value is found from

writing  $i(t) = A \sin \omega t + B \cos \omega t$  with  $A = 3, B = 4$ ,

using

$$i_{\text{rms}} = \sqrt{\langle i^2 \rangle} = \sqrt{\frac{A^2 + B^2}{2}} = \frac{\sqrt{3^2 + 4^2}}{\sqrt{2}} = \frac{5}{\sqrt{2}} \text{ A}.$$

So the correct choice is Option C:  $\frac{5}{\sqrt{2}}$  A.

---

## Question11

A 50 Hz AC circuit has a 10 mH inductor and a  $2\Omega$  resistor in series. The value of capacitance to be placed in series in the circuit to make the circuit power factor as unity is

AP EAPCET 2024 - 22th May Morning Shift

Options:



A.  $1.014 \times 10^{-6} \text{ F}$

B.  $1.014 \times 10^{-3} \text{ F}$

C.  $2.6 \times 10^{-3} \text{ F}$

D.  $4.125 \times 10^{-3} \text{ F}$

**Answer: B**

### **Solution:**

Given:

Frequency,  $f = 50 \text{ Hz}$

Inductance,  $L = 10 \text{ mH} = 10 \times 10^{-3} \text{ H}$

Resistance,  $R = 2 \Omega$

First, calculate the inductive reactance ( $X_L$ ) using the formula:

$$X_L = 2\pi fL$$

Substituting the given values:

$$X_L = 2\pi \times 50 \times 10 \times 10^{-3} = \pi$$

For the circuit to have a unit power factor, the inductive reactance ( $X_L$ ) must equal the capacitive reactance ( $X_C$ ). Therefore,

$$X_C = X_L$$

The formula for capacitive reactance is:

$$X_C = \frac{1}{2\pi fC}$$

Setting  $X_C = X_L$ , we have:

$$\pi = \frac{1}{2\pi \times 50 \times C}$$

Solving for  $C$ :

$$C = \frac{1}{2(\pi^2) \times 50}$$

$$C = \frac{1}{2 \times 9.8696 \times 50}$$

$$C = \frac{1}{973.036}$$

$$C = 1.014 \times 10^{-3} \text{ F} = 1.014 \text{ mF}$$

Thus, the required capacitance is  $1.014 \times 10^{-3} \text{ F}$ .

---

# Question12

A resistor of resistance  $R$ , inductor of inductive reactance  $2R$  and a capacitor of capacitive reactance  $X_C$  are connected in series to an AC source. If the series  $L - C - R$  circuit is in resonance, then the power factor of the circuit and the value,  $X_C$  are respectively

**AP EAPCET 2024 - 21th May Evening Shift**

**Options:**

A. 0.5 and  $4R$

B. 1 and  $2R$

C. 0.5 and  $2R$

D. 1 and  $4R$

**Answer: B**

**Solution:**

Given an  $L - C - R$  circuit in resonance, let's analyze it:

**Provided Values:**

**Inductive Reactance ( $X_L$ ):**  $2R$

**Resistance ( $R$ ):**  $R$

**Resonance Condition:**

In a resonant circuit, the inductive reactance is equal to the capacitive reactance. Therefore:

$$X_L = X_C$$

$$X_C = 2R$$

**Power Factor:**

The power factor of a circuit is calculated as:

$$P = \frac{\text{Resistance}}{\text{Impedance (Z)}}$$

The impedance in an  $L - C - R$  circuit, when in resonance and when  $X_L = X_C$ , is:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Since  $X_L = X_C$  in resonance:



$$Z = \sqrt{R^2 + (2R - 2R)^2} = R$$

Thus, the power factor is:

$$P = \frac{R}{R} = 1$$

Therefore, when the circuit is in resonance, the capacitive reactance  $X_C = 2R$ , and the power factor is 1.

---

## Question13

**An inductor and a resistor are connected in series to an AC source of voltage  $144 \sin(100\pi t + \frac{\pi}{2})$  V. If the current in the circuit is  $6 \sin(100\pi t + \frac{\pi}{6})$  A, then the resistance of the resistor is**

**AP EAPCET 2024 - 20th May Evening Shift**

**Options:**

A.  $24\Omega$

B.  $36\Omega$

C.  $12\Omega$

D.  $18\Omega$

**Answer: C**

**Solution:**

Given:

The voltage expression:  $V = 144 \sin(100\pi t + \frac{\pi}{2})$  V

The current expression:  $I = 6 \sin(100\pi t + \frac{\pi}{6})$  A

**Analysis**

**Standard Form Comparison:**

The standard forms of voltage and current are:

$$V = V_0 \sin(\omega t + \phi_v)$$

$$I = I_0 \sin(\omega t + \phi_i)$$

**Phase Difference:**



Comparing the given equations, we identify the phases:

$$\text{Voltage phase: } \phi_v = \frac{\pi}{2}$$

$$\text{Current phase: } \phi_i = \frac{\pi}{6}$$

The phase difference,  $\phi$ , between voltage and current is:

$$\phi = \phi_v - \phi_i = \frac{\pi}{2} - \frac{\pi}{6} = \frac{\pi}{3} = 60^\circ$$

### Impedance Calculation:

The impedance  $Z$  of the circuit is given by:

$$Z = \frac{V_0}{I_0} = \frac{144}{6} = 24 \Omega$$

### Resistance Calculation:

The relationship between impedance  $Z$ , resistance  $R$ , and the phase angle  $\phi$  is given by:

$$\frac{R}{Z} = \cos \phi$$

Solving for  $R$ , we have:

$$R = \cos(60^\circ) \times Z = \frac{1}{2} \times 24 = 12 \Omega$$

Therefore, the resistance of the resistor is  $12 \Omega$ .

---

## Question 14

**A resistance of  $20 \Omega$  is connected to a source of an alternating potential  $V = 200 \sin(10\pi t)$ . If  $t$  is the time taken by the current to change from the peak value to rms value, then  $t$  is (in seconds)**

### AP EAPCET 2024 - 20th May Morning Shift

**Options:**

- A.  $25 \times 10^{-1}$
- B.  $2.5 \times 10^{-4}$
- C.  $25 \times 10^{-2}$
- D.  $2.5 \times 10^{-2}$

**Answer: D**

**Solution:**

Given:

**Resistance:**  $R = 20 \Omega$

**Alternating potential:**  $V = 200 \sin(10\pi t)$

The expression for the alternating current  $I$  can be derived as follows:

$$I = \frac{V}{R} = \frac{200 \sin(10\pi t)}{20} = 10 \sin(10\pi t)$$

We know that the root mean square (RMS) current is related to the peak current by the equation:

$$I_{\text{RMS}} = \frac{I_{\text{peak}}}{\sqrt{2}}$$

Thus, the RMS current is also expressed as:

$$I_{\text{RMS}} = I_{\text{peak}} \sin(10\pi t)$$

Setting the RMS and the peak relation,

$$\frac{I_{\text{peak}}}{\sqrt{2}} = I_{\text{peak}} \sin(10\pi t)$$

This simplifies to:

$$\frac{1}{\sqrt{2}} = \sin(10\pi t)$$

The sine of  $\frac{\pi}{4}$  is known to be  $\frac{1}{\sqrt{2}}$ , so:

$$\sin\left(\frac{\pi}{4}\right) = \sin(10\pi t) \Rightarrow 10\pi t = \frac{\pi}{4}$$

Solving for  $t$ :

$$t = \frac{1}{40} \Rightarrow t = 2.5 \times 10^{-2} \text{ s}$$

---

## Question15

**A full wave rectifier circuit is operating from 50 Hz mains. The fundamental frequency in the ripple output will be**

**AP EAPCET 2024 - 20th May Morning Shift**

**Options:**

A. 50 Hz

B. 70.7 Hz

C. 100 Hz



D. 25 Hz

**Answer: C**

### Solution:

In a full-wave rectifier, both the positive and negative halves of the AC input are used, effectively doubling the frequency of the output ripple compared to the mains frequency. Here's a step-by-step explanation:

The mains frequency is 50 Hz.

The full-wave rectifier inverts the negative half cycle, so the ripple frequency becomes:


$$f_{\text{ripple}} = 2 \times 50 \text{ Hz} = 100 \text{ Hz}.$$

Therefore, the fundamental frequency in the ripple output is 100 Hz, which is Option C.

---

## Question 16

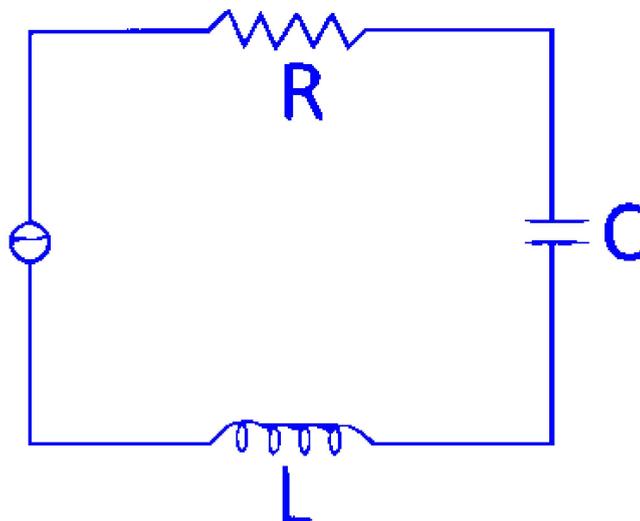**A series  $L - C - R$  circuit is shown in the figure. Where the inductance of 10 H , capacitance  $40\mu\text{ F}$  and resistance  $60\Omega$  are connected to a variable frequency 240 V source. The current at resonating frequency is**



**AP EAPCET 2024 - 19th May Evening Shift**

**Options:**

A. 4 A



B. 2 A

C. 5.4 A

D. 5.8 A

**Answer: A**

### **Solution:**

In the given LCR circuit, the components have the following values:

Inductance,  $L = 10 \text{ H}$

Capacitance,  $C = 40 \mu\text{F} = 4 \times 10^{-5} \text{ F}$

Resistance,  $R = 60 \Omega$

The circuit is connected to a variable frequency source of 240 V.

To find the resonant frequency ( $\omega_r$ ), we use the formula:

$$\omega_r = \frac{1}{\sqrt{LC}}$$

Substituting the given values:

$$\omega_r = \frac{1}{\sqrt{10 \times 4 \times 10^{-5}}} = \frac{1}{2 \times 10^{-2}} = 50 \text{ rad/s}$$

At resonance, the impedance  $Z$  of the circuit is minimized to the resistance  $R$  only. Thus, the current  $I$  at resonant frequency can be calculated by:


$$I = \frac{V}{Z} = \frac{V}{R} = \frac{240}{60} = 4 \text{ A}$$

---


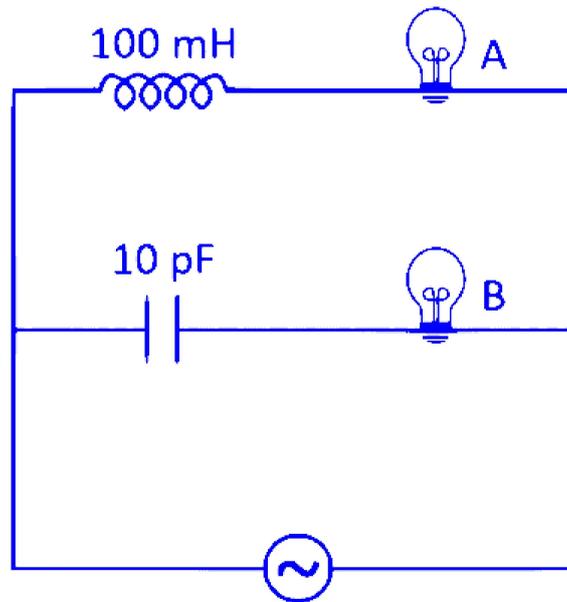
## Question17

In the figure. If  $A$  and  $B$  are identical bulbs, which bulb glows brighter.



AP EAPCET 2024 - 18th May Morning Shift


Options:

- A. A
- B. B
- C. Both with equal brightness
- D. Both do not glow

**Answer: A**

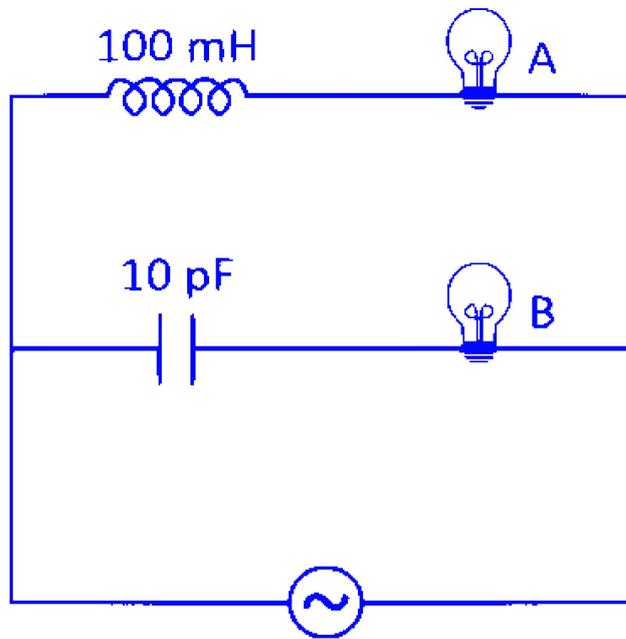**Solution:**

We know that,  $X_C = 1/\omega C$  and  $X_L = \omega L$



According to figure,

$$C = 10\text{pF} = 10 \times 10^{-12} \text{ F}$$

$$L = 100\text{mH} = 0.1\text{H}$$

Here,  $C \ll L$

$$\text{So, } X_C \gg X_L$$

$$\therefore i_A \gg i_B$$

Hence, bulb A will glow brighter.

## Question18

An  $R - L - C$  circuit consists of a  $150\Omega$  resistor,  $20\mu\text{F}$  capacitor and a  $500 \text{ mH}$  inductor connected in series with a  $100 \text{ V AC}$  supply. The angular frequency of the supply voltage is  $400\text{rads}^{-1}$ . The phase angle between current and the applied voltage is

**AP EAPCET 2022 - 5th July Morning Shift**

**Options:**

A.  $\tan^{-1}(0.8)$



B.  $\tan^{-1}(0.25)$

C.  $\tan^{-1}(0.6)$

D.  $\tan^{-1}(0.5)$

**Answer: D**

### Solution:

To determine the phase angle  $\phi$  between the current and the applied voltage in an  $R - L - C$  circuit, we need to use the following relationship:

$$\tan \phi = \frac{X_L - X_C}{R}$$

where:

- $X_L$  is the inductive reactance
- $X_C$  is the capacitive reactance
- $R$  is the resistance

Given:

- Resistance,  $R = 150\Omega$
- Capacitance,  $C = 20\mu\text{F} = 20 \times 10^{-6}\text{F}$
- Inductance,  $L = 500\text{mH} = 500 \times 10^{-3}\text{H}$
- Angular frequency,  $\omega = 400\text{rad s}^{-1}$

The inductive reactance  $X_L$  is calculated as:

$$X_L = \omega L$$

Substituting the values:

$$X_L = 400 \times 500 \times 10^{-3}$$

$$X_L = 200 \Omega$$

The capacitive reactance  $X_C$  is calculated as:

$$X_C = \frac{1}{\omega C}$$

Substituting the values:

$$X_C = \frac{1}{400 \times 20 \times 10^{-6}}$$

$$X_C = 125 \Omega$$

Now, we can find the phase angle using the equation:

$$\tan \phi = \frac{X_L - X_C}{R}$$

Substituting the values:

$$\tan \phi = \frac{200-125}{150}$$

$$\tan \phi = \frac{75}{150}$$

$$\tan \phi = 0.5$$

Therefore, the phase angle  $\phi$  is:

$$\phi = \tan^{-1}(0.5)$$

So, the correct answer is:

Option D  $\tan^{-1}(0.5)$

---

## Question19

**Capacitive reactance of a capacitor in an AC circuit is  $3\text{k}\Omega$ . If this capacitor is connected to a new AC source of double frequency, the capacitive reactance will become.**

### AP EAPCET 2022 - 4th July Evening Shift

**Options:**

A.  $1.5\text{k}\Omega$

B.  $3\text{k}\Omega$

C.  $6\text{k}\Omega$

D.  $5.2\text{k}\Omega$

**Answer: A**

**Solution:**

Given capacitive reactance,

$$X_{C_1} = 3\text{k}\Omega$$

we know that,

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\begin{aligned}\Rightarrow X_C &\propto \frac{1}{f} \Rightarrow \frac{X_{C_2}}{X_{C_1}} = \frac{f_1}{f_2} \\ &= \frac{f_1}{2f_1} = \frac{1}{2} \quad (\because f_2 = 2f_1) \\ \Rightarrow X_{C_2} &= \frac{X_{C_1}}{2} \\ &= \frac{3\text{k}\Omega}{2} = 1.5\text{k}\Omega\end{aligned}$$

---

## Question20

A coil of inductance 0.1 H and resistance  $110\Omega$  is connected to a source of 110 V and 350 Hz . The phase difference between the voltage maximum and the current maximum is

### AP EAPCET 2022 - 4th July Morning Shift

Options:

- A.  $\tan^{-1}(1.5)$
- B.  $\tan^{-1}(0.5)$
- C.  $\tan^{-1}(1.73)$
- D.  $\tan^{-1}(2)$

**Answer: D**

**Solution:**

Given, Inductance,  $L = 0.1$  H

Resistance,  $R = 110\Omega$ ;

Potential difference,  $V = 110$  V

Frequency,  $f = 350$  Hz

Phase difference between maximum voltage and maximum current is given as

$$\begin{aligned}\tan \phi &= \frac{X_L}{R} \\ &= \frac{2\pi fL}{R} = \frac{2 \times \frac{22}{7} \times 350 \times 01}{110} = 2 \\ \Rightarrow \tan \phi &= 2 \\ \Rightarrow \phi &= \tan^{-1}(2)\end{aligned}$$


---

## Question21

A 20 V AC is applied to a circuit consisting of a resistor and a coil with negligible resistance. If the voltage across the resistor is 12 V, the voltage across the coil is

**AP EAPCET 2021 - 20th August Morning Shift**

**Options:**

- A. 16 V
- B. 10 V
- C. 8 V
- D. 6 V

**Answer: A**

**Solution:**

Given,  $V_{\text{rms}} = 20 \text{ V}$

Voltage across resistance = 12 V

Let voltage across inductor be  $V_L$

As we know that,

$$\begin{aligned}V^2 &= V_R^2 + V_L^2 \\ \Rightarrow V_L^2 &= V^2 - V_R^2 = (20)^2 - (12)^2 \\ &= 400 - 144 = 256 \text{ V} \\ V_L &= 16 \text{ V}\end{aligned}$$


---

## Question22

A bulb of resistance  $280\Omega$  is supplied with a 200 V AC supply. What is the peak current?

AP EAPCET 2021 - 19th August Evening Shift

Options:

- A. Nearly 1 A
- B. Nearly 2 A
- C. Nearly 1.4 A
- D. Nearly 2.8 A

**Answer: A**

**Solution:**

Given, resistance of bulb,  $R = 280\Omega$

Supply voltage  $V_{\text{rms}} = 200 \text{ V}$

As,  $V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$  = root mean square speed

$$\Rightarrow V_0 = \sqrt{2}V_{\text{rms}}$$

where,  $V_0$  is peak voltage,

As,  $V = IR$

$$\therefore I_0 = \frac{V_0}{R} = \frac{\sqrt{2} \times 200}{280} = \frac{5\sqrt{2}}{7} = 1.010 \text{ A}$$

Which is nearly 1A.

---

## Question23

A resonant frequency of a current is  $f$ . If the capacitance is made four times the initial value, then the resonant frequency will become



## AP EAPCET 2021 - 19th August Morning Shift

Options:

A.  $\frac{f}{2}$

B.  $2f$

C.  $f$

D.  $\frac{f}{4}$

**Answer: A**

**Solution:**

Given,

Initial resonance frequency,  $f_i = f$

Initial capacitance and inductance be  $C_1 = C$  and  $L_1 = L$

Final capacitance and inductance one  $C_2 = 4C$  and  $L_2 = L$

Let final frequency be  $f'$ .

Since,  $\omega = \frac{1}{\sqrt{LC}} = 2\pi f$

where,  $\omega$  and  $f$  and angular frequency and frequency.

$$\therefore f \propto \frac{1}{\sqrt{LC}} \Rightarrow \frac{f}{f'} = \sqrt{\frac{L'C'}{LC}} = \frac{\sqrt{LAC}}{\sqrt{LC}} = \sqrt{4} = 2$$

$$\therefore f' = \frac{f}{2}$$

---

