

Capacitor

Question1

If a dielectric slab of dielectric constant 3 is introduced between the plates of a capacitor having electric field $15\pi\text{NC}^{-1}$, then the electric displacement is

AP EAPCET 2025 - 26th May Morning Shift

Options:

A.

$$1250 \times 10^{-12}\text{Cm}^{-2}$$

B.

$$250 \times 10^{-12}\text{Cm}^{-2}$$

C.

$$125 \times 10^{-9}\text{Cm}^{-2}$$

D.

$$250 \times 10^{-9}\text{Cm}^{-2}$$

Answer: A

Solution:

Given data

- Dielectric constant $K = 3$
- Electric field $E = 15\pi\text{N/C}$
- We are to find **electric displacement** D .



Step 1. Recall the relation

$$D = \epsilon_0 E + P = \epsilon_0 K E$$

(using $K = \frac{D}{\epsilon_0 E}$).

So,

$$D = \epsilon_0 K E$$

Step 2. Substitute values

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

$$D = (8.854 \times 10^{-12}) \times 3 \times (15\pi)$$

Step 3. Compute

$$D = 8.854 \times 10^{-12} \times 45\pi$$

$$45\pi \approx 141.37$$

$$D = 8.854 \times 10^{-12} \times 141.37$$

$$D \approx 1.252 \times 10^{-9} \text{ C/m}^2$$

Step 4. Express in given unit format

$$1.252 \times 10^{-9} \text{ C/m}^2 = 1250 \times 10^{-12} \text{ C/m}^2$$

✅ Final Answer:

$$D = 1250 \times 10^{-12} \text{ C/m}^2$$

Correct Option: A

Question2

A capacitor of capacitance $2\mu\text{ F}$ is charged with the help of a 60 V battery. After disconnecting the battery, if this capacitor is connected in parallel with another uncharged capacitor of capacitance $1\mu\text{ F}$, then the potential difference across the plates of $2\mu\text{ F}$ capacitor is

AP EAPCET 2025 - 26th May Evening Shift

Options:

A.

30 V

B.

60 V

C.

40 V

D.

20 V

Answer: C

Solution:

Step 1: Find the charge on the first capacitor.

The $2 \mu\text{F}$ capacitor is charged using the 60 V battery, so its charge is:

$$q_1 = C \times V = 2 \times 10^{-6} \times 60 = 120 \times 10^{-6} \text{ C}$$

Step 2: Find the charge on the second capacitor.

The $1 \mu\text{F}$ capacitor is not charged yet, so $q_2 = 0 \text{ C}$

Step 3: Find total charge after connection.

The total charge when we join them is the sum of both charges: $q_{\text{total}} = 120 \times 10^{-6} + 0 = 120 \times 10^{-6} \text{ C}$

Step 4: Find total capacitance when connected in parallel.

When capacitors are connected in parallel, their capacitances add:

$$C_{\text{total}} = 2 \mu\text{F} + 1 \mu\text{F} = 3 \mu\text{F} = 3 \times 10^{-6} \text{ F}$$

Step 5: Find the new (final) voltage across the capacitors.

The new voltage is the total charge divided by the total capacitance: $V_{\text{final}} = \frac{q_{\text{total}}}{C_{\text{total}}} = \frac{120 \times 10^{-6}}{3 \times 10^{-6}} = 40 \text{ V}$

Question3

The energy stored in a capacitor of capacitance $10 \mu\text{F}$ when charged to a potential of 6 kV is



AP EAPCET 2025 - 24th May Morning Shift

Options:

A.

100 J

B.

200 J

C.

180 J

D.

160 J

Answer: C

Solution:

Energy stored in a capacitor is,

$$U = \frac{1}{2}CV^2$$

$$\Rightarrow U = \frac{1}{2} \times 10 \times 10^{-6} \times (6 \times 10^3)^2$$

$$= \frac{1}{2} \times 10 \times 10^{-6} \times 36 \times 10^6$$

$$= 180 \text{ J}$$

Question4

A parallel plate capacitor has plates of area $0.4\pi \text{ m}^2$ and spacing of 0.5 mm . If a slab of thickness 0.5 mm and dielectric constant 4.5 is introduced in between the plates of the capacitor, then the capacitance of the capacitor is

AP EAPCET 2025 - 24th May Morning Shift

Options:

A.

100 nF

B.

60 pF

C.

100 pF

D.

60 nF

Answer: A


Solution:

Here dielectric fills the space between plates completely so,

$$\begin{aligned} C &= \frac{\epsilon_0 K A}{d} \\ &= \frac{8.85 \times 10^{-12} \times 4.5 \times 0.4\pi}{0.5 \times 10^{-3}} \\ &\approx 100\text{nF} \end{aligned}$$

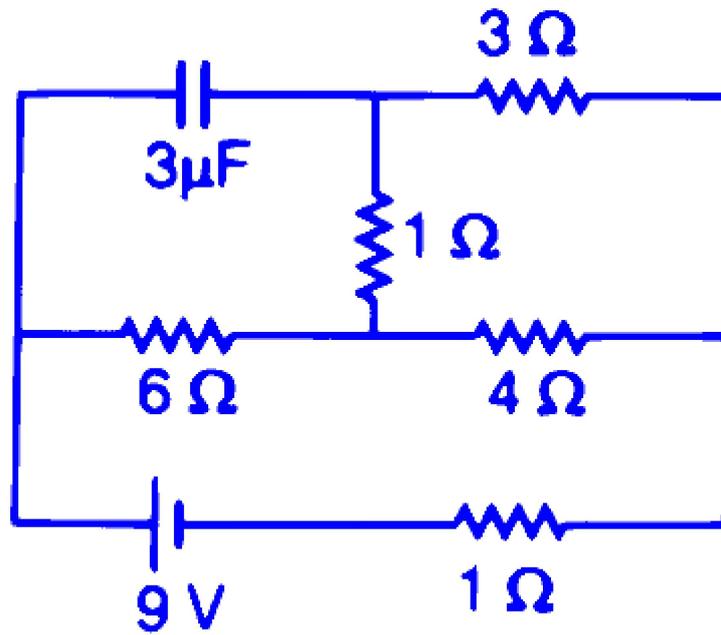Question5

In the given circuit, the potential difference across the plates of the capacitor C in steady state is



AP EAPCET 2025 - 24th May Morning Shift

Options:

A.

6.5 V

B.

6 V

C.

9 V


D.

7.5 V

Answer: A

Solution:

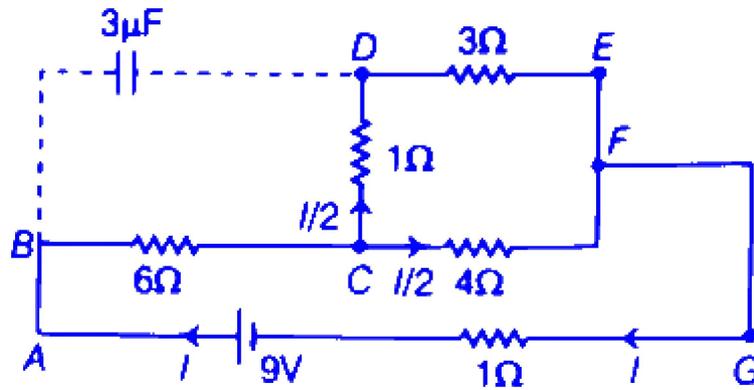In given circuit capacitor does not conduct once it is charged. So in steady state we have following circuit.



⇒ Now, let I = current drawn from cell. Then we have above current distribution.

Using KVL in loop $ABCDEFGA$; we have;

$$-6I - 1 \frac{I}{2} - \frac{3I}{2} - I + 9 = 0$$

$$\Rightarrow 9I = 9 \text{ or } I = 1 \text{ A}$$

Now, potential difference between B and D (using KVL);

$$V_B - 6 \times 1 - 1 \times \frac{1}{2} = V_D$$

$$\Rightarrow V_B - V_D = 6 + \frac{1}{2} = \frac{13}{2} = 6.5 \text{ V.}$$

Question6

One of the two identical capacitors having the same capacitance C , is charged to a potential V_1 and the other is charged to a potential V_2 . If they are connected with their like plates together, then the decrease in the electrostatic potential energy of the combined system is

AP EAPCET 2025 - 23rd May Evening Shift

Options:

A.

$$\frac{C}{4} (V_1^2 - V_2^2)$$

B.

$$\frac{C}{4} (V_1^2 + V_2^2)$$

C.

$$\frac{C}{4}(V_1 - V_2)^2$$

D.

$$\frac{C}{4}(V_1 + V_2)^2$$

Answer: C

Solution:

$$\begin{aligned} U_i &= \frac{1}{2}CV_1^2 + \frac{1}{2}CV_2^2 \\ &= \frac{1}{2}C(V_1^2 + V_2^2) \end{aligned}$$

Common potential,

$$\begin{aligned} V &= \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{CV_1 + CV_2}{C + C} \\ &= \frac{V_1 + V_2}{2} \end{aligned}$$

$$\Rightarrow V = \frac{V_1 + V_2}{2}$$

$$\begin{aligned} \therefore U_f &= \frac{1}{2}C^1V^2 \\ &= \frac{1}{2}(2C)\left(\frac{V_1 + V_2}{2}\right)^2 = C\left(\frac{V_1 + V_2}{2}\right)^2 \end{aligned}$$

$$\begin{aligned} \therefore \Delta U &= U_i - U_f \\ &= \frac{1}{2}C(V_1^2 + V_2^2) - C\left(\frac{V_1 + V_2}{2}\right)^2 \\ &= \frac{C}{2}(V_1^2 + V_2^2) - \frac{C}{4}(V_1^2 + V_2^2 + 2V_1V_2) \\ &= \frac{C}{4}[2V_1^2 + 2V_2^2 - V_1^2 - V_2^2 - 2V_1V_2] \\ &= \frac{C}{4}[V_1^2 + V_2^2 - 2V_1V_2] = \frac{C}{4}(V_1 - V_2)^2 \end{aligned}$$

Question 7

If 27 identical charged conducting spheres each of capacitance $10\mu\text{ F}$ combine to form a big sphere, then the capacitance of the big sphere is

AP EAPCET 2025 - 23rd May Morning Shift

Options:

A.

$$30\mu\text{ F}$$

B.

$$270\mu\text{ F}$$

C.

$$90\mu\text{ F}$$

D.

$$10\mu\text{ F}$$

Answer: A

Solution:

Capacitance of small conducting sphere

$$C = 4\pi\epsilon_0 r = 10\mu\text{ F}$$

$$\text{Since, } 27 \times \frac{4}{3}\pi r^3 = \frac{4}{3}\pi R^3 \Rightarrow R = 3r$$

\therefore Capacitance of big sphere

$$\begin{aligned} C' &= 4\pi\epsilon_0 R = 4\pi\epsilon_0(3r) \\ &= 3(4\pi\epsilon_0 r) = 3 \times 10 = 30\mu\text{ F} \end{aligned}$$

Question8

The capacitance of a spherical capacitor is 100 pF . If the spacing between the two spheres is 1 cm , then the radius of the inner sphere of the capacitor is

AP EAPCET 2025 - 23rd May Morning Shift

Options:

A.

9 cm

B.

10 cm

C.

19 cm

D.

20 cm

Answer: A

Solution:

$$\begin{aligned}b - a &= 1 \text{ cm} = 1 \times 10^{-2} \text{ m}, \\b &= (a + 1 \times 10^{-2}) \text{ m} \\C &= 4\pi\epsilon_0 \left(\frac{ab}{b-a} \right) \\ \Rightarrow 100 \times 10^{-12} &= \frac{1}{9 \times 10^9} \times \frac{a(a + 1 \times 10^{-2})}{1 \times 10^{-2}} \\9 \times 10^{-3} &= a^2 + 10^{-2}a \\ \Rightarrow 0.9 &= 100a^2 + a \\ \Rightarrow 100a^2 + a - 0.9 &= 0 \\ \Rightarrow a &= \frac{-1 \pm \sqrt{1^2 - 4 \times 100(-0.9)}}{2 \times 100} \\ &= -1 \pm \frac{\sqrt{361}}{200} = \frac{-1 \pm 19}{200} \\ &= \frac{-1 + 19}{200} = \frac{18}{200} \text{ m} \\ &= 0.09 \text{ m} = 9 \text{ cm}\end{aligned}$$

Question9

The energy stored in a capacitor is W . To double the charge on the plates of the capacitor, the additional work to be done is

AP EAPCET 2025 - 22nd May Morning Shift

Options:

A.

W

B.

$4W$

C.

$\frac{4}{3}W$

D.

$3W$

Answer: D

Solution:

$$W = \frac{Q^2}{2C}$$

$$W' = \frac{(2Q)^2}{2C} = 4 \left(\frac{Q^2}{2C} \right) = 4W$$

∴ Additional work done,

$$W' - W = 4W - W = 3W$$

Question10

A wire of length 10 m carrying current of 1 A is bent in to a circular loop. If a magnetic field of $2\pi \times 10^{-4}$ T is applied on the loop, then the maximum torque acting on it is

AP EAPCET 2025 - 22nd May Morning Shift

Options:

A.

100×10^{-4} N – m



B.

$$50 \times 10^{-4} \text{ N - m}$$

C.

$$25 \times 10^{-4} \text{ N - m}$$

D.

$$75 \times 10^{-4} \text{ N - M}$$

Answer: B

Solution:

$$\tau_{\max} = MB$$

$$\tau_{\max} = IAB$$

$$\text{Since, } 2\pi r = 10$$

$$\Rightarrow r = \frac{10}{2\pi}$$

\therefore Area of the loop

$$\begin{aligned} A &= \pi r^2 = \pi \left(\frac{10}{2\pi} \right)^2 \\ &= \frac{100}{4\pi} = \frac{25}{\pi} \text{ m}^2 \end{aligned}$$

$$\begin{aligned} \therefore \tau_{\max} &= LAB = 1 \times \frac{25}{\pi} \times 2\pi \times 10^{-4} \\ &= 50 \times 10^{-4} \text{ N - m} \end{aligned}$$

Question11

The radii of the inner and outer spheres of a spherical capacitor are 8 cm and 9 cm respectively. The outer sphere is earthed and the inner sphere is charged. If the space between the concentric spheres is filled with a liquid of dielectric constant 5 , the capacitance of the capacitor is

AP EAPCET 2025 - 21st May Evening Shift

Options:

A.

400 PF

B.

40 PF

C.

$400\mu\text{ F}$

D.

$40\mu\text{ F}$

Answer: A

Solution:

$$\begin{aligned} C &= 4\pi\epsilon_0 k \frac{r_1 r_2}{r_2 - r_1} \\ &= 4\pi (8.85 \times 10^{-12}) \times 5 \times \frac{(0.08)(0.09)}{0.09 - 0.08} \\ &\simeq 400 \times 10^{-12} \text{ F} \\ &\simeq 400\text{pF} \end{aligned}$$

Question12

A capacitor of capacitance $2\mu\text{ F}$ is charged to 50 V and then disconnected from the source. Later the gap between the plates of the capacitor is filled with a dielectric material. If the energy stored in the capacitor is decreased by 25% of its initial value, then the dielectric constant of the dielectric material is

AP EAPCET 2025 - 21st May Morning Shift

Options:

A.

$\frac{2}{3}$

B.

$$\frac{4}{3}$$

C.

$$\frac{3}{4}$$

D.

$$\frac{3}{2}$$

Answer: B

Solution:

Initial stored energy

$$E_i = \frac{1}{2}CV^2$$

Final stored energy,

$$E_f = E_i - 0.25E_i$$

$$E_f = 0.75E_i \quad \dots (i)$$

$$\therefore E_f = \frac{1}{2}C'V'^2$$

$$= \frac{1}{2}(KC) \left(\frac{V}{k}\right)^2$$

$$E_f = \frac{E_i}{K}$$

$$\Rightarrow 0.75E_i = \frac{E_i}{K} \quad [\text{from eq. (i)}]$$

$$\Rightarrow \frac{1}{K} = 0.75$$

$$\Rightarrow K = \frac{1}{0.75} = \frac{4}{3}$$

Question13

The space between the plates of a parallel plate capacitor is halved and a dielectric medium of relative permittivity 10 is introduced between the plates. The ratio of the final and initial capacitances of the capacitor is

AP EAPCET 2024 - 22th May Evening Shift



Options:

- A. 20
- B. 10
- C. 1/10
- D. 1/20

Answer: A

Solution:

The capacitance of a parallel plate capacitor is given by the formula:

$$C = \frac{A\epsilon_0}{d}$$

where:

A is the area of the plates,

ϵ_0 is the permittivity of free space,

d is the distance between the plates.

In this scenario, the distance between the plates is halved, and a dielectric material with a relative permittivity (k) of 10 is introduced. The new capacitance (C') can be calculated as follows:

$$C' = \frac{kA\epsilon_0}{d'} = \frac{10 \cdot A\epsilon_0}{d/2}$$

Simplifying gives:


$$C' = \frac{10 \cdot A\epsilon_0}{d/2} = \frac{20 \cdot A\epsilon_0}{d} = 20C$$

Thus, the ratio of the final capacitance to the initial capacitance is:

$$\frac{C'}{C} = 20$$

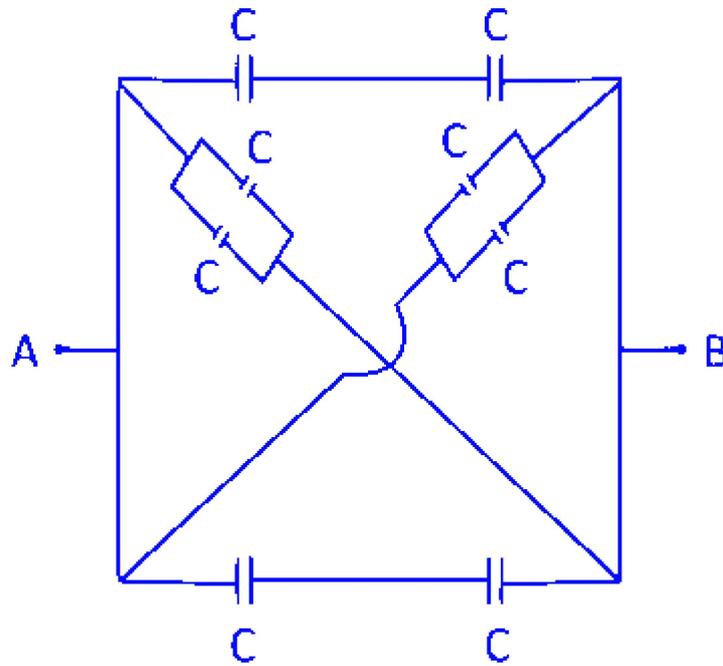Question14

Eight capacitors each of capacity 2μ F are arranged as shown in figure. The effective capacitance between A and B is



AP EAPCET 2024 - 22th May Morning Shift


Options:

- A. $10\mu\text{ F}$
- B. $12\mu\text{ F}$
- C. $16\mu\text{ F}$
- D. $4\mu\text{ F}$


Answer: A

Solution:

Given capacitance, $C = 2\mu\text{ F}$

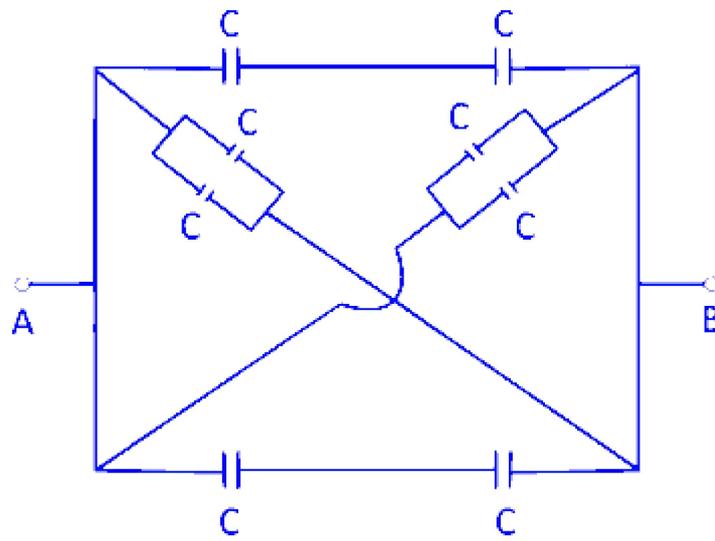

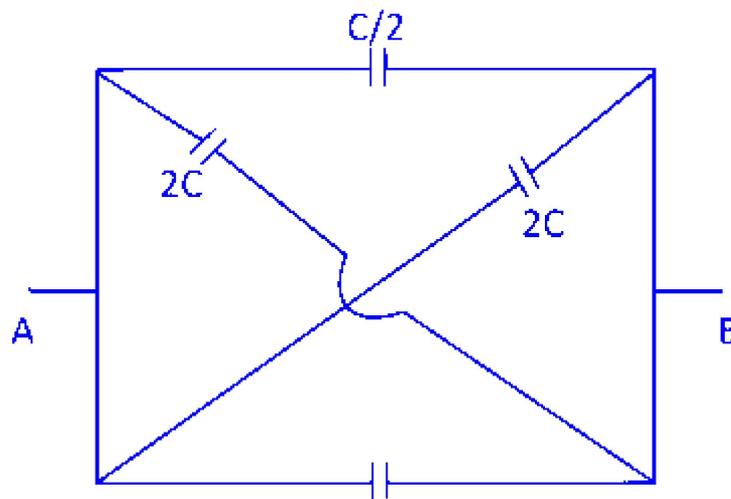Equivalent circuit, Thus, $C_{eq} = \frac{C}{2} + \frac{C}{2} + 2C + 2C$



$$= C + 4C$$

$$C_{eq} = 5C$$

$$\therefore C_{eq} = 5 \times 2 = 10\mu F$$

Question15

When a parallel plate capacitor is charged up to 95 V , its capacitance is C . If a dielectric slab of thickness 2 mm is inserted between plates and distance between the plates is increased by 1.6 mm such that the same potential difference is maintained. The dielectric constant of the material (slab) is

AP EAPCET 2024 - 21th May Evening Shift

Options:


- A. 2.4
- B. 4.5
- C. 5.0
- D. 9.0

Answer: C

Solution:

Let initial thickness = d

Thickness of dielectrics = 2 mm

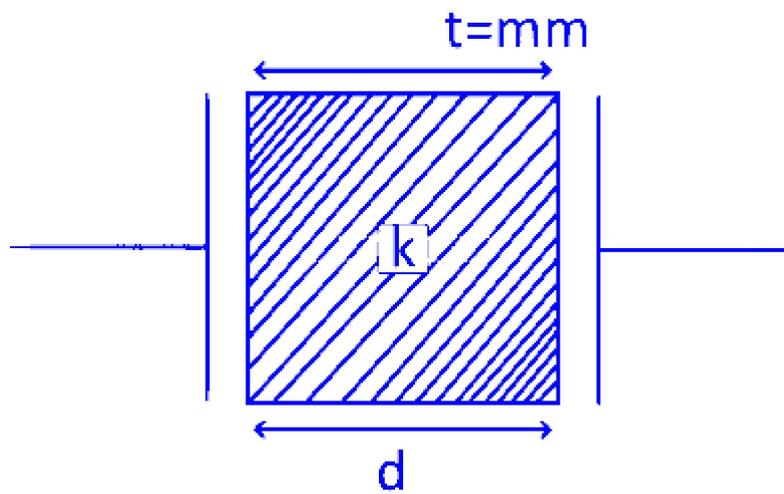

It is given that final potential is same.

Let initial capacitance = C_1

Final capacitance = C_2

$\therefore C_1 = C_2 \dots (i)$

$C_1 = \frac{A\epsilon_0}{d}$ and $C_2 = \frac{A\epsilon_0}{d' - t + \frac{t}{k}}$

where, $d' = d + 1.6$ mm

$$\Rightarrow \frac{A\epsilon_0}{d} = \frac{A\epsilon_0}{(d + 1.6) - t \left(1 - \frac{1}{k}\right)}$$

$$\Rightarrow \frac{1}{d} = \frac{1}{(d + 1.6) - 2 \left(1 - \frac{1}{k}\right)}$$

$$\Rightarrow d + 1.6 - 2 + \frac{2}{k} = d$$

$$\Rightarrow k = 5$$

Question16

The capacitance of an isolated sphere of radius r_1 is increased by 5 times, when it is enclosed by an earthed concentric sphere of radius r_2 . The ratio of their radii is

AP EAPCET 2024 - 21th May Evening Shift

Options:

A. $\frac{4}{5}$

B. $\frac{5}{4}$

C. $\frac{5}{1}$

D. $\frac{3}{5}$

Answer: A

Solution:

Given,

Radius of isolated sphere = r_1

Radius of earthed sphere = r_2

Capacitance of isolated sphere,

$$C_1 = 4\pi\epsilon_0 r_1 \quad \dots (i)$$

Capacitance of isolated sphere enclosed in earthed sphere,

$$C_2 = \frac{4\pi\epsilon_0 r_1 r_2}{r_2 - r_1} \quad \dots (ii)$$

Now, capacitance is 5 times

$$\Rightarrow 5C_1 = C_2$$

$$\Rightarrow 5(4\pi\epsilon_0 r_1) = \frac{4\pi\epsilon_0 r_1 r_2}{r_2 - r_1} \Rightarrow 5 = \frac{r_2}{r_2 - r_1}$$


$$\Rightarrow 5r_2 - 5r_1 = r_2 \Rightarrow -5r_1 = -4r_2$$

$$\Rightarrow \frac{r_1}{r_2} = \frac{4}{5}$$

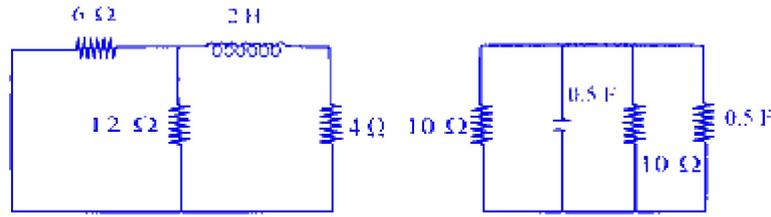Question17



Two figures are shown as Fig. A and Fig. B. The time constant of Fig. A is τ_A and time constant of Fig. B is τ_B . Then



AP EAPCET 2024 - 21th May Morning Shift


Options:

- A. $\tau_A = \frac{1}{4}$ s and $\tau_B = 5$ s
- B. $\tau_A = \frac{1}{2}$ s and $\tau_B = \frac{1}{5}$ s
- C. $\tau_A = 4$ s and $\tau_B = 5$ s
- D. $\tau_A = \frac{1}{3}$ s and $\tau_B = 10$ s

Answer: A

Solution:

For fig (A),

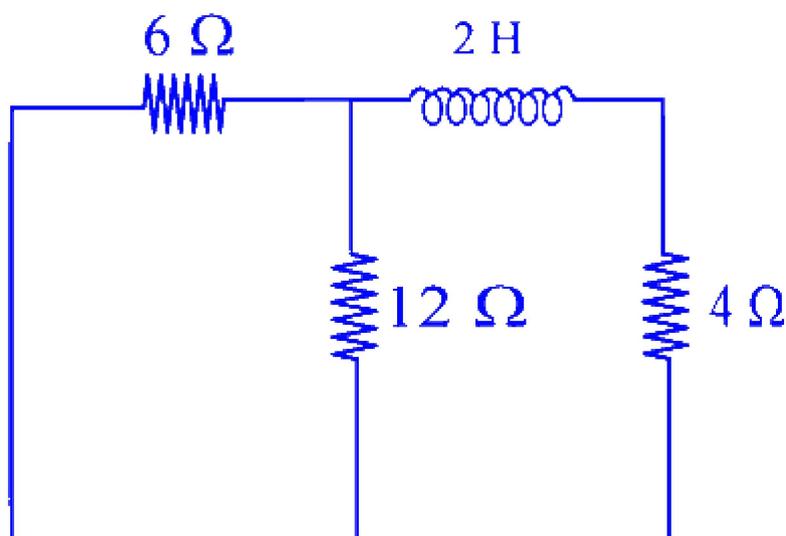


$$R' = \frac{6 \times 12}{6 + 12} + 4 = 4 + 4$$

$$R' = 8$$

∴ Time constant for circuit (A)
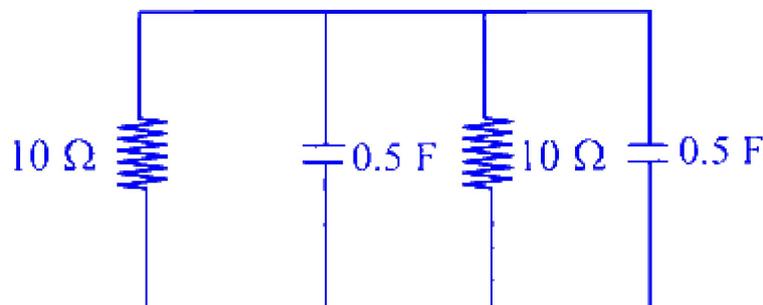
$$\tau_A = \frac{L}{R'} = \frac{2}{8} = \frac{1}{4} \text{ s}$$



Similar for figure (B)

$$R'' = \frac{10 \times 10}{10 + 10} = 5 \Omega$$

and equivalent capacitance,

$$C_{\text{eq}} = 0.5 + 0.5 = 1 \text{ F}$$

∴ Time constant, $\tau_B = RC$

$$= 5 \times 1 = 5 \text{ s}$$

Question18

Three parallel plate capacitors of capacitances $4\mu\text{ F}$, $6\mu\text{ F}$ and $12\mu\text{ F}$ are first connected in series and then in parallel. The ratio of the effective capacitances in the two cases is

AP EAPCET 2024 - 20th May Evening Shift

Options:

A. 1 : 11

B. 5 : 8

C. 3 : 7

D. 4 : 9

Answer: A



Solution:

Given the capacitances:

$$C_1 = 4 \mu\text{F}$$

$$C_2 = 6 \mu\text{F}$$

$$C_3 = 12 \mu\text{F}$$

When connected in series:

To find the equivalent capacitance for capacitors in series, we use the formula:

$$C_{\text{eq}} = \frac{C_1 C_2 C_3}{C_1 C_2 + C_2 C_3 + C_3 C_1}$$

Substituting the given values:

$$C_{\text{eq}} = \frac{4 \times 6 \times 12}{4 \times 6 + 6 \times 12 + 12 \times 4} = \frac{288}{144} = 2 \mu\text{F}$$

When connected in parallel:

For capacitors in parallel, the equivalent capacitance is the sum of the capacitances:

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

Substituting the given values:

$$C_{\text{eq}} = 4 + 6 + 12 = 22 \mu\text{F}$$

Calculating the ratio:


The ratio of the effective capacitances when connected in series to when connected in parallel is:

$$\frac{2}{22} = \frac{1}{11}$$

Thus, the ratio is 1 : 11.

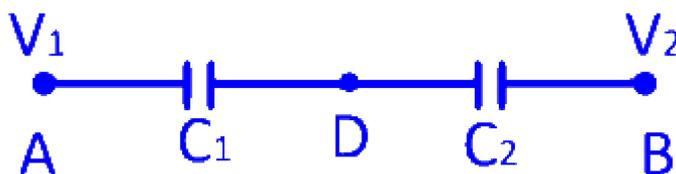Question 19

Two condensers C_1 and C_2 in a circuit are joined as shown in the figure. The potential of point A is V_1 and that of point B is V_2 . The potential at point D will be



AP EAPCET 2024 - 20th May Morning Shift

Options:

A. $\frac{1}{2}(V_1 + V_2)$


B. $\frac{C_2V_2 + C_1V_1}{C_1 + C_2}$

C. $\frac{C_1V_1 + C_2V_2}{C_1 + C_2}$

D. $\frac{C_2V_1 - C_1V_2}{C_1 + C_2}$

Answer: C

Solution:

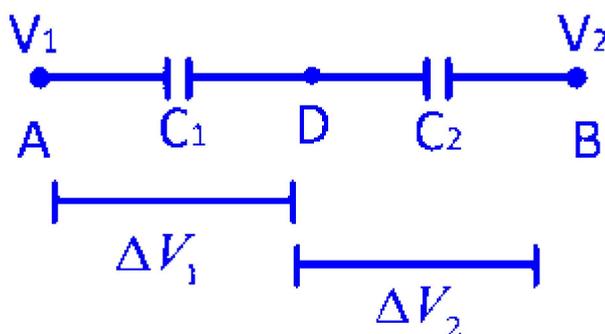

Let the potential of point D be V .

In the above figure, capacitors C_1 and C_2 are in series combination.

Potential difference across both the capacitors are,

$$\Delta V_1 = V_1 - V$$

$$\Delta V_2 = V - V_2$$

We know that in series arrangement, the charge on capacitor will be equal.

$$\Rightarrow Q_1 = Q_2$$

$$C_1(V_1 - V) = C_2(V - V_2)$$

$$\Rightarrow C_1V_1 - C_1V = C_2V - C_2V_2$$


$$\Rightarrow C_1V + C_2V = C_2V_2 + C_1V_1$$

$$\Rightarrow V(C_1 + C_2) = C_1V_1 + C_2V_2$$

$$\Rightarrow V = \frac{C_1V_1 + C_2V_2}{(C_1 + C_2)}$$

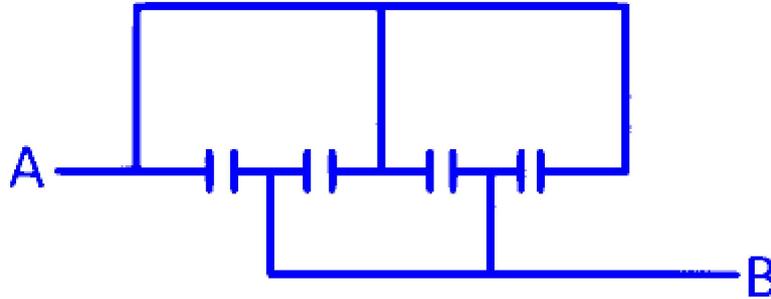Question20

Four condensers each of capacitance $8\mu\text{ F}$ are joined as shown in the figure. The equivalent capacitance between the points A and B will be



AP EAPCET 2024 - 19th May Evening Shift

Options:

A. $32\mu\text{ F}$

B. $2\mu\text{ F}$


C. $8\mu\text{ F}$

D. $16\mu\text{ F}$

Answer: A

Solution:

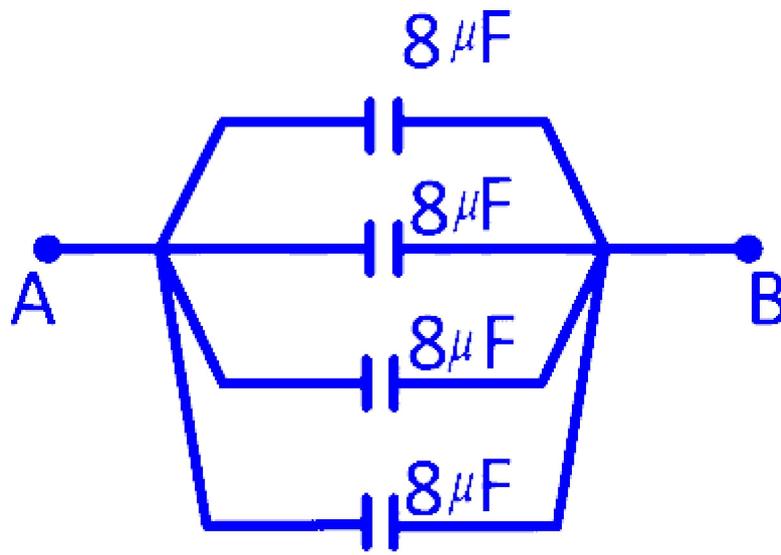
The given arrangement of capacitor are represented as



$$\therefore C_{AB} = 8 + 8 + 8 + 8 = 32 \mu\text{F}$$

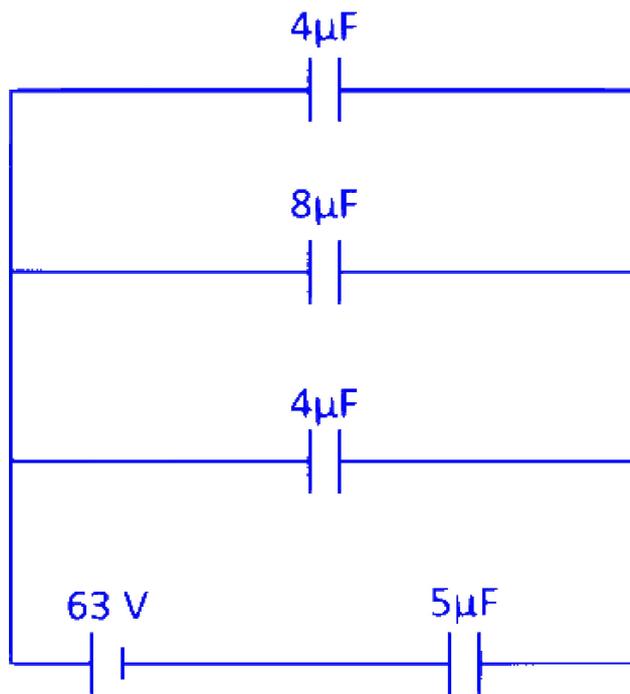Question21

In the given circuit, the potential difference across $5 \mu\text{F}$ capacitor is



AP EAPCET 2024 - 18th May Morning Shift

Options:

A. 48 V


B. 24 V

C. 63 V

D. 21 V

Answer: A

Solution:

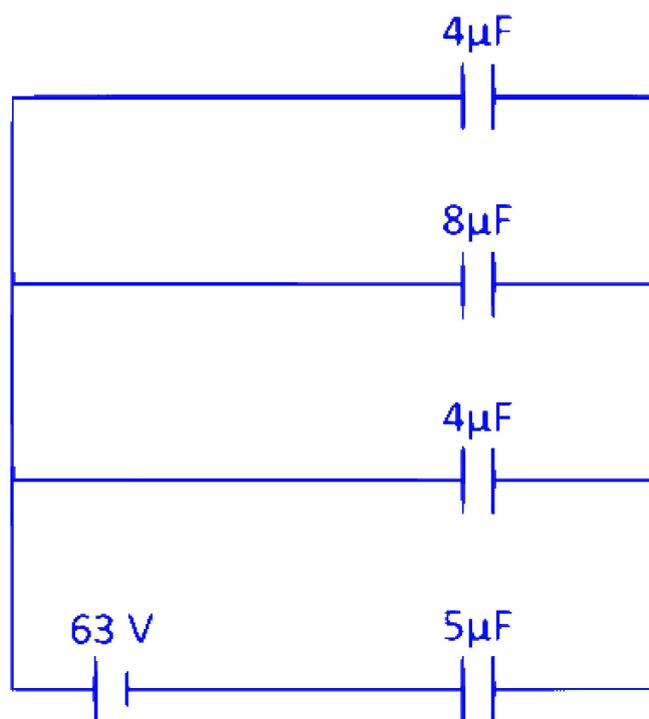

According to figure,

4 μ F, 8 μ F, 4 μ F are in parallel combination. So,

$$C' = 4 + 8 + 4 = 16 \mu F \quad \dots (i)$$

Now, C' and $5 \mu F$ are in series combination. So, total capacitance in the circuit is,

$$\frac{1}{C_{\text{total}}} = \frac{1}{5} + \frac{1}{C'}$$

$$\text{From Eq. (i), } C_{\text{total}} = \frac{16 \times 5}{16 + 5} = \frac{80}{21} \mu F$$

Total charge in the given circuit,

$$q_{\text{total}} = C_{\text{total}} \cdot V$$

$$= \frac{80}{21} \times 63 = 240\mu\text{C}$$

Charge remains same in series combination. So, $5\mu\text{F}$ also have $240\mu\text{C}$ charge.


The potential difference across $5\mu\text{F}$ capacitor is,

$$V' = \frac{Q}{C} = \frac{240}{5}$$

$$V' = 48\text{ V}$$

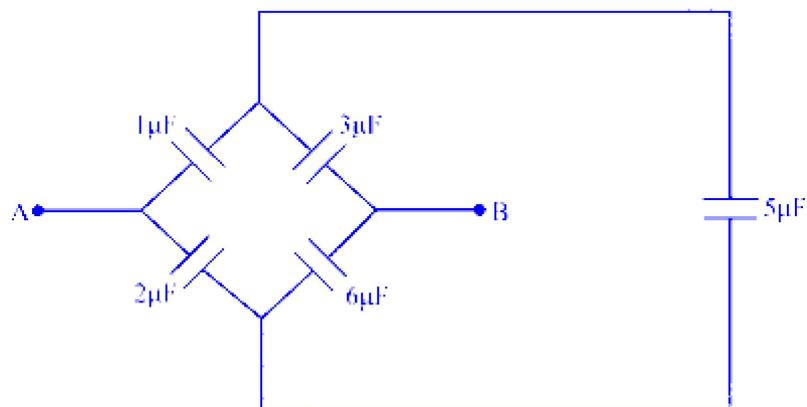Question22

The capacitance between the points A and B in the following figure.



AP EAPCET 2022 - 5th July Morning Shift

Options:

A. $\frac{3}{8}\mu\text{F}$

B. $\frac{9}{4}\mu\text{F}$


C. $\frac{4}{5}\mu\text{F}$

D. $2\mu\text{F}$

Answer: B

Solution:

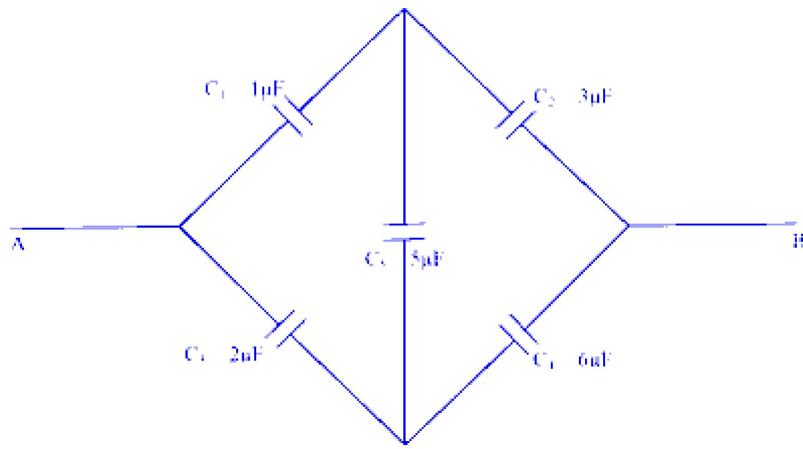The given circuit diagram can be represented as




Since, $\frac{C_1}{C_2} = \frac{C_3}{C_4} = \frac{1}{3}$

Hence, given circuit follows the condition of balance wheatstone bridge.

Hence, capacitor C_5 is ineffective.

Now, the circuit diagram is redrawn as

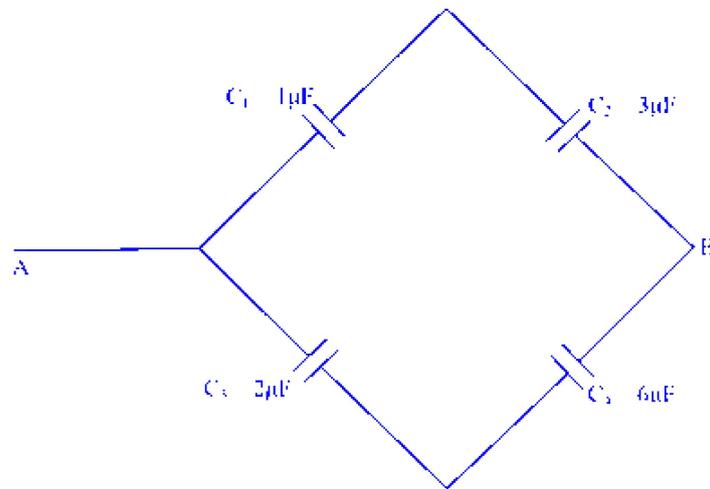


$$C_{AB} = \frac{C_1 C_2}{C_1 + C_2} + \frac{C_3 C_4}{C_3 + C_4} = \frac{1 \times 3}{1 + 3} + \frac{2 \times 6}{2 + 6}$$

$$= \frac{3}{4} + \frac{12}{8} = \frac{9}{4} \mu\text{F}$$

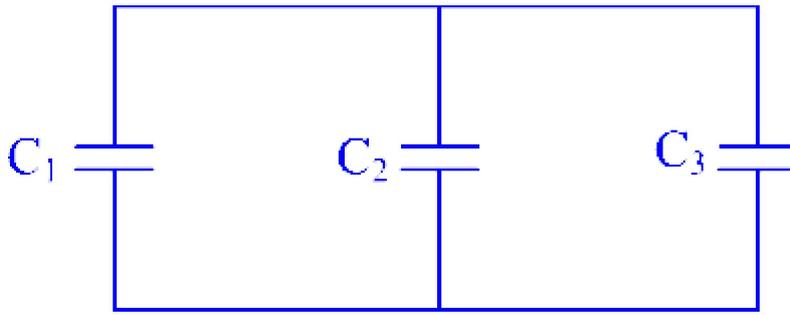Question23

A capacitor of capacitance $C_1 = 1\mu\text{F}$ is charged using a 9 V battery. C_1 is, then removed from the battery and connected to capacitors C_2 and C_3 of $2\mu\text{F}$ and $3\mu\text{F}$, respectively as shown in the figure. Find the charge on C_3 after equilibrium has reached is



AP EAPCET 2022 - 4th July Morning Shift

Options:

- A. $4.5 \times 10^{-6} \text{C}$
- B. $3.5 \times 10^{-6} \text{C}$
- C. $2.5 \times 10^{-6} \text{C}$
- D. $1.5 \times 10^{-5} \text{C}$

Answer: A

Solution:

Given, $C_1 = 1 \mu\text{F}$, $V = 9 \text{ V}$,

$C_2 = 2 \mu\text{F}$, $C_3 = 3 \mu\text{F}$

Equivalent capacitance of C_2 and C_3

$$C' = C_2 + C_3 = 2 + 3 = 5 \mu\text{F}$$

Common potential difference when C_1 and C' are combined, is given as

$$V' = \frac{\text{total charge } (Q)}{\text{total capacitance } (C_1 + C')}$$

$$V' = \frac{Q}{C_1 + C'}$$

But $Q = C_1 V$

$$\therefore V' = \frac{C_1 V}{C_1 + C'} = \frac{1 \times 9}{1 + 5} = \frac{9}{6} = 1.5 \text{ V}$$

Charge on capacitor C_3 is given as

$$\begin{aligned} Q_3 &= C_3 V' \\ &= 3 \times 10^{-6} \times 1.5 = 4.5 \times 10^{-6} \text{C} \end{aligned}$$



Question24

A $60 \mu\text{F}$ parallel plate capacitor whose plates are separated by 6 mm is charged to 250 V, and then the charging source is removed. When a slab of dielectric constant 5 and thickness 3 mm is placed between the plates, find the change in the potential difference across the capacitor.

AP EAPCET 2021 - 20th August Morning Shift

Options:

- A. 250 V
- B. 100 V
- C. 150 V
- D. 75 V

Answer: B

Solution:

Given,

Capacitance of parallel plate capacitor, $C_0 = 60 \mu\text{F}$

$$= 60 \times 10^{-6} \text{ F}$$

Separation between plates, $d = 6 \text{ mm}$

$$= 6 \times 10^{-3} \text{ m}$$

Electric potential, $V_0 = 250 \text{ V}$

Dielectric constant of slab, $K = 5$

and thickness of slab, $t = 3 \text{ mm}$

$$= 3 \times 10^{-3} \text{ m}$$

$$\text{Since, } C = \frac{q}{V} = \frac{\epsilon_0 A}{d} = \frac{\epsilon_0 A}{d - t(1 - \frac{1}{K})}$$



where, q is charge stored, V is potential, ϵ_0 is free space permittivity = $8.854 \times 10^{-12} \text{Nm}^2\text{C}^{-2}$ and A is plate area

$$\begin{aligned} \therefore q_0 &= C_0 V_0 \\ &= 60 \times 10^{-6} \times 250 = 15 \times 10^{-3} \text{C} \end{aligned}$$

$$\text{and new capacitance, } C' = \frac{\epsilon_0 A}{[6-3(1-\frac{1}{5})] \times 10^{-3}} \dots (i)$$

$$\text{and } \epsilon_0 A = C_0 d$$

$$\begin{aligned} \Rightarrow \epsilon_0 A &= 60 \times 10^{-6} \times 6 \times 10^{-3} \\ &= 360 \times 10^{-9} \end{aligned}$$

Put this value in Eq. (i), we get

$$C' = \frac{360 \times 10^{-9}}{3.6 \times 10^{-3}} = 10^{-4} \text{ F}$$


$$\text{Final potential stored in capacitor} = \frac{q_0}{C'} = \frac{15 \times 10^{-3}}{10^{-4}} = 150 \text{ V}$$

$$\text{Hence, voltage difference} = 250 - 150 = 100 \text{ V}$$

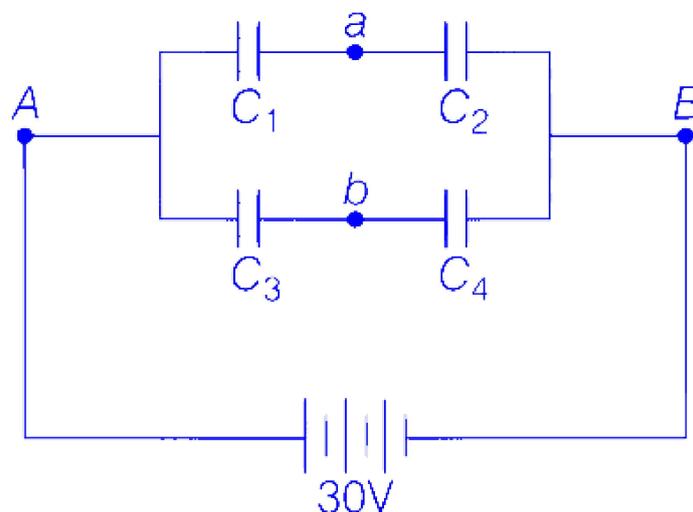Question 25

Four capacitors with capacitances

$C_1 = 1 \text{ } \mu\text{F}$, $C_2 = 1.5 \text{ } \mu\text{F}$, $C_3 = 2.5 \text{ } \mu\text{F}$ and $C_4 = 0.5 \text{ } \mu\text{F}$ are connected as shown and are connected to a 30 V source. The potential difference between points a and b is



AP EAPCET 2021 - 19th August Evening Shift

Options:


- A. 5 V
- B. 9 V
- C. 10 V
- D. 13 V

Answer: D

Solution:

Given, C_1, C_2, C_3 and C_4 are $1 \mu\text{F}, 1.5 \mu\text{F}, 2.5 \mu\text{F}$ and $0.5 \mu\text{F}$.

Supply voltage = 30 V

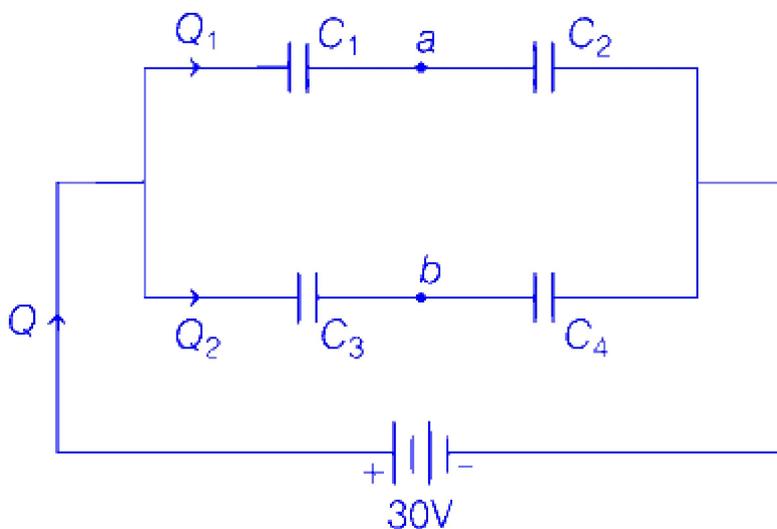

Let V_{ab} is potential across a and b ,

Q is charge in circuit and Q_1, Q_2 are branch charges.

Since, series equivalent capacitance $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$

$$\Rightarrow C_s = \frac{C_1 C_2}{C_1 + C_2}$$

and in parallel connection voltages remain same

$$\therefore Q_1 = \frac{C_1 C_2}{C_1 + C_2} V \Rightarrow Q_1 = \frac{1 \times 1.5}{1 + 1.5} \times 30$$

$$= \frac{1.5}{2.5} \times 30 = 18 \mu\text{C}$$

$$\text{Similarly, } Q_2 = \frac{2.5 \times 0.5}{2.5 + 0.5} \times 30 = 12.5 \mu\text{C}$$




$$\begin{aligned} \therefore V_{ab} &= V_a - V_b = (V - V_b) - (V - V_a) \\ &= \frac{Q_2}{C_3} - \frac{Q_1}{C_1} = \frac{12.5}{2.5} - \frac{18}{1} = -13 \text{ V} \end{aligned}$$

$$\therefore V_{ba} = 13 \text{ V}$$

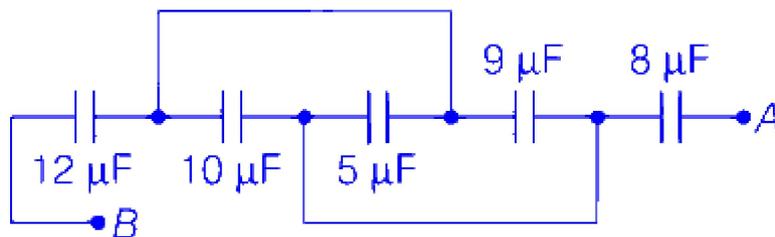Question 26

In the given circuit, if the potential difference between A and B is 80 V, then the equivalent capacitance between A and B and the charge on $10 \mu\text{F}$ capacitor respectively, are



AP EAPCET 2021 - 19th August Morning Shift


Options:

- A. $4 \mu\text{F}$ and $133 \mu\text{C}$
- B. $164 \mu\text{F}$ and $150 \mu\text{C}$
- C. $15 \mu\text{F}$ and $50 \mu\text{C}$
- D. $4 \mu\text{F}$ and $50 \mu\text{C}$

Answer: A

Solution:

According to given circuit diagram,

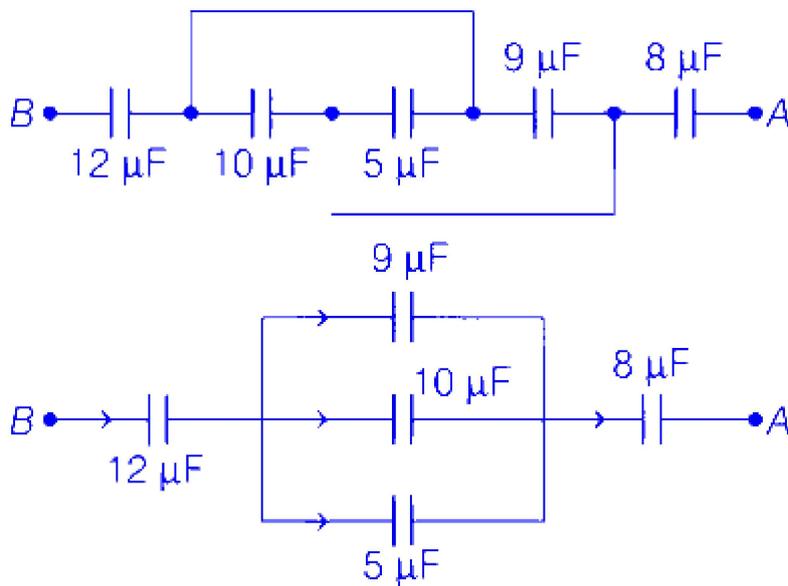

Voltage across A and B , $V_{AB} = 80 \text{ V}$

Let charge in $9 \text{ } \mu\text{F}$, $10 \text{ } \mu\text{F}$ and $5 \text{ } \mu\text{F}$ be Q_1 , Q_2 and Q_3 .

Net charge, $Q = Q_{9\mu\text{F}} + Q_{10\mu\text{F}} + Q_{5\mu\text{F}}$

As we know that,

Parallel equivalent capacitance,

$$C'_{\text{eq}} = C_1 + C_2 + C_3$$

$$\therefore C'_{\text{eq}} = 9 + 10 + 5 = 24 \text{ } \mu\text{F}$$

and series equivalent capacitance,

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}$$

$$\Rightarrow \frac{1}{C_{\text{eq}}} = \frac{1}{12} + \frac{1}{24} + \frac{1}{8} \Rightarrow \frac{1}{C_{\text{eq}}} = \frac{2+1+3}{24}$$

$$\Rightarrow C_{\text{eq}} = \frac{24}{6} \text{ } \mu\text{F} = 4 \text{ } \mu\text{F}$$

Since, $C = \frac{Q}{V}$

$$\therefore Q = CV$$

$$= 4 \times 10^{-6} \times 80 = 320 \text{ } \mu\text{C}$$

Since, in series connection,

$$V = V_{12\mu\text{F}} + V_{10\mu\text{F}} + V_{8\mu\text{F}}$$

$$\Rightarrow 80 = \frac{320}{12} + V_{10\mu\text{F}} + \frac{320}{8}$$

$$\Rightarrow V_{10\mu\text{F}} = 13.33 \text{ V}$$

$$\therefore Q_{10\mu\text{F}} = V_{10\mu\text{F}} \times 10$$

$$\simeq 133 \text{ } \mu\text{C}$$