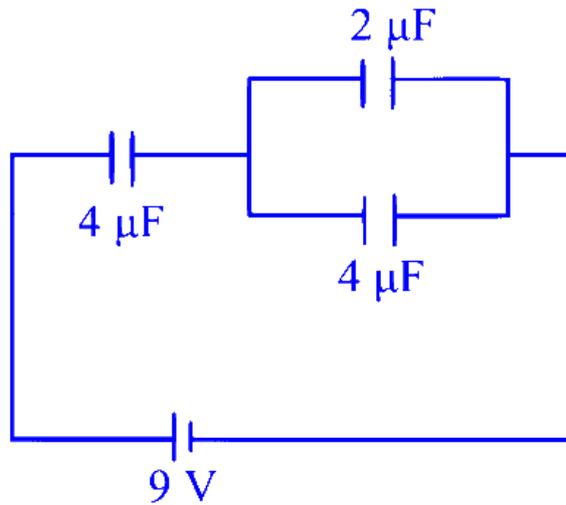


Capacitor

Question1

The potential difference across the 4 capacitor in the following circuit is



MHT CET 2025 5th May Evening Shift

Options:

A.

3.4 V

B.

4.6 V

C.

5.4 V


D.

6.2 V

Answer: C



Solution:

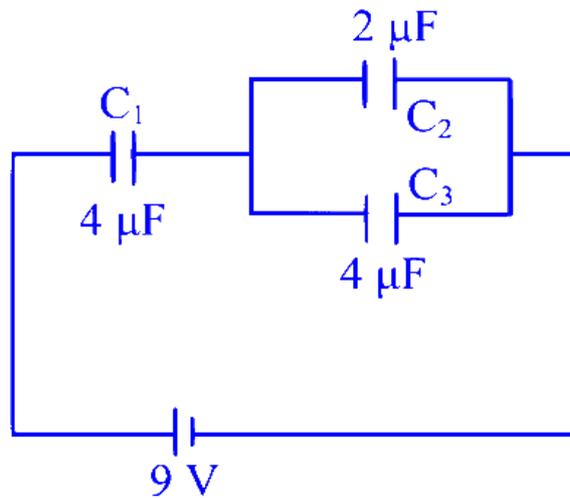

C_2 and C_3 capacitors are in parallel. Their equivalent capacitance is given by

$$C_p = C_2 + C_3 = 2 + 4 = 6\mu F$$

C_p is in series with C_1

$$V = \frac{q}{C}$$

As for series combination, the charge on the capacitors is same, therefore, potential across them is inversely proportional to their capacitances.

$$V_1 : V_p = C_p : C_1$$

$$\therefore V_1 = \frac{C_p}{C_p + C_1} V = \frac{6}{10} \times 9 = 5.4V$$

Similarly, voltage across C_2 and C_3 will be

$$\therefore V_p = 9 - 5.4 V = 3.6 V$$

The question asks for the voltage across a $4\mu F$ capacitor. However, the circuit contains two $4\mu F$ capacitors. Among the given options, 5.4 V is listed, but 3.6 V is not. Therefore, it is presumed that the voltage across the first $4\mu F$ capacitor (C_1) is intended.

Question2

A capacitor of unknown capacity is connected across a battery of V volt. The charge stored in it is Q coulomb. When potential across the capacitor is reduced by V_1 volt, the charge stored in it becomes Q_1 coulomb. The potential V is

MHT CET 2025 26th April Evening Shift

Options:

A.

$$\frac{QV_1}{Q-Q_1}$$

B.

$$\frac{Q_1V_1}{Q+Q_1}$$

C.

$$\frac{Q_1}{Q}$$

D.

$$\frac{Q}{Q_1}$$

Answer: A

Solution:

Step 1: Formula for charge stored

The charge stored in a capacitor is given by the formula: $Q = CV$ where Q is the charge, C is the capacitance, and V is the voltage.

Step 2: Charge after voltage decreases

When the voltage is reduced by V_1 , the new voltage becomes $V - V_1$. The new charge stored is:
 $Q_1 = C(V - V_1)$

Step 3: Isolate C (capacitance) from the second equation

We can find C from the second equation: $C = \frac{Q_1}{V - V_1}$



Step 4: Substitute C back into the first equation

Now, substitute C into the first equation: $Q = \left(\frac{Q_1}{V-V_1}\right)V$

Step 5: Rearranging to solve for V

Multiply both sides by $(V - V_1)$: $Q(V - V_1) = Q_1V$

Expand and bring terms involving V to one side: $QV - QV_1 = Q_1V$


Now, get all V terms together: $QV - Q_1V = QV_1$

Factor V on the left: $V(Q - Q_1) = QV_1$

Now, solve for V : $V = \frac{QV_1}{Q-Q_1}$

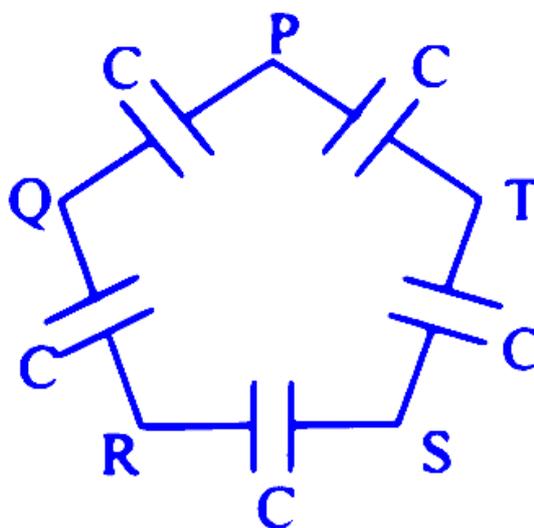Question3

Five capacitors, each of capacitance ' C ' are connected as shown in the figure. The ratio of equivalent capacitance between P and R and the equivalent capacitance between P and Q is



MHT CET 2025 26th April Evening Shift

Options:

A.

1 : 4

B.

2 : 3

C.

3 : 1


D.

5 : 2

Answer: B

Solution:

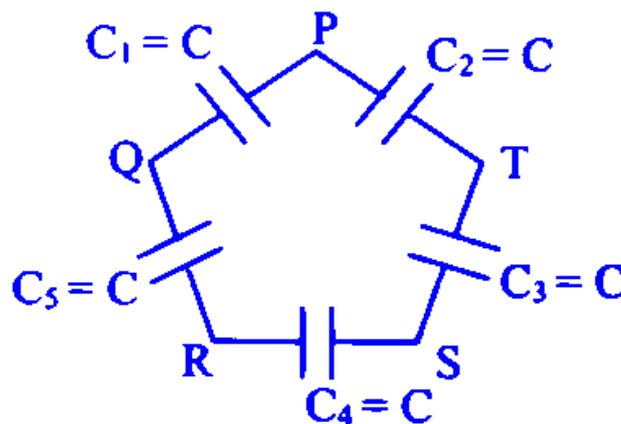Let the capacitors be C_1, C_2, C_3, C_4 and C_5



Between P and Q- C_2, C_3, C_4 and C_5 are connected in series and C_1 is connected in parallel with them.

For the series combination

$$\frac{1}{C_{\text{series}}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{4}{C}$$

Equivalent capacitance,

$$C_{PQ} = C_{\text{series}} + C = \frac{C}{4} + C = \frac{5C}{4} \quad \dots (i)$$

Between points P and R - C_2, C_3 and C_4 are connected in series and C_1 and C_5 connected in series are connected in parallel with them

Between points P and R, capacitors $C_2, C_3,$ and C_4 are connected in series, and this series combination is in parallel with another series combination of capacitors C_1 and C_5

$$\frac{1}{C_{\text{series } 1}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{3}{C} \Rightarrow C_{\text{series } 1} = \frac{C}{3}$$

$$\frac{1}{C_{\text{series } 2}} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C} \Rightarrow C_{\text{series } 2} = \frac{C}{2}$$

$$C_{PR} = C_{\text{series } 1} + C_{\text{series } 2} = \frac{C}{3} + \frac{C}{2} = \frac{5C}{6} \quad \dots (ii)$$

From (i) and (ii),

$$\frac{C_{PR}}{C_{PQ}} = \frac{5C/6}{5C/4} = \frac{2}{3}$$

Question4

The function of a dielectric in a capacitor is

MHT CET 2025 26th April Evening Shift

Options:

A.

to reduce the effective potential on plates,

B.

to increase the effective potential on plates.

C.

to decrease the capacity of capacitance.

D.

to reduce the plate area of the capacitor.

Answer: A

Solution:

The correct answer is:

Option A: to reduce the effective potential on plates.

Explanation:

- A dielectric is an insulating material placed between the plates of a capacitor.
- When a dielectric is inserted, the electric field inside the capacitor decreases because the dielectric becomes polarized.
- For the same charge stored on the plates, a lower effective potential difference exists across them.

- This leads to **increased capacitance** according to


$$C = \kappa \cdot C_0$$

where κ is the dielectric constant, C_0 is the capacitance without the dielectric.

Hence, the dielectric's role is essentially to **reduce the effective potential** on the plates, thereby increasing capacitance. ✓

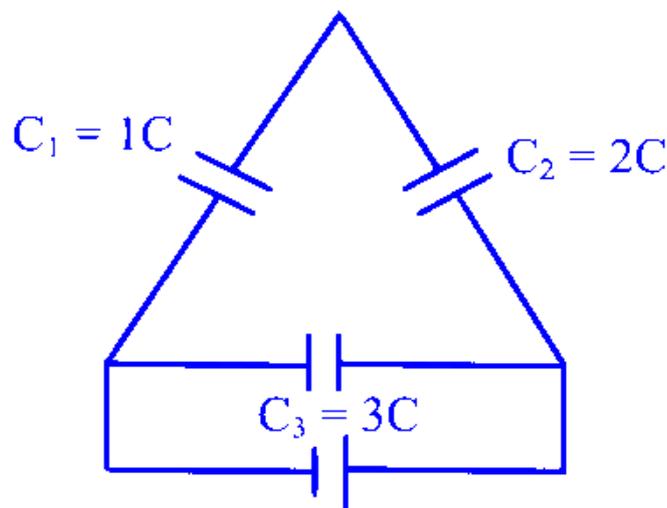Question5

Three capacitors are connected to a battery as shown in figure. The ratio of charge on capacitors C_3 and C_1 is



MHT CET 2025 26th April Morning Shift

Options:

- A. 1.5
- B. 2.5
- C. 3.5
- D. 4.5

Answer: D

Solution:

Here, C_1 and C_2 are in series

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} = \frac{2C^2}{3C} = \frac{2}{3}C$$

Also, C_3 is parallel to C_1 and C_2

$$\therefore C_{eq} = C_{12} + C_3 = \frac{2}{3}C + 3C = \frac{11}{3}C$$

Charge on capacitor C_3

$$Q_3 = C_3 \cdot V = 3CV$$

Charge on capacitor C_1


In series, charge on $C_1 = Q_1 = Q_{12}$

$$Q_{12} = C_{12} V = \frac{2}{3}CV$$

$$\therefore \frac{\text{Charge on } C_3}{\text{Charge on } C_1} = \frac{3CV}{\frac{2}{3}CV} = \frac{9}{2} = 4.5$$

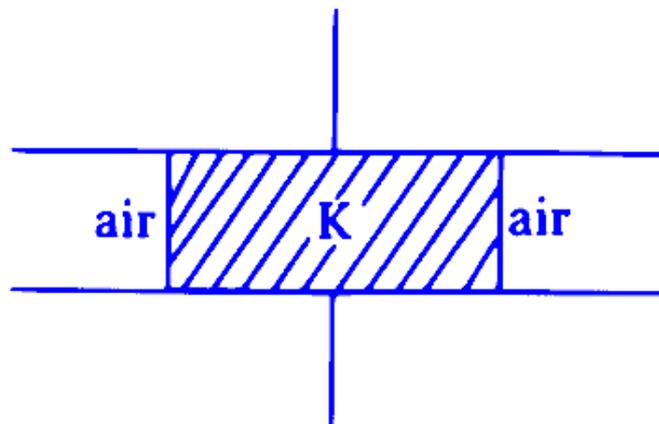Question6

The capacity of air filled parallel plate capacitor is C_0 . One-half of the space between the plates is filled with a dielectric constant 'K' as shown in figure. The new capacity becomes C_n . The ratio C_n to C_0 is



MHT CET 2025 26th April Morning Shift

Options:

A. $\left(\frac{K+1}{2}\right)$

B. $\left(\frac{K+1}{3}\right)$

C. $\left(\frac{K+1}{4}\right)$

D. $4(K + 1)$

Answer: A

Solution:

Original capacitor (air-filled): C_0

After adding dielectric (K) to half the plate area new capacitance = C

$$C_0 = \frac{\epsilon_0 A}{d}$$

The plate is split in to two halves in parallel:

One half with air: $A/2$, dielectric constant = 1

One half with dielectric K : $A/2$, dielectric constant = K

$$\therefore C_{\text{air}} = \frac{\epsilon_0(A/2)}{d} = \frac{1}{2} \cdot \frac{\epsilon_0 A}{d} = \frac{C_0}{2}$$

$$\therefore C_{\text{dielectric}} = \frac{K\epsilon_0(A/2)}{d} = \frac{K}{2} \cdot \frac{\epsilon_0 A}{d} = \frac{KC_0}{2}$$

Total Capacitance (Parallel Combination)

$$C = C_{\text{air}} + C_{\text{dielectric}} = \frac{C_0}{2} + \frac{KC_0}{2} = \frac{C_0(1 + K)}{2}$$

$$\therefore \frac{C}{C_0} = \left(\frac{K + 1}{2}\right)$$


Question7

Seven capacitors each of capacitance $2\mu\text{ F}$ are to be connected in a configuration to obtain an effective capacitance $\left(\frac{10}{11}\right)\mu\text{F}$. The combination is


MHT CET 2025 25th April Evening Shift

Options:


A.

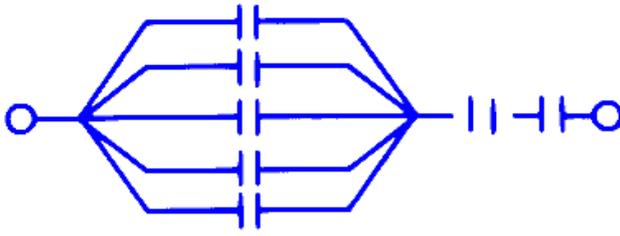


B.

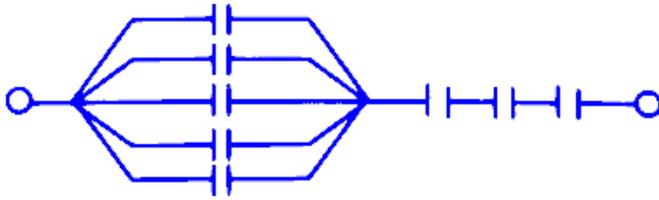

C.

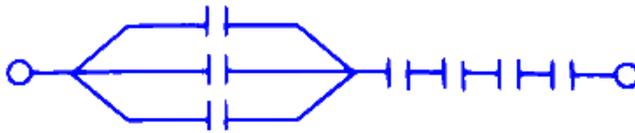

D.

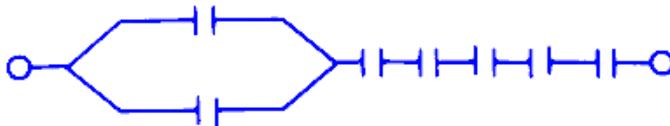

Answer: A

Solution:

As required, equivalent capacitance should be,

$$C_{eq} = \frac{10}{11} \mu F$$

For combination of the five capacitors in parallel and two in series,

$$\therefore \frac{1}{C_{eq}} = \frac{1}{5C} + \left[\frac{1}{C} + \frac{1}{C} \right] = \frac{C + 10C}{5C^2}$$

$$\therefore C_{eq} = \frac{5C}{11}$$

$$= \frac{5 \times 2}{11}$$

$$= \frac{10}{11} \mu F$$

∴ The required combination is 5 capacitors in parallel and 2 in series

Question8

Two identical metal plates are given charges q_1 and q_2 ($q_2 < q_1$) respectively. If they are now brought close together to form a parallel plate capacitor with capacitance ' C ', the potential difference ' V ' between the plates is

MHT CET 2025 25th April Evening Shift

Options:

A. $\frac{q_1 - q_2}{c}$

B. $\frac{q_1 + q_2}{C}$

C. $\frac{q_1 - q_2}{2C}$

D. $\frac{q_1 + q_2}{2C}$

Answer: C

Solution:

The effective charge on the capacitor is:

$$Q = \frac{q_1 - q_2}{2}$$

From formula for capacitance,


$$V = \frac{q}{C} = \frac{q_1 - q_2}{2C}$$

$$\therefore V = \frac{q_1 - q_2}{2C}$$

Question9

Five capacitors, each of capacity ' C ' are connected as shown in the figure. The resultant capacity between A and B is 14μ F. The

capacity of each capacitor is

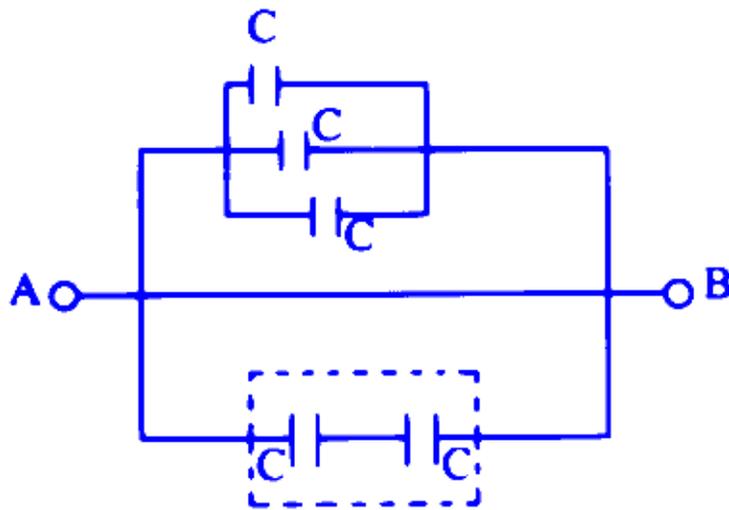


MHT CET 2025 25th April Morning Shift

Options:

- A. $2\mu\text{ F}$
- B. $3.5\mu\text{ F}$
- C. $4\mu\text{ F}$
- D. $2.8\mu\text{ F}$

Answer: C


Solution:

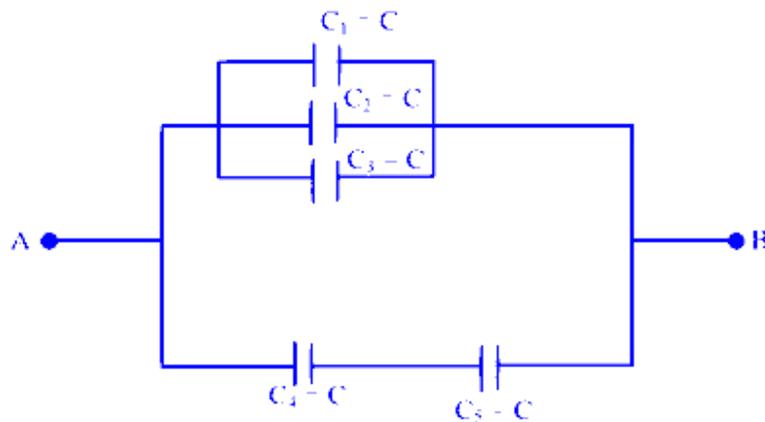

$C_1, C_2 \& C_3$ are in parallel, whereas C_4 and C_5 are in series.

$$\therefore C_{eq1} = C_1 + C_2 + C_3 = 3C$$
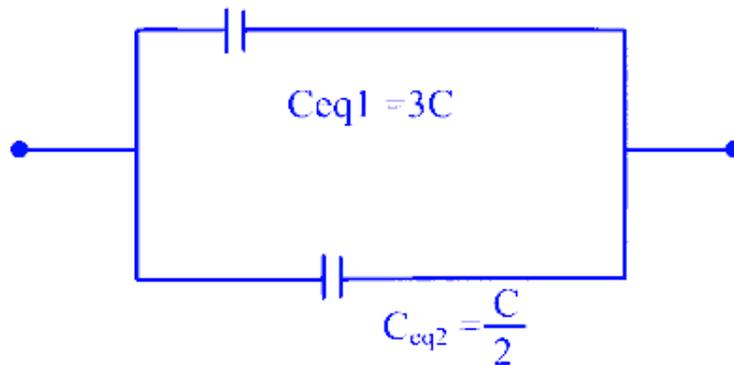
$$\therefore C_{eq2} = \frac{1}{C_4} + \frac{1}{C_5} = \frac{C}{2}$$



C_{eq1} is in parallel with C_{eq2}

$$\therefore C_{eq} = C_{eq1} + C_{eq2}$$

$$C_{eq} = \frac{7}{2}C$$

Now we know,

$$C_{eq} = 14\mu F$$

$$\therefore \frac{7}{2}C = 14\mu F$$

$$\therefore C = 4\mu F$$

Question10

Two capacitors of $100\mu F$ and $50\mu F$ are connected in parallel. If the potential difference across $100\mu F$ is $20 V$ and across $50\mu F$ is $40 V$, then the common potential of the parallel combination will be (same polarities of the capacitor connected together)

MHT CET 2025 23rd April Evening Shift

Options:

A. $20 V$

B. $60 V$

C. $\frac{3}{80}$

D. $\frac{80}{3}$ V

Answer: D

Solution:

Step 1: Find the total charge before connecting.

Total charge before connecting = charge on C_1 + charge on C_2 : $Q_{\text{total}} = C_1V_1 + C_2V_2$

Step 2: After connecting, both capacitors reach a common voltage V .

Total charge = $(C_1 + C_2)V$

Step 3: Set the total charges equal (since charge is conserved):

$$(C_1 + C_2)V = C_1V_1 + C_2V_2 \text{ So, } V = \frac{C_1V_1 + C_2V_2}{C_1 + C_2}$$

Step 4: Plug in the values.

$$C_1 = 100 \times 10^{-6} \text{ F, } V_1 = 20 \text{ V } C_2 = 50 \times 10^{-6} \text{ F, } V_2 = 40 \text{ V}$$

$$V = \frac{100 \times 10^{-6} \times 20 + 50 \times 10^{-6} \times 40}{100 \times 10^{-6} + 50 \times 10^{-6}}$$

Step 5: Calculate:

$$100 \times 10^{-6} \times 20 = 2 \times 10^{-3} \quad 50 \times 10^{-6} \times 40 = 2 \times 10^{-3} \quad \text{Total numerator} = 4 \times 10^{-3}$$

$$100 \times 10^{-6} + 50 \times 10^{-6} = 150 \times 10^{-6} = 1.5 \times 10^{-4}$$

$$V = \frac{4 \times 10^{-3}}{1.5 \times 10^{-4}} = \frac{400}{15} = \frac{80}{3}$$

Question11

A 4μ F capacitor is charged to 10 V . The battery is then disconnected and a pure 10 mH coil is connected across the capacitor so that LC oscillations are set up. The maximum current in the coil is

MHT CET 2025 23rd April Evening Shift

Options:

A. 0.2 A



B. 0.1 A

C. 0.4 A

D. 0.25 A

Answer: A

Solution:

We have an LC oscillation setup:

- Capacitance $C = 4\mu F = 4 \times 10^{-6} F$
- Initial capacitor voltage $V = 10 V$
- Inductance $L = 10 \text{ mH} = 10 \times 10^{-3} H = 0.01 H$

Step 1: Initial energy stored in the capacitor

$$E_C = \frac{1}{2} CV^2$$

$$E_C = \frac{1}{2} \cdot 4 \times 10^{-6} \cdot (10^2)$$

$$E_C = 2 \times 10^{-6} \cdot 100 = 2 \times 10^{-4} \text{ J}$$

Step 2: Maximum energy in the inductor

At peak current, **all energy resides in the inductor:**

$$E_L = \frac{1}{2} LI_{\max}^2$$

Equating:

$$\frac{1}{2} LI_{\max}^2 = E_C$$

$$\frac{1}{2} \cdot 0.01 \cdot I_{\max}^2 = 2 \times 10^{-4}$$

$$0.005 I_{\max}^2 = 2 \times 10^{-4}$$

$$I_{\max}^2 = \frac{2 \times 10^{-4}}{0.005} = \frac{2 \times 10^{-4}}{5 \times 10^{-3}} = 0.04$$

$$I_{\max} = 0.2 \text{ A}$$

 **Final Answer:**

$$I_{\max} = 0.2 \text{ A}$$

Correct Option: A (0.2 A)



Question12

A parallel plate air capacitor has capacity ' C ' and distance of separation between plates is ' d '. If a conducting sheet of thickness $\frac{2d}{3}$ is inserted in between the plates, the capacitance becomes C_1 . The ratio of $\frac{C_1}{C}$ is

MHT CET 2025 23rd April Morning Shift

Options:

- A. 2 : 1
- B. 4 : 1
- C. 3 : 1
- D. 5 : 1

Answer: C

Solution:

Before inserting conductor,

$$C = \frac{\epsilon_0 A}{d}$$

After inserting conductor of thickness $\frac{2d}{3}$,

$$d' = d - \frac{2d}{3} = \frac{d}{3}$$

$$C_1 = \frac{\epsilon_0 A}{d'} = \frac{3\epsilon_0 A}{d}$$

The required ratio,

$$\therefore \frac{C_1}{C} = \frac{\frac{3\epsilon_0 A}{d}}{\frac{\epsilon_0 A}{d}} = \frac{3}{1}$$

Question13

Initially n identical capacitors are joined in parallel and are charged to potential V . Now they are separated and joined in series. Then

MHT CET 2025 22nd April Evening Shift

Options:

- A. potential difference and total energy of the combination remain the same.
- B. potential difference remains the same and energy increases n times.
- C. potential difference becomes nV and energy remains the same.
- D. potential difference is nV and energy increases n times.

Answer: C

Solution:

Energy will remain the same due to conservation of energy

In case 1, each capacitor is charged to p.d. V . So, when they are connected in series, the p.d. will be nV

Question14

A series combination of 10 capacitors, each of value ' C_1 ' is charged by a source of potential difference ' $4V$ '. When another parallel combination of 8 capacitors, each of value ' C_2 ' is charged by a source of potential difference ' V ', it has the same total energy stored in it as in the first combination. The value of ' C_2 ' is

MHT CET 2025 22nd April Morning Shift

Options:

- A. $\frac{C_1}{5}$
- B. $\frac{8}{5}C_1$



C. $\frac{64}{5}C_1$

D. $\frac{C_1}{40}$

Answer: A

Solution:

Case 1: Series combination of 10 capacitors, each C_1 .

- Equivalent capacitance of capacitors in **series**:

$$\frac{1}{C_{eq1}} = \frac{1}{C_1} + \frac{1}{C_1} + \dots \text{ (10 terms) } = \frac{10}{C_1}$$

$$C_{eq1} = \frac{C_1}{10}.$$

- Energy stored when connected across 4 V:

$$U_1 = \frac{1}{2}C_{eq1} V^2 = \frac{1}{2} \cdot \frac{C_1}{10} \cdot (4)^2 = \frac{1}{2} \cdot \frac{C_1}{10} \cdot 16 = \frac{8}{10}C_1 = 0.8 C_1.$$

Case 2: Parallel combination of 8 capacitors, each of capacitance C_2 .

- Equivalent capacitance of capacitors in **parallel**:

$$C_{eq2} = 8C_2.$$

- Energy stored when connected across V :

$$U_2 = \frac{1}{2} C_{eq2} V^2 = \frac{1}{2} (8C_2) V^2 = 4C_2 V^2.$$

Condition: Energy equal

$$U_1 = U_2$$

$$0.8C_1 = 4C_2 V^2$$

$$C_2 = \frac{0.8}{4V^2} C_1 = \frac{0.2}{V^2} C_1 = \frac{C_1}{5V^2}.$$

Check the problem statement

The second system ("parallel combination... charged by a source of potential difference V ") uses the **same total energy** as the first.

So the relation indeed gives:

$$C_2 = \frac{C_1}{5V^2}.$$

Now, **look at the given options**:

- A. $\frac{C_1}{5}$
- B. $\frac{8}{5}C_1$



- C. $\frac{64}{5}C_1$
- D. $\frac{C_1}{40}$

This suggests in the problem, V may actually equal 1 V (i.e., the wording "charged by source potential difference 'V'" intends $V = 1\text{ volt}$).

If $V = 1$:

$$C_2 = \frac{C_1}{5}.$$


Final Answer:

$$\frac{C_1}{5}$$

So the correct option is A.

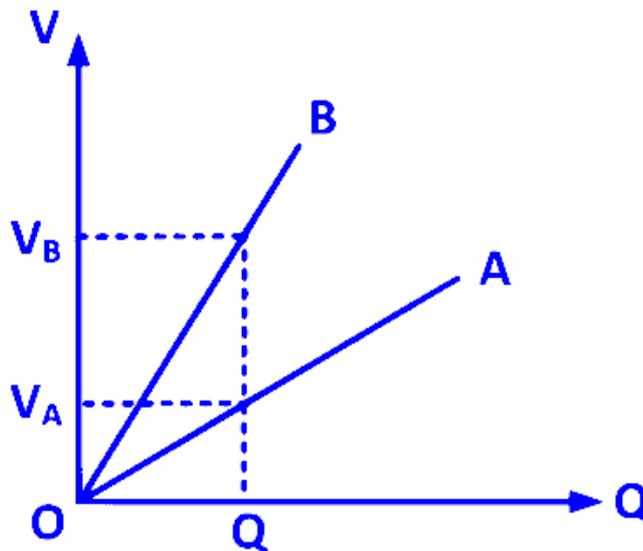Question15

The graph shows the variation of voltage (v) across the plates of two parallel plate capacitors A and B versus increase of charge Q stored in them. Then



MHT CET 2025 22nd April Morning Shift

Options:

- A. capacity of both capacitors is same.
- B. capacity of A is higher than B .
- C. capacity of B is higher than A .
- D. capacity of both is zero.

Answer: B

Solution:

In the graph, V_A and V_B are the voltages across parallel plate capacitors A and B corresponding to charge Q on each of the capacitors.

$$V_A = Q/C_A \text{ and } V_B = Q/C_B$$

$$\text{or } \frac{V_B}{V_A} = \frac{\frac{Q}{C_B}}{\frac{Q}{C_A}} = \frac{C_A}{C_B}$$

$$\text{Since, } V_B > V_A, \frac{V_B}{V_A} = \frac{C_A}{C_B} > 1$$

$\therefore C_A > C_B$, i.e. capacitor A has the higher capacitance.

Question16

Three capacitors each of capacitance ' C ' and breakdown voltage ' V ' are connected in series. The capacitance and breakdown voltage of the series combination will be respectively

MHT CET 2025 22nd April Morning Shift

Options:

A. $3C, 3V$

B. $\frac{C}{3}, \frac{V}{3}$

C. $3C, \frac{V}{3}$

D. $\frac{C}{3}, 3V$

Answer: D

Solution:

Step 1: Equivalent capacitance (for series)

For capacitors in series:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{3}{C}$$

So,

$$C_{\text{eq}} = \frac{C}{3}.$$

Step 2: Breakdown voltage

Each capacitor can withstand a maximum voltage of V before breakdown.

When three are in **series**, the total applied voltage is divided (equally, since they have the same capacitance). Thus, each capacitor gets $\frac{V_{\text{total}}}{3}$.

For safe operation, none should exceed V .

So the maximum total breakdown voltage is:

$$V_{\text{eq}} = 3V$$

Final Answer:

$$C_{\text{eq}} = \frac{C}{3}, \quad V_{\text{eq}} = 3V$$

Correct option: **D**

Question17

If the charge on the capacitor is increased by $3C$, the energy stored in it increases by 21%. The original charge on the capacitor is

MHT CET 2025 21st April Evening Shift

Options:

A. $6C$

B. $3C$

C. $30C$

D. 90 C

Answer: C

Solution:

Step 1. Recall capacitor energy formula

The energy in a capacitor in terms of charge Q and capacitance C is:

$$U = \frac{Q^2}{2C}.$$

Step 2. Let original charge = Q

Original energy:

$$U = \frac{Q^2}{2C}.$$

New charge = $Q + 3$.

New energy:

$$U' = \frac{(Q+3)^2}{2C}.$$

Step 3. Relating energies

We are told:

$$U' = U(1 + 0.21) = 1.21U.$$

So:

$$\frac{(Q+3)^2}{2C} = 1.21 \cdot \frac{Q^2}{2C}.$$

Cancel $\frac{1}{2C}$:

$$(Q + 3)^2 = 1.21Q^2.$$

Step 4. Expand

$$Q^2 + 6Q + 9 = 1.21Q^2.$$

$$6Q + 9 = 1.21Q^2 - Q^2 = 0.21Q^2.$$

$$0.21Q^2 - 6Q - 9 = 0.$$

Step 5. Solve quadratic

Multiply through by 100 to eliminate decimals:

$$21Q^2 - 600Q - 900 = 0.$$

Divide by 3:

$$7Q^2 - 200Q - 300 = 0.$$

Quadratic:

$$Q = \frac{200 \pm \sqrt{200^2 + 4 \cdot 7 \cdot 300}}{14}$$
$$= \frac{200 \pm \sqrt{40000 + 8400}}{14} = \frac{200 \pm \sqrt{48400}}{14}$$

$$\sqrt{48400} = 220.$$

So:

$$Q = \frac{200 \pm 220}{14}$$

$$\text{Case 1: } Q = \frac{200 + 220}{14} = \frac{420}{14} = 30.$$

$$\text{Case 2: } Q = \frac{200 - 220}{14} = \frac{-20}{14} = -\frac{10}{7} \text{ (not possible).}$$

Final Answer:

30 C

So the correct option is **C (30 C)**.

Question 18

A parallel plate capacitor having plate area 'A' and separation 'd' is charged to a potential difference 'V'. The charging battery is disconnected and the plates are pulled apart to four times the initial separation. The work required to increase the distance between the plates is ($\epsilon_0 =$ permittivity of free space)

MHT CET 2025 21st April Evening Shift

Options:

A. $\frac{\epsilon_0 AV^2}{3d}$

B. $\frac{\epsilon_0 AV^2}{4d}$

C. $\frac{2\epsilon_0 AV^2}{d}$

D. $\frac{3\epsilon_0 AV^2}{2d}$

Answer: D

Solution:

Step 1: Work Done Formula

The work done to separate the plates is the change in energy of the capacitor:

$$W = U_{\text{final}} - U_{\text{initial}}$$

Step 2: Initial Energy

When the plates are at the original distance, the energy stored is:

$$U_{\text{initial}} = \frac{1}{2}CV_0^2 \text{ Here, } C \text{ is the initial capacitance, and } V_0 \text{ is the voltage across the plates.}$$

Step 3: What Happens When the Plates Are Separated

After disconnecting the battery, the charge Q on the plates stays the same, but the distance is increased to $4d$.

$$\text{The new capacitance is: } C' = \frac{\epsilon_0 A}{4d} = \frac{C}{4}$$

$$\text{The voltage changes because } Q \text{ is the same: } V' = \frac{Q}{C'} = \frac{Q}{C/4} = 4V_0$$

Step 4: Final Energy

$$\text{The new stored energy is: } U_{\text{final}} = \frac{1}{2}C'V'^2 = \frac{1}{2}\left(\frac{C}{4}\right)(4V_0)^2 = \frac{1}{2} \times \frac{C}{4} \times 16V_0^2 = 2CV_0^2$$

Step 5: Calculate the Work Done

$$\text{Plugging values into the work formula: } W = U_{\text{final}} - U_{\text{initial}} = 2CV_0^2 - \frac{1}{2}CV_0^2 = \frac{3}{2}CV_0^2$$

Step 6: Substitute Capacitance

$$\text{The capacitance formula is } C = \frac{\epsilon_0 A}{d}. \text{ So, } W = \frac{3}{2} \cdot \frac{\epsilon_0 A}{d} V_0^2 = \frac{3\epsilon_0 A V_0^2}{2d}$$

Question 19

A parallel plate capacitor has plate area 50 cm^2 and plate separation 3 mm . The space between the plates is filled with a dielectric medium of thickness 1 mm and dielectric constant 4 . The capacitance becomes ($\epsilon_0 =$ permittivity of free space)

MHT CET 2025 21st April Evening Shift

Options:

A. $\frac{18\epsilon_0}{7}$

B. $\frac{20\epsilon_0}{9}$

C. $\frac{16\epsilon_0}{7}$

D. $\frac{14\epsilon_0}{5}$

Answer: B**Solution:****Step 1: Recall concept**

If a parallel-plate capacitor has partial dielectric filling in the direction of separation (i.e. layered dielectrics along thickness), then it is equivalent to capacitors **in series**.

- Plate area: $A = 50 \text{ cm}^2 = 50 \times 10^{-4} \text{ m}^2 = 5 \times 10^{-3} \text{ m}^2$.
- Separation: $d = 3 \text{ mm} = 3 \times 10^{-3} \text{ m}$.
- Thickness of dielectric: $t_d = 1 \times 10^{-3} \text{ m}$. Relative permittivity: $\epsilon_r = 4$.
- Remaining thickness (air): $t_a = d - t_d = (3 - 1) \text{ mm} = 2 \times 10^{-3} \text{ m}$.

So effectively we have:

1. A capacitor with dielectric slab: $t_d = 1 \times 10^{-3} \text{ m}$, $\epsilon = \epsilon_0 \cdot 4$.
2. Another capacitor with air gap: $t_a = 2 \times 10^{-3} \text{ m}$, $\epsilon = \epsilon_0$.

Both share same area A and are in series.

Step 2: Capacitance of each section

- Dielectric part:

$$C_1 = \frac{\epsilon_0 \epsilon_r A}{t_d} = \frac{4\epsilon_0 \cdot 5 \times 10^{-3}}{1 \times 10^{-3}} = \frac{20\epsilon_0}{1}.$$

So, $C_1 = 20\epsilon_0$.

- Air part:

$$C_2 = \frac{\epsilon_0 A}{t_a} = \frac{\epsilon_0 \cdot 5 \times 10^{-3}}{2 \times 10^{-3}} = \frac{5}{2} \epsilon_0 = 2.5\epsilon_0.$$

Step 3: Equivalent capacitance (series combination)

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}.$$

Substitute numbers:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{20\epsilon_0} + \frac{1}{2.5\epsilon_0}.$$

$$= \frac{1}{20\epsilon_0} + \frac{1}{(5/2)\epsilon_0} = \frac{1}{20\epsilon_0} + \frac{2}{5\epsilon_0}.$$

$$= \frac{1}{20\epsilon_0} + \frac{8}{20\epsilon_0} = \frac{9}{20\epsilon_0}.$$



Hence,

$$C_{\text{eq}} = \frac{20}{9} \cdot \epsilon_0 \cdot$$


Final Answer:

$$\boxed{\frac{20\epsilon_0}{9}}$$

That corresponds to **Option B**.

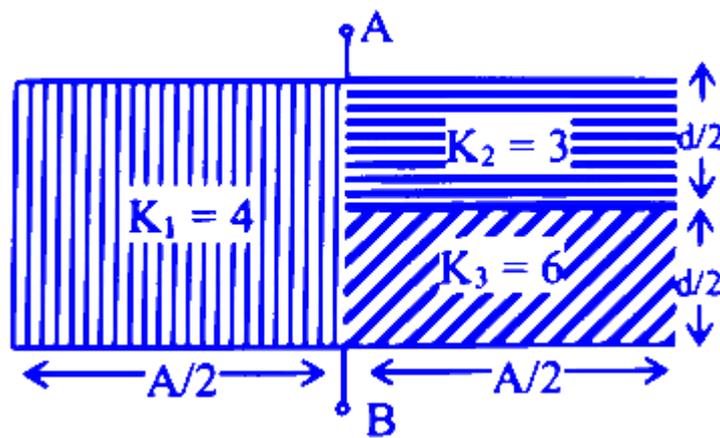Question20

The equivalent capacitance between plates 'A' and 'B' (A -area of each plate, d-separation between plates) (ϵ_0 - permittivity of free space) is



MHT CET 2025 21st April Morning Shift


Options:

- A. $\frac{A\epsilon_0}{d}$
- B. $\frac{2 A\epsilon_0}{d}$
- C. $\frac{4 A\epsilon_0}{d}$
- D. $\frac{8 A\epsilon_0}{d}$

Answer: C

Solution:

The equivalent circuit is given below

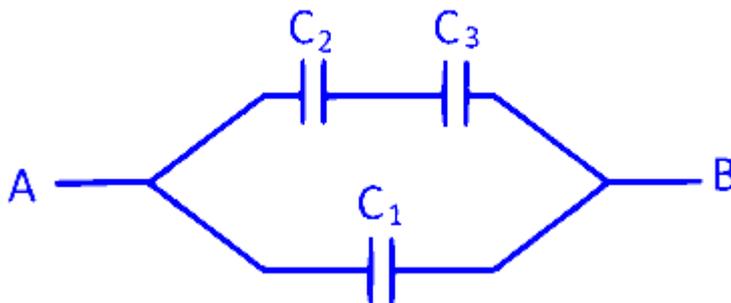

C_2 and C_3 are connected in series, and this combination is then connected in parallel with C_1 .

$$C_1 = \frac{K_1 \left(\frac{A}{2}\right) \epsilon_0}{d} = \frac{2A\epsilon_0}{d} = 2C$$

$$C_2 = \frac{K_2 \left(\frac{A}{2}\right) \epsilon_0}{\left(\frac{d}{2}\right)} = \frac{3A\epsilon_0}{d} = 3C$$

$$C_3 = \frac{K_3 \left(\frac{A}{2}\right) \epsilon_0}{\left(\frac{d}{2}\right)} = \frac{6A\epsilon_0}{d} = 6C$$

$$C_s = \frac{C_2 C_3}{C_2 + C_3} = \frac{3C \times 6C}{3C + 6C} = 2C$$

$$C_{eq} = C_1 + C_s = 2C + 2C = 4C = \frac{4A\epsilon_0}{d}$$

Question21

The voltage between the plates of a parallel plate capacitor of capacity $1\mu\text{ F}$ is changing at the rate of 4 V/s . the displacement current in the capacitor is

MHT CET 2025 21st April Morning Shift

Options:

A. $4\mu\text{ A}$

B. $3\mu\text{ A}$

C. $1\mu\text{ A}$

D. $6\mu\text{ A}$

Answer: A

Solution:

Given:

- Capacitance, $C = 1\ \mu\text{F} = 1 \times 10^{-6}\ \text{F}$
- Rate of change of voltage, $\frac{dV}{dt} = 4\ \text{V/s}$

Displacement current (I_d) in a capacitor is given by:

$$I_d = C \frac{dV}{dt}$$

Substitute the given values:

$$I_d = 1 \times 10^{-6}\ \text{F} \times 4\ \text{V/s}$$

$$I_d = 4 \times 10^{-6}\ \text{A}$$

$$I_d = 4\ \mu\text{A}$$

Answer:

Option A: $4\ \mu\text{A}$

Question22

A parallel plate air capacitor has capacitance C_P . It is equally filled with parallel layers of materials of dielectric constants K_1 and K_2 . Now its capacity becomes C_K . The ratio C_P to C_K is

MHT CET 2025 20th April Evening Shift

Options:

A. $K_1 + K_2$

B. $\frac{K_1+K_2}{K_1K_2}$

C. $\frac{K_1+K_2}{2K_1K_2}$



D. $\frac{2K_1K_2}{K_1+K_2}$

Answer: C

Solution:

When dielectrics are placed in series, the equivalent dielectric constant is:

$$\frac{1}{K_{eq}} = \frac{1}{2 K_1} + \frac{1}{2 K_2}$$

$$\frac{1}{K_{eq}} = \left(\frac{K_1 + K_2}{2 K_1 K_2} \right)$$

$$K_{eq} = \left(\frac{2 K_1 K_2}{K_1 + K_2} \right)$$

So, new capacitance:

$$C_K = K_{eq} \cdot C_P = \left(\frac{2K_1K_2}{K_1 + K_2} \right) C_P$$

$$\frac{C_P}{C_K} = \frac{K_1 + K_2}{2K_1K_2}$$

Question23

A parallel plate capacitor with plate area A and plate separation d is charged by constant current I . A plane surface of area $\frac{A}{2}$, parallel to the plates is drawn simultaneously between the plates. The displacement current through this area is

MHT CET 2025 20th April Evening Shift

Options:

A. I

B. $\frac{I}{2}$

C. $\frac{I}{4}$

D. $\frac{I}{8}$

Answer: B

Solution:

Displacement current between the plates is equal to the conduction (charging) current I for the full area. The electric field and flux are uniform between the plates, so the displacement current through any surface is proportional to the area of that surface .

$$\text{Displacement current } I_d = \frac{A/2}{A} \times I = \frac{1}{2}I$$

$$\therefore I_D = \frac{I}{2}$$

Question24

Two parallel plate air c apacitors of same capacity ' C ' are connected in parallel to a battery of e.m.f. ' E '. Then one of the capacitors is completely filled with dielectric mnaterial of constant ' K '. The change in the effective capacity of the parallel combination is

MHT CET 2025 19th April Evening Shift

Options:

A. $\frac{C}{(K-1)}$

B. $\frac{KC}{K-1}$

C. $KC + 1$

D. $C(K - 1)$

Answer: D

Solution:

Let the capacitance of each air capacitor be C .

Step 1: Initial effective capacitance (before inserting dielectric)

Since both capacitors are identical and connected in parallel:

$$C_{\text{initial}} = C + C = 2C$$

Step 2: Insert dielectric of constant K in one capacitor



The capacitance of the capacitor with dielectric becomes:

$$C' = KC$$

So the effective capacitance of the parallel combination is:

$$C_{\text{final}} = C + KC = (1 + K)C$$

Step 3: Change in effective capacitance

Change in effective capacitance is:

$$\Delta C = C_{\text{final}} - C_{\text{initial}}$$

Substitute the values:

$$\Delta C = (1 + K)C - 2C = (K - 1)C$$

Step 4: Match with the options

So, the correct answer is

$$\boxed{C(K - 1)}$$

Option D is correct.

Question25

The plates of a parallel plate capacitor are separated by a distance 'd' with air as the medium between them. A dielectric slab of dielectric constant 3 is introduced between the plates so as to increase the capacity by 50%. The thickness of the dielectric slab is

MHT CET 2025 19th April Morning Shift

Options:

A. $\frac{d}{2}$

B. $\frac{d}{3}$

C. $\frac{d}{5}$

D. $\frac{5d}{6}$

Answer: A

Solution:



Step 1: Calculate the initial capacitance of the parallel plate capacitor.

When the medium between the plates is air (or vacuum), the capacitance (C_0) is given by:

$$C_0 = \frac{\epsilon_0 A}{d}$$

where:

- ϵ_0 is the permittivity of free space.
- A is the area of each plate.
- d is the separation between the plates.

Step 2: Calculate the capacitance after introducing the dielectric slab.

When a dielectric slab of thickness t and dielectric constant K is introduced between the plates of a parallel plate capacitor, the new capacitance (C_f) is given by the formula:

$$C_f = \frac{\epsilon_0 A}{d - t + \frac{t}{K}}$$

In this problem, the dielectric constant $K = 3$. So, substituting this value:

$$C_f = \frac{\epsilon_0 A}{d - t + \frac{t}{3}}$$

To simplify the denominator:

$$C_f = \frac{\epsilon_0 A}{d - \frac{3t}{3} + \frac{t}{3}}$$

$$C_f = \frac{\epsilon_0 A}{d - \frac{2t}{3}}$$

Step 3: Use the given condition about the increase in capacity.

The problem states that the capacity increases by 50%. This means the final capacitance C_f is 150% of the initial capacitance C_0 .

$$C_f = C_0 + 50\% \text{ of } C_0$$

$$C_f = C_0 + 0.5C_0$$

$$C_f = 1.5C_0$$

Step 4: Equate the expressions for C_f and solve for the thickness t .

Now, substitute the expressions for C_f and C_0 into the equation from Step 3:

$$\frac{\epsilon_0 A}{d - \frac{2t}{3}} = 1.5 \left(\frac{\epsilon_0 A}{d} \right)$$

We can cancel out $\epsilon_0 A$ from both sides of the equation:

$$\frac{1}{d - \frac{2t}{3}} = \frac{1.5}{d}$$

Now, cross-multiply to solve for t :

$$d = 1.5 \left(d - \frac{2t}{3} \right)$$

$$d = 1.5d - 1.5 \times \frac{2t}{3}$$

$$d = 1.5d - \frac{3}{2} \times \frac{2t}{3}$$

$$d = 1.5d - t$$

Rearrange the equation to isolate t :

$$t = 1.5d - d$$

$$t = 0.5d$$


$$t = \frac{d}{2}$$

Thus, the thickness of the dielectric slab is $\frac{d}{2}$.

The final answer is $\boxed{\frac{d}{2}}$.

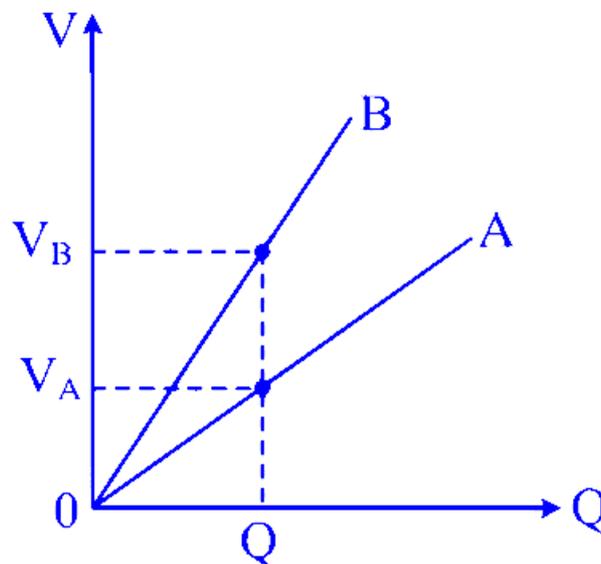Question 26

The graph shows the variation of voltage 'V' across the plates of two capacitors A and B versus increase in charge 'Q' stored in them. Then



MHT CET 2024 16th May Evening Shift

Options:

- A. capacitance A has high capacity.
- B. capacitance B has high capacity.
- C. both have same capacity.
- D. capacity of A = 2 times capacity of B.

Answer: A

Solution:

The relationship between charge Q and voltage V for a capacitor is given by:

$$Q = CV$$


This equation is analogous to $y = mx$, where C is the capacitance, equivalent to the inverse of the slope of the line on the graph. Therefore, we can express capacitance C as:

$$C = \frac{Q}{V} = \frac{1}{\text{slope of the line}}$$

Since the line representing capacitor A has a smaller slope compared to that of capacitor B , the capacitance of A is greater than that of B .

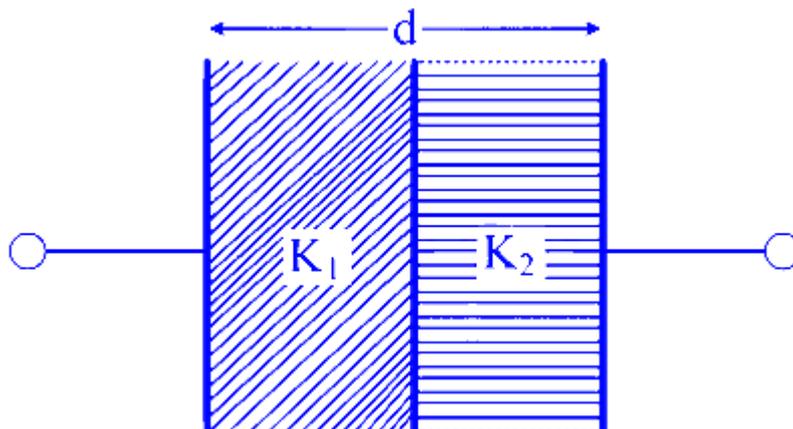Question27

Air capacitor has capacitance ' C_1 '. The space between two plates of capacitor is filled with two dielectrics as shown in figure. The new capacitance of the capacitor is ' C_2 '. The ratio $\frac{C_1}{C_2}$ is (d = distance between two plates of capacitor, K_1 and K_2 are dielectric constants of two dielectrics respectively)



MHT CET 2024 16th May Evening Shift

Options:

A. $K_1 + K_2$

B. $\frac{K_1+K_2}{K_1-K_2}$

C. $\frac{2 K_1 K_2}{K_1+K_2}$

D. $\frac{K_1+K_2}{2 K_1 K_2}$

Answer: D

Solution:

When an air capacitor has a capacitance of C_1 , it is represented as:

$$C_1 = \frac{A\epsilon_0}{d}$$

where A is the area of the plates, ϵ_0 is the permittivity of free space, and d is the distance between the plates.

When the space between the plates of this capacitor is filled with two different dielectric materials, it affects the overall capacitance. The two dielectrics are inserted as shown, and this setup functions as capacitors in series. To find the new capacitance C_2 with dielectrics, we calculate as follows:

First, the capacitance with each dielectric in place is calculated:

For the first dielectric with constant K_1 :

$$C_{K1} = \frac{A\epsilon_0 K_1}{\frac{d}{2}}$$

For the second dielectric with constant K_2 :

$$C_{K2} = \frac{A\epsilon_0 K_2}{\frac{d}{2}}$$

The capacitance of the configuration can then be represented as capacitors in series:

$$\frac{1}{C_2} = \frac{1}{C_{K1}} + \frac{1}{C_{K2}}$$

Substitute the expressions for C_{K1} and C_{K2} :

$$\frac{1}{C_2} = \frac{1}{\frac{A\epsilon_0 K_1}{\frac{d}{2}}} + \frac{1}{\frac{A\epsilon_0 K_2}{\frac{d}{2}}}$$

$$\frac{1}{C_2} = \frac{\frac{d}{2}}{A\epsilon_0 K_1} + \frac{\frac{d}{2}}{A\epsilon_0 K_2}$$

Simplify to:



$$\frac{1}{C_2} = \frac{d}{2\varepsilon_0 A} \left(\frac{1}{K_1} + \frac{1}{K_2} \right)$$

$$C_2 = \frac{2\varepsilon_0 A}{d} \left(\frac{K_1 K_2}{K_1 + K_2} \right)$$

Therefore, the ratio of the original capacitance C_1 to the new capacitance C_2 is:

$$\frac{C_1}{C_2} = \frac{K_1 + K_2}{2K_1 K_2}$$

Question28

Two identical capacitors A and B are connected in series to a battery of E.M.F., 'E'. Capacitor B contains a slab of dielectric constant K. Q_A and Q_B are the charges stored in A and B. When the dielectric slab is removed, the corresponding charges are Q'_A and Q'_B . Then

MHT CET 2024 16th May Morning Shift

Options:

A. $\frac{Q'_A}{Q_A} = \frac{K}{2}$

B. $\frac{Q'_B}{Q_B} = \frac{K+1}{2}$

C. $\frac{Q'_A}{Q_A} = \frac{K+1}{K}$

D. $\frac{Q'_B}{Q_B} = \frac{K+1}{2K}$

Answer: D

Solution:

When two capacitors, A and B, are connected in series, they will have the same charge initially due to the series configuration. Consider the capacitors connected to a battery of voltage E .

Initial Configuration with Dielectric in Capacitor B:

The capacitance of capacitor B with a dielectric is $C'_B = KC$, where C is the capacitance of capacitor A, and K is the dielectric constant.

For capacitors in series,

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C} + \frac{1}{KC} = \frac{K+1}{KC}.$$

$$C_{\text{eq}} = \frac{KC}{K+1}.$$

The charge on the capacitors in series is given by:

$$Q = C_{\text{eq}} \cdot E = \frac{KC}{K+1} \cdot E.$$

Charges on Each Capacitor:

Since $Q_A = Q_B = Q$ (initially when the dielectric is present in B),

$$Q_A = Q_B = \frac{KC}{K+1} \cdot E.$$

After Removing the Dielectric from Capacitor B:

Without the dielectric, the capacitance of B becomes C . The equivalent capacitance is now:

$$\frac{1}{C'_{\text{eq}}} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C}.$$

$$C'_{\text{eq}} = \frac{C}{2}.$$

The charge on the new configuration is:

$$Q' = C'_{\text{eq}} \cdot E = \frac{C}{2} \cdot E.$$

Since the capacitors are still in series, the charges on A and B are equal:

$$Q'_A = Q'_B = Q'.$$

Comparing the Charges:

For capacitor A:

$$\frac{Q'_A}{Q_A} = \frac{Q'}{Q_A} = \frac{\frac{C}{2} \cdot E}{\frac{KC}{K+1} \cdot E} = \frac{K+1}{2K}.$$

For capacitor B:

$$\frac{Q'_B}{Q_B} = \frac{\frac{C}{2} \cdot E}{\frac{KC}{K+1} \cdot E} = \frac{K+1}{2K}.$$

The correct option in this context would be:

Option D:

$$\frac{Q'_B}{Q_B} = \frac{K+1}{2K}$$

Question29

A series combination of n_1 capacitors, each of value C_1 is charged by a source of potential difference 6 V . Another parallel combination of n_2 capacitors, each of value C_2 is charged by a source of potential difference 2 V . Total energy of both the combinations is same. The value of C_2 in terms of C_1 is

MHT CET 2024 16th May Morning Shift

Options:

A. $\frac{3C_1}{n_1n_2}$

B. $\frac{9n_2}{n_1}C_1$

C. $\frac{3n_2}{n_1}C_1$

D. $\frac{9C_1}{n_1n_2}$

Answer: D

Solution:

When capacitors are connected in series, the equivalent capacitance is given by:

$$(C_{eq})_1 = \frac{C_1}{n_1}$$

The potential difference across this series is:

$$V_1 = 6 \text{ V}$$

For the capacitors connected in parallel, the equivalent capacitance is:

$$(C_{eq})_2 = n_2C_2$$

The potential difference across this combination is:

$$V_2 = 2 \text{ V}$$

Given that the total energy for both combinations is the same, we have:

$$U_1 = U_2$$

The energy stored in a capacitor is given by the formula:

$$U = \frac{1}{2}CV^2$$

Therefore, equating the energies, we get:

$$\frac{1}{2} \left(\frac{C_1}{n_1} \right) (6^2) = \frac{1}{2} (n_2 C_2) (2^2)$$

Simplifying the above equation:

$$\frac{1}{2} \cdot C_1 \cdot 36 = \frac{1}{2} \cdot n_2 \cdot C_2 \cdot 4$$

Further simplifying:


$$18C_1 = 2n_2C_2$$

Solving for C_2 :

$$C_2 = \frac{9C_1}{n_1n_2}$$

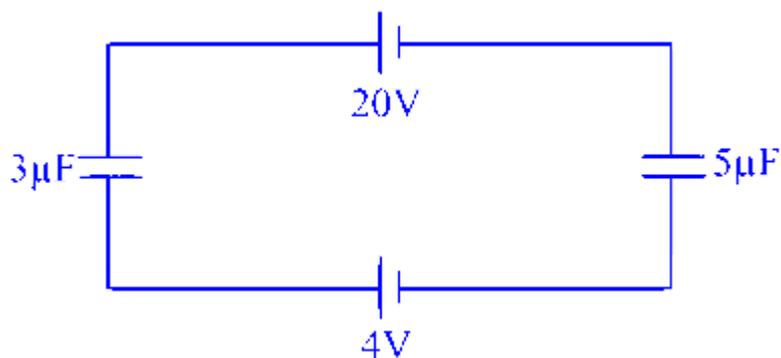Question30

In the circuit shown in the following figure, the potential difference across $3\mu\text{F}$ capacitor is



MHT CET 2024 15th May Evening Shift

Options:

- A. 4 V
- B. 6 V
- C. 10 V
- D. 16 V

Answer: C

Solution:

To find the potential difference across the $3 \mu\text{F}$ capacitor, we start by determining the equivalent voltage and equivalent capacitance in the circuit.

First, calculate the equivalent voltage (V_{eq}):

$$V_{\text{eq}} = 20 - 4 = 16 \text{ V}$$

Next, determine the equivalent capacitance (C_{eq}) for the parallel combination of the $3 \mu\text{F}$ and $5 \mu\text{F}$ capacitors:

$$C_{\text{eq}} = \frac{3 \times 5}{3 + 5} = \frac{15}{8} \mu\text{F}$$

Then, calculate the total charge (Q) using the equivalent capacitance and voltage:

$$Q = C_{\text{eq}} \times V_{\text{eq}} = \frac{15}{8} \times 16 = 30 \mu\text{C}$$

Finally, find the voltage across the $3 \mu\text{F}$ capacitor (V_3) using the formula for charge (Q):

$$V_3 = \frac{Q}{C} = \frac{30}{3} = 10 \text{ V}$$

The potential difference across the $3 \mu\text{F}$ capacitor is 10 V.

Question31

Three condensers of capacities ' C_1 ', ' C_2 ', ' C_3 ' are connected in series with a source of e.m.f. ' V '. The potentials across the three condensers are in the ratio

MHT CET 2024 15th May Morning Shift

Options:

A. $1 : 1 : 1$

B. $C_1 : C_2 : C_3$

C. $C_1^2 : C_2^2 : C_3^2$

D. $\frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$

Answer: D

Solution:

When capacitors are connected in series, they all carry the same charge. This is because the charge that is stored on one plate of a capacitor must equal the charge on the adjacent plate of the next capacitor. Therefore, if you consider the voltage across each individual capacitor, the relation can be described as follows:

For capacitors C_1 , C_2 , and C_3 with potentials V_1 , V_2 , and V_3 respectively, we have:

$$Q = C_1 V_1 = C_2 V_2 = C_3 V_3$$

Solving for the voltage, we get:

$$V_1 = \frac{Q}{C_1}, \quad V_2 = \frac{Q}{C_2}, \quad V_3 = \frac{Q}{C_3}$$

Therefore, the potential (voltage) ratios will be inversely proportional to the capacitances:

$$V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$

This relationship illustrates that the capacitor with the smallest capacitance will have the largest voltage across it, and vice versa. Hence, the potentials across the capacitors are in the ratio $\frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$.

Question32

When three capacitors of equal capacities are connected in parallel and one of the same capacity, capacitor is connected in series with the combination. The resultant capacity is $4.5\mu\text{ F}$. The capacity of each capacitor is

MHT CET 2024 11th May Morning Shift

Options:

A. $5\mu\text{ F}$


B. $7\mu\text{ F}$

C. $6\mu\text{ F}$

D. $8\mu\text{ F}$

Answer: C

Solution:

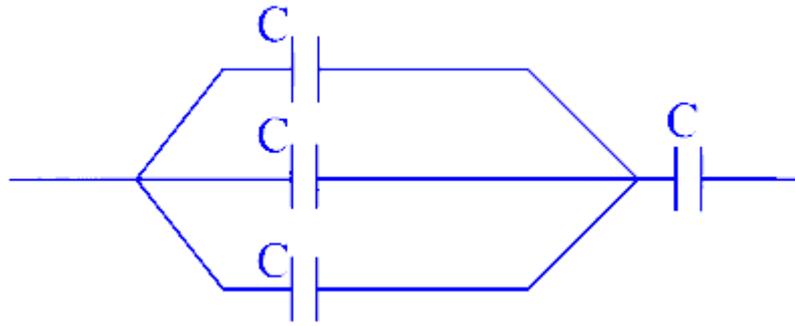

$$C_{eq} = \frac{3C \times C}{3C + C} = \frac{3C^2}{4C}$$

$$C_{eq} = \frac{3C}{4}$$

$$\therefore C = \frac{4C_{eq}}{3} = \frac{4 \times 4.5}{3} = 6\mu\text{ F}$$

Question33

Two parallel plate air capacitors of same capacity ' C ' are connected in series to a battery of emf ' E '. Then one of the capacitors is completely filled with dielectric material of constant ' K '. The change in the effective capacity of the series combination is

MHT CET 2024 11th May Morning Shift

Options:

A. $\frac{C}{2} \left[\frac{K+1}{K-1} \right]$

B. $\frac{2}{C} \left[\frac{K-1}{K+1} \right]$

C. $\frac{C}{2} \left[\frac{K-1}{K+1} \right]$

D. $\frac{C}{2} \left[\frac{K-1}{K+1} \right]^2$

Answer: C

Solution:

Let's break down the problem step by step.

Two identical air capacitors, each of capacitance C , are connected in series. The effective capacitance in series is given by

$$\frac{1}{C_{\text{series}}} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C},$$

so

$$C_{\text{series}} = \frac{C}{2}.$$

Now, one capacitor is completely filled with a dielectric of constant K . When a capacitor is fully filled with a dielectric, its capacitance increases by a factor of K , so its new capacitance becomes KC . The other capacitor remains at C .

For two capacitors in series (one with capacitance KC and the other with C), the effective capacitance becomes:

$$C' = \frac{(KC) \cdot C}{KC + C} = \frac{KC^2}{C(K+1)} = \frac{KC}{K+1}.$$

The change in effective capacitance is the difference between the new effective capacitance and the original:

$$\Delta C = C' - \frac{C}{2} = \frac{KC}{K+1} - \frac{C}{2}.$$

To combine the terms, find a common denominator:

$$\Delta C = \frac{2KC - C(K+1)}{2(K+1)} = \frac{2KC - CK - C}{2(K+1)} = \frac{C(K-1)}{2(K+1)}.$$

Thus, the change in the effective capacitance is

$$\frac{C}{2} \left(\frac{K-1}{K+1} \right),$$

which corresponds to Option C.

Question34

Seven capacitors each of capacitance $2\mu\text{ F}$ are connected in a configuration to obtain an effective capacitance $\frac{6}{13}\mu\text{ F}$. The combination which will achieve this will have

MHT CET 2024 10th May Morning Shift

Options:

A. 5 capacitors in parallel and then 2 capacitors series.

B. 4 capacitors in parallel and then 3 capacitors series.



C. 3 capacitors in parallel and then 4 capacitors in series.

D. 2 capacitors in parallel and then 5 capacitors in series.

Answer: C

Solution:

To achieve an effective capacitance of $\frac{6}{13} \mu\text{F}$ using seven capacitors, each with a capacitance of $2 \mu\text{F}$, you should arrange them with 3 capacitors in parallel and 4 capacitors in series.

Here's how the calculation works:

Parallel Connection: When capacitors are connected in parallel, their capacitances add up. So for 3 capacitors in parallel:

$$C_{\text{parallel}} = 3 \times C = 3 \times 2 \mu\text{F} = 6 \mu\text{F}$$

Series Connection: When capacitors are connected in series, the reciprocal of the total capacitance is the sum of the reciprocals of individual capacitances. For 4 capacitors, each of capacitance C , in series, the total capacitance is:

$$\frac{1}{C_{\text{series}}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{4}{C}$$

Therefore:

$$C_{\text{series}} = \frac{C}{4} = \frac{2 \mu\text{F}}{4} = 0.5 \mu\text{F}$$

Combining Series and Parallel: For combining the parallel and series connections, where C_{total} is the effective capacitance:

$$\frac{1}{C_{\text{total}}} = \frac{1}{C_{\text{parallel}}} + \frac{1}{C_{\text{series}}} = \frac{1}{6} + \frac{1}{0.5} = \frac{1+12}{6} = \frac{13}{6}$$

Consequently:

$$C_{\text{total}} = \frac{6}{13} \mu\text{F}$$

Therefore, the required configuration is 3 capacitors in parallel followed by 4 capacitors in series to yield an overall capacitance of $\frac{6}{13} \mu\text{F}$.

Question35

Two identical capacitors have the same capacitance ' C '. One of them is charged to potential V_1 and other to V_2 . The negative ends of capacitors are connected together. When positive ends are also connected, the decrease in energy of the combined system is

MHT CET 2024 10th May Morning Shift

Options:

A. $\frac{1}{4}C (V_1^2 + V_2^2)$

B. $\frac{1}{4}C (V_1^2 - V_2^2)$

C. $\frac{1}{4}C(V_1 + V_2)^2$

D. $\frac{1}{4}C(V_1 - V_2)^2$

Answer: D

Solution:

To determine the decrease in energy when two identical capacitors are connected, we start by calculating the initial energy of the system. Each capacitor has capacitance C , with one charged to a potential V_1 and the other to V_2 .

Initial Energy:

The initial energy U_i of the system is the sum of the energies stored in both capacitors:

$$U_i = \frac{1}{2}CV_1^2 + \frac{1}{2}CV_2^2 = \frac{1}{2}C(V_1^2 + V_2^2)$$

When Capacitors are Joined:

When the capacitors are connected, they share charge to reach a common potential V . The formula for this common potential is:

$$V = \frac{CV_1 + CV_2}{2C} = \frac{V_1 + V_2}{2}$$

Final Energy:

The final energy U_f of the system is given by:

$$U_f = \frac{1}{2}(2C)V^2 = \frac{1}{2}2C\left(\frac{V_1 + V_2}{2}\right)^2 = \frac{1}{4}C(V_1 + V_2)^2$$

Decrease in Energy:

The decrease in energy is the difference between the initial and final energies:

$$\text{Decrease in energy} = U_i - U_f = \frac{1}{2}C(V_1^2 + V_2^2) - \frac{1}{4}C(V_1 + V_2)^2$$

Through simplification, this can be expressed as:

$$\text{Decrease in energy} = \frac{1}{4}C(V_1 - V_2)^2$$



Question36

The potential difference that must be applied across the series and parallel combination of 4 identical capacitors is such that the energy stored in them becomes the same. The ratio of potential difference in series to parallel combination is

MHT CET 2024 9th May Evening Shift

Options:

A. 1 : 2

B. 1 : 4

C. 4 : 1

D. 2 : 1

Answer: C

Solution:

To find the ratio of the potential difference required for equal energy storage in both series and parallel combinations of four identical capacitors, let's analyze the equivalent capacitance for each configuration.

Series Combination

The equivalent capacitance for capacitors in series is given by:

$$C_1 = \frac{C}{4}$$

The potential energy stored in this series configuration is:

$$U_1 = \frac{1}{2}C_1V_1^2$$

Parallel Combination

The equivalent capacitance for capacitors in parallel is:

$$C_2 = 4C$$

The potential energy stored in the parallel configuration is:

$$U_2 = \frac{1}{2}C_2V_2^2$$

Equating Energy

Since the energy stored in both configurations is equal, we have:

$$U_1 = U_2$$

This implies:

$$C_1 V_1^2 = C_2 V_2^2$$

Substituting the expressions for C_1 and C_2 , we get:

$$\frac{C}{4} V_1^2 = 4C V_2^2$$

To find the ratio of the potential differences, solve for:

$$\frac{V_1^2}{V_2^2} = \frac{4C \times 16}{C}$$

Simplifying:

$$\frac{V_1^2}{V_2^2} = \frac{16}{1}$$


So, the ratio of the potential differences is:

$$\frac{V_1}{V_2} = \sqrt{\frac{16}{1}} = \frac{4}{1}$$

Thus, the ratio of potential difference in series to parallel combination is 4:1.

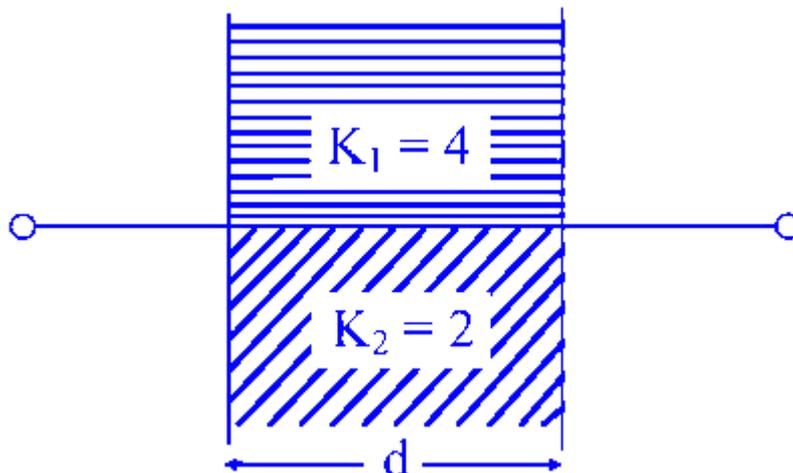Question37

Air capacitor has capacitance of $1\mu\text{ F}$. Now the space between two plates of capacitor is filled with two dielectrics as shown in figure. The capacitance of the capacitor is [d = distance between two plates of capacitor, K_1 and K_2 are dielectric constants of first dielectric and second dielectric respectively]



MHT CET 2024 9th May Evening Shift

Options:

A. $3\mu\text{ F}$

B. $6\mu\text{ F}$

C. $8\mu\text{ F}$

D. $12\mu\text{ F}$

Answer: A

Solution:

To determine the capacitance of the capacitor after inserting dielectrics, we start with the original capacitance of the air-filled parallel plate capacitor, given by:

$$C = \frac{\epsilon_0 A}{d} = 1 \mu\text{F}$$

Once the space between the plates is filled with two dielectrics, the scenario changes. The dielectrics divide the space between the plates into two sections, each with its own capacitance.

For the first dielectric with dielectric constant $K_1 = 4$, the capacitance becomes:

$$C_1 = K_1 \cdot \frac{\epsilon_0 A}{2d} = 4 \cdot \frac{1}{2} = 2 \mu\text{F}$$

Similarly, for the second dielectric with dielectric constant $K_2 = 2$, the capacitance is:

$$C_2 = K_2 \cdot \frac{\epsilon_0 A}{2d} = 2 \cdot \frac{1}{2} = 1 \mu\text{F}$$

Given that both sections are in parallel, the effective capacitance C_{eff} of the capacitor is the sum of the two individual capacitances:

$$C_{\text{eff}} = C_1 + C_2 = 2 \mu\text{F} + 1 \mu\text{F} = 3 \mu\text{F}$$

Question38

The function of dielectric in a capacitor is

MHT CET 2024 9th May Morning Shift

Options:

- A. to reduce the effective potential on plates.
- B. to increase the effective potential on plates.
- C. to decrease the capacitance.
- D. to reduce the plate area of capacitor.

Answer: A

Solution:

The correct answer is Option A.

Here's why:

When a dielectric is inserted between the plates of a capacitor, the dielectric material becomes polarized. This polarization creates an electric field that opposes the field due to the charges on the plates.

As a result, the effective electric field inside the capacitor is reduced. Since the potential difference (voltage) across the capacitor is related to the electric field by:

$$V = E \cdot d$$

(where d is the separation between the plates), reducing the electric field E also reduces the effective potential difference V between the plates.

With a lower effective potential difference for the same amount of charge, the capacitance, defined by


$$C = \frac{Q}{V},$$

increases. This explains why the dielectric increases the capacitance rather than decreasing it.

So, Option A, "to reduce the effective potential on plates," correctly describes the role of a dielectric in a capacitor.

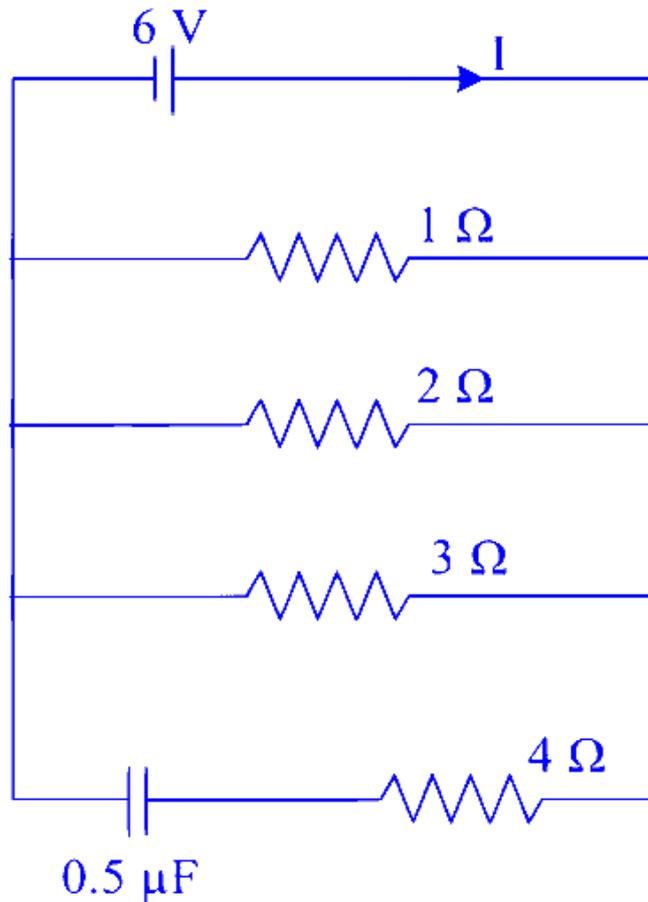Question39

In the given circuit diagram, in the steady state the current through the battery and the charge on the capacitor respectively are



MHT CET 2024 9th May Morning Shift

Options:

- A. 2 A and $3\ \mu\text{C}$
- B. $\frac{6}{11}$ A and $\frac{12}{7}\ \mu\text{C}$
- C. 11 A and $3\ \mu\text{C}$
- D. zero ampere and $3\ \mu\text{C}$

Answer: C

Solution:

In the steady state of the given circuit, the current through the capacitor is zero. This implies that there is no current flowing through the $4\ \Omega$ resistor.

To find the effective resistance (R_{eq}) for the parallel combination of the other resistors (1Ω , 2Ω , and 3Ω), we use:

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} = \frac{6+3+2}{6} = \frac{11}{6}$$

The total current (I) flowing through the circuit is given by:

$$I = \frac{V}{R_{eq}} = \frac{6 \text{ V} \times 11}{6} = 11 \text{ A}$$

For the charge on the capacitor, we use the formula $Q = CV$, where C is the capacitance and V is the voltage across the capacitor:

$$Q_C = 0.5 \mu\text{F} \times 6 \text{ V} = 3 \mu\text{C}$$

Question40

A parallel plate capacitor of capacitance ' C ' is connected to a battery and charged to a potential difference ' V '. Another capacitor of capacitance $3 C$ is similarly charged to a potential difference $3 V$. The charging battery is then disconnected and capacitors are connected in parallel to each other in such a way that positive terminal of one is connected to the negative terminal of the other. The final energy of the configuration is

MHT CET 2024 9th May Morning Shift

Options:

A. $\frac{3}{2} CV^2$

B. $8 CV^2$

C. $\frac{13}{2} CV^2$

D. $18 CV^2$

Answer: B

Solution:

When two parallel plate capacitors are connected in parallel, their combined capacitance is the sum of their individual capacitances. Here's a simplified breakdown:

Capacitance in Parallel:

Capacitor 1 has a capacitance C and is charged to a potential difference V .

Capacitor 2 has a capacitance $3C$ and is charged to a potential difference $3V$.

Combined Capacitance:

$$C_{\text{eq}} = C + 3C = 4C$$

Net Potential Difference:

The capacitors are connected such that the positive terminal of one is connected to the negative terminal of the other. This results in the net potential difference being the difference between the two:

$$V_{\text{net}} = 3V - V = 2V$$

Final Energy Calculation:

The energy stored in a capacitor is given by the formula:

$$\text{Energy} = \frac{1}{2} C_{\text{eq}} V_{\text{net}}^2$$

Substituting the calculated values:

$$\text{Energy} = \frac{1}{2} \times 4C \times (2V)^2 = 8CV^2$$

Therefore, the final energy of the configuration is $8CV^2$.

Question41

A parallel plate air capacitor, with plate separation ' d ' has a capacitance of 9 pF . The space between the plates is now filled with two dielectrics, the first having $K_1 = 3$ and thickness $d_1 = d/3$, while the 2nd has $K_2 = 6$ and thickness $d_2 = 2 d/3$. The capacitance of the new capacitor is :

MHT CET 2024 4th May Morning Shift

Options:

A. 3.8 pF

B. 20.25 pF

C. 40.5 pF



D. 45 pF

Answer: C

Solution:

For a parallel plate capacitor with a dielectric material, the capacitance is described by the formula:

$$C = \frac{A\epsilon_0 k}{d}$$

where,

C is the capacitance,

A is the area of one of the plates,

ϵ_0 is the permittivity of free space,

k is the dielectric constant of the material,

d is the separation between the plates.

Calculating Individual Capacitances

For each section with a different dielectric:

First Dielectric:

Dielectric constant $k_1 = 3$

Thickness $d_1 = \frac{d}{3}$

The capacitance C_1 is:

$$C_1 = \frac{A\epsilon_0 k_1}{d_1} = \frac{A\epsilon_0 \times 3}{d/3} = 9 \frac{A\epsilon_0}{d} = 9C$$

Second Dielectric:

Dielectric constant $k_2 = 6$

Thickness $d_2 = \frac{2d}{3}$

The capacitance C_2 is:

$$C_2 = \frac{A\epsilon_0 k_2}{d_2} = \frac{A\epsilon_0 \times 6}{2d/3} = 9 \frac{A\epsilon_0}{d} = 9C$$

Calculating Total Capacitance

Since these two sections are in series, the total capacitance C_{total} is given by:

$$C_{\text{total}} = \frac{C_1 \times C_2}{C_1 + C_2} = \frac{9C \times 9C}{9C + 9C} = \frac{81C^2}{18C} = \frac{9}{2}C$$

Given that the original capacitor had a capacitance of 9 pF, substitute this into the total capacitance equation:

$$C_{\text{total}} = \frac{9}{2} \times 9 \times 10^{-12} \text{F}$$

Thus,

$$C_{\text{total}} = 40.5 \text{ pF}$$

Therefore, the capacitance of the new capacitor is 40.5 pF.

Question42

A parallel plate capacitor has plate area 40 cm^2 and plate separation 2 mm . The space between the plates is filled with a dielectric medium of thickness 1 mm and dielectric constant 5 . The capacitance of the system is ($\epsilon_0 =$ permittivity of vacuum)

MHT CET 2024 4th May Morning Shift

Options:

A. $24\epsilon_0 \text{ F}$

B. $\frac{3}{10}\epsilon_0 \text{ F}$

C. $\frac{10}{3}\epsilon_0 \text{ F}$

D. $10\epsilon_0 \text{ F}$

Answer: C

Solution:

For a parallel plate capacitor composed of two capacitors in series, the equivalent capacitance can be calculated using the formula:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

The capacitance C_1 of the portion with the dielectric is given by:

$$C_1 = \frac{A\epsilon_0 k}{t}$$

And the capacitance C_2 of the portion without the dielectric is:

$$C_2 = \frac{A\epsilon_0}{d-t}$$

where:



A is the plate area,

ϵ_0 is the permittivity of vacuum,

k is the dielectric constant,

t is the thickness of the dielectric,

d is the total separation between the plates.

Substituting the given values:

$$\frac{1}{C_{eq}} = \frac{1}{\frac{40 \times 10^{-4} \epsilon_0 \times 5}{1 \times 10^{-3}}} + \frac{1}{\frac{40 \times 10^{-4} \epsilon_0}{2 \times 10^{-3} - 1 \times 10^{-3}}}$$

Simplifying, we calculate:

$$\frac{1}{C_{eq}} = \frac{1}{20\epsilon_0} + \frac{1}{4\epsilon_0}$$

Therefore, the equivalent capacitance C_{eq} is:

$$C_{eq} = \frac{10}{3} \epsilon_0 \text{ F}$$

Question43

A parallel plate capacitor is charged and then isolated. If the separation between the plates is increased, which one of the following statement is NOT correct?

MHT CET 2024 3rd May Evening Shift

Options:

- A. Charge remains constant after it is isolated.
- B. Potential difference across the plates decreases.
- C. Potential difference across the plates increases.
- D. Capacitance of capacitor decreases.

Answer: B

Solution:

Option B is NOT correct.

In a parallel plate capacitor, the charge Q remains constant after it is isolated, as stated in Option A. When the separation d between the plates is increased, the capacitance C of the capacitor is given by the formula:

$$C = \frac{\epsilon A}{d}$$

where ϵ is the permittivity of the dielectric material between the plates, and A is the area of the plates. Since C is inversely proportional to d , increasing the separation decreases the capacitance, as described in Option D.

The potential difference V across the plates is related to charge and capacitance by

$$V = \frac{Q}{C}$$

Since the charge Q remains constant and the capacitance C decreases when the separation is increased, the potential difference V must increase, which aligns with Option C. Therefore, the statement that the potential difference decreases (Option B) is incorrect.

Question44

Two circular metal plates each of radius ' r ' are kept parallel to each other distance ' d ' apart. The capacitance of the capacitor formed is ' C_1 '. If the radius of each of the plates is increased to $\sqrt{2}$ times the earlier radius and their distance of separation decreased to half the initial value, the capacitance now becomes ' C_2 '. The ratio of the capacitances $C_1 : C_2$ is

MHT CET 2024 3rd May Morning Shift

Options:

A. 1 : 1

B. 1 : 2

C. 1 : 4

D. 4 : 1

Answer: C

Solution:

The capacitance of a parallel plate capacitor is given by the formula:

$$C = \frac{\epsilon_0 A}{d}$$

where ϵ_0 is the permittivity of free space, A is the area of the plates, and d is the distance between the plates.

Initial Capacitance C_1 :

The area of each plate, A_1 , is:

$$A_1 = \pi r^2$$

So, the initial capacitance C_1 is:

$$C_1 = \frac{\epsilon_0 \pi r^2}{d}$$

Changed Capacitance C_2 :

The radius of each plate is increased to $\sqrt{2} \times r$, so the new area A_2 is:

$$A_2 = \pi(\sqrt{2}r)^2 = 2\pi r^2$$

The distance between the plates is decreased to $\frac{1}{2}d$.

The new capacitance C_2 is:

$$C_2 = \frac{\epsilon_0 \cdot 2\pi r^2}{\frac{1}{2}d} = \frac{2 \cdot \epsilon_0 \pi r^2}{\frac{1}{2}d} = \frac{4\epsilon_0 \pi r^2}{d}$$

Ratio $C_1 : C_2$:

$$\frac{C_1}{C_2} = \frac{\frac{\epsilon_0 \pi r^2}{d}}{\frac{4\epsilon_0 \pi r^2}{d}} = \frac{1}{4}$$

Therefore, the ratio of the capacitances $C_1 : C_2$ is:

Option C: 1 : 4

Question 45

The amount of work done in increasing the voltage across the plates of a capacitor from 5 V to 10 V is ' W '. The work done in increasing it from 10 V to 15 V will be (nearly)

MHT CET 2024 2nd May Evening Shift

Options:

A. 0.6 W

B. W

C. 1.25 W

D. 1.67 W

Answer: D

Solution:

To calculate the work done in increasing the voltage across the plates of a capacitor from 5 V to 10 V and then from 10 V to 15 V, we use the formula for the work done on a capacitor:

$$W = \frac{1}{2}CV^2$$

For a constant capacitance C , the work done, W , is proportional to the square of the voltage, V , so $W \propto V^2$.

Thus, the ratio of work done in two different voltage intervals is given by:

$$\frac{W_1}{W_2} = \frac{V_2^2 - V_1^2}{V_3^2 - V_2^2}$$

Where:

$$V_1 = 5 \text{ V}$$

$$V_2 = 10 \text{ V}$$

$$V_3 = 15 \text{ V}$$

Using these values, we find:

$$\frac{W}{W_2} = \frac{10^2 - 5^2}{15^2 - 10^2} = \frac{100 - 25}{225 - 100} = \frac{75}{125} = \frac{3}{5}$$

Solving for W_2 , we have:

$$W_2 = \frac{5}{3}W = 1.67W$$

Hence, the work done in increasing the voltage from 10 V to 15 V is approximately 1.67 W.

Question46

Charge on a parallel plate capacitor of capacity C is Q , the electric field intensity between its two plates separated by a distance of t is

MHT CET 2024 2nd May Evening Shift

Options:

A. $\frac{Qt}{C}$

B. $\frac{Q}{Ct}$

C. $\frac{C}{Qt}$

D. $\frac{Ct}{Q}$

Answer: B

Solution:

The electric field intensity (E) between the plates of a parallel plate capacitor is given by the formula:

$$E = \frac{Q}{A\epsilon} \quad \dots (i)$$

Where:

Q is the charge on the capacitor.

A is the area of the plates.

ϵ is the permittivity of the dielectric material between the plates.

The capacitance (C) of a parallel plate capacitor is expressed as:

$$C = \frac{A\epsilon}{t}$$

Solving for $A\epsilon$ gives:

$$A\epsilon = Ct \quad \dots (ii)$$

Substituting equation (ii) into equation (i):

$$E = \frac{Q}{Ct}$$

Thus, the electric field intensity between the plates is $\frac{Q}{Ct}$.

Question47

A circuit having a self inductance of 1 henry carries a current of 1 A . To prevent the sparking when the circuit is broken, a capacitor which can withstand 500 V is connected across the switch. What is the minimum value of the capacitance of the capacitor?

MHT CET 2024 2nd May Morning Shift

Options:

A. $2\mu\text{ F}$

B. $4\mu\text{ F}$

C. $6\mu\text{ F}$

D. $8\mu\text{ F}$

Answer: B

Solution:

The energy stored in an inductor is given by the expression:

$$E = \frac{1}{2}LI^2$$

where L is the inductance and I is the current. In this case, the energy is stored in a self-inductance $L = 1$ henry with a current $I = 1$ ampere. Substituting these values into the expression:

$$E = \frac{1}{2} \times 1 \times 1^2 = \frac{1}{2} \text{ joule}$$

To prevent sparking, the energy from the inductor is transferred to a capacitor when the circuit is broken. The energy stored in a capacitor is given by:

$$E = \frac{1}{2}CV^2$$

where C is the capacitance and V is the voltage across the capacitor. The maximum voltage the capacitor can withstand is $V = 500$ volts. Equating the two expressions for energy:

$$\frac{1}{2}LI^2 = \frac{1}{2}CV^2$$

Simplifying, we find:

$$LI^2 = CV^2$$

Solving for C , the minimum capacitance, we have:

$$C = \frac{LI^2}{V^2}$$

Substitute the given values $L = 1$ henry, $I = 1$ ampere, and $V = 500$ volts:

$$C = \frac{1 \times 1^2}{500^2} = \frac{1}{250000}$$

Converting to microfarads:


$$C = 4 \times 10^{-6} \text{ farads} = 4\mu\text{F}$$

Thus, the minimum value of the capacitance of the capacitor is:

Option B: $4 \mu\text{F}$

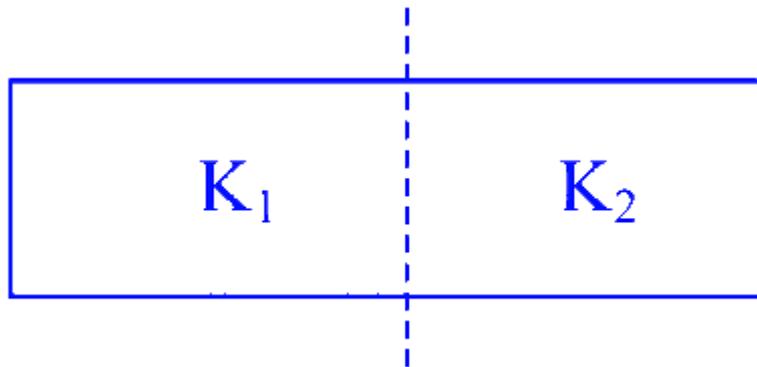Question48

A parallel plate capacitor with air medium between the plates has a capacitance of $10 \mu\text{F}$. The area of capacitor is divided into two equal halves and filled with two media (as shown in figure) having dielectric constant $K_1 = 2$ and $K_2 = 4$. The capacitance of the system will be



MHT CET 2023 14th May Evening Shift

Options:

A. $10 \mu\text{F}$

B. $20 \mu\text{F}$

C. $30 \mu\text{F}$

D. $40 \mu\text{F}$

Answer: C

Solution:


$$C = \frac{\epsilon_0 A}{d} = 10 \mu\text{F}$$

After dividing the area into two equal halves, the resultant capacitance is calculated as,

$$\begin{aligned}
 C_{\text{eq}} &= C_1 + C_2 \\
 &= \frac{K_1 \epsilon_0 A_1}{d} + \frac{K_2 \epsilon_0 A_2}{d} = \frac{2\epsilon_0 A}{d} + \frac{4\epsilon_0 A}{d} \\
 \therefore C_{\text{eq}} &= \frac{\epsilon_0 A}{d} + \frac{2\epsilon_0 A}{d} = \frac{3\epsilon_0 A}{d} = 3 \times 10 = 30\mu\text{F}
 \end{aligned}$$

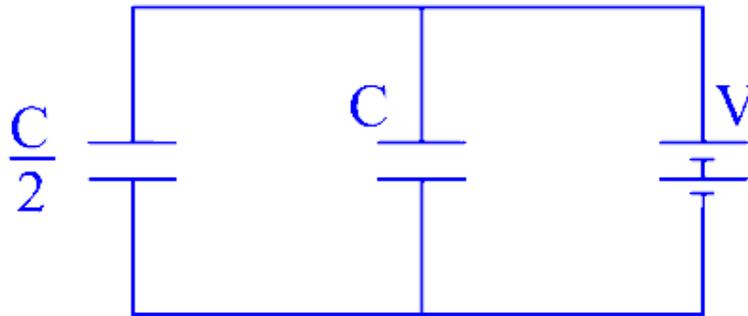Question49

Two condensers one of capacity $\frac{C}{2}$ and other capacity C are connected to a battery of voltage V as shown. The work done in charging fully both the condensers is



MHT CET 2023 14th May Evening Shift

Options:

- A. $\frac{1}{2} CV^2$
- B. $\frac{3}{4} CV^2$
- C. $\frac{3}{2} CV^2$
- D. $2 CV^2$

Answer: B

Solution:

The two condensers are in parallel. Their equivalent capacitance is $C_c = C + \frac{C}{2} = \frac{3C}{2}$

The formula for work done is

$$W = \frac{1}{2} C_e V^2$$

$$W = \frac{1}{2} \left(\frac{3C}{2} \right) V^2$$

$$W = \frac{3}{4} C V^2$$

Question50

Which of the following combination of 7 identical capacitors each of $2\mu\text{F}$ gives a capacitance of $\frac{10}{11}\mu\text{F}$?

MHT CET 2023 14th May Morning Shift

Options:

- A. 5 in parallel and 2 in series
- B. 4 in parallel and 3 in series
- C. 3 in parallel and 4 in series
- D. 2 in parallel and 5 in series

Answer: A

Solution:

For n identical capacitors connected in series, the equivalent capacitance is, $C_s = \frac{C}{n}$

Similarly, for m identical capacitors connected parallel to each other, the equivalent capacitance is, $C_p = mC$

Assuming the two combinations are connected in series, the net capacitance,

$$\frac{1}{C_{\text{net}}} = \frac{1}{mC} + \frac{n}{C} = \frac{11}{10}\mu\text{F} \quad \dots \left(\because C_{\text{net}} = \frac{10}{11}\mu\text{F} \right)$$

\therefore for $C = 2\mu\text{F}$,

$$\frac{11 \times 2}{10} = \frac{1}{m} + n$$

$$\therefore \frac{1}{m} + n = \frac{11}{5} \quad \dots (i)$$

Substituting the values for m and n in equation (i) from each option, the correct answer can be found to be (A).

Question51

In a parallel plate capacitor with air between the plates, the distance d between the plates is changed and the space is filled with dielectric constant 8. The capacity of the capacitor is increased 16 times, the distance between the plates is

MHT CET 2023 13th May Evening Shift

Options:

- A. $2d$
- B. $4d$
- C. $d/2$
- D. $d/4$

Answer: C

Solution:

Capacitance of a parallel plate capacitor is given by, $C = \frac{\epsilon_0 A}{d}$

When capacitor is completely filled with dielectric K then, $C' = \frac{\epsilon_0 K A}{d'}$

According to question, $\frac{C'}{C} = \frac{16}{1} = \frac{\frac{\epsilon_0 \times 8 \times A}{d'}}{\frac{\epsilon_0 \times A}{d}}$


$$\Rightarrow \frac{16}{1} = \frac{8d}{d'}$$

$$\Rightarrow d' = \frac{d}{2}$$

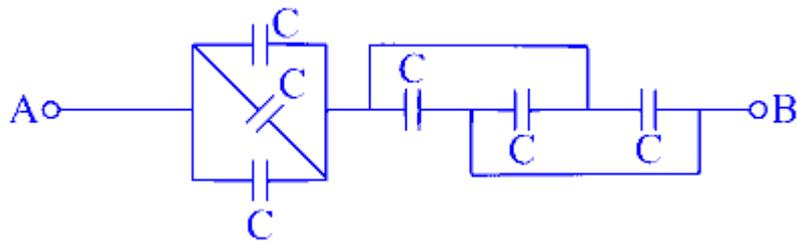Question52

In the given figure, the equivalent capacitance between points A and B is





MHT CET 2023 13th May Evening Shift


Options:

- A. $1.5 C$
- B. $2 C$
- C. $3 C$
- D. $6 C$

Answer: A

Solution:

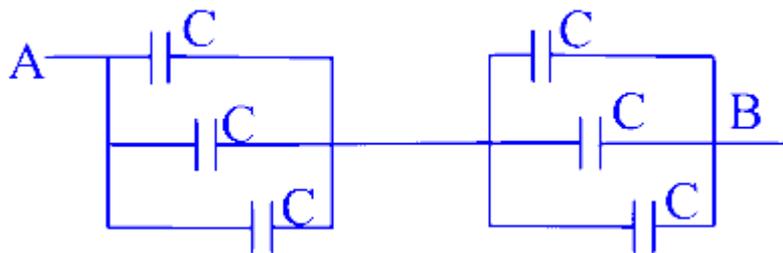The given circuit can also be redrawn as,



Thus, the parallel capacitors are calculated as $C_p = C + C + C = 3C$

Hence,



The equivalent capacitance between A and B is

$$\frac{1}{C_{\text{eq}}} = \frac{1}{3C} + \frac{1}{3C}$$
$$\Rightarrow \frac{1}{C_{\text{eq}}} = \frac{2}{3C}$$
$$\Rightarrow C_{\text{eq}} = \frac{3}{2}C$$
$$\Rightarrow C_{\text{eq}} = 1.5C$$

Question53

If the charge on the capacitor is increased by 3 coulombs, the energy stored in it increases by 44%. The original charge on the capacitor is

MHT CET 2023 12th May Evening Shift

Options:

- A. 10 C
- B. 15 C
- C. 20 C
- D. 25 C

Answer: B

Solution:

Energy stored in a charged capacitor is

$$U = \frac{Q^2}{2C} \Rightarrow U \propto Q^2$$

As per given condition, when, $Q_2 = (Q_1 + 3)$,

$$\therefore U_2 = 44\% \text{ of } U_1 = \frac{144}{100} U_1$$

$$\therefore \frac{Q_2^2}{2C} = \frac{144}{100} \times \frac{Q_1^2}{2C}$$

$$\therefore Q_1 = \frac{10}{12} Q_2$$


$$\therefore Q_1 = \frac{5}{6} (Q_1 + 3)$$

$$\therefore 6Q_1 = 5Q_1 + 15$$

$$\therefore Q_1 = 15C$$

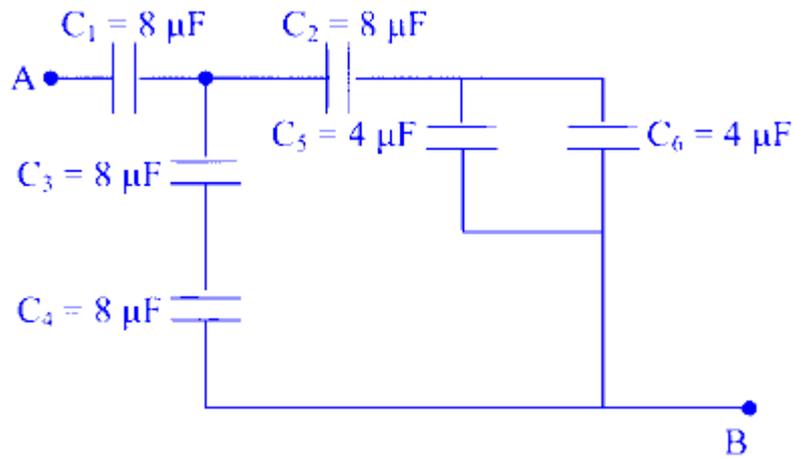Question54

In the given capacitive network the resultant capacitance between point A and B is



MHT CET 2023 12th May Morning Shift

Options:

- A. $8 \mu\text{F}$
- B. $4 \mu\text{F}$
- C. $2 \mu\text{F}$
- D. $16 \mu\text{F}$

Answer: B

Solution:

In the given circuit, C_3 and C_4 are in series and $C_3 = C_4 = 8 \mu\text{F}$

$$\therefore \frac{1}{C_s} = \frac{1}{C_3} + \frac{1}{C_4}$$

$$\therefore C_s = \frac{C_3^2}{2C_3}$$

$$C_s = \frac{C_3}{2}$$

$$\therefore C_s = 4 \mu\text{F} \quad \dots (i)$$


C_5 and C_6 are in parallel and $C_5 = C_6 = 4 \mu\text{F}$



$$C_P = C_5 + C_6$$

$$\therefore C_P = 8\mu\text{F}$$

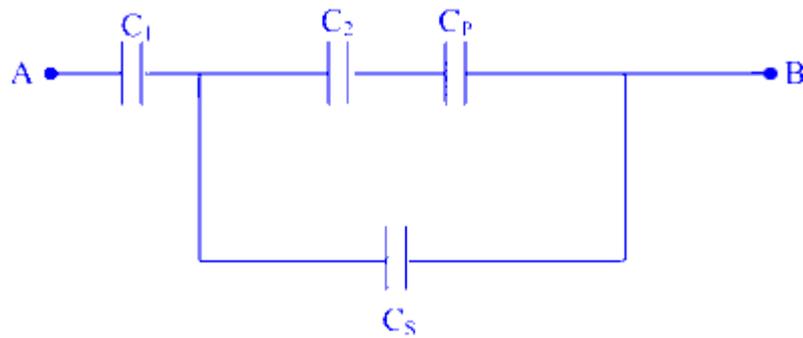\therefore Equivalent circuit is as shown in figure.



Now, C_2 and C_P are in series and their combination in parallel with C_S

$$\therefore C_E = \frac{C_2 C_P}{C_2 + C_P} + C_S$$

$$C_E = \frac{(8)(8)}{16} + 4$$

$$\therefore C_E = 8\mu\text{F}$$

Now, C_1 and C_E are in series,


$$\therefore C = \frac{C_1 C_E}{C_1 + C_E}$$

$$\therefore C = \frac{(8)(8)}{16}$$

$$\therefore C = 4\mu\text{F}$$

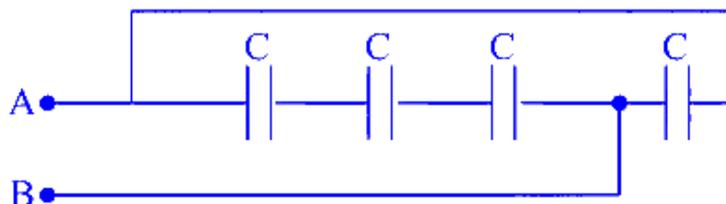Question55

The equivalent capacity between terminal A and B is



MHT CET 2023 12th May Morning Shift

Options:

A. $\frac{C}{4}$


B. $\frac{3C}{4}$

C. $\frac{C}{3}$

D. $\frac{4C}{3}$

Answer: D

Solution:

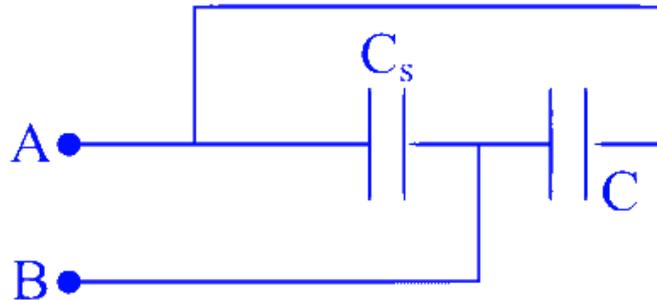

$$\frac{1}{C_s} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C}$$

$$\therefore C_s = \frac{C}{3}$$

Now, C_s and C are connected in parallel,

$$\therefore C_{\text{net}} = C_s + C = \frac{C}{3} + C = \frac{4C}{3}$$

Question56

The potential on the plates of capacitor are $+20\text{ V}$ and -20 V . The charge on the plate is 40C . The capacitance of the capacitor is

MHT CET 2023 12th May Morning Shift

Options:

A. 2 F

B. 1 F

C. 4 F

D. 0.5 F

Answer: B

Solution:

$$V = 20 - (-20) = 40 \text{ volt}$$

$$Q = 40C$$

$$C = \frac{Q}{V}$$

$$\therefore C = \frac{40}{40}$$

$$\therefore C = 1F$$

Question57

Two spherical conductors of capacities $3\mu\text{F}$ and $2\mu\text{F}$ are charged to same potential having radii 3 cm and 2 cm respectively. If ' σ_1 ' and ' σ_2 ' represent surface density of charge on respective conductors then $\frac{\sigma_1}{\sigma_2}$ is

MHT CET 2023 11th May Evening Shift

Options:

A. $\frac{1}{3}$

B. $\frac{1}{2}$

C. $\frac{2}{3}$

D. $\frac{3}{4}$

Answer: C

Solution:



We know, $C = \frac{Q}{V}$

As both the charged spheres are at the same potential, the charge on both spheres is

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

The charge densities of both spheres are

$$\sigma_1 = \frac{Q_1}{A_1} = \frac{C_1 V}{4\pi r_1^2}$$

Similarly,

$$\sigma_2 = \frac{Q_2}{A_2} = \frac{C_2 V}{4\pi r_2^2}$$

Taking the ratios,

$$\frac{\sigma_2}{\sigma_1} = \frac{C_2 r_1^2}{C_1 r_2^2}$$

$$\frac{\sigma_2}{\sigma_1} = \frac{2 \times 10^{-6} \times (0.03)^2}{3 \times 10^{-6} \times (0.02)^2} = \frac{3}{2}$$

$$\therefore \frac{\sigma_1}{\sigma_2} = \frac{2}{3}$$

Question58

Three identical capacitors of capacitance 'C' each are connected in series and this connection is connected in parallel with one more such identical capacitor. Then the capacitance of whole combination is

MHT CET 2023 11th May Evening Shift

Options:

A. $3C$

B. $2C$

C. $\frac{4}{3}C$

D. $\frac{3}{4}C$

Answer: C

Solution:

The equivalent capacitance of three capacitances connected in series is

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C}$$

$$\frac{1}{C_{eq}} = \frac{3}{C}$$

$$C_{eq} = \frac{C}{3}$$

This capacitance is connected in parallel with another capacitance.

$$\Rightarrow C_{total} = \frac{C}{3} + C$$

$$C_{total} = \frac{4C}{3}$$

Question59

A parallel plate capacitor is charged by a battery and battery remains connected. The dielectric slab of constant 'K' is inserted between the plates and then taken out. Then electric field between the plates

MHT CET 2023 11th May Evening Shift

Options:

- A. remains the same
- B. increases
- C. decreases
- D. becomes zero

Answer: A

Solution:

✔ Correct Answer: A. remains the same

✔ Explanation

A parallel-plate capacitor is connected to a battery, and the battery remains connected. This means:

👉 The voltage V across the capacitor remains constant.

Electric field between the plates is:

$$E = \frac{V}{d}$$

Where:

- V = voltage (constant because battery is connected)
- d = plate separation (unchanged)

So electric field remains constant, no matter what dielectric you insert or remove.

✔ What happens when dielectric is inserted?

- Capacitance increases:

$$C' = KC$$

- Charge increases because:

$$Q = CV \quad (V \text{ constant})$$

- Electric field does NOT change, because $E = V/d$.
-

✔ What happens when the dielectric is removed?

- Capacitance returns to original.
- Charge returns to original (battery keeps V fixed).
- Electric field remains:

$$E = \frac{V}{d}$$

Question60

Two identical capacitors have the same capacitance ' C '. One of them is charged to a potential V_1 and the other to V_2 . The negative ends of the capacitors are connected together. When the positive ends are also connected, the decrease in energy of the combined system is

MHT CET 2023 11th May Morning Shift

Options:

A. $\frac{1}{4}C (V_1^2 - V_2^2)$

B. $\frac{1}{4}C (V_1^2 + V_2^2)$

C. $\frac{1}{4}C(V_1 - V_2)^2$

D. $\frac{1}{4}C(V_1 + V_2)^2$

Answer: C

Solution:

Initial energy of the combined system

$$U_1 = \frac{1}{2}CV_1^2 + \frac{1}{2}CV_2^2 = \frac{C}{2} (V_1^2 + V_2^2)$$

On joining the two condensers in parallel, common potential,

$$V = \frac{V_1 + V_2}{2}$$

∴ Final energy of the combined system:

$$U_2 = \frac{1}{2}(C + C) \left(\frac{V_1 + V_2}{2} \right)^2$$

∴ Decrease in energy will be:

$$\begin{aligned} \Delta U &= U_1 - U_2 \\ &= \frac{C}{2} (V_1^2 + V_2^2) - \frac{1}{2}(C + C) \left(\frac{V_1 + V_2}{2} \right)^2 \\ &= \frac{1}{4}C(V_1 - V_2)^2 \end{aligned}$$

Question61

If a capacitor of capacity $900 \mu\text{F}$ is charged to 100 V and its total energy is transferred to a capacitor of capacity $100 \mu\text{F}$, then its potential will be

MHT CET 2023 10th May Evening Shift

Options:

- A. 30 V
- B. 200 V
- C. 300 V
- D. 400 V

Answer: C

Solution:

Let the unknown potential be V_u

Energy of a capacitor = $\frac{1}{2}CV^2$

$$\Rightarrow \frac{1}{2}C_1V_1^2 = \frac{1}{2}C_2(V_u)^2$$

$$\frac{1}{2} \times 900 \times 10^{-6} \times (100)^2 = \frac{1}{2} \times 100 \times 10^{-6} \times (V_u)^2$$


$$(V_u)^2 = 9 \times 100^2$$

$$\therefore V_u = 300 \text{ V}$$

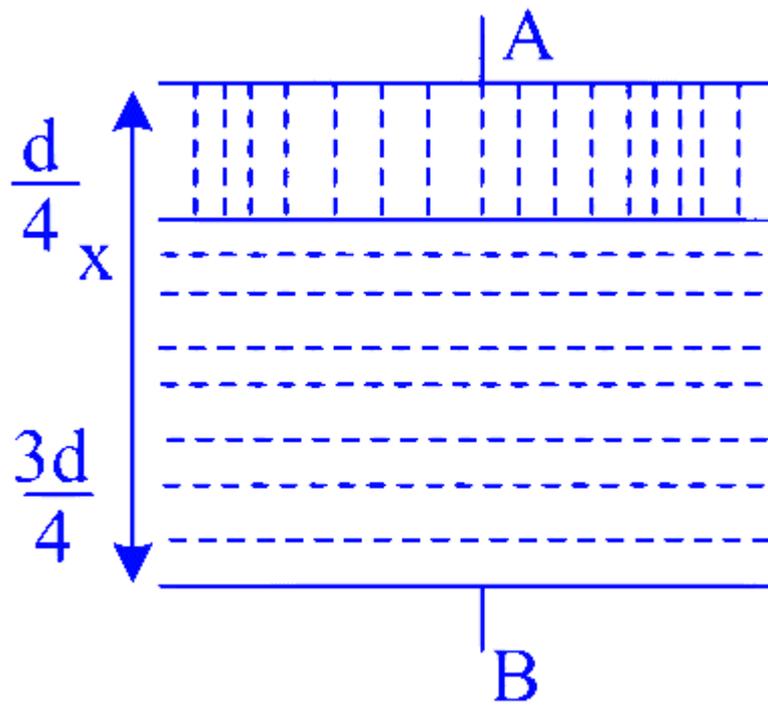Question62

Two dielectric slabs having dielectric constant ' K_1 ' and ' K_2 ' of thickness $\frac{d}{4}$ and $\frac{3d}{4}$ are inserted between the plates as shown in figure. The net capacitance between A and B is [ϵ_0 is permittivity of free space]





MHT CET 2023 10th May Evening Shift

Options:

A. $\frac{2 A \epsilon_0}{d} \left[\frac{K_1 K_2}{3 K_1 + K_2} \right]$

B. $\frac{3 A \epsilon_0}{d} \left[\frac{K_1 + K_2}{K_1 K_2} \right]$

C. $\frac{3 A_0}{2 d} \left[\frac{K_1 + K_2}{K_1 K_2} \right]$

D. $\frac{4 A \epsilon_0}{d} \left[\frac{K_1 K_2}{3 K_1 + K_2} \right]$

Answer: D

Solution:

Capacity of 1st Capacitor,

$$C_1 = \frac{K_1 \epsilon_0 A}{d/4} = \frac{4 K_1 \epsilon_0 A}{d}$$

Capacity of 2nd Capacitor,

$$C_2 = \frac{K_2 \epsilon_0 A}{3 d/4} = \frac{4 K_2 \epsilon_0 A}{3 d}$$

Equivalent capacitance $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$



$$\frac{1}{C_1} = \frac{d}{4 K_1 \epsilon_0 A}; \frac{1}{C_2} = \frac{3d}{4 K_2 \epsilon_0 A}$$

$$\frac{1}{C} = \frac{d}{4 K_1 \epsilon_0 A} + \frac{3d}{4 K_2 \epsilon_0 A}$$

$$\frac{1}{C} = \frac{d}{4 \epsilon_0 A} \left[\frac{1}{K_1} + \frac{3}{K_2} \right]$$

$$\frac{1}{C} = \frac{d}{4 \epsilon_0 A} \left[\frac{K_2 + 3 K_1}{K_1 K_2} \right]$$

$$\therefore C = \frac{4 \epsilon_0 A}{d} \left[\frac{K_1 K_2}{3 K_1 + K_2} \right]$$

Question63

A parallel plate capacitor has plate area 'A' and separation between plates is 'd'. It is charged to a potential difference of V_0 volt. The charging battery is then disconnected and plates are pulled apart three times the initial distance. The work done to increase the distance between the plates is ($\epsilon_0 =$ permittivity of free space)

MHT CET 2023 10th May Morning Shift

Options:

A. $\frac{3\epsilon_0 A V_0^2}{d}$

B. $\frac{\epsilon_0 A V_0^2}{2d}$

C. $\frac{\epsilon_0 A V_0^2}{3d}$

D. $\frac{\epsilon_0 A V_0^2}{d}$

Answer: D

Solution:

Let the initial capacitance be $C_0 = \frac{\epsilon_0 A}{d}$

Let the charge on the capacitor be $Q_{\text{initial}} = C_0 V_0$

Plate separation is increased by 3 times i.e., $d' = 3d$

$$C_{\text{final}} = \frac{\varepsilon_0 A}{3d} = \frac{1}{3} \left(\frac{\varepsilon_0 A}{d} \right) = \frac{C_0}{3}$$

Let Q_{final} be the final charge on the capacitor and V_{final} be the final potential on the capacitor.

$$\therefore Q_{\text{final}} = C_{\text{final}} V_{\text{final}} = \frac{1}{3} C_0 V_{\text{final}}$$

As the capacitor is isolated,

$$Q_{\text{final}} = Q_{\text{initial}},$$

$$C_0 V_0 = \frac{1}{3} C_0 V_{\text{final}}$$

$$\therefore V_{\text{final}} = 3 V_0$$

Work done = Final P.E - Initial P.E

$$= \frac{1}{2} C_{\text{final}} (V_{\text{final}})^2 - \frac{1}{2} C_0 (V_0)^2$$

$$= \frac{1}{2} \frac{C_0}{3} 9 V_0^2 - \frac{1}{2} C_0 V_0^2$$

$$= C_0 V_0^2 \left(\frac{3}{2} - \frac{1}{2} \right)$$

$$= C_0 V_0^2$$

$$= \frac{\varepsilon_0 A V_0^2}{d} \dots \left(\because C_0 = \frac{\varepsilon_0 A}{d} \right)$$

Question64

Two capacitors $C_1 = 3\mu\text{F}$ and $C_2 = 2\mu\text{F}$ are connected in series across d.c. source of 100 V. The ratio of the potential across C_2 to C_1 is

MHT CET 2023 10th May Morning Shift

Options:

A. 2 : 3

B. 3 : 2

C. 6 : 5

D. 5 : 6

Answer: B

Solution:

$$C_1 = 3\mu\text{F} \text{ and } C_2 = 2\mu\text{F}$$

$$\therefore C_{\text{series}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{6}{5}\mu\text{F}$$

$$\text{Also, } Q = CV$$

$$Q = C_{\text{series}} \times V$$

$$= \frac{6}{5} \times 100 = 120\mu\text{C}$$

Q will be the same across both the capacitors as they are in series.

\therefore Potential across capacitors,

$$V_1 = \frac{Q}{C_1} = \frac{120}{3} = 40 \text{ V}$$

$$V_2 = \frac{Q}{C_2} = \frac{120}{2} = 60 \text{ V}$$

$$\therefore V_2 : V_1 = 60 : 40 = 3 : 2$$

Question65

The mean electrical energy density between plates of a charged air capacitor is (where q = charge on capacitor, A = Area of capacitor plate)

MHT CET 2023 10th May Morning Shift

Options:

A. $\frac{q^2}{2\varepsilon_0 A^2}$

B. $\frac{q}{2\varepsilon_0 A^2}$

C. $\frac{q^2}{2\varepsilon_0 A}$

D. $\frac{\varepsilon_0 A}{q^2}$

Answer: A

Solution:



For a parallel plate capacitor, the energy density = $\frac{1}{2} E^2 \epsilon_0$

But $E = \frac{\sigma}{\epsilon_0}$

$$\begin{aligned} \therefore \text{Energy density} &= \frac{1}{2} \frac{\sigma^2}{\epsilon_0^2} \times \epsilon_0 \\ &= \frac{\sigma^2}{2\epsilon_0} \\ &= \frac{\left(\frac{q}{A}\right)^2}{2\epsilon_0} \quad \dots (\because \sigma = q/A) \\ &= \frac{q^2}{2 A^2 \cdot \epsilon_0} \end{aligned}$$

Question66

A parallel combination of two capacitors of capacities '2 C' and 'C' is connected across 5 V battery. When they are fully charged, the charges and energies stored in them be ' Q_1 ', ' Q_2 ' and ' E_1 ', ' E_2 ' respectively. Then $\frac{E_1 - E_2}{Q_1 - Q_2}$ in J/C is (capacity is in Farad, charge in Coulomb and energy in J)


MHT CET 2023 9th May Evening Shift

Options:

- A. $\frac{5}{4}$
- B. $\frac{4}{5}$
- C. $\frac{5}{2}$
- D. $\frac{2}{5}$

Answer: C

Solution:

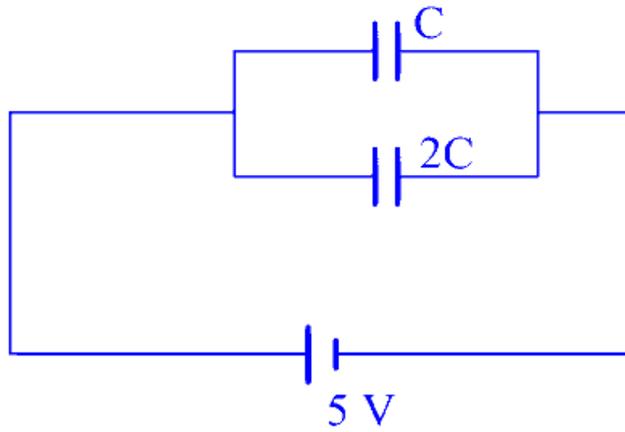

We know, $Q = C \cdot V$

$$\therefore Q_1 = 10C \text{ and } Q_2 = 5C$$

$$\text{Energy stored, } E = \frac{1}{2}CV^2$$


$$\therefore E_1 = \frac{1}{2}C_1 V^2 = \frac{1}{2} \times 2C \times 25 = 25 \text{ J}$$

$$\text{Similarly, } E_2 = \frac{1}{2}C_2 V^2 = \frac{1}{2} \times C \times 25 = 12.5 \text{ J}$$

$$\therefore \frac{E_1 - E_2}{Q_1 - Q_2} = \frac{12.5}{5} = \frac{5}{2}$$

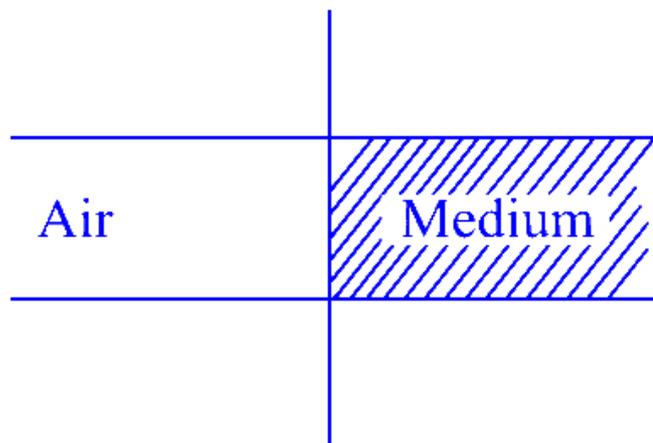Question 67

The capacitance of a parallel plate capacitor is $2.5 \mu\text{F}$. When it is half filled with a dielectric as shown in figure, its capacitance becomes $5 \mu\text{F}$. The dielectric constant of the dielectric is



MHT CET 2023 9th May Morning Shift

Options:

A. 7.5

B. 3

C. 4

D. 5

Answer: B

Solution:

$$\text{Given } C = \frac{\epsilon_0 A}{d} = 2.5 \mu\text{F}$$

When half filled with air,

$$C_1 = \frac{\epsilon_0 (A/2)}{d} = \frac{\epsilon_0 A}{2d} \dots\dots (\because \epsilon_r = 1)$$

When half filled with a dielectric,

$$C_2 = \frac{\epsilon_r \epsilon_0 (A/2)}{d} = \frac{\epsilon_r \epsilon_0 A}{2d}$$

From the figure, it can be seen that C_1 and C_2 are in parallel configuration.

$$\therefore C_{\text{eq}} = C_1 + C_2$$

$$\text{Given, } C_{\text{eq}} = 5\mu\text{F}$$

$$\Rightarrow 5\mu\text{F} = \frac{\epsilon_0 A}{2d} + \frac{\epsilon_r \epsilon_0 A}{2d}$$

$$5 = \frac{2.5}{2} + \epsilon_r \frac{2.5}{2}$$

$$\frac{3.75}{1.25} = \epsilon_r$$

$$\therefore \epsilon_r = 3$$

Question68

The ratio of potential difference that must be applied across parallel and series combination of two capacitors C_1 and C_2 with their capacitance in the ratio 1 : 2 so that energy stored in these two cases becomes same is

MHT CET 2023 9th May Morning Shift

Options:

A. $3 : \sqrt{2}$

B. $\sqrt{2} : 3$

C. $2 : 9$

D. $9 : 2$

Answer: B

Solution:

Given: $C_1 : C_2 = 1 : 2$

$$\therefore C_2 = 2C_1$$

$$C_P = C_1 + C_2 = C_1 + 2C_1 = 3C_1$$

$$C_S = \frac{C_1 C_2}{C_1 + C_2} = \frac{2C_1^2}{3C_1} = \frac{2}{3}C_1$$

Let V_P and V_S be the potentials applied across the parallel and series combinations respectively, then using $E = \frac{1}{2}CV^2$ we can write,

$$\frac{1}{2}C_P V_P^2 = \frac{1}{2}C_S V_S^2$$

$$\therefore \frac{V_P^2}{V_S^2} = \frac{C_S}{C_P}$$

$$\frac{V_P}{V_S} = \sqrt{\frac{\frac{2}{3}C_1}{3C_1}} = \frac{\sqrt{2}}{3}$$

Question69

The potential energy of charged parallel plate capacitor is v_0 . If a slab of dielectric constant K is inserted between the plates, then the new potential energy will be

MHT CET 2023 9th May Morning Shift

Options:

A. $\frac{v_0}{K}$



B. $v_0 K^2$

C. $\frac{v_0}{K^2}$

D. v_0^2

Answer: A

Solution:

We know, $v_0 = \frac{Q^2}{2C}$

On inserting the slab of dielectric constant k , the new capacitance $C' = KC$

\therefore New potential energy $v'_0 = \frac{Q^2}{2C'}$

$$v_0^1 = \frac{Q^2}{2KC} = \frac{v_0}{K}$$

Question 70

A parallel plate air capacitor has a uniform electric field 'E' in the space between the plates. Area of each plate is A and the distance between the plates is 'd'. The energy stored in the capacitor is [$\epsilon_0 =$ permittivity of free space)

MHT CET 2022 11th August Evening Shift

Options:

A. $2\epsilon_0 EAd$

B. $\frac{1}{2}\epsilon_0 E^2 Ad$

C. $\frac{\epsilon_0 E^2}{2Ad}$

D. $\frac{E^2 Ad}{2\epsilon_0}$

Answer: B

Solution:

The intensity of the electric field (E) between two plane parallel sheets of equal and opposite charges is given by $E = \frac{\sigma}{\epsilon_0}$

$\therefore \sigma = E\epsilon_0$ where $\sigma =$ surface density of charge $= \frac{Q}{A}$

\therefore Charge on either plate of the capacitor is $Q = \sigma A = \epsilon_0 EA$ and $C = \frac{\epsilon_0 A}{d}$

\therefore The energy stored in the capacitor is

$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{(\epsilon_0 EA)^2}{2 \cdot \frac{\epsilon_0 A}{d}} = \frac{\epsilon_0^2 A^2 E^2 \times d}{2\epsilon_0 A}$$

$$\therefore U = \frac{1}{2} \epsilon_0 E^2 Ad$$

Question 71

A parallel plate capacitor is charged and then disconnected from the charging battery. If the plates are now moved further apart by pulling them by means of insulating handles, then

MHT CET 2022 11th August Evening Shift

Options:

- A. the capacitance of the capacitor increases
- B. the charge on the capacitor decreases
- C. the voltage across the capacitor increases
- D. the energy stored in the capacitor decreases

Answer: C

Solution:

For a parallel plate capacitor, $C = \frac{\epsilon_0 A}{d}$

When the charging battery is disconnected and d is increased then

- (a) Q remains constant
- (b) $C \propto \frac{1}{d}$ hence if d is increased, C is decreased.



(c) $C = \frac{Q}{V}$ or $V = \frac{Q}{C}$ if C is decreased, V will increase

(d) $E = \frac{1}{2} \frac{Q^2}{C}$ if C is decreased, then E will increase

Thus (a), (b) and (d) are wrong. Only (c) is correct.

Question 72

The force between the plates of a parallel plate capacitor of capacitance ' C ' and distance of separation of the plates ' d ' with a potential difference ' V ' between the plates is

MHT CET 2022 11th August Evening Shift

Options:

A. $\frac{V^2 d}{C}$

B. $\frac{C^2 V^2}{d^2}$

C. $\frac{CV^2}{2d}$

D. $\frac{C^2 V^2}{2d^2}$

Answer: C

Solution:

The force of attraction between the plates of a parallel plate capacitor is

$$\begin{aligned} F &= \frac{\sigma^2 A}{2\epsilon_0} = \frac{Q^2}{A^2} \times \frac{A}{2\epsilon_0} \left(\because \sigma = \frac{Q}{A} \right) \\ &= \frac{Q^2}{2\epsilon_0 A} = \frac{C^2 V^2}{2\epsilon_0 A} \left(\because Q = CV \right) \\ \therefore F &= C \left[\frac{CV^2}{2\epsilon_0 A} \right] = \frac{\epsilon_0 A}{d} \times \frac{CV^2}{2\epsilon_0 A} \\ \therefore F &= \frac{1}{2} \frac{CV^2}{d} \end{aligned}$$

Question73

A battery is used to charge a parallel plate capacitor till the potential difference between the plates becomes equal to the e.m.f. of the battery. The ratio of the energy stored in the capacitor to the work done by the battery will be

MHT CET 2021 24th September Evening Shift

Options:

A. 2

B. $\frac{1}{2}$

C. 1

D. $\frac{1}{4}$

Answer: B

Solution:

Energy stored in the capacitor $U = \frac{1}{2}qV$

Work done by the battery $W = qV$

$$\therefore \frac{U}{W} = \frac{1}{2}$$

Question74

Capacitors of capacities C_1 , C_2 and C_3 are connected in series. If the combination is connected to a supply of 'V' volt, then potential difference across capacitor ' C_1 ' is

MHT CET 2021 24th September Evening Shift

Options:

A. $\frac{C_2C_3+C_1C_3+C_1C_2}{C_1C_2V}$

B. $\frac{C_2C_3+C_1C_3+C_1C_2}{C_1C_2C_3V}$

C. $\frac{C_2C_3V}{C_2C_3+C_1C_3+C_1C_2}$

D. $\frac{C_1C_2C_3V}{C_2C_3+C_1C_3+C_1C_2}$

Answer: C

Solution:

In series combination, the equivalent capacitance C is given by

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
$$\therefore \frac{1}{C} = \frac{C_2C_3 + C_1C_3 + C_1C_2}{C_1C_2C_3}$$
$$\therefore C = \frac{C_1C_2C_3}{C_2C_3 + C_1C_3 + C_1C_2}$$

Charge Q stored by the combinations is given by

$$Q = CV = \frac{C_1C_2C_3V}{C_2C_3+C_1C_3+C_1C_2}$$

Charge on each capacitor is same. Hence potential difference across C_1 is $V_1 = \frac{Q}{C_1}$

$$\therefore V_1 = \frac{C_2C_3V}{C_2C_3+C_1C_3+C_1C_2}$$

Question 75

The plates of a parallel plate capacitor of capacity ' C_1 ' are moved closer together until they are half their original separation. The new capacitance ' C_2 ' is

MHT CET 2021 24th September Morning Shift

Options:

A. $C_2 = \frac{C_1}{2}$

B. $C_2 = C_1$

C. $C_2 = 2C_1$

D. $C_2 = 3C_1$

Answer: C

Solution:

✔ Correct Answer: $C_2 = 2C_1$

✔ Explanation

For a parallel-plate capacitor:

$$C = \frac{\epsilon_0 A}{d}$$

Where

- A = plate area
 - d = separation between plates
-

✔ Given:

Plate separation is made half of its original value.

Initially:

$$C_1 = \frac{\epsilon_0 A}{d}$$

After halving distance:

$$C_2 = \frac{\epsilon_0 A}{d/2}$$

$$C_2 = 2 \cdot \frac{\epsilon_0 A}{d} = 2C_1$$

Question76

Two identical capacitors have the same capacitance 'C'. One of them is charged to potential ' V_1 ' and the other to V_2 . The negative ends of the capacitors are connected together. When positive ends are also connected, the decrease in energy of the combined system is



MHT CET 2021 24th September Morning Shift

Options:

A. $\frac{1}{4}C(V_1 - V_2)^2$

B. $\frac{1}{2}C(v_1^2 + v_2^2)$

C. $\frac{1}{2}C(V_1^2 - V_2^2)$

D. $\frac{1}{2}C(V_1 + V_2)^2$

Answer: A

Solution:

$$Q_1 = CV_1, Q_2 = CV_2, Q = Q_1 + Q_2 = 2CV$$

$$\therefore CV_1 + CV_2 = 2CV$$

$$\therefore V = \frac{V_1 + V_2}{2}$$

$$\begin{aligned} \text{Decrease in energy} &= \frac{1}{2}CV_1^2 + \frac{1}{2}CV_2^2 - \frac{1}{2}(2C)\left(\frac{V_1 + V_2}{2}\right)^2 \\ &= \frac{1}{2}C \left[V_1^2 + V_2^2 - 2\left(\frac{V_1 + V_2}{2}\right)^2 \right] \\ &= \frac{1}{2}C \left[V_1^2 + V_2^2 - \frac{1}{2}(V_1 + V_2)^2 \right] \\ &= \frac{1}{4}C \left[2V_1^2 + 2V_2^2 - (V_1 + V_2)^2 \right] \\ &= \frac{1}{4}C(V_1 - V_2)^2 \end{aligned}$$

Question 77

If the potential difference across a capacitor is increased from 5 V to 15 V, then the ratio of final energy to initial energy stored in the capacitor is

MHT CET 2021 23rd September Evening Shift

Options:

- A. 1 : 3
- B. 27 : 1
- C. 3 : 1
- D. 9 : 1

Answer: D

Solution:


$$\text{Initial energy } W_1 = \frac{1}{2}CV_1^2$$

$$\text{Final energy } W_2 = \frac{1}{2}CV_2^2$$

$$\therefore \frac{W_2}{W_1} = \left(\frac{V_2}{V_1}\right)^2 = \left(\frac{15}{5}\right)^2 = (3)^2 = 9$$

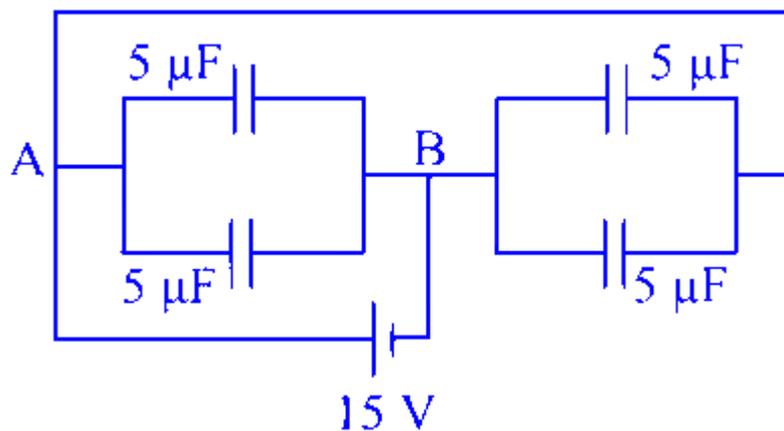Question 78

The charge on each capacitor when a voltage source of 15 V is connected in the circuit as shown, is



MHT CET 2021 23rd September Evening Shift

Options:

- A. 75 μC


B. $150 \mu\text{C}$

C. $30 \mu\text{C}$

D. $60 \mu\text{C}$

Answer: A

Solution:

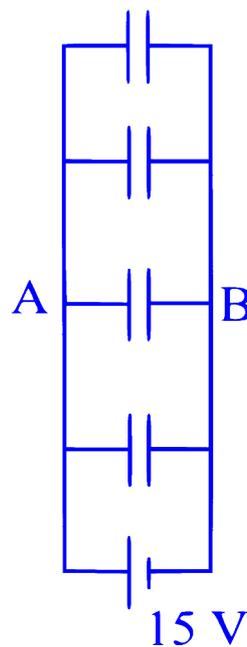

The circuit can be drawn as shown

Each capacitor has capacitance of $5\mu\text{F}$.

The capacitors are in parallel. Hence equivalent capacitance $C = 20\mu\text{F}$

The charge stored by the combination

$$Q = CV = 20 \times 15 = 300\mu\text{C}$$


\therefore The charge on each capacitor is

$$\frac{300}{4} = 75\mu\text{C}$$

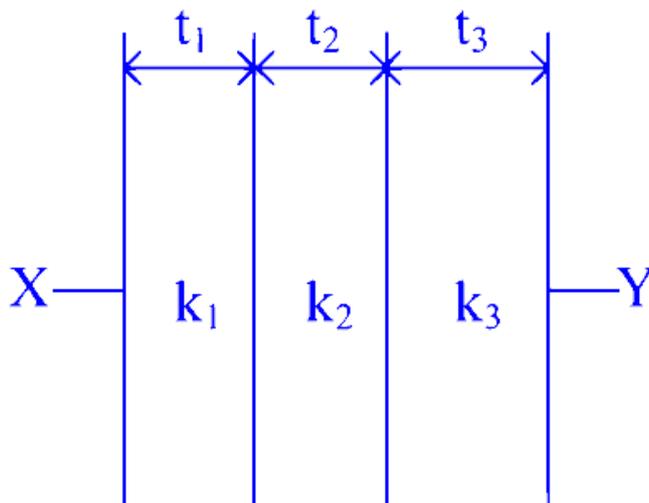Question79



Two parallel plates with dielectric placed between the plates are as shown in figure. The resultant capacity of capacitor will be [A = area of plate. t_1, t_2 and t_3 are thickness of dielectric slabs, k_1, k_2 and k_3 are dielectric constants.



MHT CET 2021 23th September Morning Shift

Options:

A. $\frac{A\epsilon_0}{\left[\frac{t_1+t_2+t_3}{k_1+k_2+k_3}\right]}$

B. $\frac{A\epsilon_0(k_1k_2k_3)}{t_1t_2t_3}$

C. $A\epsilon_0 \left[\frac{k_1}{t_1} + \frac{k_2}{t_2} + \frac{k_3}{t_3} \right]$

D. $\frac{A\epsilon_0}{\left[\frac{t_1}{k_1} + \frac{t_2}{k_2} + \frac{t_3}{k_3}\right]}$

Answer: C

Solution:



✔ Correct Answer: C (the expression with $A\epsilon_0 \left[\frac{k_1}{t_1} + \frac{k_2}{t_2} + \frac{k_3}{t_3} \right]$)

✔ Explanation

In this setup, three dielectric slabs of dielectric constants

$$k_1, k_2, k_3$$

and thicknesses

$$t_1, t_2, t_3$$

are placed between parallel plates side by side, fully filling the area between plates.

🔑 Key idea:

When dielectric slabs are placed *side-by-side*, each forms a separate capacitor in parallel.

So the effective capacitance is:

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

Each capacitor has capacitance:

$$C_i = \frac{\epsilon_0 k_i A}{t_i}$$

Therefore:

$$C_{\text{eq}} = \frac{\epsilon_0 k_1 A}{t_1} + \frac{\epsilon_0 k_2 A}{t_2} + \frac{\epsilon_0 k_3 A}{t_3}$$

Factor out $A\epsilon_0$:

$$C_{\text{eq}} = A\epsilon_0 \left(\frac{k_1}{t_1} + \frac{k_2}{t_2} + \frac{k_3}{t_3} \right)$$

This matches Option C.

Question80

In parallel plate capacitor, electric field between the plates is ' E '. If the charge on the plates is ' Q ' then the force on each plate is

MHT CET 2021 22th September Evening Shift

Options:

A. QE

B. $\frac{QE^2}{2}$

C. QE^2

D. $\frac{QE}{2}$

Answer: D

Solution:

The field produced by charge on each plate is $\frac{E}{2}$.

Hence force on each plate is given by

$$F = Q \times (\text{Field produced by the other plate})$$

$$= \frac{QE}{2}$$

Question81

If the charge on the capacitor is increased by 2 C the energy stored in it increased by 21%. Total original charge on the capacitor is

MHT CET 2021 22th September Morning Shift

Options:

A. 10 C

B. 5 C



C. 20 C

D. 15 C

Answer: C

Solution:

Let's start by recalling the formula for the energy stored in a capacitor. The energy U stored in a capacitor with capacitance C and charge Q is given by:

$$U = \frac{Q^2}{2C}$$

Since we do not know the capacitance C , we will manipulate the formula using given information. If the charge on the capacitor is increased by 2 C, the new charge Q' becomes $Q + 2$. Thus, the new energy U' becomes:

$$U' = \frac{(Q+2)^2}{2C}$$

We are given that this new energy is 21% greater than the original energy. Therefore, we can write:

$$U' = 1.21U$$

Substituting the expressions for U and U' , we get:

$$\frac{(Q+2)^2}{2C} = 1.21 \cdot \frac{Q^2}{2C}$$

Since C is a common factor in the numerator and denominator, it cancels out. Hence, we can simplify to:

$$(Q + 2)^2 = 1.21Q^2$$

Expanding and rearranging the equation, we obtain:

$$Q^2 + 4Q + 4 = 1.21Q^2$$

$$0.21Q^2 - 4Q - 4 = 0$$

Solving this quadratic equation using the quadratic formula, where $a = 0.21$, $b = -4$, and $c = -4$, we get:

$$Q = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

Substitute the values of a , b , and c :

$$Q = \frac{4 \pm \sqrt{(-4)^2 - 4 \cdot 0.21 \cdot (-4)}}{2 \cdot 0.21}$$

$$Q = \frac{4 \pm \sqrt{16 + 3.36}}{0.42}$$

$$Q = \frac{4 \pm \sqrt{19.36}}{0.42}$$

$$Q = \frac{4 \pm 4.4}{0.42}$$



Therefore, we have two possible solutions for Q :

$$Q = \frac{4+4.4}{0.42} = 20$$

$$Q = \frac{4-4.4}{0.42} = -0.95 \text{ (not practical)}$$

Since a negative charge is not practical in this context, the original charge on the capacitor is:

Option C: 20 C

Question82

When the battery across the plates of a charged condenser is disconnected and a dielectric slab is introduced between its plates then the energy stored

MHT CET 2021 22th September Morning Shift

Options:

- A. becomes infinity
- B. does not change
- C. increases
- D. decreases

Answer: D

Solution:

To understand what happens to the energy stored in a charged capacitor when a dielectric slab is introduced between its plates (after disconnecting the battery), let's break down the concepts involved.

A capacitor stores energy in the electric field between its plates. The energy stored in a capacitor is given by the formula:

$$U = \frac{1}{2} \frac{Q^2}{C}$$

where:

- U is the energy stored.
- Q is the charge on the capacitor.
- C is the capacitance of the capacitor.

The capacitance of a capacitor is given by:

$$C = \frac{\epsilon_0 A}{d}$$

where:

- ϵ_0 is the permittivity of free space.
- A is the area of the plates.
- d is the distance between the plates.

When a dielectric slab with dielectric constant κ is introduced between the plates, the new capacitance C' becomes:

$$C' = \kappa C$$

Since the battery is disconnected, the charge Q on the capacitor remains constant. Let's understand the impact of the increased capacitance (due to the dielectric slab) on the stored energy.

The new energy stored U' can be expressed as:

$$U' = \frac{1}{2} \frac{Q^2}{C'}$$

Substituting $C' = \kappa C$, we get:

$$U' = \frac{1}{2} \frac{Q^2}{\kappa C}$$

This equation shows that:

$$U' = \frac{U}{\kappa}$$

We know that $\kappa > 1$, therefore:

$$U' < U$$

This indicates that the energy stored in the capacitor decreases when a dielectric slab is introduced between its plates (after disconnecting the battery).


So, the correct answer is:

Option D: decreases

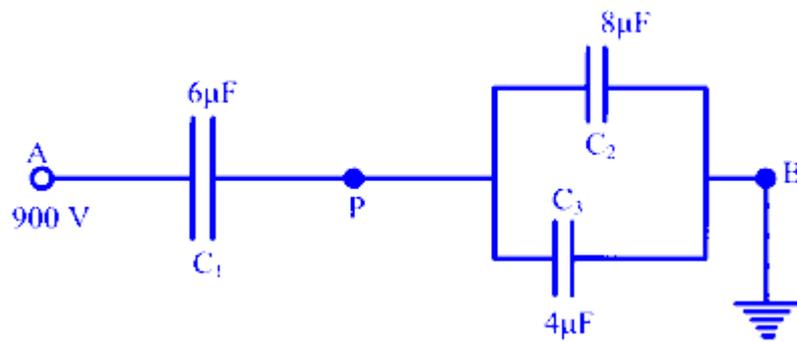Question83

In the given figure potential at point 'A' is 900 volt and point 'B' is earthed. What will be the potential at point 'P' ?





MHT CET 2021 22th September Morning Shift

Options:

- A. 900 V
- B. 100 V
- C. 300 V
- D. 600 V

Answer: C

Solution:

Capacitors C_2 and C_3 are in parallel. Hence their equivalent capacitance

$$C_4 = C_2 + C_3 = 8 + 4 = 12\mu\text{F}$$

C_4 and C_1 are in series.

$$\text{Their equivalent capacitance } C = \frac{12 \times 6}{12 + 6} = \frac{72}{18} = 4\mu\text{F}$$

Charge stored by the combination

$$\begin{aligned} q &= CV = 4 \times 900 \\ &= 3600\mu\text{C} \end{aligned}$$

In the series combination, charge is same on each capacitor.

$$\therefore \text{Charge on } C_1 = 3600\mu\text{C}$$

$$P, D, \text{ across } C_1 \text{ is } V_1 = \frac{q}{C_1} = \frac{3600}{6} = 600 \text{ V}$$

$$\therefore V_A - V_P = 600 \quad \therefore 900 - V_P = 600$$

$$\therefore V_P = 300 \text{ V}$$

Question84

Two identical parallel plate air capacitors are connected in series to a battery of emf 'V'. If one of the capacitor is inserted in liquid of dielectric constant 'K' then, potential difference of the other capacitor will become

MHT CET 2021 21th September Evening Shift

Options:

A. $\frac{K-1}{KV}$

B. $\frac{K+1}{KV}$

C. $\left(\frac{KV}{K+1}\right)$

D. $\frac{KV}{K-1}$

Answer: C

Solution:

Let the capacitance of capacitors are C initially.

So, afterward $C_1 = kC$ and $C_2 = C$

p.d. across capacitor C_2 is

$$V_2 = \frac{C_2 V}{C_1 + C_2} = \frac{kCV}{C + kC} = \frac{kV}{k+1}$$

Question85

A condenser of capacity ' C_1 ' is charged to potential ' V_1 ' and then disconnected. Uncharged capacitor of capacity ' C_2 ' is connected in parallel with ' C_1 '. The resultant potential ' V_2 ' is

MHT CET 2021 21th September Evening Shift

Options:

A. $\frac{V_1 C_2}{C_1}$

B. $\frac{C_2}{C_1 + C_2}$

C. $\frac{C_1 V_1}{C_2}$

D. $\frac{C_1 V_1}{C_1 + C_2}$

Answer: D

Solution:

The charge stored by the charged condenser is


$$Q = C_1 V_1$$

When the uncharged condenser is connected in parallel, the effective capacitance becomes $(C_1 + C_2)$

$$\text{Hence the potential } V_2 = \frac{Q}{C_1 + C_2} = \frac{C_1 V_1}{C_1 + C_2}$$

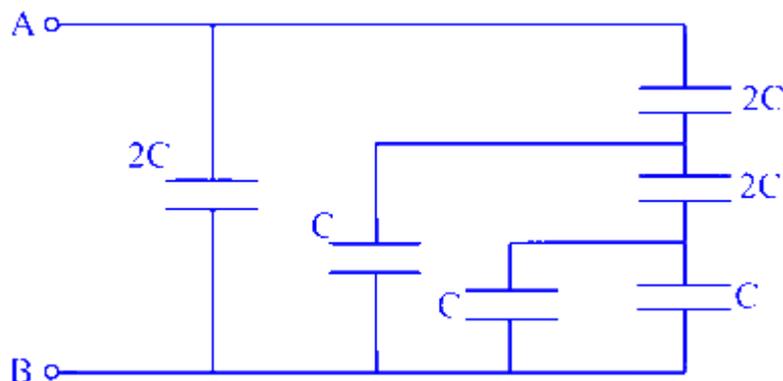Question 86

The resultant capacity between points A and B in the given circuit is



MHT CET 2021 21th September Morning Shift



Options:

A. C


B. $\frac{C}{3}$

C. $3C$

D. $2C$

Answer: C

Solution:

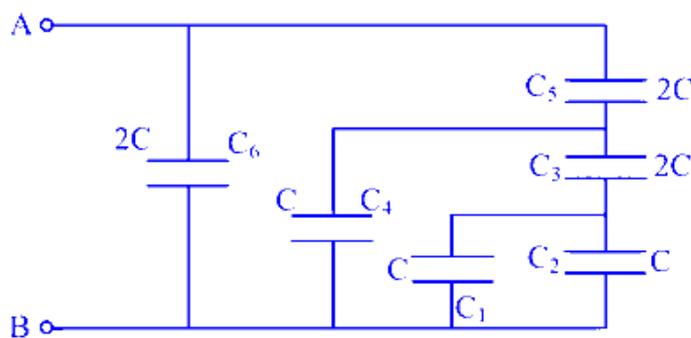

C_1 and C_2 are in parallel

Their equivalent capacitance $C_7 = 2C$

C_7 and C_3 are in series

Their equivalent capacitance is $C_8 = C$

C_8 and C_4 are in parallel

Their equivalent capacitance is $C_9 = 2C$

C_9 and C_5 are in series. Their equivalent capacitance $C_{10} = C$

C_{10} and C_6 are in parallel. Their equivalent capacitance is $3C$.

Hence equivalent capacitance between A and B is $3C$.

Question 87

An air filled parallel plate capacitor has a capacity 2 pF. The separation of the plates is doubled and the interspace between the plates is filled with dielectric material, then the capacity is increased to 6 pF. The dielectric constant of the material is



MHT CET 2021 21th September Morning Shift

Options:

A. 3

B. 6

C. 2

D. 4

Answer: B

Solution:

$$C = \frac{KA\epsilon_0}{d}$$


$$\therefore \frac{C_2}{C_1} = \frac{k_2}{k_1} \cdot \frac{d_1}{d_2}$$

$$\therefore \frac{6}{2} = \frac{k_2}{1} \cdot \frac{1}{2}$$

$$\therefore k_2 = 6$$

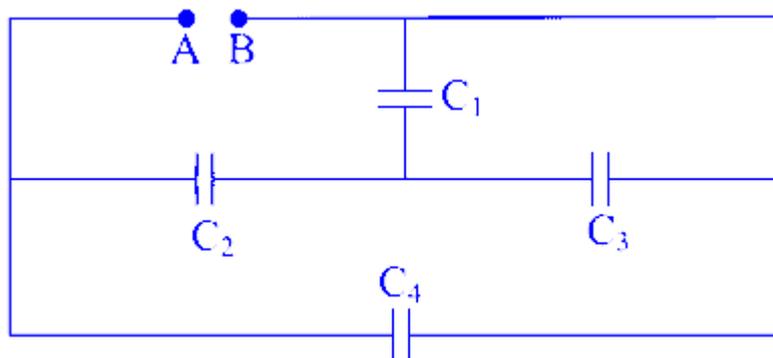Question88

In the arrangement of the capacitors as shown in figure, each capacitor is of $6 \mu\text{F}$, then equivalent capacity between points A and B is



MHT CET 2021 20th September Evening Shift

Options:

A. $12 \mu\text{F}$


B. $6 \mu\text{F}$

C. $4 \mu\text{F}$

D. $10 \mu\text{F}$

Answer: D

Solution:

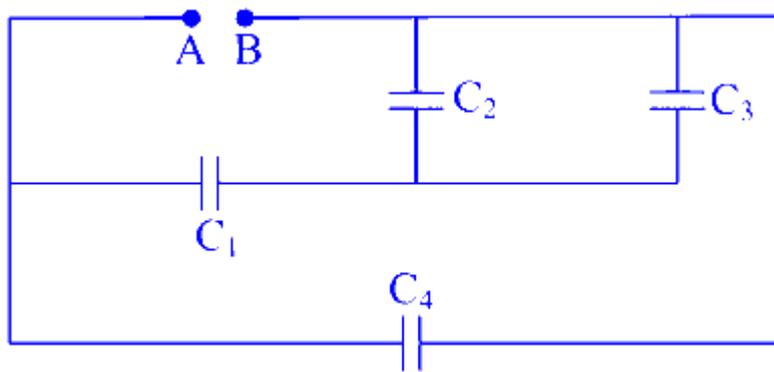

$$C_1 = C_2 = C_3 = C_4 = 6 \mu\text{F}$$

C_2 and C_3 are in parallel.

Hence their equivalent capacitance, $C_5 = 2 \times 6 = 12 \mu\text{F}$

C_5 and C_1 in series.

Hence their equivalent capacitance C_6 is given by

$$\frac{1}{C_6} = \frac{1}{12} + \frac{1}{6} = \frac{3}{12} = \frac{1}{4}$$

$$\therefore C_6 = 4 \mu\text{F}$$

C_6 and C_4 are in parallel.

Hence their equivalent capacitance is $C = 4 + 6 = 10 \mu\text{F}$

Question89

A parallel plate air capacitor is charged upto 100 V. A plate 2 mm thick is inserted between the plates. Then to maintain the same potential difference, the distance between the plates is increased by 1.6 mm. The dielectric constant of the thick plate is

MHT CET 2021 20th September Evening Shift

Options:

- A. 4
- B. 5
- C. 2
- D. 3

Answer: B

Solution:

If d is the initial distance between the plates then capacitance is given by $C = \frac{kA\epsilon_0}{d}$

When a plate of thickness $t = 2$ mm is inserted between the plates the capacitance,

$$C_1 = \frac{kA\epsilon_0}{(d-t+\frac{t}{k})}$$

If distance between the plates is increased by $x = 1.6$ mm

$$\text{Capacitance becomes, } C_2 = \frac{kA\epsilon_0}{(d+x-t+\frac{t}{k})} \quad \text{But } C_2 = C$$

$$\therefore d + x - t + \frac{t}{k} = d$$

$$\therefore t - x = \frac{t}{k}$$

$$\therefore 2 - 1.6 = \frac{2}{k}$$

$$\therefore 0.4 = \frac{2}{k} \quad \therefore k = 5$$

Question90



A parallel plate capacitor filled with oil of a dielectric constant 3 between the plates has capacitance 'C'. If the oil is removed, then the capacitance of the capacitor will be

MHT CET 2021 20th September Morning Shift

Options:

A. $\frac{C}{\sqrt{3}}$

B. $3C$

C. $\sqrt{3}C$

D. $\frac{C}{3}$

Answer: D

Solution:

✔ Correct Answer: D. $\frac{C}{3}$

✔ Explanation \

A parallel-plate capacitor completely filled with a dielectric of dielectric constant $K = 3$ has capacitance:

$$C = KC_0$$

Where C_0 is the capacitance **without** dielectric.

Given:

$$C = 3C_0$$

We are asked to find the capacitance after the oil (dielectric) is removed, which means the capacitor returns to its original value:

$$C_0 = \frac{C}{3}$$

Hence:

✔ New capacitance = $\frac{C}{3}$

Question91

Two capacitors of capacities $2\mu\text{ F}$ and $4\mu\text{ F}$ are connected in parallel. A third capacitor of $6\mu\text{ F}$ capacity is connected in series with this combination. A battery of 12 V is connected across this combination. The charge on $2\mu\text{ F}$ capacitor is

MHT CET 2020 19th October Evening Shift


Options:

- A. $12\mu\text{C}$
- B. $11\mu\text{C}$
- C. $14\mu\text{C}$
- D. $16\mu\text{C}$

Answer: A

Solution:

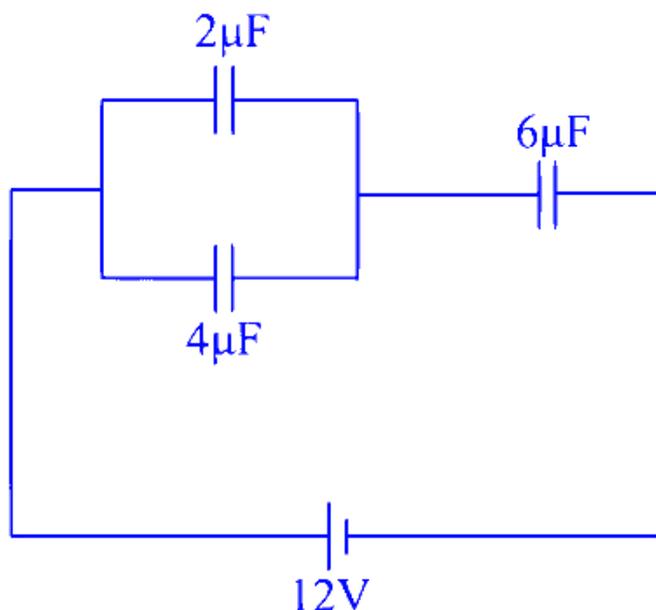
The circuit diagram of given situation is as shown below



The equivalent capacitance of $2\mu\text{ F}$ and $4\mu\text{ F}$ capacitors connected in parallel is

$$C_{\text{eq}} = 2 + 4 = 6\mu\text{F}$$

The circuit now becomes

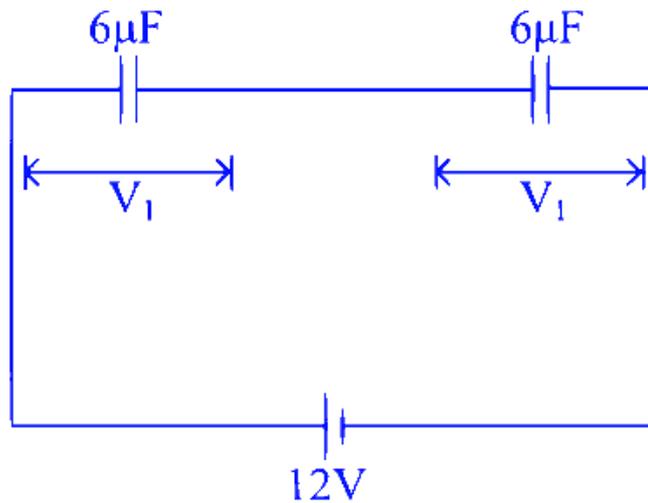

As, both the capacitors are of same capacitance, so potential of 12 V is equally divided in them. i.e.


$$V_1 = V_2 = 6\text{V}$$

In parallel combination, potential remains same.

$$\therefore \text{Charge on } 2\mu\text{F}, Q = 2 \times V_1 = 2 \times 6 = 12\mu\text{C}$$

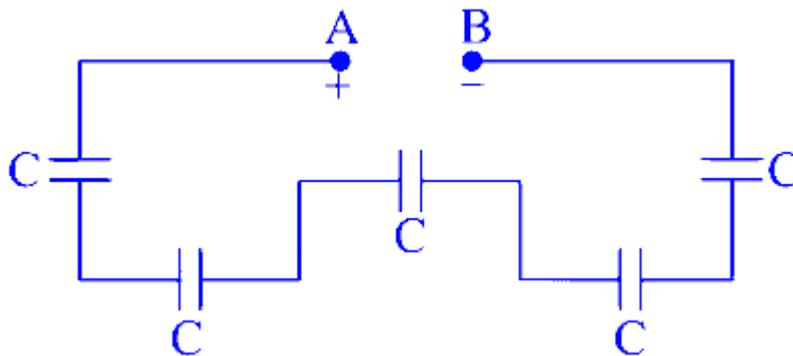Question92

Five capacitors each of capacity C are connected as shown in figure. If their resultant capacity is $2\mu\text{F}$, then the capacity of each condenser is



MHT CET 2020 16th October Evening Shift

Options:

A. $5 \mu\text{F}$

B. $2 \mu\text{F}$

C. $2.5 \mu\text{F}$

D. $10 \mu\text{F}$

Answer: D

Solution:

Given that the resultant capacitance $C_{\text{eq}} = 2 \mu\text{F}$:

The capacitors are connected in series. Therefore, the formula for the equivalent capacitance of capacitors in series is:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C}$$

This simplifies to:

$$\frac{1}{C_{\text{eq}}} = \frac{5}{C}$$

Substitute the given equivalent capacitance:

$$\frac{1}{2 \mu\text{F}} = \frac{5}{C}$$

Solving for C :

$$C = 10 \mu\text{F}$$

Therefore, each capacitor has a capacitance of $10 \mu\text{F}$.

Question93

The capacitance of a parallel plate capacitor with air as medium is $3 \mu\text{F}$. With the introduction of a dielectric medium between the plates, the capacitance becomes $15 \mu\text{F}$. The permittivity of the medium in SI unit is $[\epsilon_0 = 8.85 \times 10^{-12} \text{SI unit}]$

MHT CET 2020 16th October Morning Shift

Options:

A. 8.845×10^{-11}

B. 0.4425×10^{-10}

C. 15

D. 5

Answer: B

Solution:

The capacitance of a parallel plate capacitor with air is

$$C = \frac{\epsilon_0 A}{d} \quad \dots (i)$$

where, ϵ_0 = permittivity of free space or air. The capacitance with a dielectric medium between the plates is

$$C' = \frac{\epsilon_m A}{d} \quad \dots (ii)$$

where, ϵ_m = permittivity of medium.

Here, $C' = 15\mu\text{F}$, $C = 3\mu\text{F}$

and $\epsilon_0 = 8.85 \times 10^{-12}$ SI unit

From Eqs. (i) and (ii), we get

$$\begin{aligned} \frac{C'}{C} &= \frac{\epsilon_m A}{d} \times \frac{d}{\epsilon_0 A} = \frac{\epsilon_m}{\epsilon_0} \\ \epsilon_m &= \frac{\epsilon_0 C'}{C} = \frac{8.85 \times 10^{-12} \times 15 \times 10^{-6}}{3 \times 10^{-6}} \\ &= 44.25 \times 10^{-12} \text{ SI unit} \\ &= 0.4425 \times 10^{-10} \text{ SI unit} \end{aligned}$$

Question94

In a parallel plate air capacitor the distance between plates is reduced to one fourth and the space between them is filled with a dielectric medium of constant 2 . If the initial capacity of the capacitor is $4\mu\text{ F}$. then its new capacity is

MHT CET 2019 2nd May Evening Shift

Options:

A. $32\mu\text{ F}$

B. $18\mu\text{ F}$

C. $8\mu\text{ F}$

D. $44\mu\text{ F}$

Answer: A

Solution:

The capacitance of a parallel plate air capacitor is given by

$$C_0 = \frac{\epsilon_0 A}{d} \quad \dots \text{ (i)}$$

where, ϵ_0 = permittivity of the medium,

A = area of plates

and d = distance between the plates

When the distance between plates is reduced and a dielectric slab is introduced, then the capacitance becomes

$$C = \frac{K\epsilon_0 A}{d_1} \quad \dots \text{ (ii)}$$

Where, K = dielectric constant of medium.

Here, $K = 2$, $d_1 = \frac{d}{4}$ and $C_0 = 4\mu\text{ F} = 4 \times 10^{-6}\text{ F}$

From Eq. (ii), we get

$$\begin{aligned} C &= 4 \left(\frac{K\epsilon_0 A}{d_1} \right) = 4K \left(\frac{\epsilon_0 A}{d} \right) \\ &= 4KC_0 \quad \dots \text{ (iii) [from Eq. (i)]} \end{aligned}$$

Substituting given values in Eq. (iii), we get

$$C = 4 \times 2 \times 4 = 32\mu\text{ F}$$

Question95

Which of the following combinations of 7 identical capacitors each of $2\mu\text{ F}$ gives a resultant capacitance of $10/11\mu\text{ F}$?



MHT CET 2019 2nd May Morning Shift

Options:

- A. 3 in parallel and 4 in series
- B. 2 in parallel and 5 in series
- C. 4 in parallel and 3 in series
- D. 5 in parallel and 2 in series

Answer: D

Solution:

For n capacitors i.e., C_1, C_2, \dots, C_n their equivalent capacitance, when connected in


(a) series is given as, $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

and

(b) parallel is given as, $C_p = C_1 + C_2 + \dots$

In the given problem, we will check the net capacitance in each option and compare it with the desired capacitance mentioned in it.

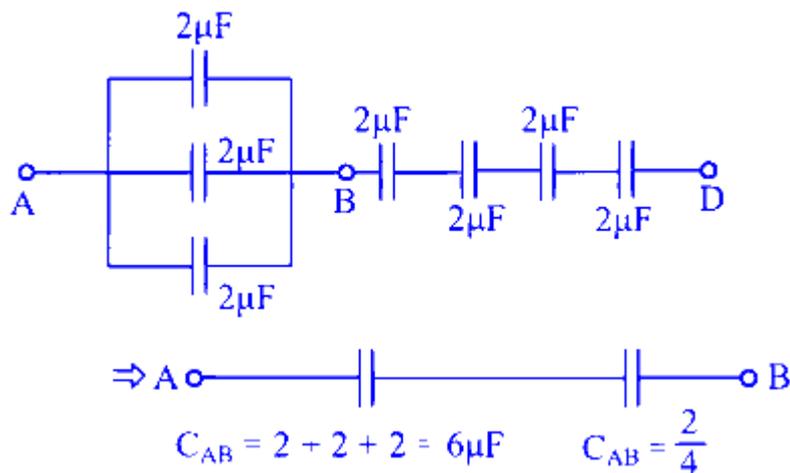
(a) 3 capacitors are in parallel and 4 capacitors are connect in series, i.e.,



where, C_{AB} is the equivalent capacitance of parallel branches between A and B and C_{BD} is equivalent capacitance of series capacitors between B and D . So, equivalent capacitance.

$$C_{eq} = \frac{C_{AB} \cdot C_{BD}}{C_{AB} + C_{BD}} = \frac{6 \times \frac{2}{4}}{6 + \frac{2}{4}} = \frac{6}{13} \mu\text{F}$$

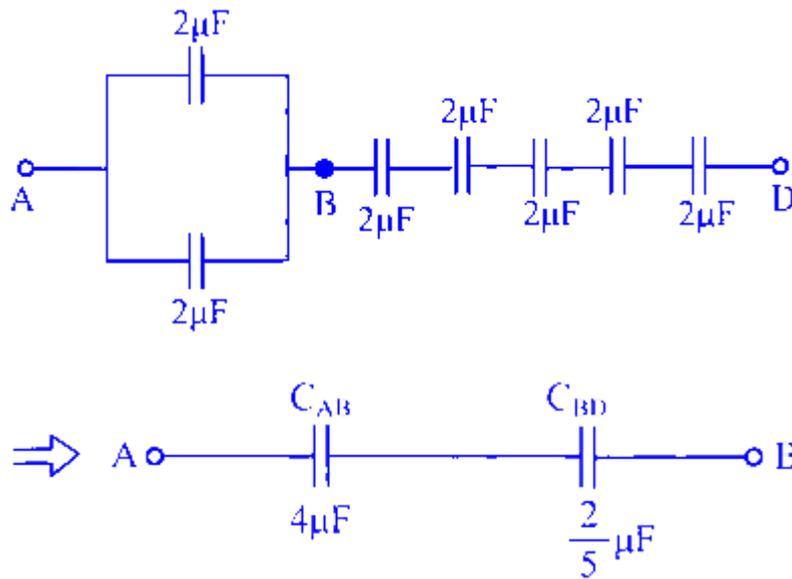
Similarly, (b) 2 capacitors are in parallel and 5 capacitors are connect in series i.e.,



So, equivalent capacitance,

$$C_{eq} = \frac{4 \times \frac{2}{5}}{4 + \frac{2}{5}} = \frac{4}{11} \mu F$$

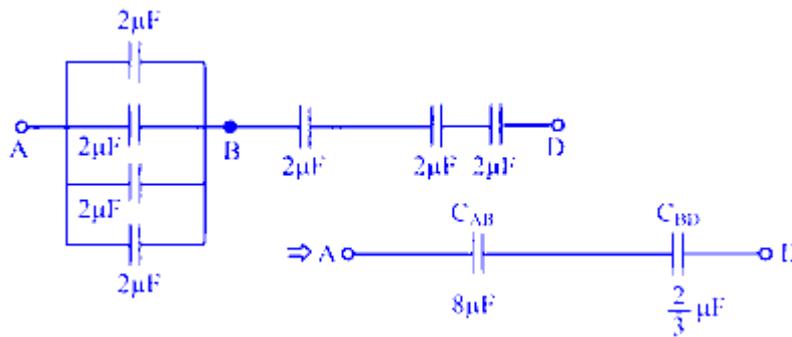
(c) 4 capacitors are in parallel and 3 capacitors are connect in series i.e.,



So, equivalent capacitance,

$$C_{eq} = \frac{8 \times \frac{2}{3}}{8 + \frac{2}{3}} = \frac{16}{26} = \frac{8}{13} \mu F$$

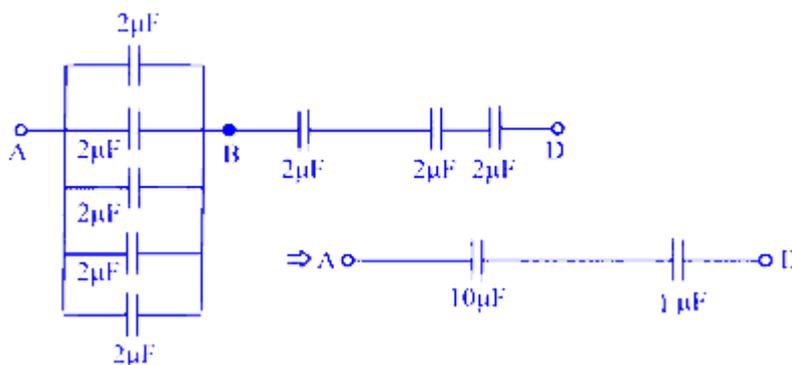(d) 5 capacitors are in parallel and 2 capacitors are connect in series i.e.,



So, equivalent capacitance,

$$C_{eq} = \frac{10 \times 1}{10 + 1} = \frac{10}{11} \mu F$$

So, the correct option is (d).