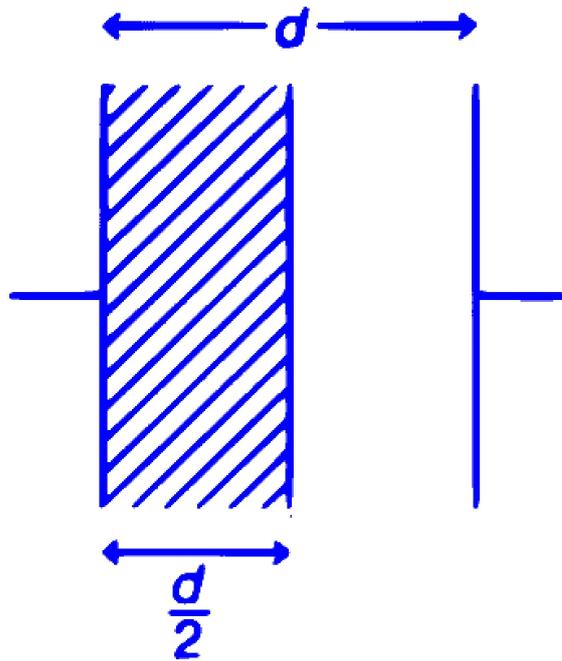


Capacitor

Question1

As shown in the figure, a dielectric of constant K is placed between the plates of a parallel plate capacitor and is charged to a potential V using a battery. If the dielectric is pulled out after disconnecting the battery from the capacitor, the final potential difference across the plates of the capacitor is



TG EAPCET 2025 (Online) 2nd May Morning Shift

Options:

A.

$$\left(1 + \frac{1}{K}\right)2V$$

B.

$$2KV$$



C.

$$\frac{2V}{\left(1 + \frac{1}{K}\right)}$$

D.

$$\frac{V}{2} \left(1 + \frac{1}{K}\right)$$

Answer: C

Solution:

When dielectric is filled, we model this as two capacitors in series.

For capacitor with dielectric,

$$C_1 = \frac{\epsilon_0 A}{\frac{d}{2K}} = \frac{2KA\epsilon_0}{d}$$

For capacitor without dielectric,

$$C_2 = \frac{\epsilon_0 A}{\frac{d}{2}} = \frac{2\epsilon_0 A}{d}$$

For series combination,

$$C = \frac{C_1 \times C_2}{C_1 + C_2}$$
$$C = \frac{\frac{2KA\epsilon_0}{d} \times \frac{2\epsilon_0 A}{d}}{\frac{2KA\epsilon_0}{d} + \frac{2\epsilon_0 A}{d}}$$
$$C = \frac{2\epsilon_0 A}{d \left(1 + \frac{1}{K}\right)}$$

Charge stored initially,

$$Q = CV = \frac{2\epsilon_0 A}{d \left(1 + \frac{1}{K}\right)} \cdot V$$

Now, the entire capacitor just vacuum,

$$C' = \frac{\epsilon_0 A}{d}$$

So, final voltage, $V' = \frac{Q}{C'}$

$$= \frac{2\epsilon_0 AV}{d \left(1 + \frac{1}{K}\right)} \times \frac{d}{\epsilon_0 A}$$
$$V' = \frac{2V}{\left(1 + \frac{1}{K}\right)}$$



Question2

A capacitor of capacitance C is charged to a potential V and disconnected from the battery. Now, if the space between the plates is completely filled with a substance of dielectric constant K , the final charge and the final potential on the capacitor are respectively.

TG EAPCET 2024 (Online) 11th May Morning Shift

Options:

A. KCV and $\frac{V}{K}$

B. CV and $\frac{V}{K}$

C. $\frac{CV}{K}$ and KV

D. $\frac{CV}{K}$ and $\frac{V}{K}$

Answer: B

Solution:

When a capacitor of capacitance C is charged to a potential V , then initial charge on capacitor is,

$$Q = CV$$

When a dielectric material with dielectric constant K is inserted between the plates then new capacitance,

$$C' = KC$$

Charge on the capacitor remains the same because it is disconnected from the battery.

$$Q' = Q = CV$$

Final potential on the capacitor,

$$V' = \frac{Q'}{C'} = \frac{CV}{KC}$$

$$V' = \frac{V}{K}$$

Question3

For the displacement current through the plates of a parallel plate capacitor of capacitance $30\mu\text{ F}$ to be $150\mu\text{ A}$, the potential difference



across the plates of the capacitor has to vary at the rate of

TG EAPCET 2024 (Online) 11th May Morning Shift

Options:

A. 10Vs^{-1}

B. 5Vs^{-1}

C. 15Vs^{-1}

D. 20Vs^{-1}

Answer: B

Solution:

Given,

Current, $i_C = 150\mu\text{ A}$

Capacitance of capacitor, $C = 30\mu\text{ F}$

Rate of change of potential, $\frac{dV}{dt} = ?$

We know that,

$$C = \frac{q}{V}$$

$$q = CV$$

Differentiate the Eq. (i) w.r.t. to time t , we have

$$\frac{dq}{dt} = C \frac{dV}{dt}$$

As we know the rate to change of charge per unit of time is equal to the current, then

$$i_C = C \cdot \frac{dV}{dt}$$

Putting the value,

$$150 \times 10^{-6} = 30 \times 10^{-6} \times \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{150}{30}$$

$$\frac{dV}{dt} = 5\text{Vs}^{-1}$$



Question4

A capacitor of capacitance $(4.0 \pm 0.2)\mu\text{F}$ is charged to a potential of $(10.0 \pm 0.1)\text{V}$. The charge on the capacitor is

TG EAPCET 2024 (Online) 10th May Evening Shift

Options:

A. $2.5\mu\text{C} \pm 3\%$

B. $2.5\mu\text{C} \pm 6\%$

C. $40\mu\text{C} \pm 6\%$

D. $2.5\mu\text{C} \pm 3\%$

Answer: C

Solution:

A capacitor has a capacitance of $(4.0 \pm 0.2)\mu\text{F}$ and is charged to a potential of $(10.0 \pm 0.1)\text{V}$.

Given:

Capacitance, $C = (4.0 \pm 0.2)\mu\text{F}$

Voltage, $V = (10.0 \pm 0.1)\text{V}$

The charge Q on the capacitor can be calculated using the formula:

$$Q = C \times V$$

So, the absolute charge value is:

$$Q = 4.0\mu\text{F} \times 10.0\text{V} = 40\mu\text{C}$$

To find the error in the charge, we use the formula for the combined relative error:

$$\frac{\Delta Q}{Q} = \frac{\Delta C}{C} + \frac{\Delta V}{V}$$

Substitute the given values:

$$\frac{\Delta Q}{Q} = \left(\frac{0.2}{4.0}\right) + \left(\frac{0.1}{10.0}\right) = 0.05 + 0.01 = 0.06$$

Therefore, the percentage error in the charge Q is:

$$\frac{\Delta Q}{Q} \times 100 = 0.06 \times 100\% = 6\%$$

The final charge on the capacitor, including the percentage error, is:

$$Q = (40 \mu\text{C} \pm 6\%)$$

Question5

Two capacitors of capacitances $1 \mu\text{F}$ and $2 \mu\text{F}$ can separately withstand potentials of 6 kV and 4 kV respectively. The total potential, they together can withstand when they are connected in series is

TG EAPCET 2024 (Online) 10th May Evening Shift

Options:


- A. 9 kV
- B. 4 kV
- C. 6 kV
- D. 2 kV

Answer: A

Solution:

Capacitor, $C_1 = 1 \mu\text{F}$

$C_2 = 2 \mu\text{F}$

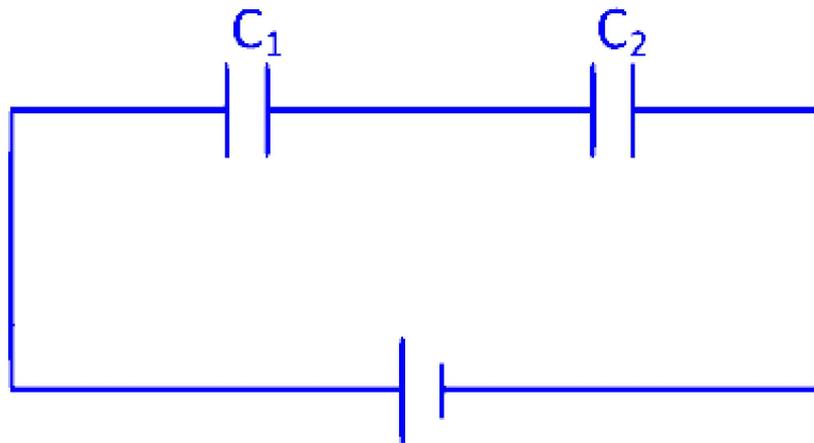

According to question, maximum potential with stand by C_1 is 6 kV .

$$\Rightarrow V_{1 \max} = \frac{Q_{\max}}{C_1}$$



$$Q_{\max} = C_1 V_{1\max}$$

$$\Rightarrow 1 \times 10^{-6} \times 6 \times 10^3$$

$$Q_{\max} = 6 \times 10^{-3}$$

On first capacitor

When C_1 and C_2 are connected in series, the charge on each capacitor is equal and is equal to the maximum charge the combination can withstand.

$$\text{Since } C_1 V_{1\max} < C_2 V_{2\max}$$

The resultant capacitance of combination is

$$C_R = \frac{C_2 C_1}{C_1 + C_2} = \frac{2 \times 1}{2 + 1}$$

$$C_R = \frac{2}{3} \times 10^{-6} \text{ F}$$

$$V_{\max} = \frac{Q_{\max}}{C_R} = \frac{6 \times 10^{-3}}{\frac{2}{3} \times 10^{-6}}$$

$$V_{\max} = 9 \times 10^3 \text{ V}$$

$$V_{\max} = 9 \text{ kV}$$

Question6

A $10\mu\text{ F}$ capacitor is charged by a 100 V battery. It is disconnected from the battery and is connected to another uncharged capacitor of capacitance $30\mu\text{ F}$. During this process, the electrostatic energy lost by the first capacitor is

TG EAPCET 2024 (Online) 10th May Morning Shift

Options:

A. $5 \times 10^{-2} \text{ J}$

B. $125 \times 10^{-2} \text{ J}$

C. $2.75 \times 10^{-2} \text{ J}$

D. $375 \times 10^{-2} \text{ J}$



Answer: D

Solution:

Capacitor $C_1 = 10\mu\text{ F}$

Charging voltage, $V = 100\text{ V}$

Initial stored energy of capacitor

$$\begin{aligned}U_{\text{initial}} &= \frac{1}{2}C_1V^2 \\&= \frac{1}{2} \times 10^{-6} \times 100 \times 100 \\&= 0.5 \times 10^{-2}\text{ J}\end{aligned}$$

Energy lost when connect to uncharged capacitor

$$\Delta U = \frac{1}{2} \frac{(C_1C_2)}{C_1+C_2} (V_1 - V_2)^2$$

$$V_2 = 0$$

$$\Delta U = \frac{1}{2} \times \frac{10 \times 30 \times 10^{-6}}{40} \times 100 \times 100$$

$$\Delta U = \frac{3}{80} \times 10^{-2} \times 100 = 0.0375$$

$$\text{or } \Delta U = 3.75 \times 10^{-2}\text{ J}$$

Question7

If half of the space between the plates of a parallel plate capacitor is filled with a medium of dielectric constant 4 , the capacitance is C_1 . If one-third of the space between the plates of the capacitor is filled with the medium of dielectric constant 4 , the capacitance is C_2 . If in both cases, the dielectric is placed parallel to the plated of the capacitor, then $C_1 : C_2 =$

TG EAPCET 2024 (Online) 9th May Evening Shift

Options:

A. 2 : 3



B. 4 : 3

C. 6 : 5

D. 7 : 5

Answer: C

Solution:

Let us assume that the area of the plates is A and the separation between them is d

$$\therefore C = \frac{\epsilon_0 A}{d}$$

The capacitance with the dielectric of thickness, $t = \frac{d}{2}$,

$$\begin{aligned} C_1 &= \frac{\epsilon_0 A}{d - t + \frac{t}{K}} = \frac{\epsilon_0 A}{d - \frac{d}{2} + \frac{d}{2K}} \\ &= \frac{2\epsilon_0 AK}{d(K+1)} = \frac{2KC}{(K+1)} \\ &= \frac{2 \times 4 \times C}{(5)} = \frac{8C}{5} \end{aligned}$$

Again, when capacitor is filled upto $t = ?$

$$\begin{aligned} \therefore C_2 &= \frac{\epsilon_0 A}{d - t + \frac{t}{K}} = \frac{\epsilon_0 A}{d - \frac{d}{3} + \frac{d}{3K}} \\ &= \frac{\epsilon_0 A}{\frac{2d}{3} + \frac{d}{3K}} = \frac{\epsilon_0 A}{d \left(\frac{2K+1}{3K} \right)} \end{aligned}$$

$$\Rightarrow \frac{\epsilon_0 A}{d} \frac{3K}{(2K+1)} = C \times \frac{3K}{(2K+1)}$$

$$C_2 = \frac{C \times 3 \times 4}{9} = \frac{4}{3}C$$

$$\text{Now, } \frac{C_1}{C_2} = \frac{\frac{8}{5}C}{\frac{4}{3}C} \Rightarrow \frac{8}{5} \times \frac{3}{4} = \frac{6}{5}$$

Question8

The natural frequency of an $L - C$ circuit is 120 kHz . When the capacitor in the circuit is totally filled dielectric material, the natural frequency of the circuit decreases by 20 kHz . Dielectric constant of



material is

TG EAPCET 2024 (Online) 9th May Evening Shift

Options:

A. 3.33

B. 1.44

C. 2.12

D. 1.91

Answer: B

Solution:

Natural frequency of $L - C$ circuit

$$2\pi v = \frac{1}{\sqrt{LC}}$$

When capacitor is filled with dielectric,

$$C' = KC$$

$$\text{Thus } \omega_1 = \frac{1}{\sqrt{LC_1}} \text{ and } \omega_2 = \frac{1}{\sqrt{LC_2}}$$

$$\text{According to question, } 2\pi \times 120 = \frac{1}{\sqrt{LC}}$$

$$\text{and } 2\pi \times 100 = \frac{1}{\sqrt{LKC}}$$

$$\Rightarrow \frac{2\pi \times 120}{2\pi \times 100} = \frac{1}{\sqrt{LC}} \times \frac{\sqrt{LKC}}{1}$$

$$\frac{120}{100} = \sqrt{K}$$

$$1.2 = \sqrt{K}$$

$$\Rightarrow K = (1.2)^2 = 1.44$$

Question9

Three capacitors of capacitances $10\mu\text{ F}$, $5\mu\text{ F}$ and $20\mu\text{ F}$ are connected in series with a 14 V DC supply. The charge on $5\mu\text{ F}$



capacitor is

TG EAPCET 2024 (Online) 9th May Morning Shift

Options:

A. $20\mu\text{C}$

B. $40\mu\text{C}$

C. $70\mu\text{C}$


D. $2.8\mu\text{C}$

Answer: B

Solution:

When capacitor are connected in series, the total capacitance C_{Total} ,
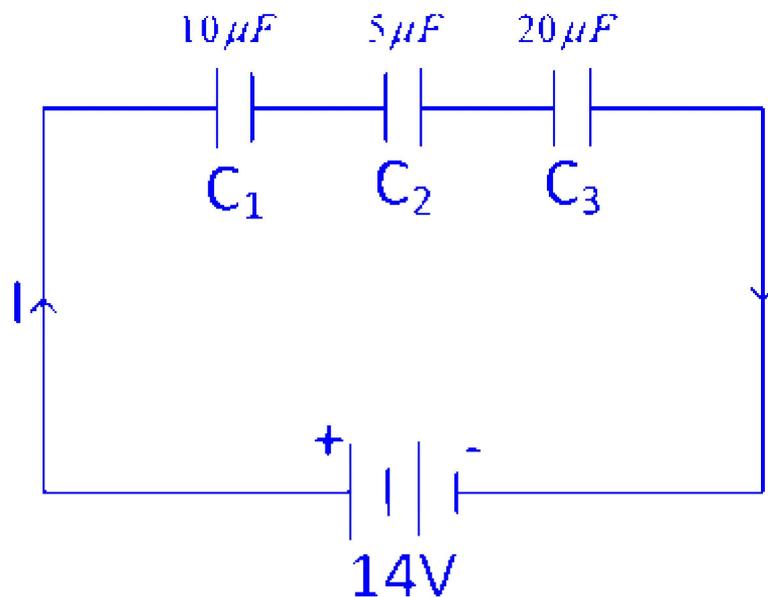
$$\frac{1}{C_{\text{Total}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



Given,

$$C_1 = 10\mu\text{ F}, \quad C_2 = 5\mu\text{ F}, \quad C_3 = 20\mu\text{ F}$$

$$\frac{1}{C_{\text{Toul}}} = \frac{1}{10} + \frac{1}{5} + \frac{1}{20}$$

$$= \frac{2}{20} + \frac{4}{20} + \frac{1}{20} = \frac{7}{20}$$

For, $5\mu\text{C}$,

$$Q = C_{\text{Total}} \times V$$

$$= \frac{20}{7} \times 14 = \frac{280}{7} = 40\mu\text{C}$$

Question10

If a capacitor of capacitance $100\mu\text{ F}$ is charged at a steady rate of $100\mu\text{Cs}^{-1}$, then the time taken to produce a potential difference of 100 V between the capacitor plates is

TS EAMCET 2023 (Online) 12th May Evening Shift

Options:

- A. 50 s
- B. 200 s
- C. 150 s
- D. 100 s

Answer: D

Solution:

Given:

Capacitance $C = 100\mu\text{F}$

Charging rate $q = 100\mu\text{C/s}$

Desired potential difference $V = 100\text{ V}$

To find the time t required to achieve a potential difference of 100 V , use the relationship between charge, capacitance, and potential difference:

$$Q = C \cdot V$$

Since charge Q is also given by:

$$Q = q \cdot t$$

Equate the two expressions:

$$C \cdot V = q \cdot t$$

Rearrange to solve for time t :

$$t = \frac{C \cdot V}{q}$$

Insert the given values:

$$t = \frac{100 \times 10^{-6} \text{ F} \times 100 \text{ V}}{100 \times 10^{-6} \text{ C/s}}$$

$$t = 100 \text{ s}$$

Therefore, the time required to produce a potential difference of 100 V between the capacitor plates is 100 seconds.
